

Computing power going “Platinum”

By Michael O’Loughlin
Senior Applications Engineer

Introduction

The 80 PLUS™ and Climate Savers Computing™ initiatives have set a very aggressive efficiency standard for computer power supplies. The “Platinum” level of these standards specifies that computer power supplies must have an efficiency of 90% at 20% of rated load, 94% at 50% load, and 91% at 100% load. To meet these standards, some power-supply designers have chosen to use a phase-shifted, full-bridge DC/DC converter with synchronous rectification. This topology is a good choice because it can achieve zero voltage switching (ZVS) on the primary FETs. A popular way to drive the synchronous rectifiers is with signals that are already present driving the primary FETs. The only problem with doing this is that dead times on these primary FETs are required to achieve ZVS. This results in both synchronous rectifiers being off simultaneously during the freewheeling period, allowing excessive body-diode conduction and reducing system efficiency. The purpose of this article is to propose different timing for driving these synchronous rectifiers to reduce body-diode conduction and improve overall system efficiency.


There are a few pulse-width modulators (PWMs) on the market that were developed for controlling a phase-shifted, full-bridge converter but were not set up for driving synchronous rectifiers (QE and QF). To use these controllers in this application, engineers have found they can control the synchronous FETs with control signals OUTA and OUTB from the PWM controller. Figure 1 shows a functional schematic of one of these converters.

The problem

The PWM controllers help achieve ZVS in these converters by delaying the turn-on of the FETs in the H bridge (QA, QB, QC, QD). The delay (t_{Delay}) between the turn-on and turn-off transitions of FETs QA and QB will cause synchronous FETs QE and QF to be off simultaneously, allowing their body diodes to conduct as already stated. The following equation is a good estimate of the body-diode conduction losses in QE and QF during the freewheeling period:

$$P_{\text{Diode}} = \frac{P_{\text{OUT}}}{V_{\text{OUT}}} \times V_{\text{D}} \times t_{\text{Delay}} \times f_{\text{s}}$$

Figure 1. Phase-shifted, full-bridge converter modified for synchronous rectification

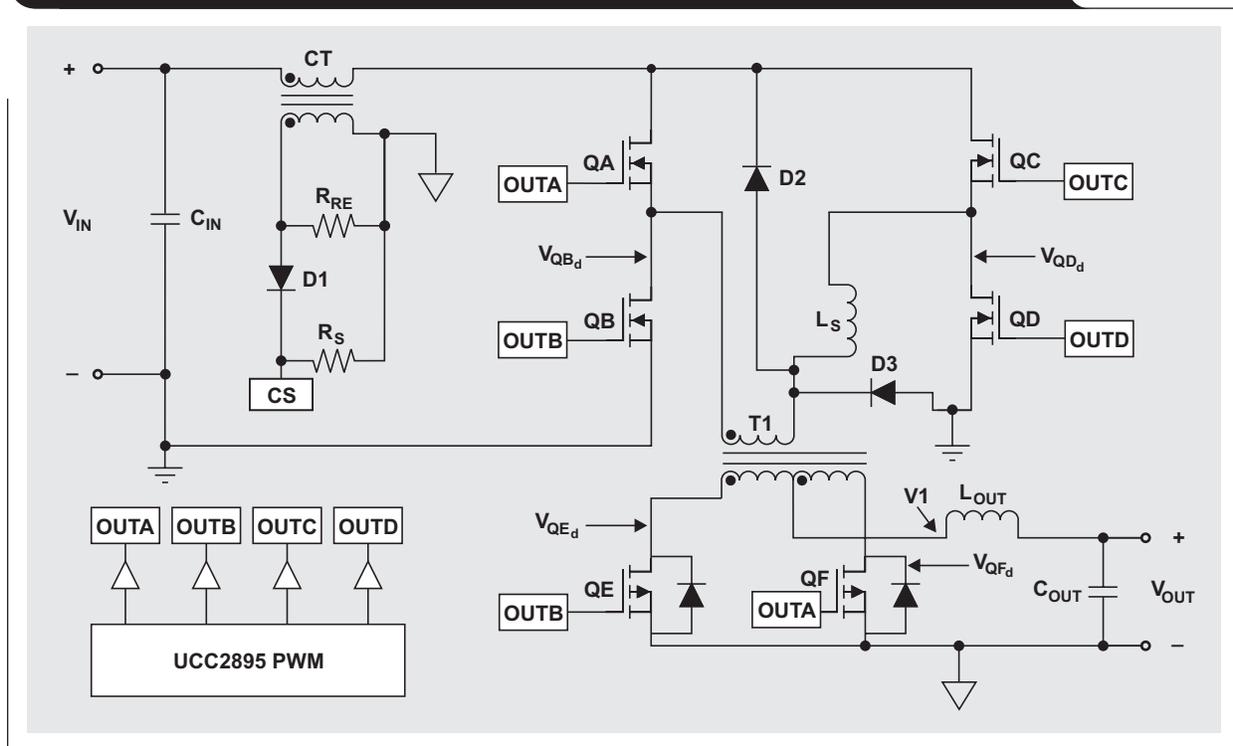

where P_{OUT} is the output power, V_{OUT} is the output voltage, V_D is the forward voltage drop of the body diode, and f_s is the inductor switching frequency.


The excessive body-diode conduction losses of QE and QF (P_{Diode}) could cause the design not to meet the Platinum standard. Please refer to Figures 1 and 2 for details. As shown, OUTA drives FETs QA and QF, while OUTB drives FETs QB and QE. V1 is the voltage presented to the input of the L_{OUT} and C_{OUT} filter network, and

V_{QE_d} and V_{QF_d} are the voltages across the respective synchronous rectifiers QE and QF.

The solution

To reduce QE and QF body-diode conduction, it would be better to have these synchronous rectifiers on during the QA and QB delay periods (t_{Delay}). To accomplish this, FETs QE and QF would have to be driven with their own outputs where the ON times would overlap instead of the OFF

Figure 2. Timing diagrams for converter in Figure 1

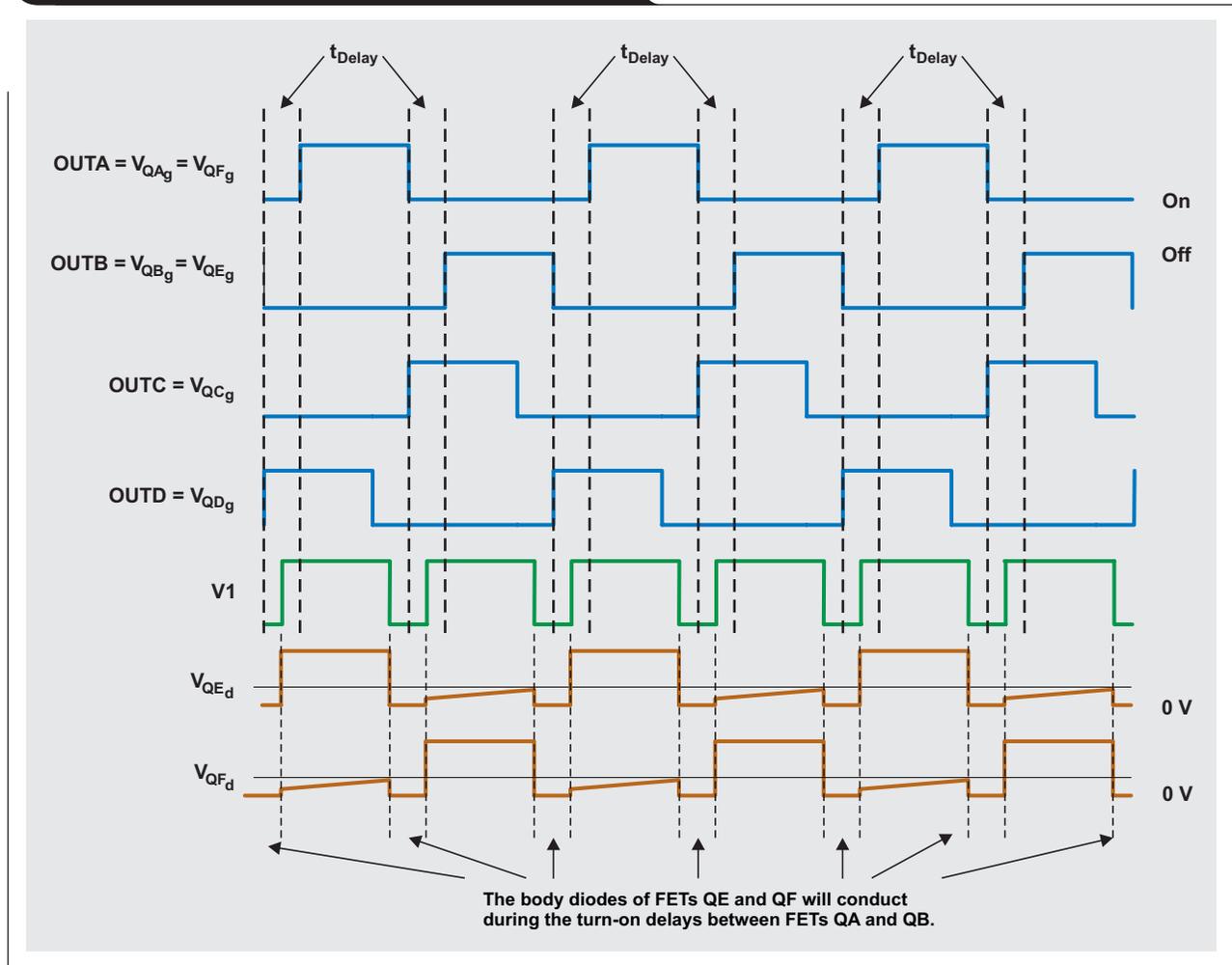


times being simultaneous. Figure 3 shows a functional schematic of the phase-shifted, full-bridge converter with six separate drive signals (OUTA through OUTF). The signals for QE (OUTE) and QF (OUTF) can be generated by turning OUTE and OUTF on and off based on the edges of QA through QD. The timing needed to accomplish this

Table 1. OUTE and OUTF on/off transitions

OUTE	Turns on when OUTC turns on	Turns off when OUTB turns off
OUTF	Turns on when OUTD turns on	Turns off when OUTA turns off

Figure 3. Phase-shifted, full-bridge converter using the timing from Table 1

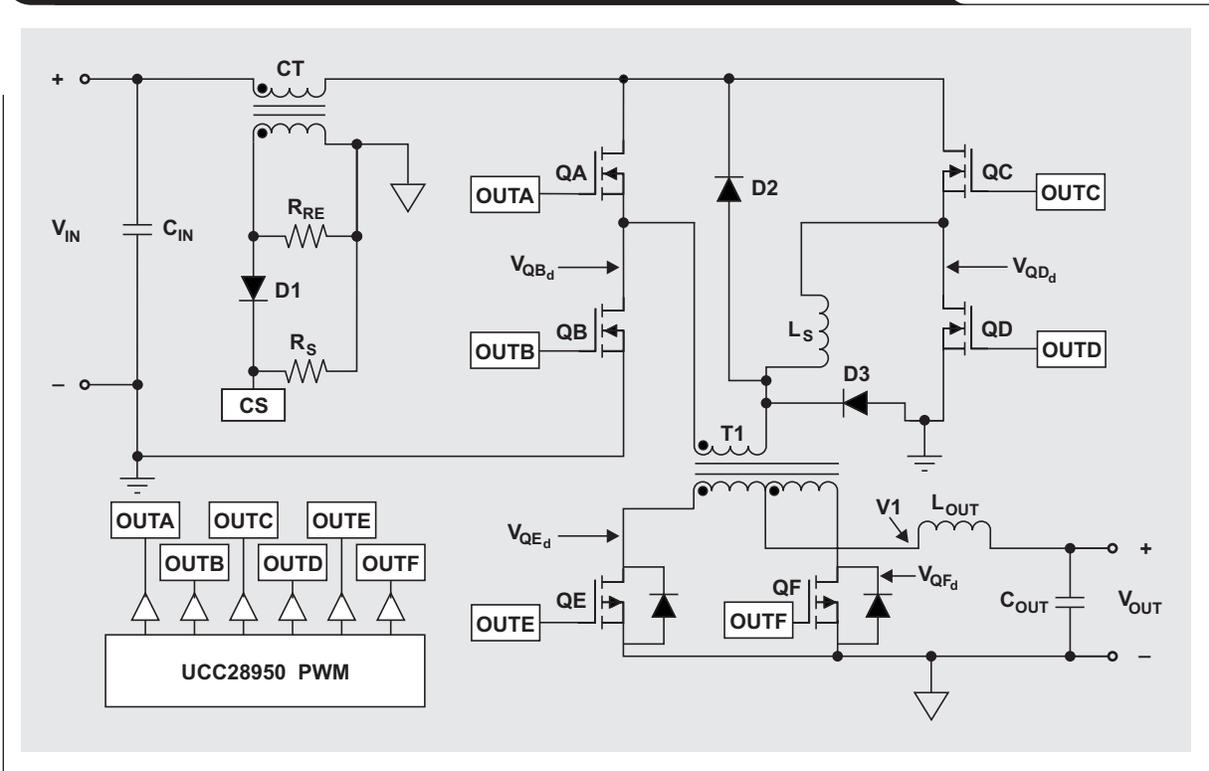

is presented in Table 1 and Figure 4. The theoretical waveforms in Figure 4 show that this technique removes the body-diode conduction that would be present if both gate drives were off during t_{Delay} with the gate-drive signals presented in Figure 2.

Experimental results

To see how well this technique worked for reducing body-diode conduction, a 390- to 12-V phase-shifted, full-bridge converter was modified to drive the FETs with the signals shown in Figures 2 and 4.

Figure 4. Timing diagram for reducing QE and QF body-diode conduction

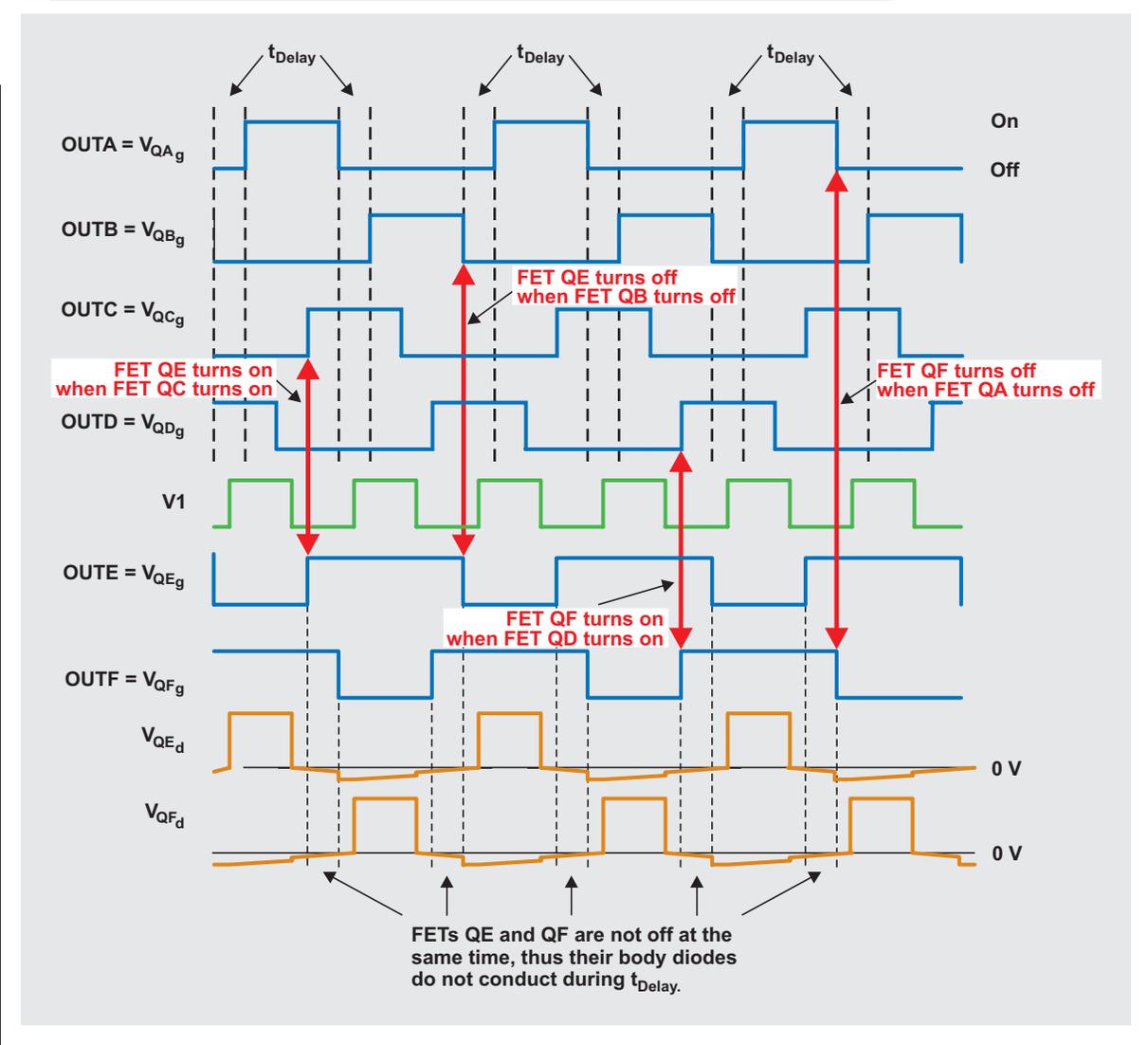


Figure 5 shows a scope plot of the gates of the synchronous FETs (QE and QF) while they were driven with the OUTA and OUTB PWM outputs. In this figure, body conduction can be observed during the delay times (t_{Delay}) between OUTA and OUTB.

Figure 6 on the next page shows a scope plot of the gates of the synchronous FETs (QE and QF) while they were driven with the OUTE and OUTF signals presented in Figure 3. These signals were generated from TI's new UCC28950 phase-shifted, full-bridge controller. Figure 6 shows that the body diodes did not conduct when FETs QE and QF were on at the same time. Some body-diode conduction is still visible, but there is not as much as in Figure 5.

The 600-W DC/DC converter's efficiency was measured for both drive schemes—OUTA and OUTB versus OUTE and OUTF—from 20% to full load. The efficiency data of the converter for these two drive schemes is presented in Figure 7 on the next page. It can be observed that using OUTE and OUTF was roughly 0.4% more efficient at a 50 to 100% load than using OUTA and OUTB. A 0.4% efficiency gain may not seem like a lot but could make a difference when the designer is trying to achieve the Platinum standard.

Conclusion

Even though it is possible to control a phase-shifted, full-bridge converter that has synchronous rectifiers with a phase-shifted, full-bridge controller that was not designed for synchronous rectification (OUTA and OUTB drive scheme), the turn-on delay between OUTA and OUTB required to achieve ZVS causes both synchronous FETs to be off at the same time (t_{Delay}). This delay results in excessive body-diode conduction during the FET's freewheeling period. This article has shown that it is more efficient to overlap the ON time of the synchronous rectifiers during the freewheeling time so that the body diodes do not conduct. Even though the body-diode conduction is not completely removed with this technique, it is drastically reduced, improving overall system efficiency and making the Platinum efficiency standard easier to meet.

Related Web sites

power.ti.com

www.ti.com/sc/device/UCC2895

www.ti.com/sc/device/UCC28950

Figure 5. Scope plot of QE and QF body-diode conduction

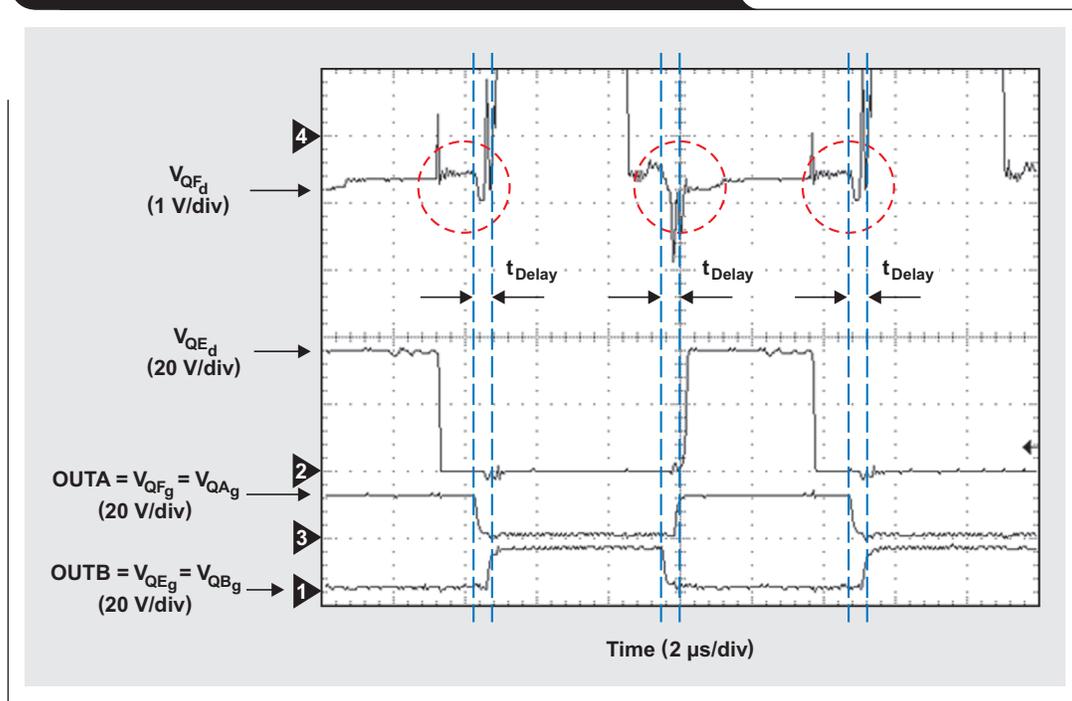


Figure 6. Scope plot showing reduced body-diode conduction of QE and QF


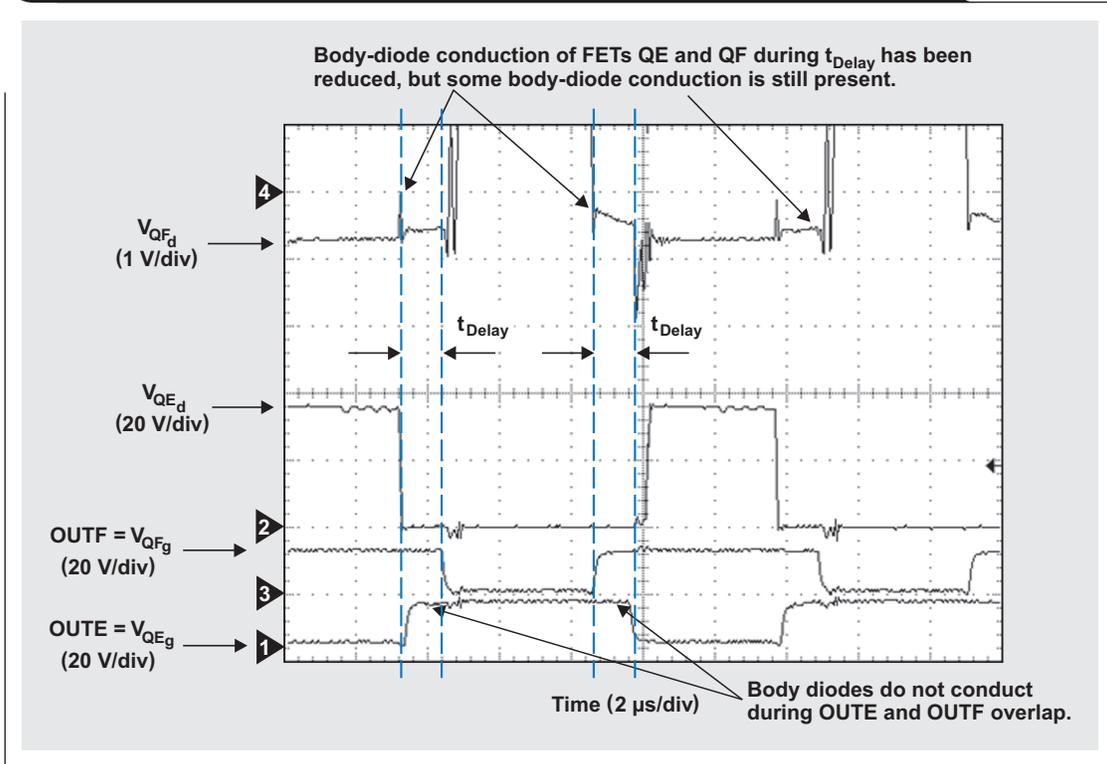


Figure 7. Efficiency of 600-W DC/DC converter with different QE and QF drive schemes

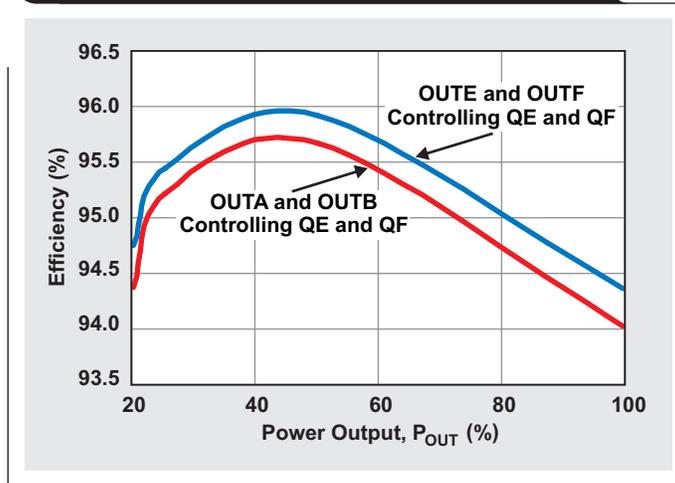

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page

support.ti.com

TI E2E™ Community Home Page

e2e.ti.com

Product Information Centers

Americas	Phone	+1(972) 644-5580
Brazil	Phone	0800-891-2616
Mexico	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

Phone	
European Free Call	00800-ASK-TEXAS (00800 275 83927)
International	+49 (0) 8161 80 2121
Russian Support	+7 (4) 95 98 10 701

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	support.ti.com/sc/pic/euro.htm

Japan

Phone	Domestic	0120-92-3326
Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

Asia

Phone	
International	+91-80-41381665
Domestic	<u>Toll-Free Number</u>
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	1-800-425-7888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
Fax	+886-2-2378-6808
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A042210

E2E is a trademark of Texas Instruments. Climate Savers Computing is a service mark of World Wide Fund for Nature (formerly World Wildlife Fund). 80 PLUS is a service mark of Ecos Consulting Inc. All other trademarks are the property of their respective owners.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DLP® Products	www.dlp.com	Communications and Telecom	www.ti.com/communications
DSP	dsp.ti.com	Computers and Peripherals	www.ti.com/computers
Clocks and Timers	www.ti.com/clocks	Consumer Electronics	www.ti.com/consumer-apps
Interface	interface.ti.com	Energy	www.ti.com/energy
Logic	logic.ti.com	Industrial	www.ti.com/industrial
Power Mgmt	power.ti.com	Medical	www.ti.com/medical
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
RFID	www.ti-rfid.com	Space, Avionics & Defense	www.ti.com/space-avionics-defense
RF/IF and ZigBee® Solutions	www.ti.com/lprf	Video and Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless-apps