

# Implementation of microprocessor-controlled, wide-input-voltage, SMBus smart battery charger

By Keith Keller

Analog Field Applications/Power Management

With the increasing popularity of lithium-ion chemistries in all types of electronics designs, innovative solutions for charging these batteries are becoming essential. For the utmost in system flexibility, a microprocessor can be used to control all aspects of battery charging, including unique charging algorithms to increase the charging rate and lifetime of the cells. This method also allows for higher-voltage battery-pack implementations.

This article describes using a microprocessor to control the power-stage board of a wide-input-voltage DC/DC controller. This solution can support an input voltage of up to 55 V; a battery-charging voltage ranging from 5 to 51 V; and up to 10 A of output current in most cases. Both the hardware and software discussed in this article have been developed and tested by Texas Instruments (TI) applications staff to allow customers to quickly prototype the solution.

For ease of development, the battery charger is split into two separate boards: the microprocessor controller board and the DC/DC-converter power-stage board (see Figure 1). The positive and negative battery terminals are connected to the power-stage board, while the system-management bus (SMBus) communication lines are connected to the microprocessor board. The smart battery sends the desired charging voltage and current information to the microprocessor, which then sends two pulse-width-modulated (PWM) signals to the DC/DC-converter power-stage board to set the actual output voltage and current.

To permit the use of a standard wide-input-voltage DC/DC converter, the power-stage board is designed with a

special feedback circuit (see Figure 2) to properly control the charging of the battery. The charging sequence that the microprocessor follows is to first limit the charge current until the battery voltage approaches its specified maximum voltage. When the maximum voltage is reached, the charge voltage is held constant, allowing the charge current to taper down until the battery is deemed fully charged. At this point the PWM output signals are shut off.

The initial current-limiting charge rate could have two current levels. When a battery has been overly discharged, a fractional charge rate is used until the battery voltage is at a safe enough level to accept the normal charge rate.

In the feedback circuit shown in Figure 2, U3:B compares the PWM-current reference voltage (I\_PWM1) to the measured current (ISNS1) being delivered to the battery. If the PWM reference voltage is higher than the measured current, the output of the amplifier is high. If the reference voltage is lower, the output of the amplifier is low.

A resistor divider (R30 and R34) is used to measure the output voltage at the VBATT1 input to U3:A. This voltage is compared to the PWM-output reference voltage (V\_PWM1). If this reference voltage is higher, the output of the amplifier is high. If the reference voltage is lower, the output of the amplifier is low. The maximum output voltage is dictated by

$$V_{OUT(max)} = \frac{VBATT1}{R34 \times (R34 + R30)}$$

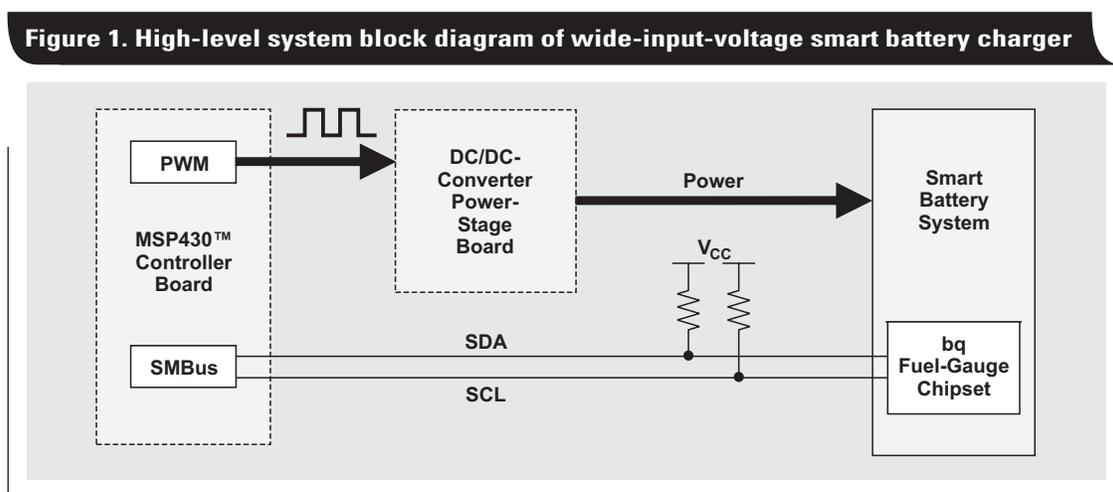


Figure 2. Constant-current/voltage-feedback circuitry to properly charge a battery


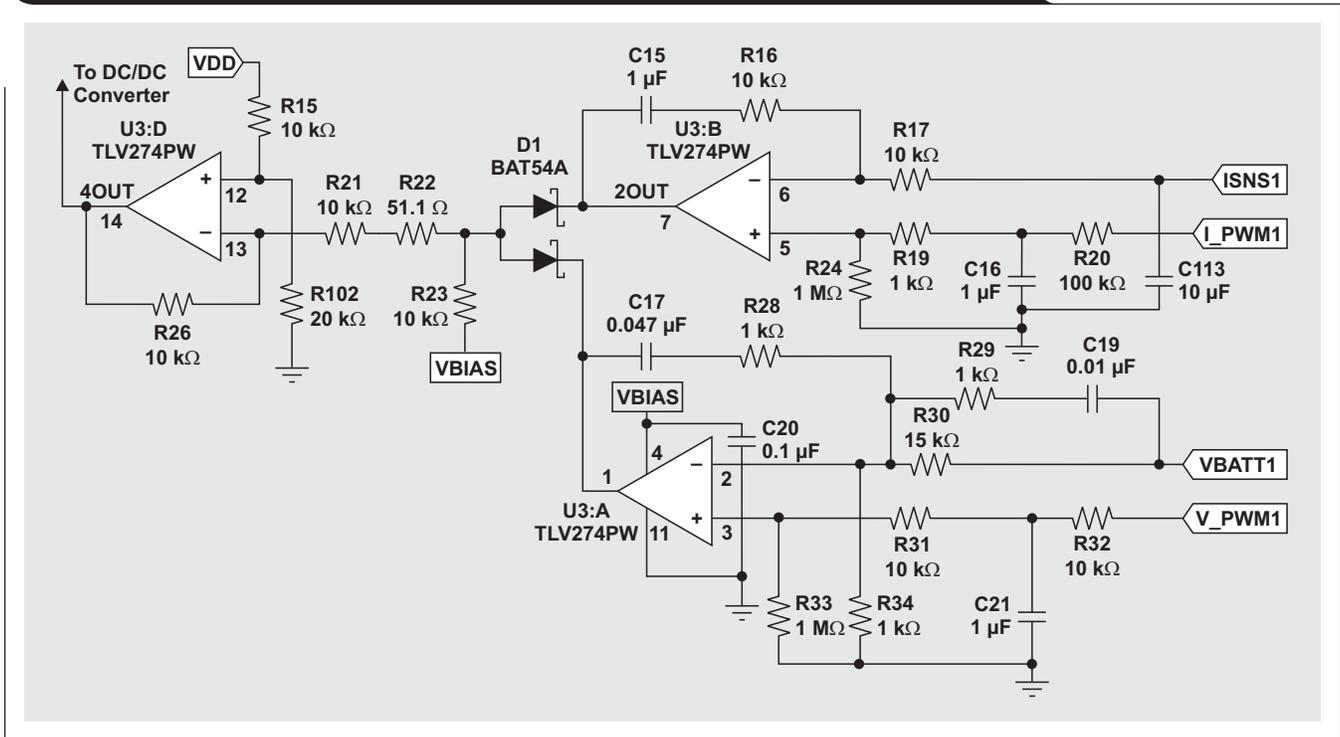


Figure 3. Overvoltage and reverse-polarity protection circuitry

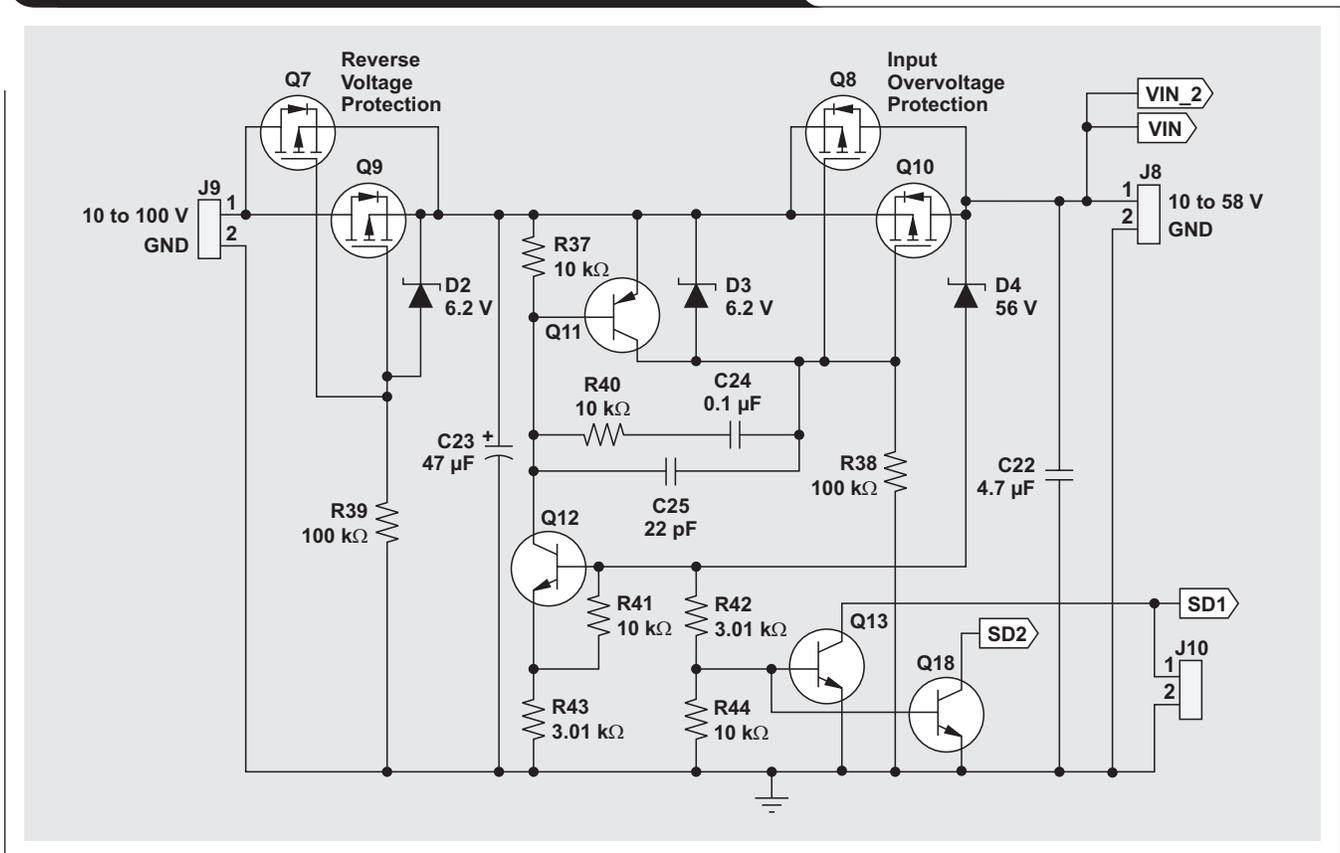

The D1 diodes combine the outputs of the two amplifiers with a logical OR. The voltage that is lowest is fed into an inverting amplifier (U3:D) that makes the error signal's polarity correct for the DC/DC controller (in this case TI's TPS40170). The basic operation is that the controller tries to send a set current; and, if the load can accept this current, the controller regulates to that current level. If the load cannot accept the full amount of current, the voltage begins to rise and eventually reaches  $V_{OUT(max)}$ . When this happens, the voltage loop takes over and regulates the output voltage.

To enhance the safety of the solution, also included on the power-stage board is protection circuitry both for overvoltage conditions (up to 100 V) and for reverse-voltage connections (where the positive and negative leads are swapped). This circuitry is shown in Figure 3.

Reverse-voltage protection is provided by MOSFETs Q7 and Q9 along with D2 in case the input voltage is connected backwards. This does not allow a negative voltage to be applied to the system. Input-overvoltage protection is provided by MOSFETs Q8 and Q10. Zener diode D4 sets the voltage that the circuit starts to clamp. Once the Zener voltage is exceeded, the gate-to-source voltage of the FETs starts to drop. This causes the FETs to operate in the linear region and

allows the microprocessor to continue to be powered. At the same time, the DC/DC converters are turned off, with signals SD1 and SD2 being pulled to ground.


The software implementation is equally as important as the hardware. The abbreviated software flowchart is shown in Figure 4. The microprocessor interrogates the battery via SMBus for its desired charging voltage and current. After confirming the values, it sets two PWM outputs accordingly to regulate the output voltage and current going to the battery. If at any time the battery issues a charging alarm, the PWM outputs will shut off. Additionally, the PWM outputs will shut off as soon as the battery's state of charge reaches 100% or the fully charged bit is set.

Safety is of utmost concern during battery charging. Any solution should allow for several levels of protection. The first level of protection is the smart battery itself with its internal protection MOSFETs. During charging, the microprocessor should communicate with the battery on a regular basis (every 2 seconds is good) and monitor for any safety flags in the "Battery Status" register. The flag bits that require action are the overcharge alarm (OCA), terminate-charge alarm (TCA), overtemperature alarm (OTA), and fully charged (FC) condition. The microprocessor's onboard analog-to-digital converter can be used as a secondary check for an overvoltage or overcurrent event.

## Conclusion

A fully programmable, wide-input-voltage battery charger can be designed by using a microprocessor in conjunction with a wide-input-voltage DC/DC controller. This article

**Figure 4. Abbreviated overview of software flowchart**

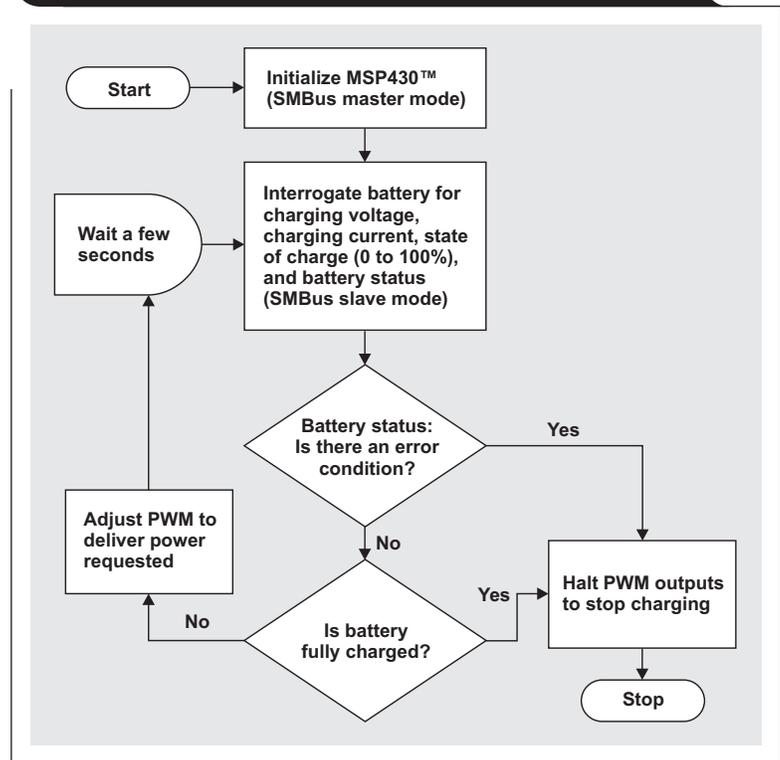

has presented a solution that uses TI's low-power MSP430F5510 microprocessor together with the TPS40170 DC/DC controller, a configuration that can support an input voltage of up to 55 V. The special feedback network developed by TI applications staff for proper battery charging has been described. Additionally, a novel solution was shown for overvoltage protection, and reverse-voltage protection was discussed. The software required to communicate to a smart battery via SMBus communications protocol can be downloaded from a link in Reference 1, which is an application report. Detailed information on the SMBus smart battery charger is also available in Reference 1.

## Reference

For more information related to this article, you can download an Acrobat® Reader® file at [www.ti.com/lit/litnumber](http://www.ti.com/lit/litnumber) and replace "litnumber" with the **TI Lit. #** for the materials listed below.

- | Document Title  | TI Lit. # |
|---|-----------|
| 1. Abhishek A. Joshi and Keith J. Keller, "Wide-Vin battery charger using SMBus communication interface between MSP430™ MCUs and bq fuel gauges," Application Report. . . . . | slaa476   |

## Related Web sites

[power.ti.com](http://power.ti.com)  
[www.ti.com/sc/device/MSP430F5510](http://www.ti.com/sc/device/MSP430F5510)  
[www.ti.com/sc/device/TPS40170](http://www.ti.com/sc/device/TPS40170)

# TI Worldwide Technical Support

---

## Internet

### TI Semiconductor Product Information Center Home Page

support.ti.com

### TI E2E™ Community Home Page

e2e.ti.com

## Product Information Centers

<b>Americas</b>	Phone	+1(972) 644-5580
<b>Brazil</b>	Phone	0800-891-2616
<b>Mexico</b>	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

## Europe, Middle East, and Africa

Phone	
European Free Call	00800-ASK-TEXAS (00800 275 83927)
International	+49 (0) 8161 80 2121
Russian Support	+7 (4) 95 98 10 701

**Note:** The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	support.ti.com/sc/pic/euro.htm
Direct Email	asktexas@ti.com

## Japan

Phone	Domestic	0120-92-3326
Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

## Asia

Phone	
International	+91-80-41381665
Domestic	Toll-Free Number
<b>Note:</b> Toll-free numbers do not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	1-800-425-7888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010

Fax	+8621-23073686
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

**Important Notice:** The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

**A122010**

E2E and MSP430 are trademarks of Texas Instruments. Acrobat and Reader are registered trademarks of Adobe Systems Incorporated. All other trademarks are the property of their respective owners.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
RF/IF and ZigBee® Solutions	<a href="http://www.ti.com/lprf">www.ti.com/lprf</a>

### Applications

Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Transportation and Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
Wireless	<a href="http://www.ti.com/wireless-apps">www.ti.com/wireless-apps</a>

TI E2E Community Home Page

[e2e.ti.com](http://e2e.ti.com)

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2011, Texas Instruments Incorporated