

Extending the SPI bus for long-distance communication

By Thomas Kugelstadt
Senior Applications Engineer

The serial peripheral interface (SPI) bus is an unbalanced or single-ended serial interface designed for short-distance communication between integrated circuits. Typically, a master device exchanges data with one or multiple slave devices. The data exchange is full-duplex and requires synchronization to an interface clock signal. However, recent trends in the design of industrial data-acquisition systems have not taken this synchronization requirement into account, and distances between the microcontroller and the corresponding analog-to-digital and digital-to-analog converters (ADCs and DACs) can reach 100 m or more.

The impact of the added propagation delay on the data-to-clock synchronicity is often ignored, and interface designs that operate perfectly in the lab environment cease operation when implemented on the factory floor. There can be multiple reasons for the interface malfunction. This article tries to shed light on the major ones, including:

- Lack of synchronization due to large propagation delays of the signal path
- Reduced noise immunity due to long-distance, unbalanced signal paths
- Damaged transceivers due to large ground-potential differences (GPDs)
- Data transmission errors due to unterminated data lines
- Transceiver latch-up and network downtime due to large electrical transients

Synchronicity

An SPI primarily uses three interface lines:

- An interface clock initiated by the master device to ensure synchronous data transfers
- A data line for data sent from the master to a slave
- A data line for data sent from a slave to the master


A fourth wire that carries what is known as the slave-select signal is not required for controlling interface flow but is needed for addressing a specific slave out of a range of slave devices. Figure 1a shows a simplified schematic of a microcontroller unit (MCU) operating as the master that controls two data converters representing the slaves.

With byte lengths ranging from 8 to 12 bits and multiples thereof, and data rates ranging from 1 to 20 Mbps, the standard SPI configuration allows for short propagation times and hence only short distances in order to maintain synchronicity between the interface clock and the data transmitted in both directions. Figure 1b shows the interface timing of the first three data bits when the SPI is configured to change data at the rising clock edge and to sample data at the falling clock edge.

Over long distances, however, the transmission cable introduces significant propagation delay into the signal path. Assuming a typical signal velocity of 5 ns/m, a 100-m cable will cause a propagation delay of 500 ns. Because the data sent from the master to the slave experiences the same delay as the master-initiated interface clock, both will remain in sync across the entire data link. In the opposite direction, however, the slave sends data to the master only when the first clock edge reaches the slave. Furthermore, this data will experience a second delay on its way back to the master, so the slave data will be out of sync by twice the cable's propagation delay.

Of course, communicating across a 100-m cable won't be possible without appropriate line drivers and receivers. These components will further increase the propagation delay by about another 50 ns, for a total of 550 ns. The slave data will therefore lag behind the first clock edge by a total of 1100 ns, or 11 bits when a data rate of 10 Mbps is assumed.

Figure 1. Simplified schematic of an SPI

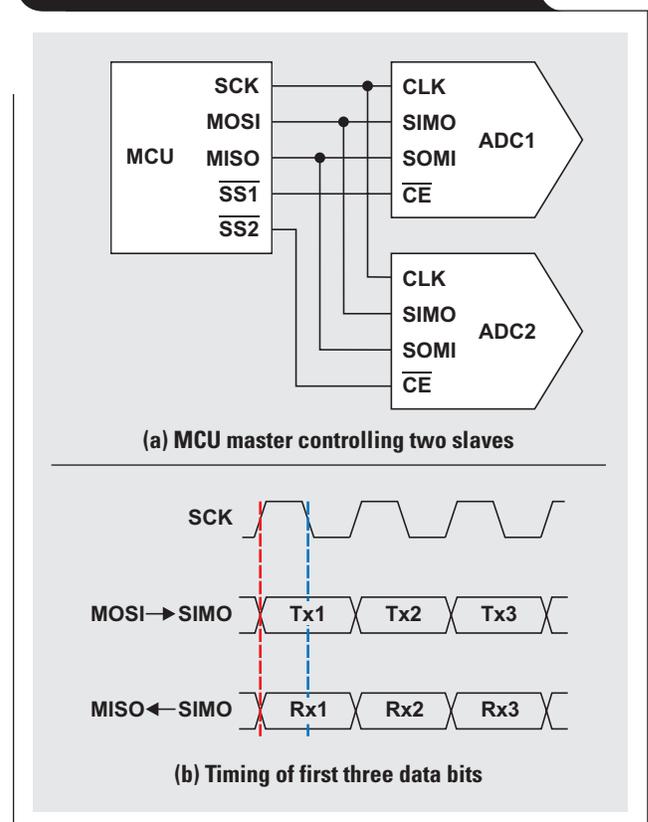


The only possible solution for restoring synchronicity between the slave data and the interface clock while maintaining a high data rate is to feed the clock signal from the slave back to the master. Figure 2 clarifies the benefit of clock feedback. Here t_0 represents the first rising clock edge, or the start of a data transmission, and t_p is the data-link propagation delay. After traversing the data link, both the master clock (SCK_M) and the master data (MOSI) remain in sync. Feeding back the master clock signal synchronizes the clock with the slave data so that both arrive equally delayed at the master. The only requirement is that the master provide two independent SPI ports, one configured as a master (SPI1) and the other configured as a slave (SPI2). Most modern microcontrollers possess two or more SPI ports, so this requirement poses no problem.

Nevertheless, implementing a long-distance, SPI-compatible interface in the real world is not a trivial task. Long-distance data links are always subject to external noise sources, ground-potential differences (GPDs), voltage and current surges due to inductive load switching, and often even reflections due to wrong or no termination. The flowing schematic in Figure 3 (see next page) tries to cover all of these aspects by showcasing the various transceiver and protection circuits that can counteract the derogating effects.

Increasing noise immunity

Unbalanced or single-ended drivers and receivers are inadequate for accomplishing a robust data link over long distances, as they are susceptible to common-mode noise. An excellent method to eliminate common-mode noise in a synchronous, full-duplex interface such as an SPI is the use of RS-422 differential driver and receiver circuits in combination with twisted-pair cable.

Figure 2. Clock-feedback path restores synchronicity

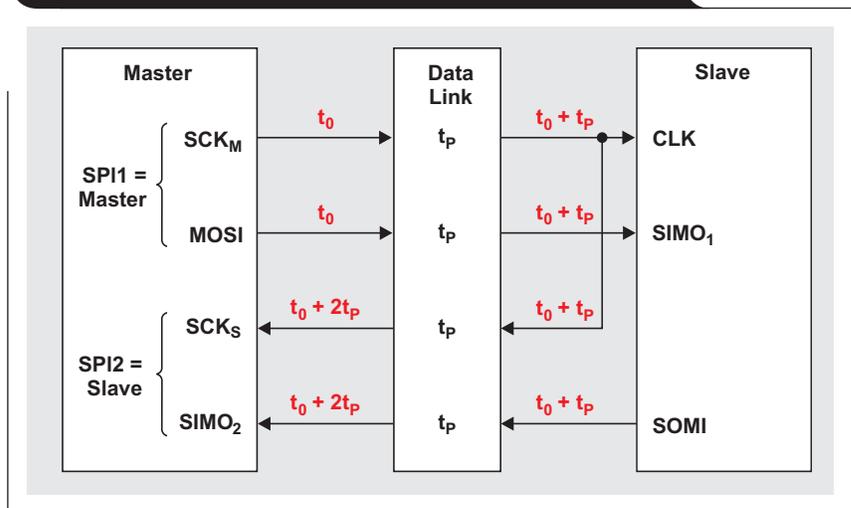


Because the conductors of twisted-pair cable are closely electrically coupled, external noise induced equally into both conductors appears as common-mode noise at the receiver input. Although differential receivers are sensitive to signal differences, they are immune to common-mode signals. The receiver therefore rejects common-mode noise, and signal integrity is maintained.

Another benefit of close electric coupling is that the currents in the two conductors create magnetic fields that cancel each other. The initial transversal electromagnetic (TEM) waves of the two conductors are therefore largely reduced to electric fields that cannot radiate into the environment (see Figure 4). Only the far smaller fringing fields outside the conductor loop can radiate, thus yielding much lower electromagnetic interference (EMI).

Eliminating ground loops and GPDs

While the RS-485 and RS-422 standards specify that a data link without a ground wire can be operated with a GPD of up to ± 7 V, it is advisable not to assume that these values

Figure 4. TEM-wave radiation effects

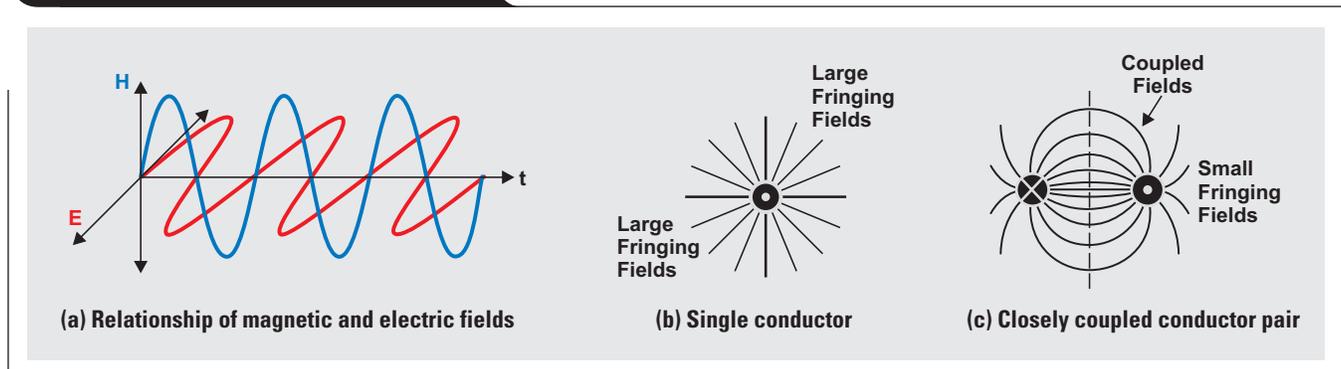

represent the maximum GPD. Much higher values are often encountered in industrial plants, sometimes reaching several hundreds and even thousands of volts. Because GPDs largely depend on factors outside the system designer's control, such as the electric installation and/or the number of electric motors and generators, the most secure way to prevent transceiver damage from large ground-potential variations is to galvanically isolate any remote network node from the bus. The circuit in Figure 3 demonstrates this by having only the remote transceiver connected to the bus, while the data-converter circuit is galvanically isolated.

Also, to provide the input and output signals of the remote transceiver with a stable ground reference, the transceiver's ground terminal as well as the digital isolator's ground terminal (GND1) are connected to the master ground potential via a separate ground conductor. This form of grounding is known as a single ground reference.

Avoiding antennas through line termination

The data link in Figure 3 is terminated with 100-Ω resistors, as suggested by the RS-422 standard, matching the characteristic impedance of the bus cable. A myth exists that bus cables of a few meters in length or data links operating at low data rates don't need termination. Don't believe it. Operating the bus without termination can turn the transmission line into a nasty receiver/transmitter antenna. The lack of termination resistors, which usually absorb the incident wave power sent by the driver, causes standing waves to occur; and the entire incident wave is reflected into the bus. The reflected waves mix with other incident waves, thus yielding standing waves for signal frequencies whose quarter wavelengths, or multiples thereof, equal the length of the data link.


Depending on their location, the wave nodes (minima) and antinodes (maxima) can have varying effects on the bus transceivers (see Figure 5). A driver close to an antinode sees a high impedance and therefore transfers insufficient energy to the bus. A driver close to a node sees a very low impedance or a short. The resulting output current can exceed the driver's maximum drive capability and even trigger its current limit at around 250 mA. Receivers located at antinodes can be damaged by excessively large input signals that exceed the receiver's common-mode input range. Receivers close to nodes experience insufficient signal strength and are highly susceptible to noise and EMI. Any of the foregoing events will result in data errors from either the transmission or the reception of wrong data.

Protecting the network against damaging transients

Electrical overstress transients caused by electrostatic discharge (ESD), switching of inductive loads, or lightning strikes will corrupt data transmission and damage bus transceivers unless effective measures are taken to diminish their impact. Modern transient-voltage suppressors, such as the ones in Figure 3, are the preferred protection components for high-speed data transmission due to their low capacitance, which allows them to be designed into every node of a multinode network without requiring a reduction in data rate.

Depending on the power rating of the transient-voltage suppressor chosen, the maximum clamp voltages can range from 25 to 35 V, which is higher than a standard transceiver's maximum bus voltage of 14 V. In this case, the internal protection circuit of the transceiver must

Figure 5. Effects of an unterminated bus

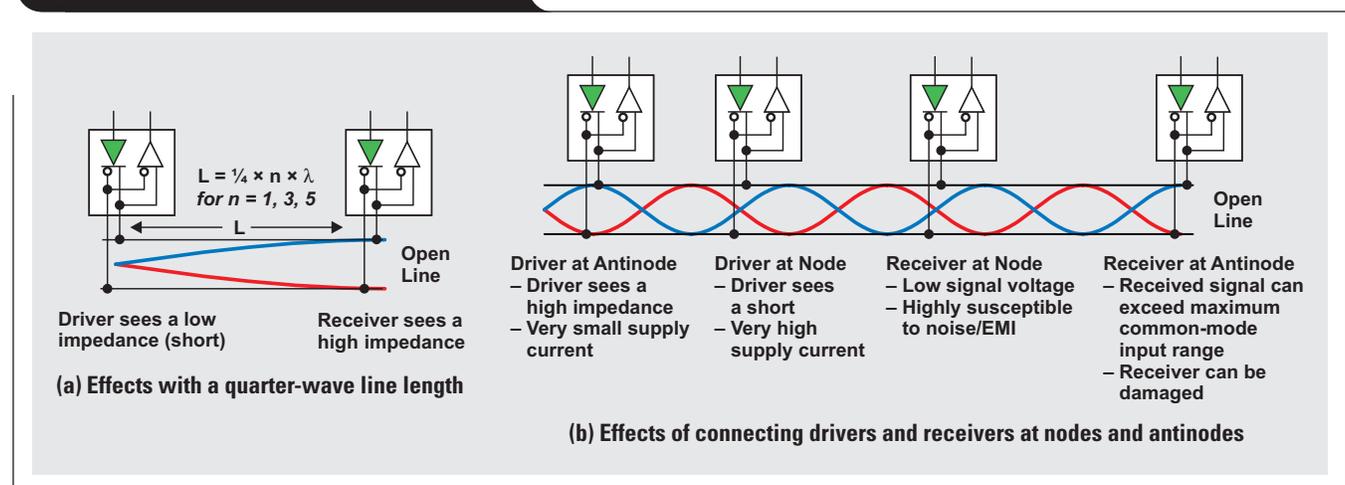

absorb the remaining clamp energy to protect the device from damage.

For ESD and burst transients, the clamp energy is rather low due to the short pulse duration and does not pose a problem to the internal ESD cells. Clamp energy from surge transients, however, can present a serious challenge due to the much longer pulse duration. For transceivers specified with low ESD immunity, series resistors might be necessary to reduce the remaining current flowing into the transceiver. Common resistor values range from 5 to 10 Ω . Note that these resistors must be surge-rated to provide high pulse robustness.

Although the transient-voltage suppressor's diodes divert large transient currents to ground, it must be ensured that these currents are further diverted to true earth potential without disturbing the ground reference of the remaining circuitry. Often this is accomplished by implementing a

high-voltage capacitor that has one plate connected to ground and the other plate connected to a protective-earth (PE) island. This island is then connected via a short, low-inductance earthing wire to the PE terminal of the local mains supply.

In addition to the suppressor's action on the bus side, further protection against signal degradation is required on the transceiver's single-ended sides. This is accomplished with R-C low-pass filters, which filter transient remnants in the reception path and stop high-frequency noise from entering the transmission path.

Related Web sites

interface.ti.com

www.ti.com/product/ISO7242C

www.ti.com/product/SN65C1167

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page

support.ti.com

TI E2E™ Community Home Page

e2e.ti.com

Product Information Centers

Americas	Phone	+1(972) 644-5580
Brazil	Phone	0800-891-2616
Mexico	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

Phone	
European Free Call	00800-ASK-TEXAS (00800 275 83927)
International	+49 (0) 8161 80 2121
Russian Support	+7 (4) 95 98 10 701

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	support.ti.com/sc/pic/euro.htm
Direct Email	asktexas@ti.com

Japan

Phone	Domestic	0120-92-3326
Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

Asia

Phone	
International	+91-80-41381665
Domestic	<u>Toll-Free Number</u>
Note: Toll-free numbers do not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	1-800-425-7888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010

Fax	+8621-23073686
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A122010

E2E is a trademark of Texas Instruments. All other trademarks are the property of their respective owners.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated