

35-V, single-channel gate drivers for IGBT and MOSFET renewable-energy applications

By John Stevens

Systems Engineer, High-Performance Isolated Power

Introduction

The electronics market segment labeled as renewable energy is a complex and diverse arena for electric power conversion. In point-of-load applications, the switching power converter typically is non-isolated; power levels are fairly low (<200 W); and the power is usually converted from one DC voltage to another, such as from 12 V to 3.3 V. Further, the power-stage switches are integrated or capable of being driven by low-current controllers or transistors. Integration between the controller and power stage is being realized today. Silicon (Si) MOSFETs dominate this arena, where higher switching frequencies are preferred and can reach speeds of greater than 1 MHz. These power switches generally are driven by a 5- or 12-V IC gate driver or similar solution.

Challenges to efficiently managing renewable-energy systems

In the electronic power train from a wind or photovoltaic power generator, there are some unique performance challenges. Typical power levels for renewable energy can range from 1 to 3 kW for micro-inverters, 3 to 10 kW for string inverters, and 10 kW to 1 MW for large central-inverter stations. In addition to DC-to-DC conversion, DC-to-AC and AC-to-DC conversion can also be used, and sometimes a combination of the two.

Older wind turbines were tied directly to the power grid but had to run at the power-line frequency. This made them inefficient across the many operating points they experienced. Newer wind turbines (Figure 1) often convert AC to DC and then DC back to AC so that the wind-driven generator can run at variable speeds for maximum efficiency.

Conversely, photovoltaic cells produce DC voltage/current. Generally, the voltage is boosted higher and then sent through a DC-to-AC inverter before being tied to the grid.

Renewable-energy trends

For most countries, generating renewable energy from sources such as wind and solar power makes up only a small percentage of their total power portfolio. In recent history, growth has been consistent year by year. There are places where renewable energy makes up a large share of the available power. Denmark, for example, generated nearly 34% of its total electricity from wind power alone

in the first half of 2012, according to the Danish Energy Agency. According to its parent agency, the Danish Ministry of Climate, Energy and Building, Denmark has committed to having 50% of its total power supply come from wind by 2020. When wind energy makes up that large a portion of a country's total power, reliability of the conversion system becomes critical. This—together with the high-power connection to the grid, isolation safety requirements, and the cost of large renewable-energy conversion systems—means that system reliability is always the design priority, followed by efficiency. Therefore, protection features and reliability are preferred at all levels, from the controller all the way down to the FET/IGBT driver itself.

Typical power-management configuration

High power levels lead to higher system voltages, and therefore higher standoff voltages, for the components used within the converter. For lower power loss at greater than 400 V, most circuit designers prefer to use insulated-gate bipolar transistors (IGBTs) or the latest silicon carbide (SiC) FETs. These devices can have standoff voltages of up to 1200 V, with lower ON resistance than equivalent Si MOSFETs. These complex power systems often are managed by a digital signal processor, a microcontroller, or a dedicated digital power controller. Thus, they usually require both power and signal isolation from the noisy switching environment of the power stage. Even during steady-state switching cycles, the circuit can see massive changes in both voltage and current that can create significant ground bouncing.

Figure 1. Simplified power flow from wind turbine to grid

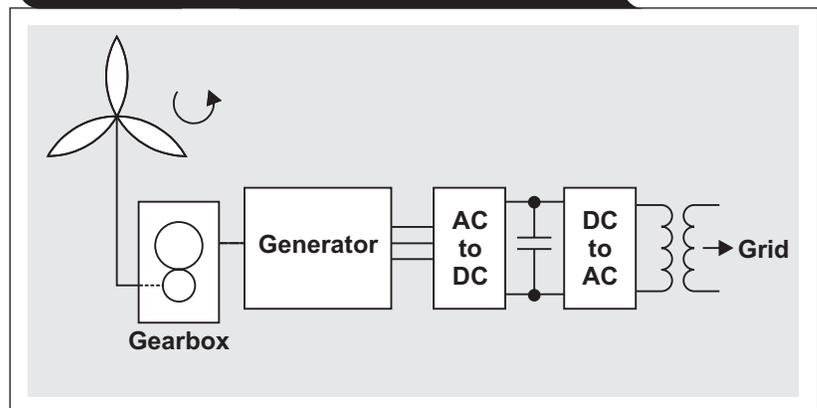


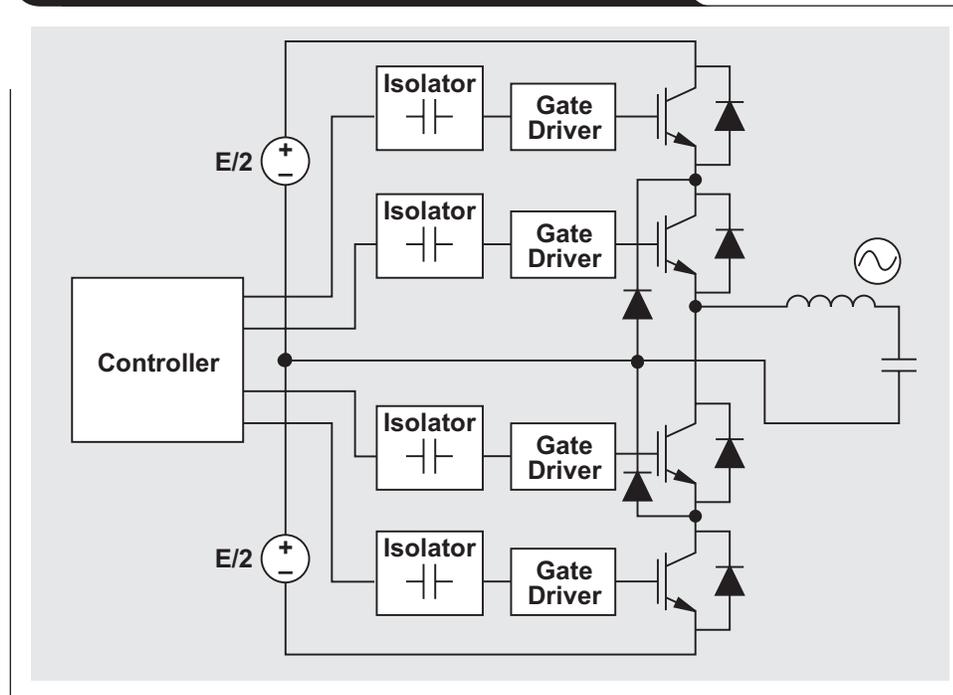
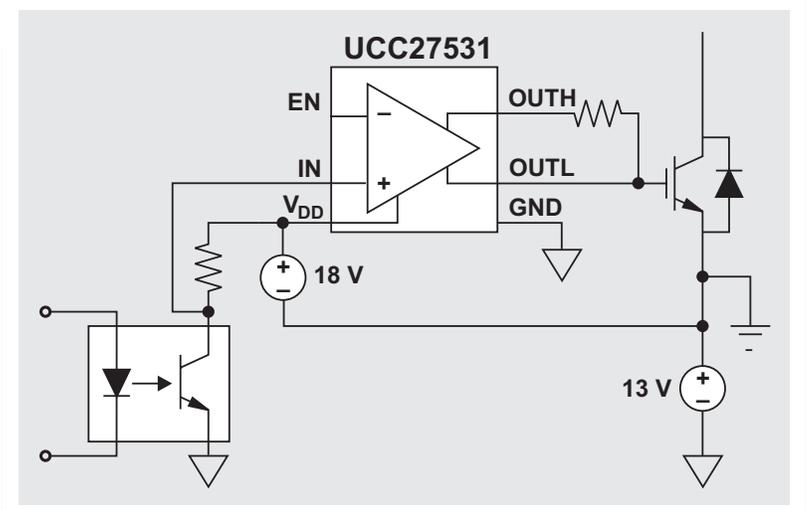
Figure 2. Basic structure of single-phase inverter

Figure 2 shows that even for a single-phase DC-to-AC inverter, there are many gate drivers needed to properly switch the IGBTs in the power stage. As a single-channel gate driver, the Texas Instruments UCC27531 can drive any of the switches in the switch bridge if it has the necessary signal and bias isolation. Signal isolation is achieved by using an optocoupler or digital isolator. For bias isolation, the designer can use a bootstrap circuit with a diode and a capacitor, or an isolated-bias supply. Another option is to connect the gate driver on the same side of the isolation as the controller, then drive the switch through a gate transformer after the gate driver itself. This option allows the driver to be biased with a non-isolated supply on the control side.

Gate drivers in renewable energy

As a small, non-isolated gate driver, the single-channel UCC27531 is a good fit for the environment described. Its input signals to the IC are provided by an optocoupler or digital isolator. Its high supply/output-drive voltage range of 10 to 35 V makes it ideal for 12-V Si MOSFET applications as well as for IGBT/SiC FET applications. Here, a higher positive gate drive is typical, as well as a negative voltage pull-down on shutoff to prevent the power switch from false turn-on. Typically, SiC FETs are driven by a +20/-5-V gate driver relative to the source. Similarly, for IGBTs, system designers may use a +18/-13-V gate drive, for example (see Figure 3).

Figure 3. Driving a power switch with FET/IGBT single-gate drivers

Since the UCC27531 is a rail-to-rail driver, OUTH pulls up the power-switch gate to its V_{DD} of 18 V relative to the emitter. OUTL pulls down the gate to the driver's GND of -13 V relative to the emitter. The driver effectively sees +18 to -13 V, or 31 V from V_{DD} relative to its own GND. Further, the 35-V rating provides a margin to prevent overvoltage failure of the IC due to noise and ringing.

The split output with both OUTH and OUTL permits the user to control the turn-on (sourcing) current and turn-off (sinking) current separately. This helps to maximize efficiency and maintain control of the switching times to

comply with requirements for noise and electromagnetic interference. Further, even with a split output, the single-gate driver maintains a minimum inductance on the output stage, preventing excessive ringing and overshoot. By having an asymmetrical drive (2.5-A turn-on and 5-A turn-off), the UCC27531 is optimized for average switch timing in high-power renewable-energy applications. Further, with the low pull-down impedance, this driver increases reliability by ensuring that the gate does not experience voltage spikes that could lead to false turn-on from the parasitic Miller-effect capacitance between the collector and gate for IGBTs and between the drain and gate for FETs. This internal capacitance can lead the gate to exceed the turn-on threshold voltage by pulling up on the gate when the collector/drain voltage rapidly increases during turn-off of the switch.

The input stage of the UCC27531 is also designed for high-reliability systems like renewable energy. It has a so-called TTL/CMOS input that is independent of the supply voltage, allowing for compatibility with standard TTL-level signals. It provides a higher hysteresis of about 1 V when compared to the usual 0.5-V hysteresis seen in classic TTL. If the input signal is lost and becomes floating for any reason, the output is pulled low. Also, with the large changes in voltage on the GND of the driver IC, it is possible for the input signals to appear negative if the GND bounces high during a switching edge. This driver addresses this concern by handling up to -5 V continuously on the input (IN) or enable (EN) during these events.

The UCC27531 comes in a 3 x 3-mm, industry-standard SOT-23 package, which is very competitive with a discrete two-transistor solution that has a discrete level shifter without negative-input capability or added protections. Beyond the obvious space savings, integrating the UCC27531's functions into a single IC package increases the system's overall reliability.

This single-channel driver is an attractive option because it can be located very close to the power-switch gate. Placement is more flexible than for a combination high-side/low-side gate driver in a single IC. This flexibility helps minimize the inductance between the driver and

power switch and gives the designer better control of the switch's gate. Figure 2 shows how many high-power switches are in just a single phase of a DC-to-AC stage. Over a complete three-phase system with multiple conversions between DC and AC and back, and with boost stages of DC-to-DC conversion also needed in some applications, there becomes a need for many gate drivers. Each one must be strategically placed on the PCB to ensure a proper design.

Conclusion

In renewable-energy applications, conversion of power generated from solar arrays and wind turbines presents unique challenges to the system designer. These challenges include high voltages and power levels, meeting safety and reliability requirements, and the overall complexity of the completely interconnected system. Although gate drivers for power switches seem like a small part of the total system control and power flow, they are actually very important to the overall design performance.

References

1. F. Blaabjerg et al., "Power electronics and reliability in renewable energy systems," presented at 21st IEEE International Symposium on Industrial Electronics, Hangzhou, China, May 28–31, 2012.
2. Veda Prakash Galigekere and Marian K. Kazimierczuk. (year, month). "Role of power electronics in renewable energy systems" [Online]. Available under "White Papers" at www.magnelab.com
3. Bob Calanan. (2011, Jan.). "Application considerations for silicon carbide MOSFETs" [Online]. Available under "Power Application Notes" at www.cree.com/power/document-library

Related Web sites

Power Management:

www.ti.com/power-aaaj

www.ti.com/ucc27531-aaaj

Subscribe to the AAJ:

www.ti.com/subscribe-aaaj

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page

support.ti.com

TI E2E™ Community Home Page

e2e.ti.com

Product Information Centers

Americas	Phone	+1(512) 434-1560
Brazil	Phone	0800-891-2616
Mexico	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

Phone	
European Free Call	00800-ASK-TEXAS (00800 275 83927)
International	+49 (0) 8161 80 2121
Russian Support	+7 (4) 95 98 10 701

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	www.ti.com/asktexas
Direct Email	asktexas@ti.com

Japan

Phone	Domestic	0120-92-3326
Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

Asia

Phone	
International	+91-80-41381665
Domestic	<u>Toll-Free Number</u>
Note: Toll-free numbers do not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	1-800-425-7888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
Fax	+8621-23073686
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A090712

E2E is a trademark of Texas Instruments. All other trademarks are the property of their respective owners.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com