


# AC cycle skipping improves PFC light-load efficiency

By Bosheng Sun  
Systems Engineer

For power supplies with an input power of 75 watts or greater, power factor correction (PFC) is usually required. It forces the input current to follow the input voltage, so that any electrical load appears like a resistor to the voltage source that powers it. This is essential for many server, telecommunications and industrial applications, where energy efficiency and power quality have become more and more strict. The most important criteria to judge PFC performance is efficiency, total harmonic distortion (THD), and power factor (PF). With the help of new semiconductor devices and new control methods, the modern PFC circuit has achieved very good performance at middle and heavy loads. However, during light-load conditions, the efficiency, THD and PF deteriorate significantly.

A typical PFC efficiency curve is shown in Figure 1. Notice how the efficiency gets lower and lower at light loads. This is because the switching loss, driving loss, and reverse-recovery loss of semiconductor components become dominant at light loads. Meanwhile, a PFC may transition from continuous-conduction mode (CCM) to discontinuous-conduction mode (DCM), which causes

**Figure 1. Example of a typical PFC efficiency curve**

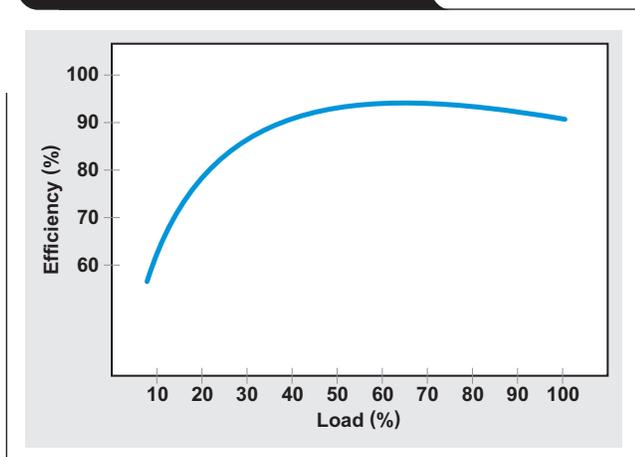


the converter dynamics to change abruptly and the current-loop bandwidth to reduce significantly. The small current-feedback signal also makes control very difficult. As a result, the THD of the current waveform increases (Figure 2).

This article provides a novel method to increase efficiency and reduce THD when the PFC enters the light-load condition. In this method, when the load is reduced to less than a predefined threshold, the PFC enters a special burst-mode. In this mode, depending on the load, one or more AC cycles are skipped by the PFC. In other words, the PFC turns off for one or more AC cycles, and turns back on for the next AC cycle. The turn-on/turn-off instance is at the AC zero-crossing, such that the whole AC cycle is skipped. Moreover, since PFC turn-on/turn-off occurs when the current equals zero, less stress and electromagnetic interference (EMI) noise are generated. This is different than the traditional PWM pulse-skipping burst-mode, where the PWM pulses are skipped randomly.

The number of AC cycles to be skipped is inversely proportional to the load. If the load continues to decrease below the threshold, additional AC cycles will be skipped.


**Figure 2. Example of a typical PFC THD curve**

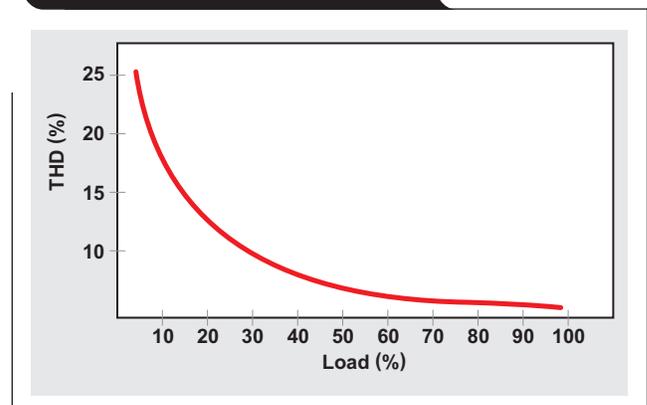

A look-up table can be generated with the load versus the number of cycles to be skipped. This table will show the maximum number of AC cycles can be skipped while maintaining the output voltage ripple within a specified range. Figure 3 shows four different AC cycles that are skipped at different loads.

Once the PFC turns off, the switching loss, driving loss, and reverse-recovery loss are all reduced to zero, and the power loss is just the PFC stand-by power. Since the current is zero, THD is zero. When the PFC turns on, it delivers more than the power required by a light load because it needs to compensate for the turn-off period. Because

**Figure 3. AC cycles being skipped at different loads**

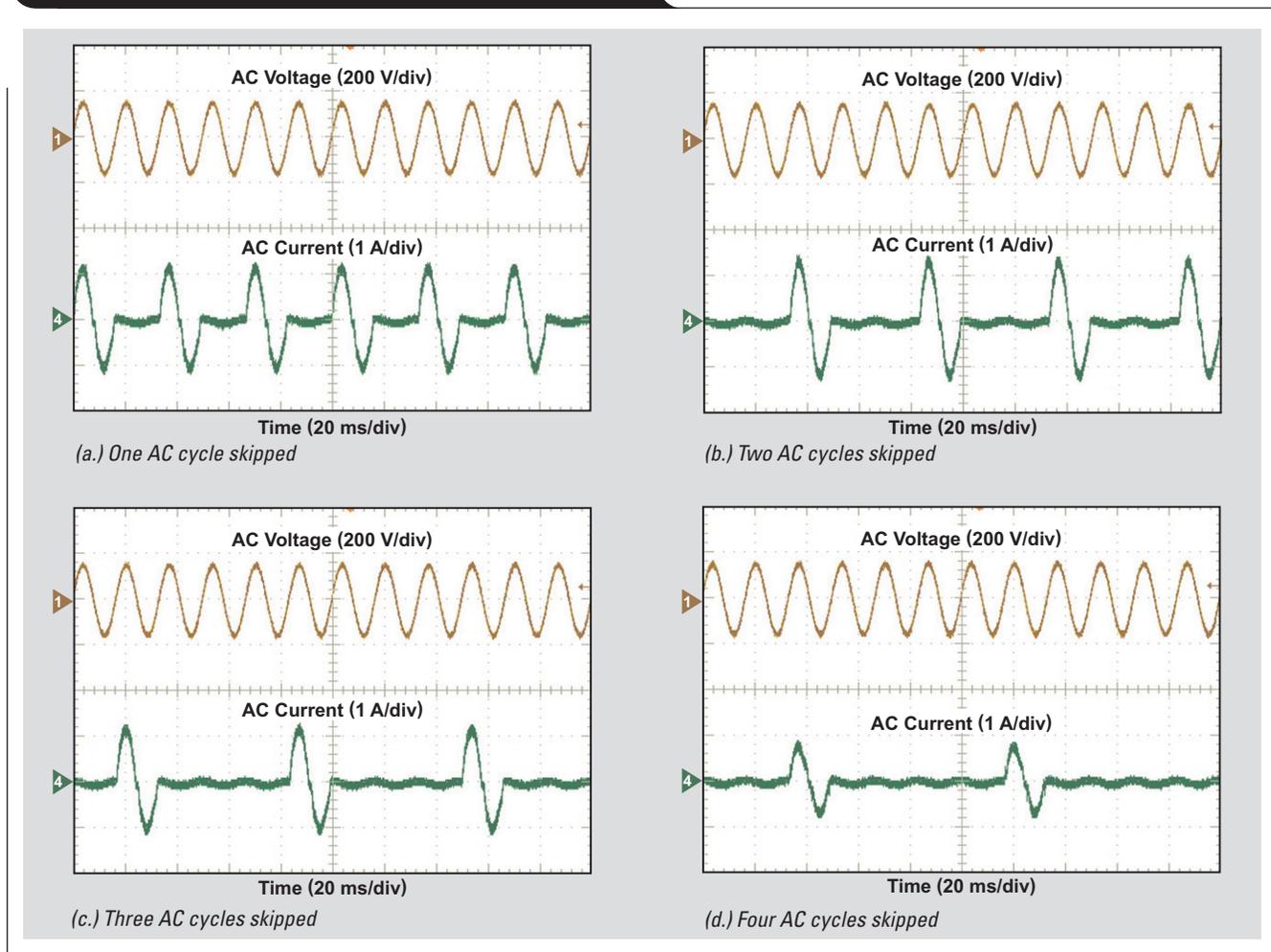

the PFC now operates at middle load or completely shuts off to skip AC cycles, the light-load efficiency is increased and THD is reduced. Figures 4 and 5 show the efficiency and THD improvements with this special burst-mode.


Note that when PFC turns off to skip AC cycles, both the current loop and voltage loop need to be frozen. Otherwise, the integrators in these loops build up to generate a big PWM pulse when the PFC turns back on, which causes a large current spike.

To determine whether or not the PFC enters the light-load condition, the load information needs to be monitored. Normally there is no current sensor at the PFC output, so to directly measuring output load is not


feasible. However, the PFC voltage-loop output is proportional to the load when  $V_{IN}$  is fixed. Therefore, the loop output can be used as a rough indicator to determine whether or not the PFC is operating with a light load.


If there is a requirement for the precise number of AC cycles to be skipped in order to maintain the output voltage ripple within a specified range, accurate load information is required. Since there is a current shunt measuring input current for PFC current-loop regulation, the input power of a PFC can be measured. The input current and voltage can be monitored by analog-to-digital converters (ADCs), and then used to calculate the real input power. This accurate input-power information can be used to

**Figure 4: Efficiency comparison**

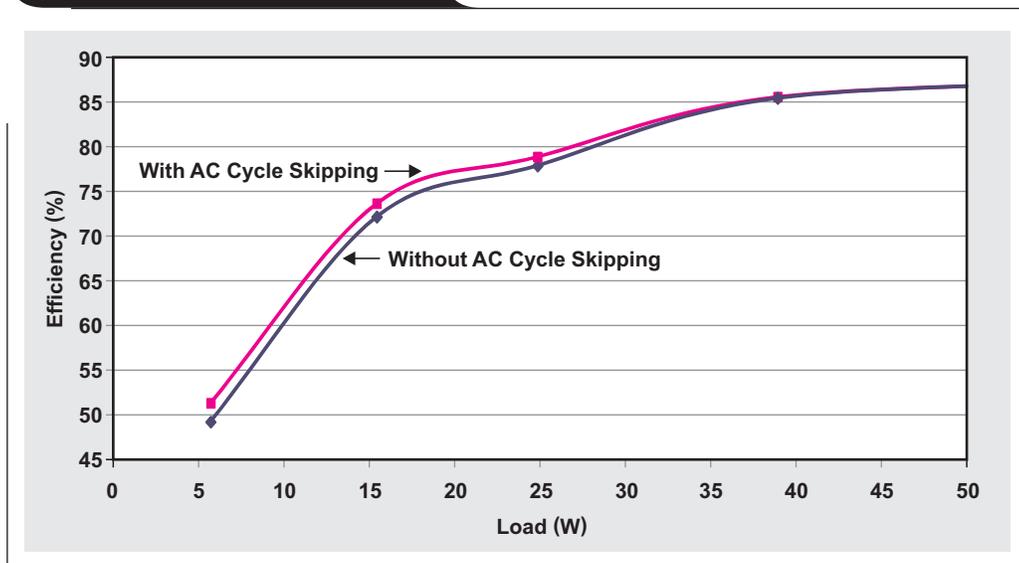

**Figure 5: THD comparison**

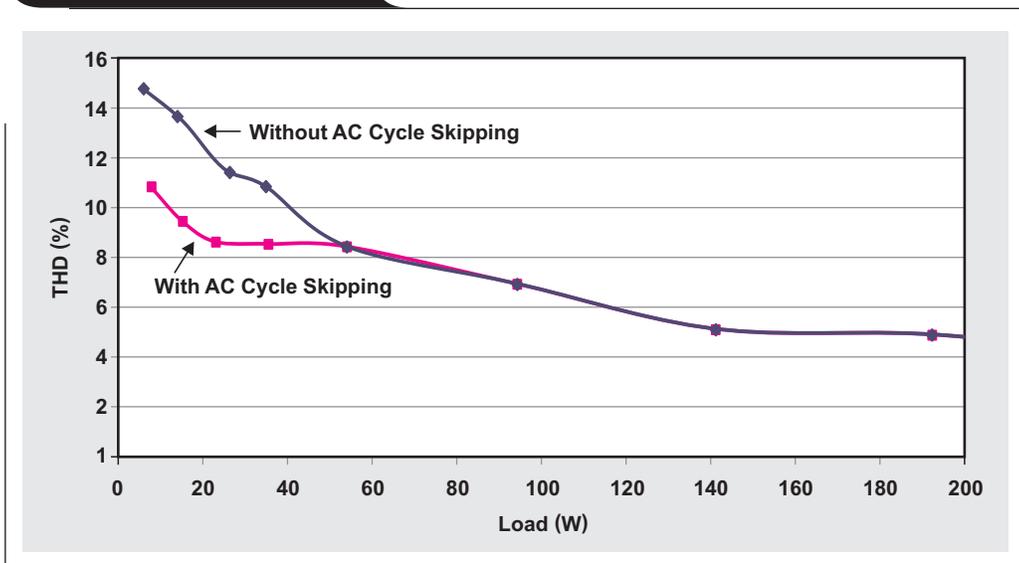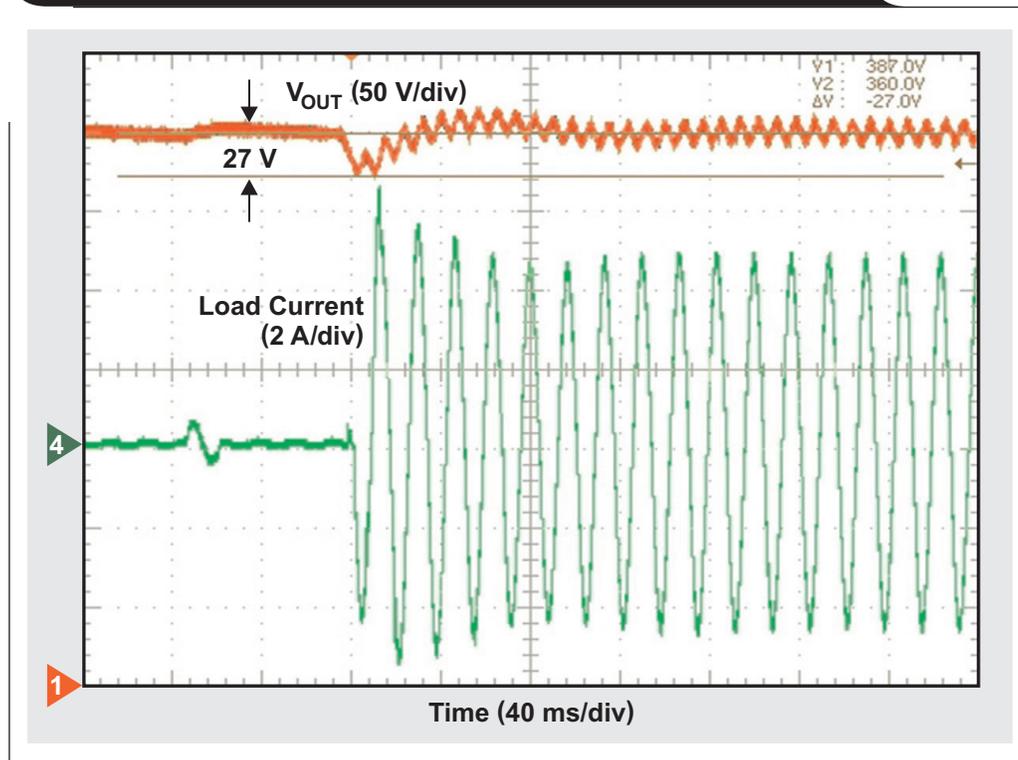

**Figure 6. Load transient from zero to 100% during AC cycle skipping**


precisely adjust the number of AC cycles to be skipped. There is no need for any extra hardware. For details of accurate PFC input-power measurement, please see Reference 1.

A big concern of this approach is the output voltage drop during a load transient. Assuming a load step-up occurs when the PFC is off,  $V_{OUT}$  may drop too much. To address this issue,  $V_{OUT}$  is compared with a predefined threshold through a comparator. Once  $V_{OUT}$  is below this threshold, the PFC will immediately exit the burst mode, AC cycle skipping is disabled, and the PFC returns to normal operation. It will handle transient response as if there is no special burst mode. Figure 6 shows the effects of a load transient from 0 to 100% during AC cycle skipping. Note that the  $V_{OUT}$  drop during the transient is only 27 V, which is very normal for a 360-W PFC.

## Conclusion

A novel PFC burst mode allows one or more AC cycles to be skipped when a PFC operates with a light load. As a result, both efficiency and THD are improved. Moreover,

since the PFC turns on/off at AC zero-crossing, circuit stress and EMI noise are reduced. The number of AC cycles to be skipped can be precisely adjusted based on load to maximize performance and maintain the output voltage ripple within a specified range. If a load transient occurs when the PFC is off, the burst mode is disabled immediately and the PFC handles the effects of the load transient normally. Finally, the implementation is easy with a digital controller, and no extra hardware is needed.

## References

1. Bosheng Sun, "Low-cost solution for measuring input power and RMS current," Analog Applications Journal, Texas Instruments, 4Q 2013. Available: [www.ti.com/3q14-SLYT545](http://www.ti.com/3q14-SLYT545)

## Related Web sites

[www.ti.com/3q14-UCD3138](http://www.ti.com/3q14-UCD3138)

Subscribe to the AAJ:

[www.ti.com/subscribe-aaaj](http://www.ti.com/subscribe-aaaj)

## TI Worldwide Technical Support

### Internet

#### TI Semiconductor Product Information Center Home Page

support.ti.com

#### TI E2E™ Community Home Page

e2e.ti.com

### Product Information Centers

<b>Americas</b>	Phone	+1(512) 434-1560
<b>Brazil</b>	Phone	0800-891-2616
<b>Mexico</b>	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

#### Europe, Middle East, and Africa

Phone		
European Free Call	00800-ASK-TEXAS (00800 275 83927)	
International	+49 (0) 8161 80 2121	
Russian Support	+7 (4) 95 98 10 701	

**Note:** The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	www.ti.com/asktexas
Direct Email	asktexas@ti.com

#### Japan

Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

#### Asia

Phone	<u>Toll-Free Number</u>
<b>Note:</b> Toll-free numbers may not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	000-800-100-8888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
International	+86-21-23073444
Fax	+86-21-23073686
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

**Important Notice:** The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A021014

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)