

# Designing an anti-aliasing filter for ADCs in the frequency domain


By Bonnie C. Baker

Senior Applications Engineer

## Introduction

Data acquisition (DAQ) systems are found across numerous applications where there is an interest to digitize a real-world signal. These applications can range from measuring temperatures to sensing light. When developing a DAQ system, it is usually necessary to place an anti-aliasing filter before the analog-to-digital converter (ADC) to rid the analog system of higher-frequency noise and signals. Figure 1 shows the general circuit diagram for this type of application.

Figure 1. Basic topology of a DAQ circuit

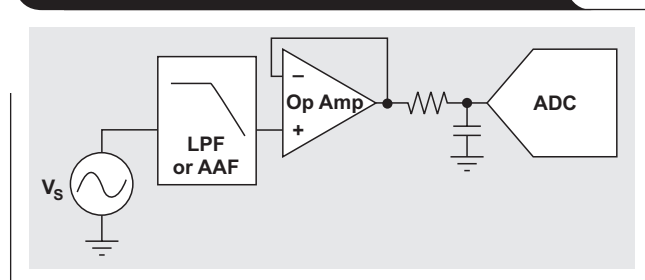

The DAQ system starts with a signal, such as a waveform from a sensor,  $V_s$ . Next is the low-pass filter (LPF) or anti-aliasing filter (AAF) and the operational amplifier (op amp) configured as a buffer. At the output of the buffer amplifier is a resistor/capacitor pair that drives the ADC's input. The ADC is a successive-approximation-converter ADC (SAR ADC).


Typically, evaluations of this type of circuit consist of the offset, gain, linearity, and noise. Another perspective in evaluation involves the placement of events in the frequency domain.

There are six frequencies that impact the design of this system:

1.  $f_{\text{SIGNAL}}$  – Input signal bandwidth
2.  $f_{\text{LSB}}$  – Filter frequency with a tolerated gain error that has a desired number of least significant bits (LSBs). It is preferable that  $f_{\text{LSB}}$  is equal to  $f_{\text{SIGNAL}}$
3.  $f_c$  – LPF corner frequency
4.  $f_{\text{PEAK}}$  – Amplifier maximum full-scale output versus frequency
5.  $f_s$  – ADC sampling frequency
6.  $f_{\text{GBW}}$  – Amplifier gain bandwidth frequency

Figure 2 shows the general relationship between these frequencies.

Figure 2. Basic relationship of  $f_s$ ,  $f_{\text{GBW}}$ ,  $f_{\text{PEAK}}$ , and  $f_c$

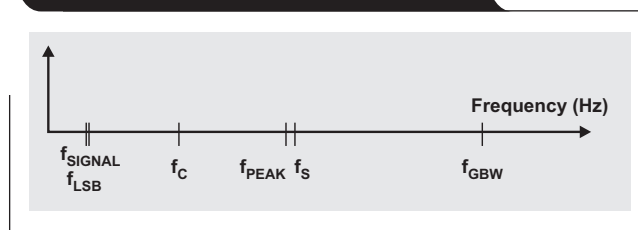

For the following evaluation, the example system uses the following throughout:

- Input signal bandwidth of 1 kHz ( $f_{\text{SIGNAL}}$ )
- Low-pass filter corner frequency of 10 kHz ( $f_c$ )
- SAR-ADC sampling frequency of 100 kHz ( $f_s$ )
- Dual operational amplifier, single-supply OPA2314

## Determine maximum signal frequency ( $f_{\text{SIGNAL}}$ , $f_{\text{LSB}}$ ) and acceptable gain error

The first action is to determine the bandwidth of the input signal ( $f_{\text{SIGNAL}}$ ). Next, determine the magnitude of the acceptable gain error from the LPF or AAF<sup>[1]</sup>. This gain error does not occur instantaneously at the frequency that is chosen to be measured. Actually, at DC, this gain error is zero. The LPF gain error progressively gets larger with frequency. An LSB error in dB equals

$$20 \times \log [(2^N - \text{err})/2^N],$$

where  $N$  is the number of converter bits and the whole number,  $\text{err}$ , is the allowable bit error. This error is found by examining the SPICE closed-loop gain curve.

In this example, the signal bandwidth is 1 kHz and acceptable gain error is equal to one code, which is equivalent to 1 LSB. For a 12-bit ADC where  $\text{err}$  equals 1 and  $N$  equals 12, the gain error equals  $-2.12$  mdB.

Using a TINA-TI™ SPICE model to analyze a fourth-order, 10-kHz low-pass Butterworth filter, the closed-loop gain response is shown in Figures 3 and 4. In both figures, the location of the “b” cursor identifies the point where gain error is  $-2$  dB ( $f_{1-LSB} = 1.04$  kHz).

In Figure 3, the measurement window shows that the marker at “b” is at 1.04 kHz. The window also shows the  $-2$  dB<sup>[2]</sup> difference between frequency markers “a” and “b” on the y-axis.

Figure 4 zooms in on the y-axis of the Butterworth filter’s action before the filter passes through its corner frequency ( $f_C$ ). The first observation of this response is that the gain curve has a slight up-shoot before it begins to slope downwards. This upward peak reaches a magnitude of approximately  $+38$  dB. This is a fundamental characteristic of a fourth-order, Butterworth low-pass filter.

If a higher gain error is acceptable, Table 1 shows the change in  $f_{1-LSB}$ , versus the LSB value.


**Table 1. LSB error versus  $f_{1-LSB}$**

LSB error (LSB)	LSB error (dB)	$f_{1-LSB}$
1	-0.002	1.04 kHz
2	-0.004	1.47 kHz
3	-0.006	1.82 kHz
4	-0.008	2.11 kHz


### Filter corner frequency ( $f_C$ )

Note that the corner frequency ( $f_C$ ) of the low-pass filter at the frequency where the attenuation of closed-loop frequency response is  $-3$  dB. If a fourth-order LPF is chosen,  $f_C$  is approximately ten times higher than  $f_{1-LSB}$ . SPICE simulations with the WEBENCH® Filter Designer allows this value to be determined quickly. When designing a single-supply filter in the filter designer, select the multiple-feedback (MFB) topology, which exercises the amplifiers with a static DC common-mode voltage that is at mid-supply. Figure 5 shows a circuit diagram of this fourth-order, 10-kHz Butterworth LPF.


**Figure 3. Gain error at 1.04 kHz equals  $-2$  dB of a fourth-order, 10-kHz Butterworth LPF**

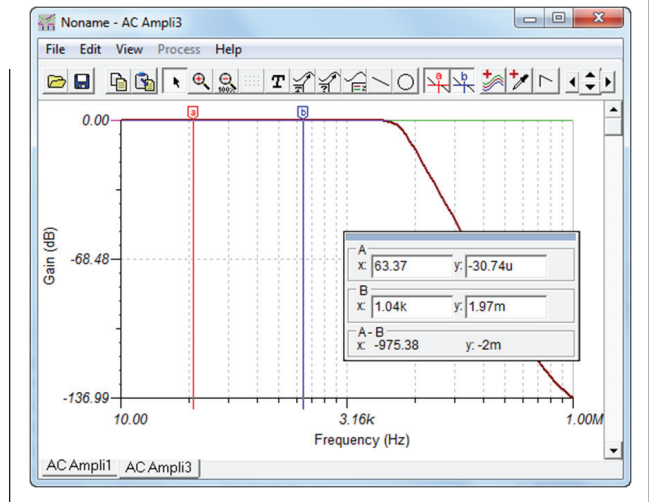

**Figure 4. Closed-loop gain response of a fourth-order, 10-kHz Butterworth filter**

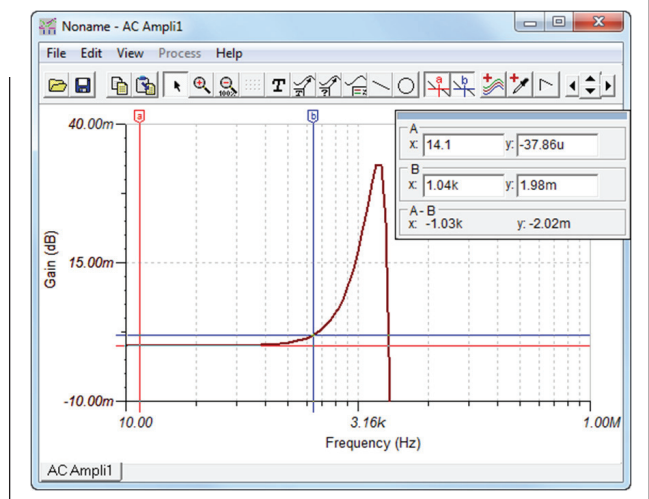

**Figure 5. Fourth-order, Butterworth LPF with  $f_C = 10$  kHz**

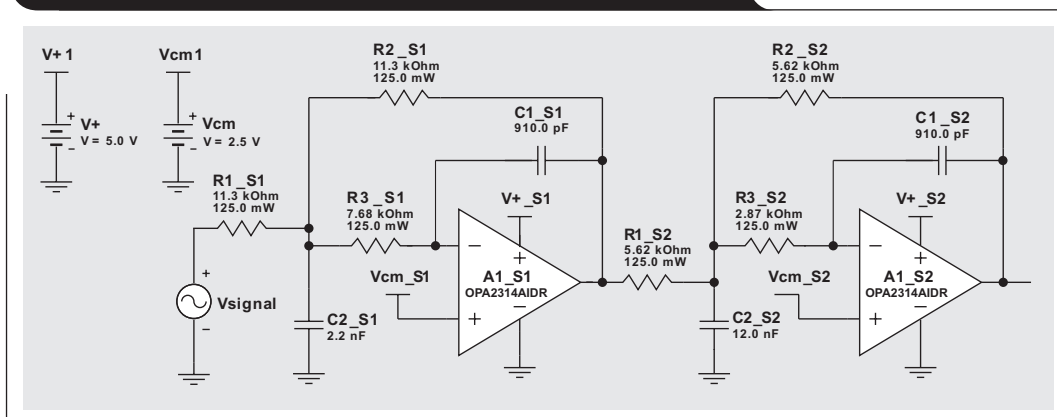

## Define the amplifier's gain bandwidth frequency ( $f_{GBW}$ )

The low-pass filter's Q factor, gain (G), and corner frequency ( $f_C$ ) determine the amplifier's minimum allowable gain bandwidth ( $f_{GBW}$ ). When finding the Q factor, first identify the type of filter approximation (Butterworth, Bessel, Chebyshev, etc.) and the filter order<sup>[2]</sup>. As previously specified, the corner frequency is 10 kHz. In this example, the filter approximation is Butterworth and the gain is 1 V/V. Finally, this is a fourth-order filter. The determination of the gain bandwidth of the amplifier is:

$$f_{GBW} = 100 \times Q \times G \times f_C \quad (1)$$

In this system,  $f_{GBW}$  must be equal to or greater than 1.31 MHz (as verified by WEBENCH Filter Designer). The gain bandwidth of the OPA2314 dual amplifier is 2.7 MHz.

## Amplifier's maximum full-scale output


In most applications, it is imperative that the amplifier is capable of delivering its full-scale output. This may or may not be true. One check is to get a rough estimate from the amplifier's slew-rate specification.

A conservative definition of the maximum output voltage per frequency for an amplifier is equal to approximately  $f_{PEAK} = SR / (V_{PP} \times \pi)$ , where SR is the amplifier's datasheet slew rate and  $V_{PP}$  is the peak-to-peak specified output swing. Note that the amplifier's rise and fall times may not be exactly equal. So the slew-rate specification of the datasheet is an estimate.

The datasheet slew rate of the OPA2314 amplifier is 1.5 V/ $\mu$ s and in the 5.5-V system,  $V_{PP}$  equals 5.46 V. While the amplifier is in the linear region, the rail-to-rail output with a 5.5-V power supply is equal to 5.46 V. Figure 6 shows the tested behavior of the OPA2314 with an output range that goes beyond the linear region of the amplifier.

The calculated maximum output voltage of the OPA2314 occurs at approximately 87.5 kHz. However, in Figure 6, the maximum value with bench data is shown to be approximately 70 kHz. This discrepancy exists because of

**Figure 6. OPA2314 maximum output voltage**

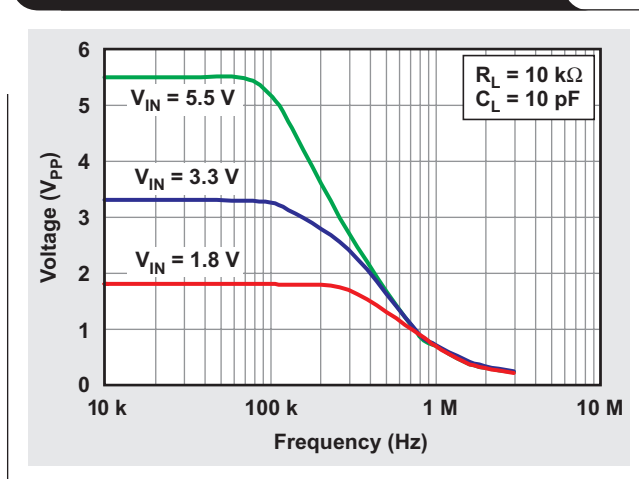

the mismatches between the amplifier rise and fall times and the responsiveness of the amplifier at the peaks and valleys of the sinusoidal input voltage swing.

## SAR-ADC sampling frequency

The challenge now is to identify the sampling frequency of the SAR ADC. Given a 1-kHz maximum input signal, it is imperative that the SAR ADC samples the signal more than one cycle per second. Actually, over ten times is preferable. This implies that a 10-kHz sampling ADC will work.

Additionally, it is important to eliminate signal-path noise when possible. If the SAR ADC is converting at higher frequencies above the corner frequency of the filter, that portion of the noise will not be aliased back into the system. Consequently, a 100-kHz sampling SAR ADC meets the requirements.

If the sampling frequency is 100 kHz, the Nyquist frequency is 50 kHz. At 50 kHz, the frequency response of the low-pass filter is down by approximately 50 dB. This level of attenuation limits the impact on noise going through the system.

## Conclusion

The development of a DAQ system in the frequency domain can present interesting challenges. A system consisting of a filter and a SAR ADC is usually evaluated with the performance specifications of the DC- and AC-amplifier and the converter. This article, however, evaluated the system's signal path from a frequency perspective.

The important frequency specifications are the signal bandwidth, filter corner frequency, amplifier bandwidth, and converter sampling speed. Even though the signal bandwidth is small, 1 kHz, the required AAF corner frequency should be 10 times higher than the signal bandwidth in an effort to reduce high-frequency gain errors. Additionally, the converter's sampling frequency is higher than expected in an effort to reduce complications caused by noise aliasing.

## References

1. Bonnie Baker, "Analog filters and specifications swimming: Mapping to your ADC," On Board with Bonnie, TI Blog, Nov 5, 2014.
2. Bonnie Baker, "Analog Filters and Specification Swimming: Selecting the right bandwidth for your filter," On Board with Bonnie, TI blog, Nov 8, 2013.

## Related Web sites

TINA-TI™ WEBENCH® tool:

[www.ti.com/tina-ti](http://www.ti.com/tina-ti)

Product information:

[www.ti.com/OPA2314](http://www.ti.com/OPA2314)

Subscribe to the AAJ:

[www.ti.com/subscribe-aaaj](http://www.ti.com/subscribe-aaaj)

## TI Worldwide Technical Support

### Internet

#### TI Semiconductor Product Information Center Home Page

support.ti.com

#### TI E2E™ Community Home Page

e2e.ti.com

### Product Information Centers

<b>Americas</b>	Phone	+1(512) 434-1560
<b>Brazil</b>	Phone	0800-891-2616
<b>Mexico</b>	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

#### Europe, Middle East, and Africa

Phone		
European Free Call	00800-ASK-TEXAS (00800 275 83927)	
International	+49 (0) 8161 80 2121	
Russian Support	+7 (4) 95 98 10 701	

**Note:** The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	www.ti.com/asktexas
Direct Email	asktexas@ti.com

#### Japan

Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

#### Asia

Phone	<u>Toll-Free Number</u>
<b>Note:</b> Toll-free numbers may not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	000-800-100-8888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
International	+86-21-23073444
Fax	+86-21-23073686
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

**Important Notice:** The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A021014

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)