

Measuring the linear operating region of instrumentation amplifiers

By Pete Semig, Analog Applications Engineer, Precision Amplifiers
 Collin Wells, Analog Applications Engineer, Precision Amplifiers

Introduction

There are numerous publications from the past two years that discuss the theoretical linear operating region of instrumentation amplifiers. The publications cover the three primary topologies of instrumentation amplifiers: three-op-amp,^[1] two-op-amp,^[2] and two-op-amp with gain stage,^[3] which are shown in Figure 1.

Figure 1. Topologies for instrumentation amplifiers



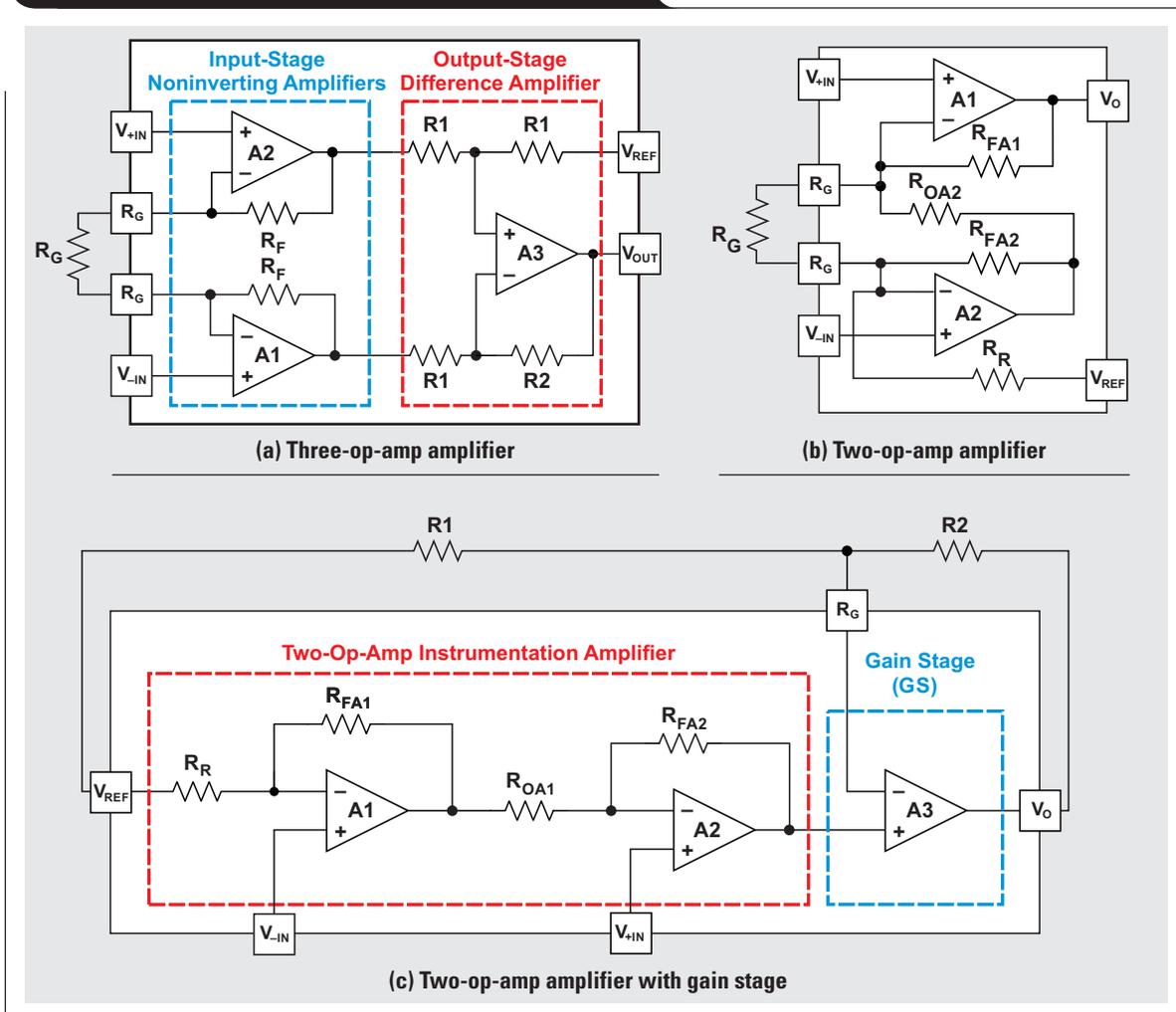



Figure 2. V_{CM} vs. V_{OUT} plots for three topologies

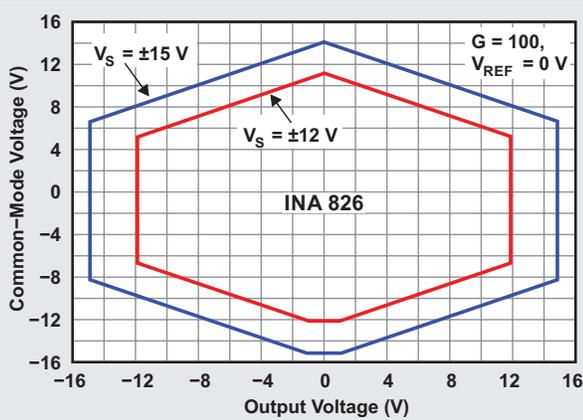

(a) Three-op-amp amplifier

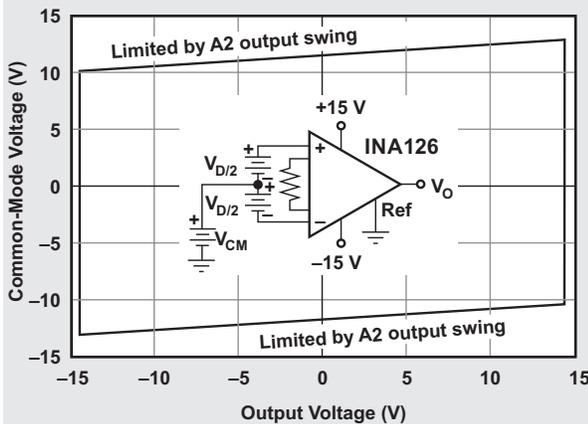

(b) Two-op-amp amplifier

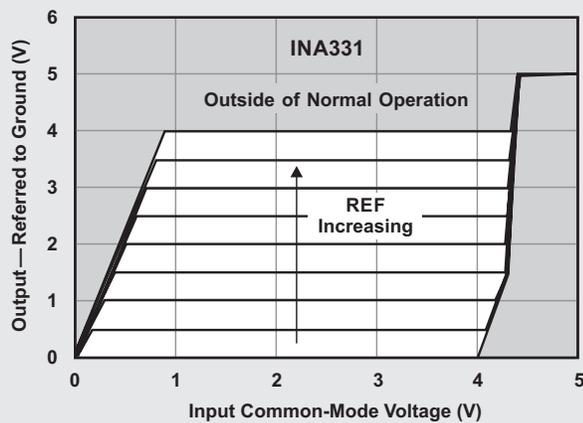


(c) Two-op-amp amplifier with gain stage

Each publication derives the node equations that define the linear operating region of the device, which is represented by a plot of common-mode voltage (V_{CM}) versus output voltage (V_{OUT}). In addition to topology, the V_{CM} vs. V_{OUT} plot depends on supply voltage, gain (G), and reference voltage (V_{REF}). Example plots for each topology are shown in Figure 2.

While plots for commonly used circuit configurations are usually included in the devices' data sheets, systems may have other requirements. Given the complex nature of the linear operating region and limited selection of plots in instrumentation-amplifier data sheets, an easy-to-use software tool is necessary. Therefore, the stand-alone downloadable V_{CM} vs. V_{OUT} Calculator tool was developed to enable designers to generate V_{CM} vs. V_{OUT} plots for many different instrumentation amplifiers based on topology, supply voltage, gain, and reference voltage. Figure 3 depicts the graphical user interface for the software tool.

Figure 3. Downloadable V_{CM} vs. V_{OUT} calculator

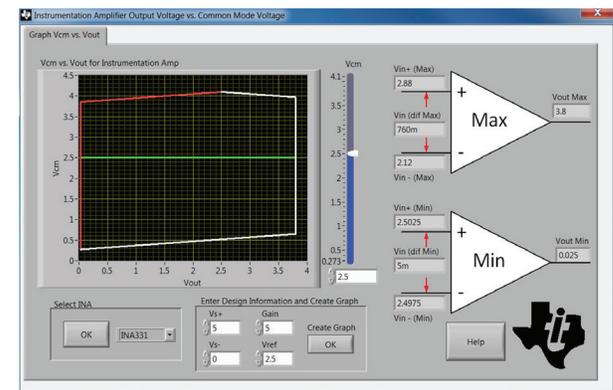

To reinforce the understanding of the linear operating region of instrumentation amplifiers, this article focuses on the correlation of theoretical and measured results. The linear operating region of instrumentation amplifiers was measured and compared to theoretical results.

Measurement system

To create a V_{CM} vs. V_{OUT} plot for an instrumentation amplifier, the measurement tool must be able to vary the instrumentation amplifier's common-mode input voltage and the differential input voltage (V_{DIFF}) while monitoring the output voltage.

To detect small deviations in the linearity of the output signal, the system must have an accuracy that is greater than or equal to the linearity specification of the instrumentation amplifier under test. The typical input-stage nonlinearity of an instrumentation-amplifier is in the range of 0.05% to 0.001%, which defines the accuracy requirement for the measurement system. Furthermore, the gain and offset errors of the instrumentation amplifier must be removed at each common-mode voltage to identify only the linearity error.

Measurement system hardware

There are three main requirements of the measurement system hardware. First, three power supplies are required to control the supply voltages (V_+ , V_-) and V_{REF} of the instrumentation amplifier.

Secondly, two accurate, high-resolution voltage sources are required for controlling the instrumentation-amplifier V_{DIFF} and V_{CM} voltages. The first source controls the common-mode voltage by connecting between GND and the negative input ($-IN$) of the instrumentation amplifier. The second source controls the differential voltage by connecting between the $-IN$ and $+IN$ inputs. This setup allows for fine control of the V_{DIFF} voltage and course/fine control of the V_{CM} voltage.

The third requirement is for high-accuracy voltmeters to monitor the V_{DIFF} and V_{OUT} voltages. The highest precision DC voltmeters available should be used to accurately monitor V_{DIFF} and V_{OUT} . Monitoring the input voltage accurately is extremely important because most voltage sources lack the accuracy to control the input to levels less than the linearity of the instrumentation amplifier. A meter is not required for V_{REF} because when V_{DIFF} is set to zero, V_{OUT} will equal V_{REF} plus the offset voltage of the instrumentation amplifier, which is calibrated at each V_{CM} voltage level. Figure 4 shows a circuit representation of the V_{CM} vs. V_{OUT} test system.

Measurement-system software

The measurement-system software automates the generation of the V_{CM} vs. V_{OUT} plots for different configurations of instrumentation amplifiers. The software controls the V_{DIFF} voltages to produce V_{OUT} voltages over the full power-supply range and monitors for deviations greater than the data-sheet nonlinearity specification. The software performs this function at each desired V_{CM} level. The system selects appropriate input voltages based on the gain, power supply, and reference voltage. A binary search algorithm intelligently manipulates the inputs to determine the final output voltage within the programmed linearity specification. A simplified flow chart for the software system is shown in Figure 5.

Figure 4. Circuit schematic depicting the V_{CM} vs. V_{OUT} measurement system


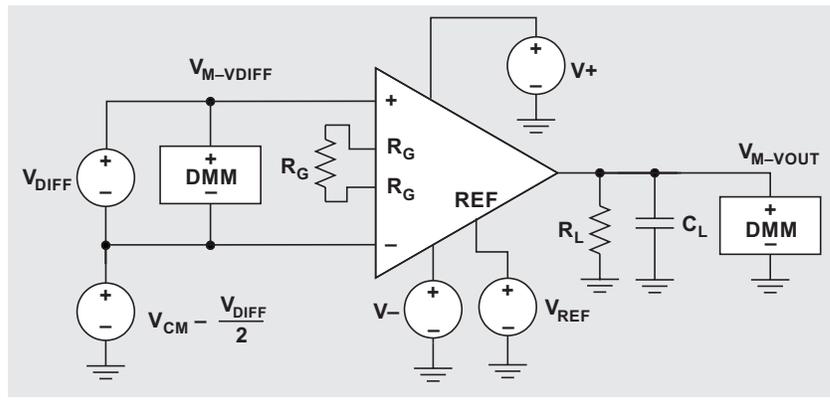


Figure 5. Simplified flowchart of measurement-system software

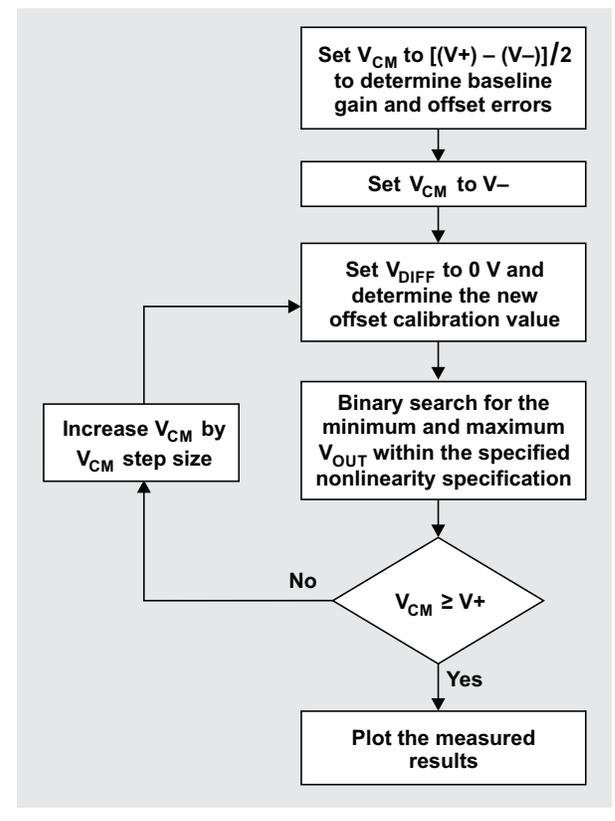

Summary of Results

Using the measurement system, the linear operating region of multiple instrumentation amplifiers was measured to verify correlation with theoretical results. Figure 6 shows the results for a three-op-amp instrumentation amplifier. Figure 7 depicts the results for a two-op-amp instrumentation amplifier.

Notice that both Figure 6 and Figure 7 have very high correlation between theoretical and measured results. Figure 8 depicts the results for a two-op-amp with gain-stage instrumentation amplifier.

While Figure 8 shows high correlation between the V_{CM} Calculator and data-sheet results, notice that there are some regions where the measured results extend beyond the theoretical results. These instances are especially apparent near the minimum and maximum output voltages. There are many possible reasons for this, including process shift, temperature, load current, and so on.

Note that the V_{CM} vs. V_{OUT} plot(s) in instrumentation-amplifier data sheets are considered typical specifications, which represent approximately 68% of all devices. While it is possible to obtain a device whose measured linear operating region is a superset of that shown in the data sheet, the opposite is also possible. There are a couple such regions shown in Figure 8. Therefore, it is good design practice to operate well within the linear operating region of the instrumentation amplifier as shown in Figure 9 on the following page.

Figure 6. Measured and theoretical results for three-op-amp topology

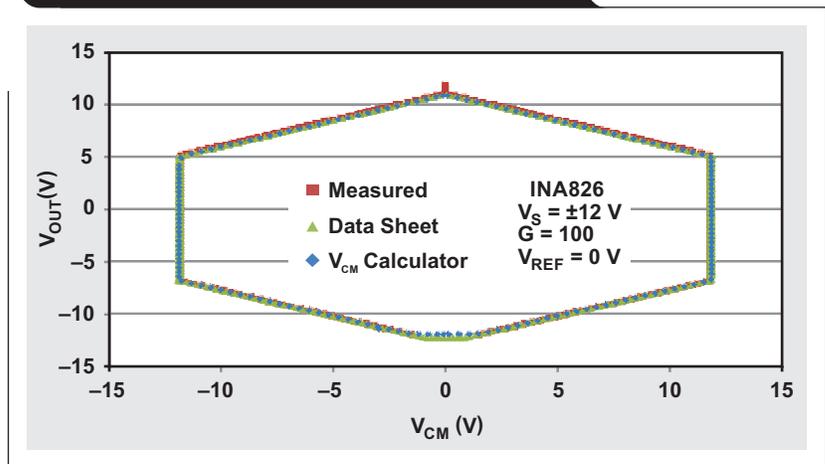


Figure 7. Measured and theoretical results for two-op-amp topology


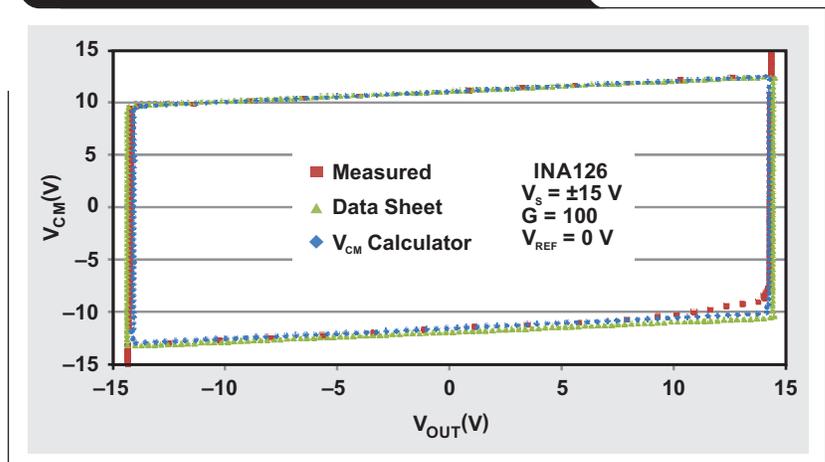


Figure 8. Measured and theoretical results for two-op-amp with gain-stage topology

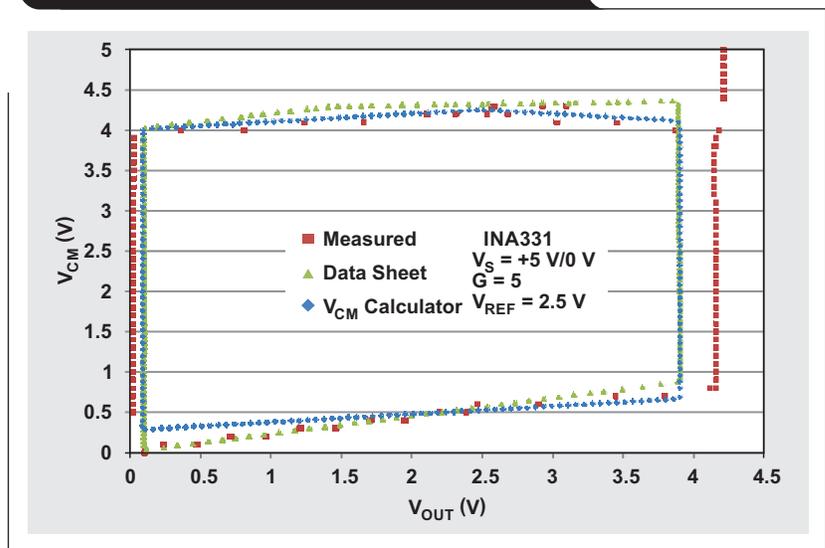

Conclusion

This article verified the theoretical linear operating region of the three most common topologies of instrumentation amplifiers by presenting a sophisticated measurement system for V_{CM} vs. V_{OUT} plots. The measured results correlate well with the theoretical linear operating region. This correlation supports using the V_{CM} vs. V_{OUT} Calculator to determine the linear operating region of instrumentation amplifiers with atypical configurations. To simplify the task of identifying the linear operating regions of instrumentation amplifiers in future designs, regularly download and install V_{CM} vs. V_{OUT} Calculator. Finally, be sure to operate well within the plot to account for variations over process and temperature.

References

1. Peter Semig and Collin Wells, "Instrumentation amplifier V_{CM} vs. V_{OUT} plots," Part 1, Part 2 and Part 3, EDN Network, December 2014
2. Peter Semig, " V_{CM} vs. V_{OUT} plots for instrumentation amplifiers with two op amps," Analog Applications Journal (SLYT647), 4Q 2015
3. Peter Semig, "Linear operating region of two-op-amp instrumentation amplifiers with gain stages," Analog Applications Journal (SLYT683), 3Q 2016

Related Web sites


Software tool:

V_{CM} vs. V_{OUT} Calculator

Product information:

INA826, INA126, INA331

Figure 9. Recommended operating region

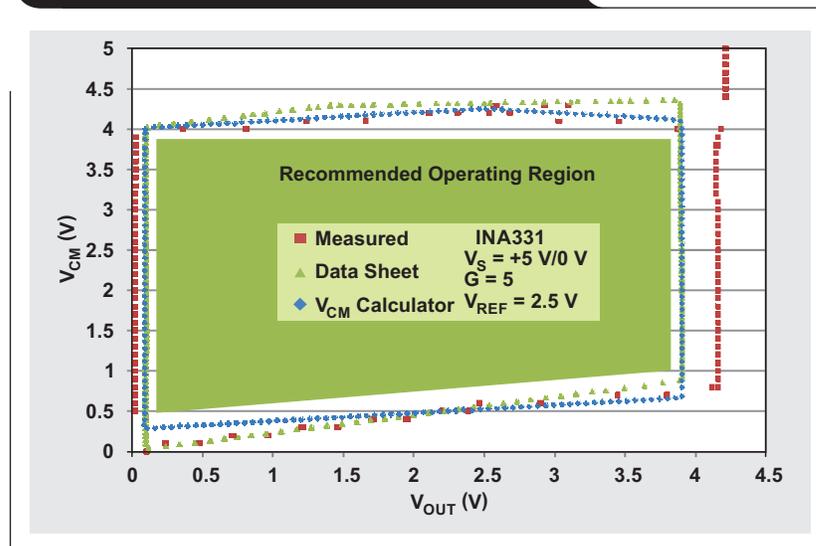

Acknowledgements

The authors would like to thank Shreenidhi Patil for his technical contributions to the software component of the measurement system and data collection. They would also like to thank Art Kay for developing the V_{CM} vs. V_{OUT} Calculator software tool.

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page

support.ti.com

TI E2E™ Community Home Page

e2e.ti.com

Product Information Centers

Americas	Phone	+1(512) 434-1560
Brazil	Phone	0800-891-2616
Mexico	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

Phone		
European Free Call	00800-ASK-TEXAS (00800 275 83927)	
International	+49 (0) 8161 80 2121	
Russian Support	+7 (4) 95 98 10 701	

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	www.ti.com/asktexas
Direct Email	asktexas@ti.com

Japan

Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	support.ti.com/sc/pic/japan.htm
	Domestic	www.tij.co.jp/pic

E2E is a trademark of Texas Instruments. All other trademarks are the property of their respective owners.

Asia

Phone	<u>Toll-Free Number</u>
Note: Toll-free numbers may not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	000-800-100-8888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
International	+86-21-23073444
Fax	+86-21-23073686
Email	tiasia@ti.com or ti-china@ti.com
Internet	support.ti.com/sc/pic/asia.htm

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A021014

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com