

# ***AN-2156 Configuring the LMH0387 for an Equalizer-Only Application***

---

## **ABSTRACT**

This application note discusses how to configure the LMH0387 for an equalizer-only application.

---

### **Contents**

1	Introduction .....	2
2	How to Configure the LMH0387 for Equalizer-Only Use .....	2
3	LMH0387 Benefits over Dedicated Equalizer .....	3
	3.1 Superior Return Loss .....	3
	3.2 Reduced BOM Costs .....	4
	3.3 Simplified Layout and PCB Space Savings .....	4
4	Conclusion .....	5
5	References .....	5

### **List of Figures**

1	LMH0387 Circuit for Equalizer-Only Mode .....	3
2	LMH0387 Input Return Loss.....	4
3	Input Circuit Required for Dedicated Equalizer ( <i>left</i> ) and LMH0387 ( <i>right</i> ) .....	4
4	Input Circuit PCB Layout for Dedicated Equalizer ( <i>left</i> ) and LMH0387 ( <i>right</i> ) .....	5

### **List of Tables**

1	LMH0387 Connections for Equalizer-Only Mode .....	2
---	---	---

## 1 Introduction

The adaptive cable equalizer is an important component in the Serial Digital Interface (SDI) used for transmission of digital video signals. It restores the SDI signal after it passes through hundreds of meters of coaxial cable, automatically adjusting to reverse the effects of the cable loss. The cable driver's role is to set the appropriate amplitude, slew rate, and eye shape to drive an SDI signal into the coaxial cable so that it can be properly recovered by the equalizer at the other end.

The LMH0387 SDI configurable I/O accomplishes both of these tasks with a single pin, allowing a BNC attached to the device to be used as either an input or output. It provides the full functionality of an adaptive cable equalizer and cable driver. The LMH0387 includes an integrated return loss network which enables very good return loss and easy compliance to the Society of Motion Picture and Television Engineers (SMPTE) return loss specifications. The versatility of the LMH0387 allows it to replace an equalizer or cable driver (or both) while providing several additional benefits.

## 2 How to Configure the LMH0387 for Equalizer-Only Use

In sockets that only require the equalizer function (input only), the LMH0387 may be configured as an equalizer by disabling the internal cable driver. One method to do this is to set the device per the typical application (see the datasheet) with the TX\_EN pin tied low to disable the cable driver. While disabled, the cable driver consumes a small amount of power (4 mW). With this configuration, the cable driver can be enabled to change the port from input to output by pulling the TX\_EN pin high.


Alternatively, if the cable driver will never be used, the LMH0387 can be configured for equalizer-only mode (with no cable driver option) by connecting all pins associated with the cable driver to ground. This saves components, reduces power consumption, and simplifies the PCB layout.

To configure the LMH0387 for equalizer-only use in this manner, connect the following nine LMH0387 pins to ground as shown in [Table 1](#). The cable driver will consume no power and only the equalizer portion of the LMH0387 will be active. [Figure 1](#) shows the complete LMH0387 circuit for equalizer-only mode.

**Table 1. LMH0387 Connections for Equalizer-Only Mode**

Pin	Name	Connection
2, 3, 43	$V_{\text{CCTX}}$	GND
33, 34	SDI, $\overline{\text{SDI}}$	GND
36	$R_{\text{REF}}$	GND
40	TX_EN	GND
44	SD/ $\overline{\text{HD}}$	GND
45	TERM <sub>TX</sub>	GND



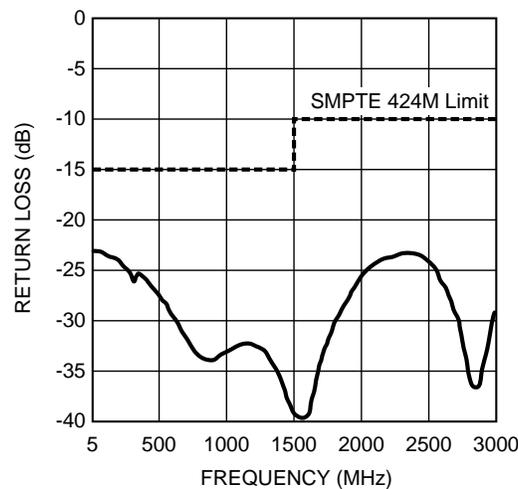


**Figure 2. LMH0387 Input Return Loss**

### 3.2 Reduced BOM Costs

The LMH0387 reduces bill of materials (BOM) costs and simplifies the PCB circuit required for equalizer operation. The passive components required for return loss and the equalizer input termination are all integrated within the package, greatly reducing the number external components.

Figure 3 shows the schematic of the input network typically required for a dedicated equalizer and the corresponding schematic for the LMH0387. For the LMH0387, only a single capacitor is required between the input pin and the BNC.

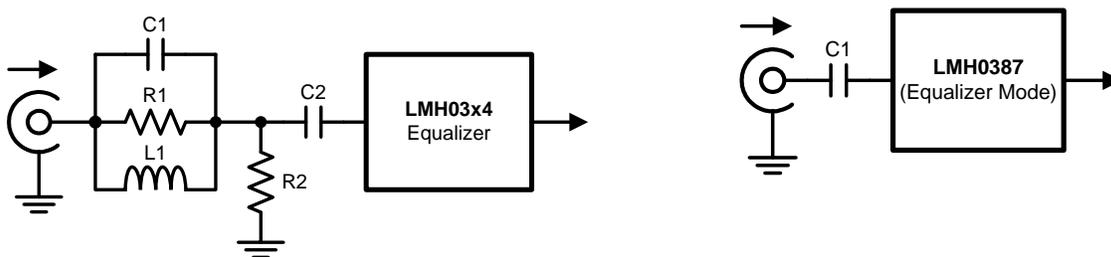


**Figure 3. Input Circuit Required for Dedicated Equalizer (left) and LMH0387 (right)**

### 3.3 Simplified Layout and PCB Space Savings

The LMH0387 greatly simplifies PCB layout while saving board space. For a dedicated equalizer, the layout of the input network components is crucial for optimal operation and good return loss. This is not a concern for the LMH0387 since this network is integrated. The LMH0387 layout is simple since all that is required is the AC-coupling capacitor, and the placement of this capacitor is not critical.

While the LMH0387 device package is larger than the device package for a dedicated equalizer, the PCB board area required for the LMH0387 is actually less than the area required for a dedicated equalizer such as the LMH0384 or LMH0344, due to the additional external components necessary for the dedicated equalizer. The LMH0387 can be placed closer to the BNC.

Figure 4 shows the PCB layout for the input network of a dedicated equalizer and the corresponding PCB layout for the LMH0387.

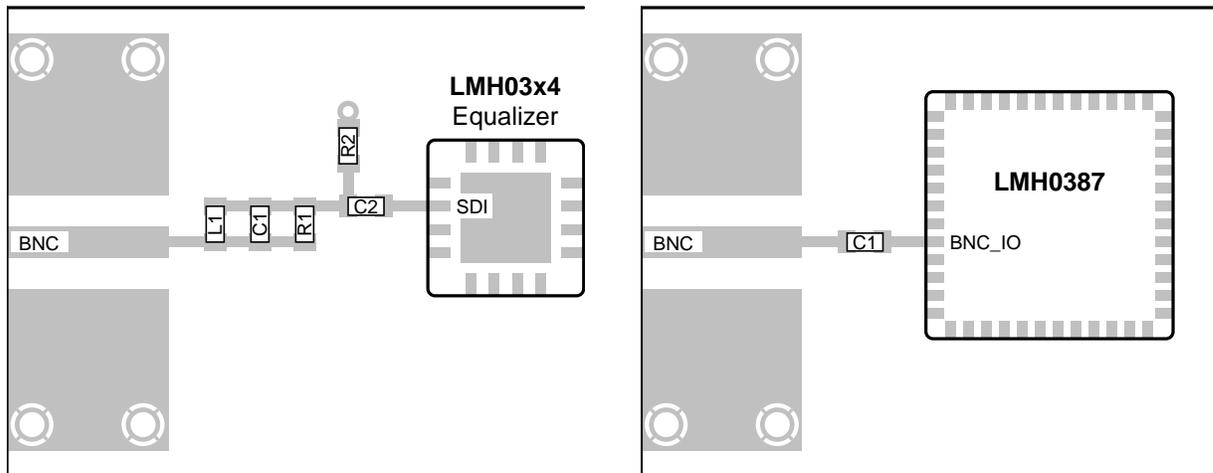

**Figure 4. Input Circuit PCB Layout for Dedicated Equalizer (left) and LMH0387 (right)**

#### 4 Conclusion

The LMH0387 configurable I/O can replace a dedicated adaptive cable equalizer in many SDI applications. It is simple to configure the LMH0387 for equalizer-only use, and it provides several benefits, including superior return loss, reduced BOM costs, easier PCB layout, and board space savings.

#### 5 References

1. The SMPTE 424M, 292M, and 259M standards specify the requirements for the Serial Digital Interface (SDI) used for transmission of digital video signals over a coaxial cable at 3G, HD, and SD data rates, respectively. These standards specify the return loss requirements, and are listed below:
  - SMPTE 424M-2006: 3 Gb/s Signal/Data Serial Interface
  - SMPTE 292M-1998: Bit-Serial Digital Interface for High Definition Television Systems
  - SMPTE 259M-2006: SDTV Digital Signal/Data – Serial Digital Interface
2. Return loss is dependent on board design. The following references discuss how to optimize PCB board layout for SDI designs:
  - Tsun-Kit Chin, *Optimizing BNC PCB Footprint Designs for Digital Video Equipment* ([videsignwire.com/optimizing-bnc-pcb-footprint-designs-for-digital-video-equipment/](http://videsignwire.com/optimizing-bnc-pcb-footprint-designs-for-digital-video-equipment/)).
  - Tsun-Kit Chin, *High-Speed Board Layout Challenges in FPGA/SDI Sub-Systems* ([SNLA158](#)).
3. *LMH0387 3 Gbps HD/SD SDI Configurable I/O Adaptive Cable Equalizer / Cable Driver Data Sheet* ([SNLS315](#)).

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)