

# How to Use a 3.3-V LVDS Buffer as a Low-Voltage LVDS Driver

Yaser Ibrahim, High-Speed Data and Clocks Group



This document discusses how to use a 3.3-V LVDS buffer as an LVDS driver that supports 1.8-V (or other low-voltage) LVTTTL/LVCMOS input signals.

## Introduction

An LVDS driver, such as the DS90LV011A or SN65LVDS1, accepts a single-ended LVTTTL/LVCMOS input and translates it to a differential LVDS output, as shown in Figure 1. An LVDS buffer like the DS90LV001 or SN65LVDS100, on the other hand, accepts a differential LVDS input and outputs a differential LVDS signal, as shown in Figure 2.

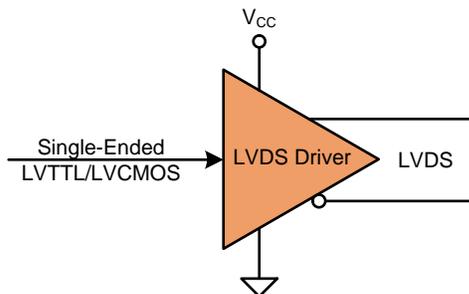


Figure 1. LVDS Driver

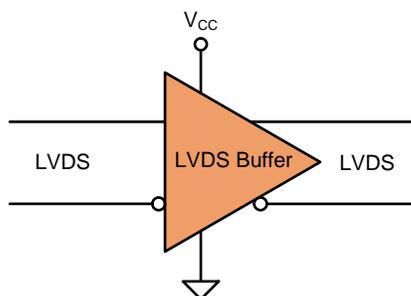


Figure 2. LVDS Buffer

Most LVDS drivers available on the market have a 3.3-V supply and only support 3.3-V LVTTTL/LVCMOS signals. Sometimes the LVTTTL/LVCMOS signals that need to be converted to LVDS are originating from devices that are powered by low voltages (such as 1.2 V, 1.8 V, 2.5 V, and so forth). Therefore, these signal normally have low-voltage swings ( $V_{OH} - V_{OL}$ ) that follow the supply voltage (see Figure 3). In this case, the LVDS driver must support input single-ended signals with low-voltage swings. The approach described in this document achieves this using a 3.3-V LVDS buffer.

On the receiving side, a low-voltage LVDS receiver may also be needed to interface with a device powered from a low voltage. The SN65LVDS4 is an LVDS receiver from TI that is able to output 1.8-V or 2.5-V LVTTTL/LVCMOS signals, and can be used in this case.

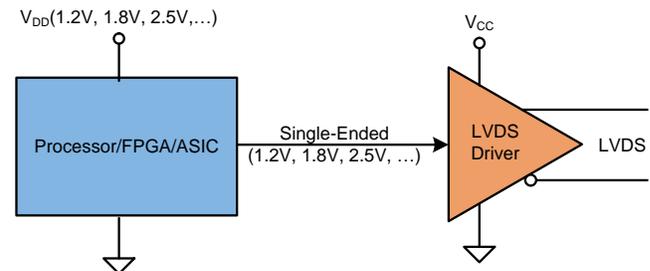


Figure 3. The Need for Low-Voltage LVDS Driver

## Solution

Figure 4 shows the approach to solve this problem. An LVDS buffer, such as the DS90LV001 or SN65LVDS100, which is powered from 3.3-V supply, is used. The inverting input of the LVDS buffer is biased at a reference voltage ( $V_{REF}$ ) that is appropriate for the input single-ended logic signal. This means that  $V_{REF}$  is set to be in the middle of the range between  $V_{OH}(\min)$  and  $V_{OL}(\max)$  of the input logic signal. A simple way to provide this reference voltage is to use a resistor divider with the 2 resistors ( $R_1$  and  $R_2$  in Figure 4) selected to generate the desired reference voltage.  $R_1$  and  $R_2$  should be large (k $\Omega$  range) to limit the quiescent current consumption.

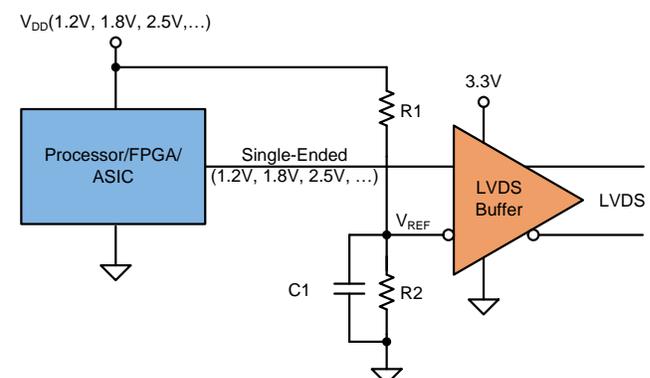


Figure 4. LVDS Buffer Used as a Low-Voltage LVDS Driver

The input single-ended LVCMOS/LVTTL signal is applied to the noninverting input of the LVDS buffer. When the input signal is logic high (specifically, when it is greater than  $V_{REF}$  by the amount of the threshold voltage of the LVDS buffer, which is usually 100 mV), the differential output of the LVDS buffer will be +350 mV. When the input signal is logic low (less than  $V_{REF}$  by the amount of the threshold voltage), the LVDS differential output will be -350 mV.

As an example, if the single-ended input is a 1.8-V signal, with  $V_{OH(min)} = 1.17$  V, and  $V_{OL(max)} = 0.63$  V, the reference voltage at the inverting input should be set to a voltage equal to  $(V_{OH(min)} + V_{OL(max)})/2$ , which is equal to 0.9 V. Suggested resistor values in this case are  $R1 = R2 = 10$  k $\Omega$ .

Notice that the resistor divider is powered from the voltage supply of the source of the single-ended signal. This helps minimize duty cycle distortion. TI also recommends to add a capacitor ( $C1 = 0.01$   $\mu$ F) in parallel with  $R2$  for stability.

The supported input voltage is, generally, any voltage in the input common-mode voltage range of the LVDS buffer. Most LVDS buffers support a wide input common-mode range (for example, 0 V to 4 V for the SN65LVDS100), therefore input voltage swings as low as 0.8 V (or even lower) can be supported with this approach.

### Solution Cost

The cost of an LVDS buffer is generally comparable to the cost of an LVDS driver. There is additional cost for the two resistors and capacitor that are necessary for this solution, which is generally small. The additional PCB area necessary for this solution is also small, but it is dependent on the size of the chosen resistors and capacitor.

### Limitations

Some of the limitations for this approach are:

- A buffer with integrated 100- $\Omega$  termination resistor cannot be used, because the termination resistor will alter the reference voltage on the inverting input and make it dependent on the input signal applied to the noninverting input.
- The data rate supported with this approach is only limited by the data rate supported by the LVDS buffer (like 800 Mbps for the DS90LV001 or 2 Gbps for the SN65LVDS100, for example).
- There is a small increase in the quiescent current consumption due to the current flowing through the voltage divider. The amount of this current depends on the values of the resistors  $R1$  and  $R2$  and it can be minimized by using large values for  $R1$  and  $R2$ .

### Conclusion

The approach described in this document provides a practical and inexpensive way to support the conversion of low-voltage LVTTL/LVCMOS signals to LVDS. It uses a 3.3-V LVDS buffer with a few passive components as an LVDS driver that supports input logic signals with voltage swings as low as 0.8 V.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale ([www.ti.com/legal/termsofsale.html](http://www.ti.com/legal/termsofsale.html)) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2019, Texas Instruments Incorporated