

# **AN-116 Use the LM158/LM258/LM358 Dual, Single Supply Op Amp**

---

## **ABSTRACT**

This application note discusses the use of the LM158/LM258/LM358 dual op amp when operated from a single supply.

---

### **Contents**

1	Introduction .....	2
2	Single Supply Operation .....	2
3	AC Gain .....	3
4	Inverting DC Gain .....	4
5	Non-Inverting DC Gain .....	4
6	Zero T.C. Input Bias Current .....	4
7	Balanced Supply Operation .....	5

### **List of Figures**

1	Worst Case Signal Levels with +12V Supply.....	3
2	Operating with AC Signals.....	3
3	Typical DC Coupled Inverting Gain.....	5
4	Typical DC Coupled Non-Inverting Gain.....	5
5	Split Supply Operation of LM358 .....	6

### **List of Tables**

1	Comparison of Dual Op Amps LM1458 and LM358 .....	2
2	Conventional Op Amp Circuits Suitable for Single Supply Operation.....	6

## 1 Introduction

Using the LM158/LM258/LM358 dual op amp with a single supply in place of the LM1458/LM1558 with split supply will reap profits in terms of:

- Input and output voltage range down to the negative (ground) rail
- Single supply operation
- Lower standby power dissipation
- Higher output voltage swing
- Lower input offset current
- Generally similar performance otherwise

The main advantage, of course, is that you can eliminate the negative supply in many applications and still retain equivalent op amp performance. Additionally, and in some cases more importantly, the input and output levels are permitted to swing down to ground (negative rail) potential. [Table 1](#) shows the relative performance of the two in terms of guaranteed and/or typical specifications.

In many applications the LM158/LM258/LM358 can also be used directly in place of LM1558 for split supply operation.

## 2 Single Supply Operation

The LM1458/LM1558 or similar op amps exhibit several important limitations when operated from a single positive (or negative) supply. Chief among these is that input and output signal swing is severely limited for a given supply as shown in [Figure 1](#). For linear operation, the input voltage must not reach within 3 volts of ground or of the supply, and output range is similarly limited to within 3–5 volts of ground or supply. This means that operation with a +12V supply could be limited as low as 2 Vp-p output swing. The LM358 however, allows a 10.5 Vp-p output swing for the same 12V supply. Admittedly these are worst case specification limits, but they serve to illustrate the problem.

**Table 1. Comparison of Dual Op Amps LM1458 and LM358**

Characteristic	LM1458	LM358
$V_{IO}$	6 mV Max	7 mV Max
CM $V_I$	24 Vp-p <sup>(1)</sup>	0–28.5V <sup>(1)</sup>
$I_{IO}$	200 nA	50 nA
$I_{OB}$	500 nA	–500 nA
CMRR	60 dB Min @ 100 Hz 90 dB Typ	85 dB Typ @ DC
$\bar{e}_n$ @ 1 kHz, $R_{GEN}$ 10 k $\Omega$	45 nV/ $\sqrt{Hz}$ Typ	40 nV/ $\sqrt{Hz}$ Typ <sup>(2)</sup>
$Z_{IN}$	200 M $\Omega$ Typ	Typ 100 M $\Omega$
$A_{VOL}$	20k Min 100k Typ	100k Typ
$f_c$	1.1 MHz Typ	1 MHz Typ <sup>(2)</sup>
$P_{BW}$	14 kHz Typ	11 kHz Typ <sup>(2)</sup>
$dV_o/dt$	0.8V/ $\mu$ s Typ	0.5V/ $\mu$ s Ty <sup>(2)</sup>
$V_o$ @ $R_L = 10k/2k$	24/20 Vp-p <sup>(1)</sup>	28.5 Vp-p
$I_{SC}$	20 mA Typ	Source 20 mA Min (40 Typ) Sink 10 mA Min (20 Typ)
PSRR @ DC	37 dB Min 90 dB Typ	100 dB Typ
$I_D$ ( $R_L = \infty$ )	8 mA Max	2 mA Max

<sup>(1)</sup> From laboratory measurement based on  $V_S = 30V$  on LM358 only, or  $V_S = \pm 15V$

<sup>(2)</sup> From data sheet typical curves

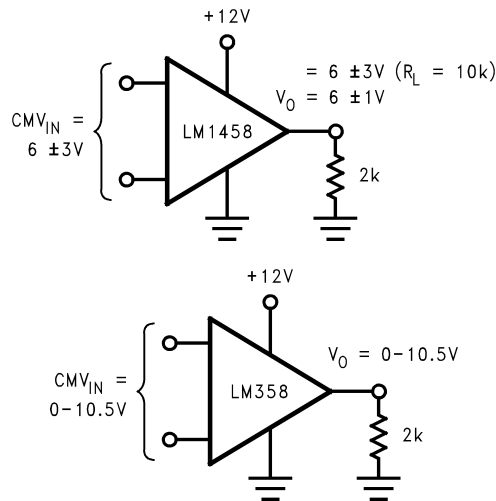


Figure 1. Worst Case Signal Levels with +12V Supply

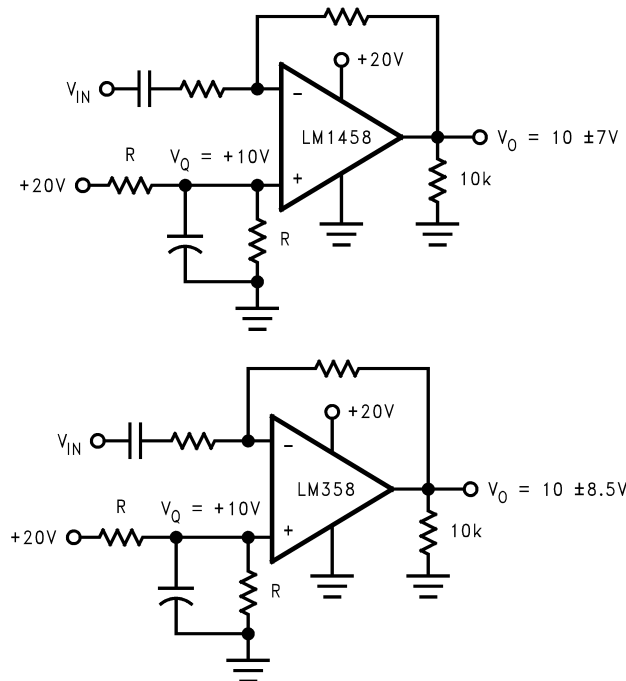


Figure 2. Operating with AC Signals

### 3 AC Gain

For AC signals the input can be capacitor coupled. The input common mode and quiescent output voltages are fixed at one-half the supply voltage by a resistive divider at the non-inverting input as shown in Figure 2. This quiescent output could be set at a lower voltage to minimize power dissipation in the LM358, if desired, so long as  $V_Q \geq V_{IN\text{ pk}}$ . For the LM1458 the quiescent output must be higher,  $V_Q \geq 3V + V_{IN\text{ pk}}$  thus, for small signals, power dissipation is much greater with the LM1458. Example: Required  $V_O = V_Q \pm 1V$  pk into 2k,  $V_{SUPPLY} =$  as required. Find quiescent dissipation in load and amplifier for LM1458 and LM358.

**LM358**

$$V_Q = +1V$$

$$V_{\text{SUPPLY}} = +3.5V$$

$$P_{\text{LOAD}} = \frac{E_L^2}{R_L} = \frac{1}{2k} = 0.5 \text{ mW}$$

$$P_D = V_S I_{S^*} + (V_S - V_Q) I_L$$

$$= 3.5V \times 0.7 \text{ mA} + (3.5 - 1) \frac{1V}{2k}$$

$$P_D = 2.45 + 1.25 = 3.7 \text{ mW}$$

$$P_{\text{TOTAL}} = 3.7 + 0.5 = 4.2 \text{ mW}$$

\*From typical characteristics

(1)

**LM1458**

$$V_Q = 4V$$

$$V_{\text{SUPPLY}} = 8V$$

$$P_{\text{LOAD}} = \frac{4^2}{2k} = 8 \text{ mW}$$

$$P_D = P_{D^*} + (V_S - V_Q) I_L$$

$$= 22 \text{ mW} + (8 - 4) \frac{4V}{2k}$$

$$P_D = 22 + 8 = 30 \text{ mW}$$

$$P_{\text{TOTAL}} = 30 + 8 = 38 \text{ mW}$$

\*From typical characteristics

(2)

The LM1458 requires over twice the supply voltage and nearly 10 times the supply power of the LM358 in this application.

#### 4 Inverting DC Gain

Connections and biasing for DC inverting gain are essentially the same as for the AC coupled case. Note, of course, that the output cannot swing negative when operated from a single positive supply. [Figure 3](#) shows the connections and signal limitations.

#### 5 Non-Inverting DC Gain

The non-inverting gain connection does not require the  $V_Q$  biasing as before; the inverting input can be returned to ground in the usual manner for gains greater than unity, (see [Figure 4](#)). A tremendous advantage of the LM358 in this connection is that input signals and output may extend all the way to ground; therefore DC signals in the low-millivolt range can be handled. The LM1458 still requires that  $V_{\text{IN}} = 3V-17V$ . Therefore maximum gain is limited to  $A_V = (V_O-3)/3$ , or  $A_V \text{ max} = 5.4$  for a 20V supply.

There is no similar limitation for the LM358.

#### 6 Zero T.C. Input Bias Current

An interesting and unusual characteristic is that  $I_{\text{IN}}$  has a zero temperature coefficient. This means that matched resistance is not required at the input, allowing omission of one resistor per op amp from the circuit in most cases.

## 7 Balanced Supply Operation

The LM358 will operate satisfactorily in balanced supply operation so long as a load is maintained from output to the negative supply.

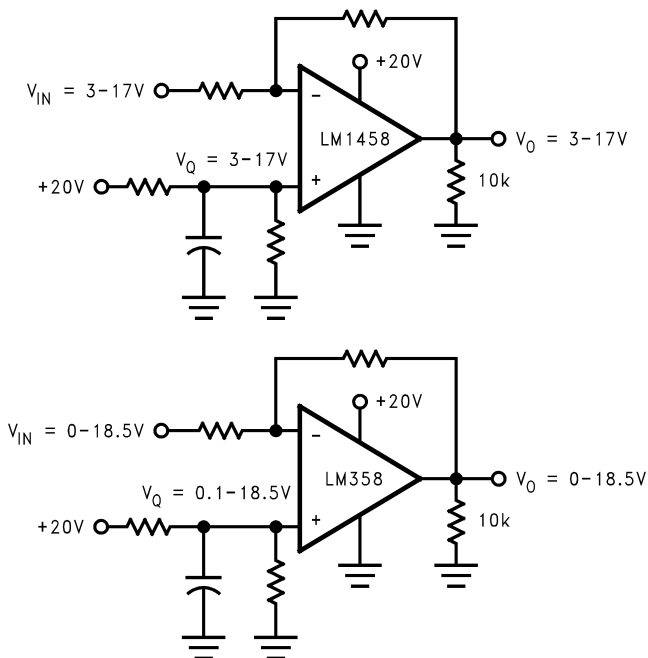


Figure 3. Typical DC Coupled Inverting Gain


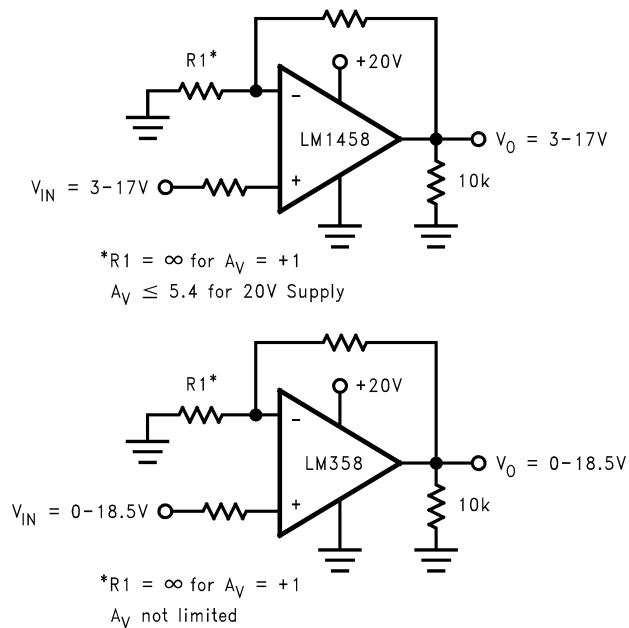


Figure 4. Typical DC Coupled Non-Inverting Gain

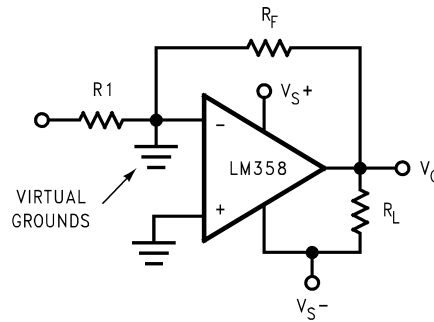

$$\text{Crossover (distortion) occurs at } V_O = V_S - \frac{R_F}{R_L + R_F}$$

**Figure 5. Split Supply Operation of LM358**

The output load to negative supply forces the amplifier to source some minimum current at all times, thus eliminating crossover distortion. Crossover distortion without this load would be more severe than that expected with the normal op amp. Since the single supply design took notice of this normal load connection to ground, a class AB output stage was not included. Where ground referenced feedback resistors are used as in Figure 5, the required load to the negative supply depends upon the peak negative output signal level desired without exhibiting crossover distortion.  $R_L$  to the negative rail should be chosen small enough that the voltage divider formed by  $R_F$  and  $R_L$  will permit  $V_o$  to swing negative to the desired point according to the equation:

$$R_L = R_F \frac{V_S - V_o}{V_o} \tag{3}$$

$R_L$  could also be returned to the positive supply with the advantage that  $V_o$  max would never exceed  $(V_S - 1.5V)$ . Then with  $\pm 15V$  supplies  $R_{L\text{ MIN}}$  would be  $0.12 R_F$ . The disadvantage would be that the LM358 can source twice as much current as it can sink, therefore  $R_L$  to negative supply can be one-half the value of  $R_L$  to positive supply.

The need for single or split supply is based on system requirements which may be other than op amp oriented. However if the only need for balanced supplies is to simplify the biasing of op amps, there are many systems which can find a cost effective benefit in operating LM358's from single supplies rather than standard op amps from balanced supplies. Of the usual op amp circuits, Table 2 shows those few which have limited function with single supply operation. Most are based on the premise that to operate from a single supply, a reference  $V_Q$  at about one-half the supply be available for bias or (zero) signal reference. The basic circuits are those listed in AN-20.

**Table 2. Conventional Op Amp Circuits Suitable for Single Supply Operation<sup>(1)(2)(3)</sup>**

Application	Limitations
AC Coupled amp	$V_Q$
Inverting amp	$V_Q$
Non-inverting amp	OK
Unity gain buffer	OK
Summing amp	$V_Q$
Difference amp	$V_Q$
Differentiator	$V_Q$
Integrator	$V_Q$
LP Filter	$V_Q$
I-V Connector	$V_Q$
PE Cell Amp	OK

(1) See AN-20 for conventional circuits  
 (2)  $V_Q$  denotes need for a reference voltage, usually at about  $V_S/2$ .  
 (3) OK means no reference voltage required

**Table 2. Conventional Op Amp Circuits Suitable for Single Supply Operation<sup>(1)(2)(3)</sup> (continued)**

Application	Limitations
I Source	$I_{O\ MIN} = \frac{1.5}{R_1}$
I Sink	OK
Volt Ref	OK
FW Rectifier	$V_Q$ or modified circuit
Sine wave osc	$V_Q$
Triangular generator	$V_Q$
Threshold detector	OK
Tracking, regulator PS	Not practical
Programmable PS	OK
Peak Detector	OK to $V_{IN} = 0$

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)