

# AN-263 Sine Wave Generation Techniques

---

## ABSTRACT

This application note describes the sine wave generation techniques to control frequency, amplitude, and distortion levels.

---

### Contents

1	Introduction .....	3
2	Phase Shift Oscillator .....	3
3	Low Distortion Oscillation .....	4
4	High Voltage AC Calibrator .....	5
5	Negative Resistance Oscillator .....	7
6	Resonant Element Oscillator—Tuning Fork .....	8
7	Resonant Element Oscillator—Quartz Crystal .....	10
8	Approximation Methods .....	10
9	Sine Approximation—Breakpoint Shaper .....	11
10	Sine Approximation—Logarithmic Shaping .....	12
11	Sine Approximation—Voltage Controlled Sine Oscillator .....	13
12	Sine Approximation—Digital Methods .....	14

### List of Figures

1	Phase-Shift Wave Oscillator .....	3
2	Basic Wein Bridge .....	5
3	More Complex Wein Bridge .....	6
4	Wein Bridge Waveforms .....	6
5	Generate High-Voltage Sine Waves Using IC-Based Circuits by Driving a Transformer in a Step-Up Mode .....	7
6	LC Sine Wave Sources Offer High Stability and Reasonable Distortion Levels .....	8
7	Tuning Fork Based Oscillator .....	9
8	Output Levels Provided by the Tuning Fork Oscillator .....	9
9	Stable Quartz-Crystal Oscillators Can Operate with a Single Active Device .....	10
10	Achieve Maximum Frequency Stability by Mounting the Oscillator in an Oven and Using a Temperature-Controlling Circuit .....	10
11	A Varactor Network Can Fine Tune a Crystal .....	11
12	Breakpoint Shaping Networks Employ Diodes That Conduct in Direct Proportion to an Input Triangle Wave Amplitude .....	11
13	Breakpoint Shaping Network Waveforms .....	12
14	Logarithmic Shaping Scheme .....	13
15	Voltage-Tunable Oscillator .....	14
16	Voltage-Tunable Oscillator Waveforms .....	14
17	Logarithmic Shaper Waveforms .....	15
18	Log Shaper .....	16
19	Filtered Sine Output .....	17
20	Distortion Levels .....	17

All trademarks are the property of their respective owners.

## List of Tables


1	Sine-Wave-Generation Techniques .....	4
---	---------------------------------------	---

## 1 Introduction

Producing and manipulating the sine wave function is a common problem encountered by circuit designers. Sine wave circuits pose a significant design challenge because they represent a constantly controlled linear oscillator. Sine wave circuitry is required in a number of diverse areas, including audio testing, calibration equipment, transducer drives, power conditioning and automatic test equipment (ATE). Control of frequency, amplitude or distortion level is often required and all three parameters must be simultaneously controlled in many applications. A number of techniques utilizing both analog and digital approaches are available for a variety of applications. Each individual circuit approach has inherent strengths and weaknesses which must be matched against any given application (see [Table 1](#)).
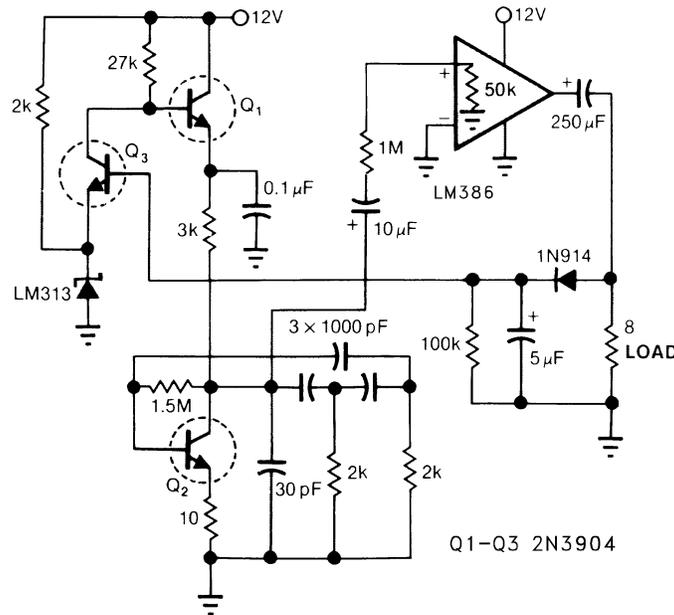
## 2 Phase Shift Oscillator

A simple inexpensive amplitude stabilized phase shift sine wave oscillator which requires one IC package, three transistors and runs off a single supply appears in [Figure 1](#). Q2, in combination with the RC network comprises a phase shift configuration and oscillates at about 12 kHz. The remaining circuitry provides amplitude stability. The high impedance output at Q2's collector is fed to the input of the LM386 via the 10  $\mu$ F-1M series network. The 1M resistor in combination with the internal 50 k $\Omega$  unit in the LM386 divides Q2's output by 20. This is necessary because the LM386 has a fixed gain of 20. In this manner the amplifier functions as a unity gain current buffer which will drive an 8 $\Omega$  load. The positive peaks at the amplifier output are rectified and stored in the 5  $\mu$ F capacitor. This potential is fed to the base of Q3. Q3's collector current will vary with the difference between its base and emitter voltages. Since the emitter voltage is fixed by the LM313 1.2V reference, Q3 performs a comparison function and its collector current modulates Q1's base voltage. Q1, an emitter follower, provides servo controlled drive to the Q2 oscillator. If the emitter of Q2 is opened up and driven by a control voltage, the amplitude of the circuit output may be varied. The LM386 output will drive 5V (1.75 Vrms) peak-to-peak into 8 $\Omega$  with about 2% distortion. A  $\pm$ 3V power supply variation causes less than  $\pm$ 0.1 dB amplitude shift at the output.



- A Phase-shift sine wave oscillators combine simplicity with versatility. This 12 kHz design can deliver 5 Vp-p to the 8 $\Omega$  load with about 2% distortion.

**Figure 1. Phase-Shift Wave Oscillator**

**Table 1. Sine-Wave-Generation Techniques**

Type	Typical Frequency Range	Typical Distortion (%)	Typical Amplitude Stability (%)	Comments
<b>Phase Shift</b>	10 Hz–1 MHz	1–3	3 (Tighter with Servo Control)	Simple, inexpensive technique. Easily amplitude servo controlled. Resistively tunable over 2:1 range with little trouble. Good choice for cost-sensitive, moderate-performance applications. Quick starting and settling.
<b>Wein Bridge</b>	1 Hz–1 MHz	0.01	1	Extremely low distortion. Excellent for high-grade instrumentation and audio applications. Relatively difficult to tune—requires dual variable resistor with good tracking. Take considerable time to settle after a step change in frequency or amplitude.
<b>LC Negative Resistance</b>	1 kHz–10 MHz	1–3	3	Difficult to tune over wide ranges. Higher Q than RC types. Quick starting and easy to operate in high frequency ranges.
<b>Tuning Fork</b>	60 Hz–3 kHz	0.25	0.01	Frequency-stable over wide ranges of temperature and supply voltage. Relatively unaffected by severe shock or vibration. Basically untunable.
<b>Crystal</b>	30 kHz–200 MHz	0.1	1	Highest frequency stability. Only slight (ppm) tuning possible. Fragile.
<b>Triangle-Driven Break-Point Shaper</b>	< 1 Hz–500 kHz	1–2	1	Wide tuning range possible with quick settling to new frequency or amplitude.
<b>Triangle-Driven Logarithmic Shaper</b>	< 1 Hz–500 kHz	0.3	0.25	Wide tuning range possible with quick settling to new frequency or amplitude. Triangle and square wave also available. Excellent choice for general-purpose requirements needing frequency-sweep capability with low-distortion output.
<b>DAC-Driven Logarithmic Shaper</b>	<1 Hz–500 kHz	0.3	0.25	Similar to above but DAC-generated triangle wave generally easier to amplitude-stabilize or vary. Also, DAC can be addressed by counters synchronized to a master system clock.
<b>ROM-Driven DAC</b>	1 Hz–20 MHz	0.1	0.01	Powerful digital technique that yields fast amplitude and frequency slewing with little dynamic error. Chief detriments are requirements for high-speed clock (e.g., 8-bit DAC requires a clock that is 256 x output sine wave frequency) and DAC glitching and settling, which will introduce significant distortion as output frequency increases.

### 3 Low Distortion Oscillation

In many applications the distortion levels of a phase shift oscillator are unacceptable. Very low distortion levels are provided by Wein bridge techniques. In a Wein bridge stable oscillation can only occur if the loop gain is maintained at unity at the oscillation frequency. In [Figure 3](#) this is achieved by using the positive temperature coefficient of a small lamp to regulate gain as the output attempts to vary. This is a classic technique and has been used by numerous circuit designers\* to achieve low distortion. The smooth limiting action of the positive temperature coefficient bulb in combination with the near ideal characteristics of the Wein network allow very high performance. The photo of [Figure 4](#) shows the output

of the circuit of Figure 2. The upper trace is the oscillator output. The middle trace is the downward slope of the waveform shown greatly expanded. The slight aberration is due to crossover distortion in the FET-input LF155. This crossover distortion is almost totally responsible for the sum of the measured 0.01% distortion in this oscillator. The output of the distortion analyzer is shown in the bottom trace. In the circuit of Figure 3, an electronic equivalent of the light bulb is used to control loop gain. The zener diode determines the output amplitude and the loop time constant is set by the 1M-2.2  $\mu\text{F}$  combination.

The 2N3819 FET, biased by the voltage across the 2.2  $\mu\text{F}$  capacitor, is used to control the AC loop gain by shunting the feedback path. This circuit is more complex than Figure 2 but offers a way to control the loop time constant while maintaining distortion performance almost as good as in Figure 3.

---


**NOTE:** \* Including William Hewlett and David Packard who built a few of these type circuits in a Palo Alto garage about forty years ago.

---
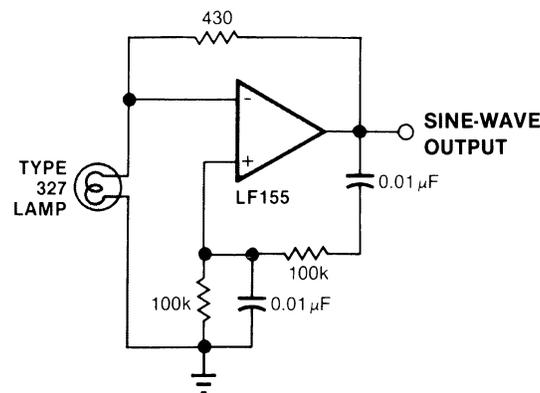
#### 4 High Voltage AC Calibrator


Another dimension in sine wave oscillator design is stable control of amplitude. In this circuit, not only is the amplitude stabilized by servo control but voltage gain is included within the servo loop.

A 100 Vrms output stabilized to 0.025% is achieved by the circuit of Figure 2. Although complex in appearance this circuit requires just 3 IC packages. Here, a transformer is used to provide voltage gain within a tightly controlled servo loop. The LM3900 Norton amplifiers comprise a 1 kHz amplitude controllable oscillator. The LH0002 buffer provides low impedance drive to the LS-52 audio transformer. A voltage gain of 100 is achieved by driving the secondary of the transformer and taking the output from the primary. A current-sensitive negative absolute value amplifier composed of two amplifiers of an LF347 quad generates a negative rectified feedback signal. This is compared to the LM329 DC reference at the third LF347 which amplifies the difference at a gain of 100. The 10  $\mu\text{F}$  feedback capacitor is used to set the frequency response of the loop. The output of this amplifier controls the amplitude of the LM3900 oscillator thereby closing the loop. As shown the circuit oscillates at 1 kHz with under 0.1% distortion for a 100 Vrms (285 Vp-p) output. If the summing resistors from the LM329 are replaced with a potentiometer the loop is stable for output settings ranging from 3 Vrms to 190 Vrms (542 Vp-p!) with no change in frequency. If the DAC1280 D/A converter shown in dashed lines replaces the LM329 reference, the AC output voltage can be controlled by the digital code input with 3 digit calibrated accuracy.




A A basic Wein bridge design employs a lamp's positive temperature coefficient to achieve amplitude stability.

**Figure 2. Basic Wein Bridge**

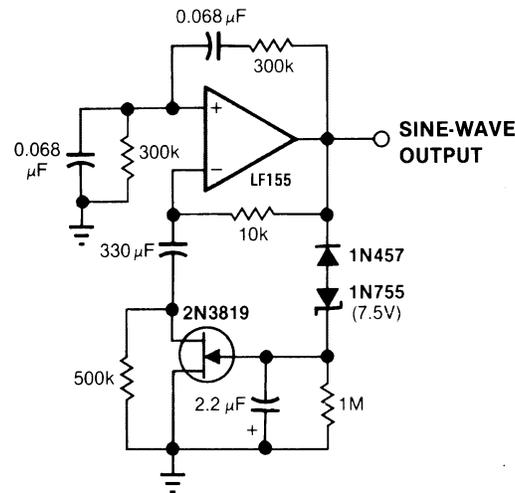

- A A more complex version of the Wein bridge design provides the same feature with the additional advantage of loop time-constant control.


**Figure 3. More Complex Wein Bridge**

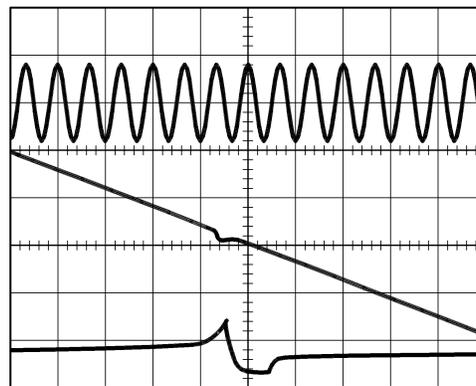

- A Low-distortion output (top trace) is a Wein bridge oscillator feature. The very low crossover distortion level (middle) results from the LF155's output stage. A distortion analyzer's output signal (bottom) indicates this design's 0.01% distortion level.

**Figure 4. Wein Bridge Waveforms**

Trace	Vertical	Horizontal
Top	10V/DIV	10 ms/DIV
Middle	1V/DIV	500 ns/DIV
Bottom	0.5V/DIV	500 ns/DIV

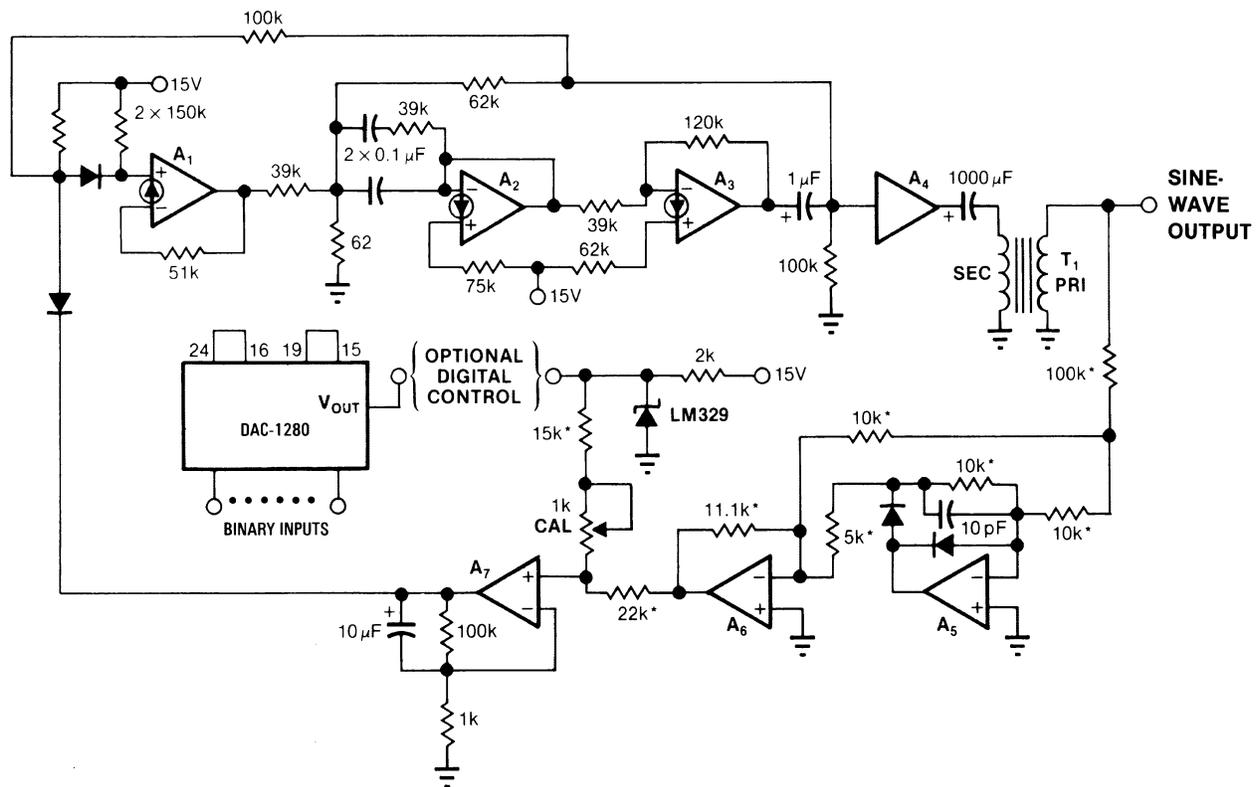

- A A1–A3 = ¼ LM3900
- A4 = LH0002
- A5–A7 = ¼ LF347
- T1 = UTC LS-52
- All diodes = 1N914
- \* = low-TC, metal-film types
- B You can realize digital amplitude control by replacing the LM329 voltage reference with the DAC1287.


**Figure 5. Generate High-Voltage Sine Waves Using IC-Based Circuits by Driving a Transformer in a Step-Up Mode**
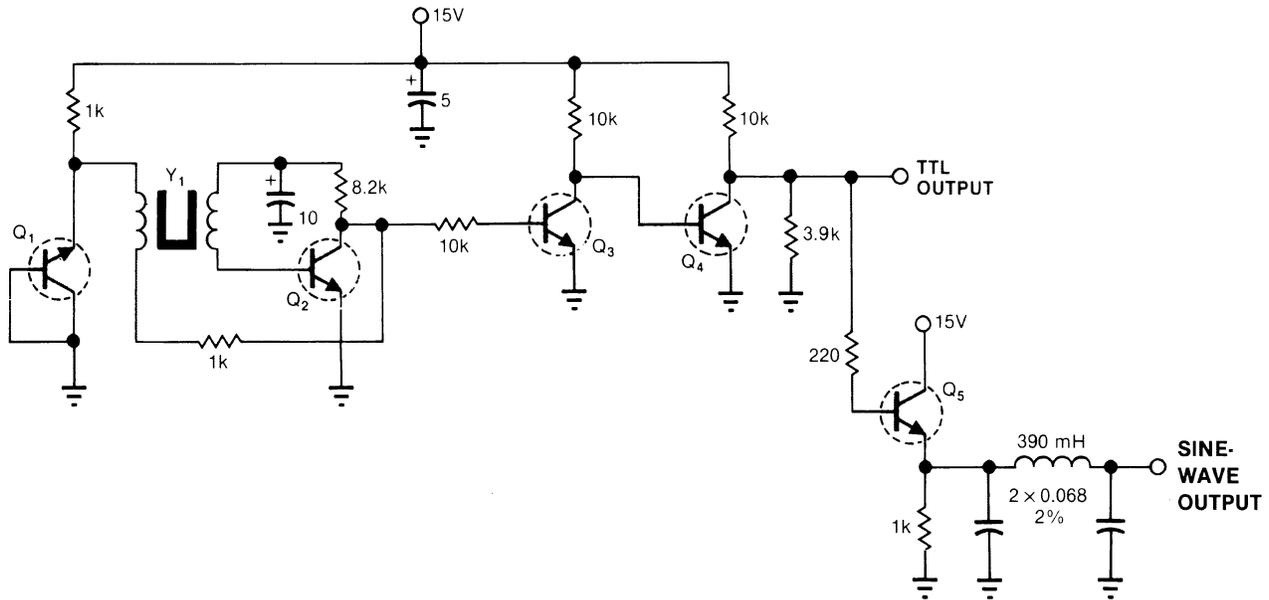
## 5 Negative Resistance Oscillator

All of the preceding circuits rely on RC time constants to achieve resonance. LC combinations can also be used and offer good frequency stability, high Q and fast starting.


In [Figure 6](#) a negative resistance configuration is used to generate the sine wave. The Q1-Q2 pair provides a 15 µA current source. Q2's collector current sets Q3's peak collector current. The 300 kΩ resistor and the Q4-Q5 LM394 matched pair accomplish a voltage-to-current conversion that decreases Q3's base current when its collector voltage rises. This negative resistance characteristic permits oscillation. The frequency of operation is determined by the LC in the Q3-Q5 collector line. The LF353 FET amplifier provides gain and buffering. Power supply dependence is eliminated by the zener diode and the LF353 unity gain follower. This circuit starts quickly and distortion is inside 1.5%.





- A Q1–Q5 = LM3045 array  
Y1 = 1 kHz tuning fork, Fork Standards Inc.  
All capacitors in  $\mu\text{F}$
- B Tuning fork based oscillators don't inherently produce sinusoidal outputs. But when you do use them for this purpose, you achieve maximum stability when the oscillator stage (Q1, Q2) limits. Q3 and Q4 provide a TTL compatible signal, which Q5 then converts to a sine wave.

Figure 7. Tuning Fork Based Oscillator

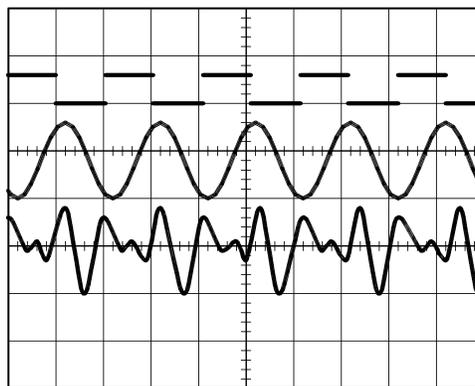

- A This design easily produces a TTL compatible signal (top trace) because the oscillator is allowed to limit.
- B Low-pass filtering this square wave generates a sine wave (middle).
- C The oscillator's 0.7% distortion level is indicated (bottom) by an analyzer's output.

Figure 8. Output Levels Provided by the Tuning Fork Oscillator

Trace	Vertical	Horizontal
Top	5V/DIV	
Middle	50V/DIV	500 $\mu\text{s}$ /DIV
Bottom	0.2V/DIV	

## 7 Resonant Element Oscillator—Quartz Crystal

Quartz crystals allow high frequency stability in the face of changing power supply and temperature parameters. Figure 9 shows a simple 100 kHz crystal oscillator. This Colpitts class circuit uses a JFET for low loading of the crystal, aiding stability. Regulation will eliminate the small effects ( $\sim 5$  ppm for 20% shift) that supply variation has on this circuit. Shunting the crystal with a small amount of capacitance allows very fine trimming of frequency. Crystals typically drift less than  $1$  ppm/ $^{\circ}\text{C}$  and temperature controlled ovens can be used to eliminate this term (Figure 10). The RC feedback values will depend upon the thermal time constants of the oven used. The values shown are typical. The temperature of the oven should be set so that it coincides with the crystal's zero temperature coefficient or "turning point" temperature which is manufacturer specified. An alternative to temperature control uses a varactor diode placed across the crystal (Figure 11). The varactor is biased by a temperature dependent voltage from a circuit which could be very similar to Figure 10 without the output transistor. As ambient temperature varies the circuit changes the voltage across the varactor, which in turn changes its capacitance. This shift in capacitance trims the oscillator frequency.

## 8 Approximation Methods

All of the preceding circuits are *inherent* sine wave generators. Their normal mode of operation supports and maintains a sinusoidal characteristic. Another class of oscillator is made up of circuits which *approximate* the sine function through a variety of techniques. This approach is usually more complex but offers increased flexibility in controlling amplitude and frequency of oscillation. The capability of this type of circuit for a digitally controlled interface has markedly increased the popularity of the approach.

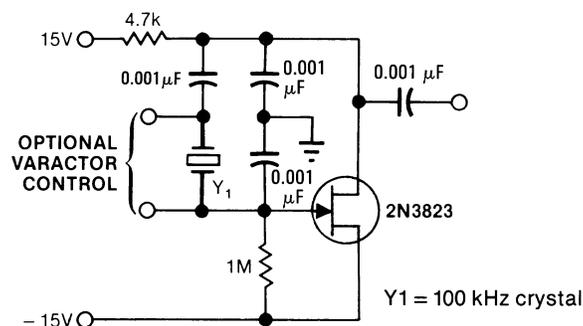


Figure 9. Stable Quartz-Crystal Oscillators Can Operate with a Single Active Device


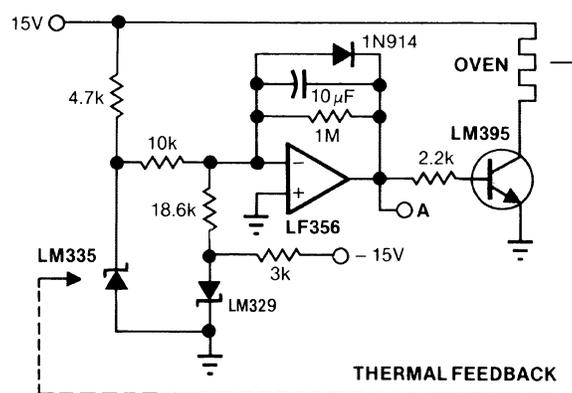


Figure 10. Achieve Maximum Frequency Stability by Mounting the Oscillator in an Oven and Using a Temperature-Controlling Circuit

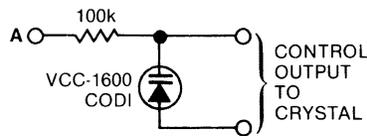


A Here, the varactor replaces the oven and retunes the crystal by changing its load capacitances.

**Figure 11. A Varactor Network Can Fine Tune a Crystal**


## 9 Sine Approximation—Breakpoint Shaper

Figure 12 diagrams a circuit which will “shape” a 20 Vp-p wave input into a sine wave output. The amplifiers serve to establish stable bias potentials for the diode shaping network. The shaper operates by having individual diodes turn on or off depending upon the amplitude of the input triangle. This changes the gain of the output amplifier and gives the circuit its characteristic non-linear, shaped output response. The values of the resistors associated with the diodes determine the shaped waveform's appearance. Individual diodes in the DC bias circuitry provide first order temperature compensation for the shaper diodes. Figure 13 shows the circuit's performance. Trace A is the filtered output (note 1000 pF capacitor across the output amplifier). Trace B shows the waveform with no filtering (1000 pF capacitor removed) and trace C is the output of a distortion analyzer. In trace B the breakpoint action is just detectable at the top and bottom of the waveform, but all the breakpoints are clearly identifiable in the distortion analyzer output of trace C. In this circuit, if the amplitude or symmetry of the input triangle wave shifts, the output waveform will degrade badly. Typically, a D/A converter will be used to provide input drive. Distortion in this circuit is less than 1.5% for a filtered output. If no filter is used, this figure rises to about 2.7%.

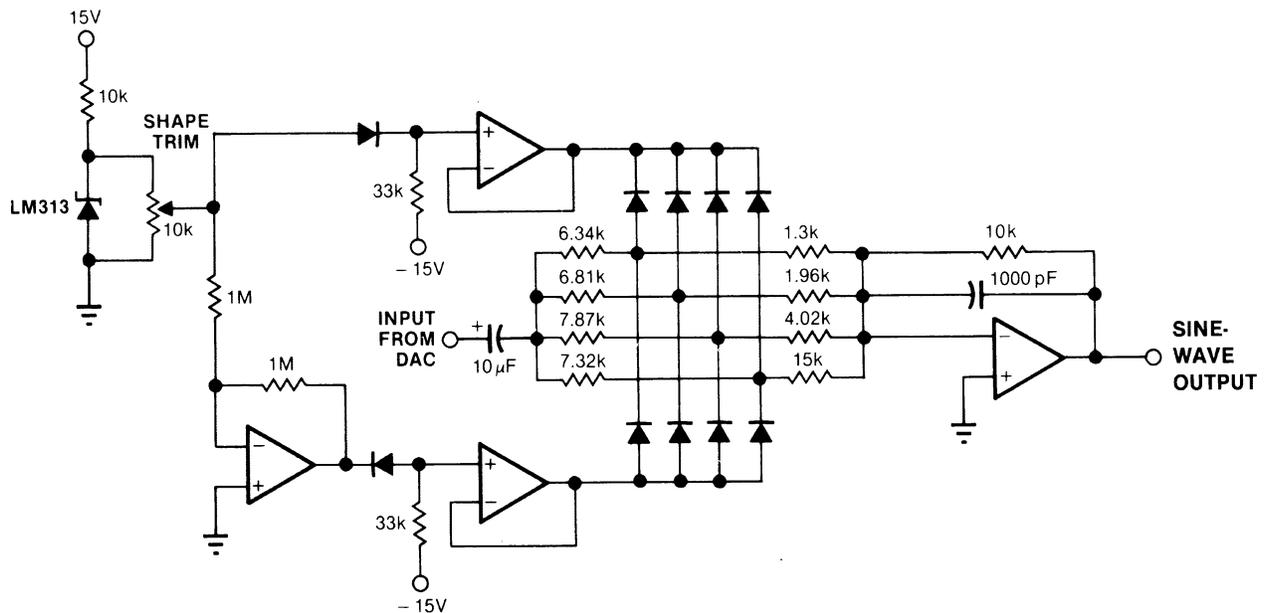

- A All diodes = 1N4148  
All op amps = ¼ LF347
- B This action changes the output amplifier's gain to produce the sine function.

**Figure 12. Breakpoint Shaping Networks Employ Diodes That Conduct in Direct Proportion to an Input Triangle Wave Amplitude**

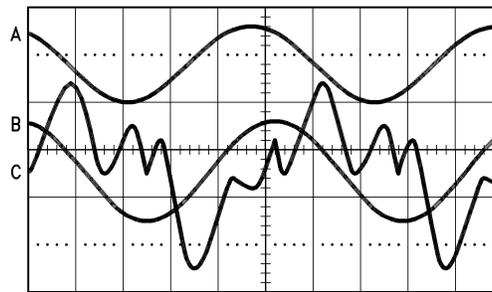


- A A clean sine wave results (trace A) when [Figure 12](#) circuit's output includes a 1000 pF capacitor. When the capacitor isn't used, the diode network's breakpoint action becomes apparent (trace B). The distortion analyzer's output (trace C) clearly shows all the breakpoints.

**Figure 13. Breakpoint Shaping Network Waveforms**

Trace	Vertical	Horizontal
A	5V/DIV	
B	5V/DIV	20 $\mu$ s/DIV
C	0.5V/DIV	
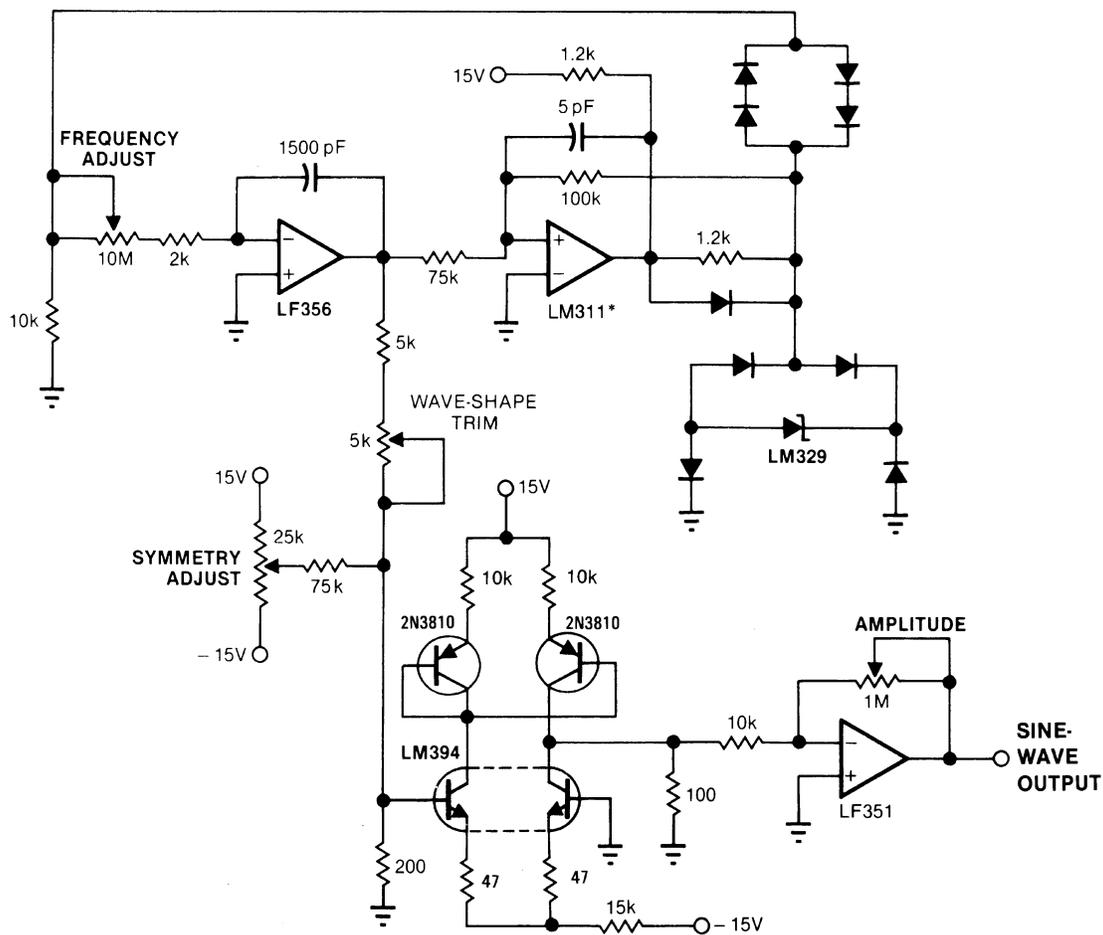
## 10 Sine Approximation—Logarithmic Shaping

[Figure 14](#) shows a complete sine wave oscillator which may be tuned from 1 Hz to 10 kHz with a single variable resistor. Amplitude stability is inside 0.02%/°C and distortion is 0.35%. In addition, desired frequency shifts occur instantaneously because no control loop time constants are employed. The circuit works by placing an integrator inside the positive feedback loop of a comparator. The LM311 drives symmetrical, temperature-compensated clamp arrangement. The output of the clamp biases the LF356 integrator. The LF356 integrates this current into a linear ramp at its output. This ramp is summed with the clamp output at the LM311 input. When the ramp voltage nulls out the bound voltage, the comparator changes state and the integrator output reverses. The resultant, repetitive triangle waveform is applied to the sine shaper configuration. The sine shaper utilizes the non-linear, logarithmic relationship between  $V_{be}$  and collector current in transistors to smooth the triangle wave. The LM394 dual transistor is used to generate the actual shaping while the 2N3810 provides current drive. The LF351 allows adjustable, low impedance, output amplitude control. Waveforms of operation are shown in [Figure 17](#).




- A All diodes = 1N4148  
Adjust symmetry and wave-shape controls for minimum distortion  
\* LM311 Ground Pin (Pin 1) at -15V
- B Logarithmic shaping schemes produce a sine wave oscillator that you can tune from 1 Hz to 10 kHz with a single control. Additionally, you can shift frequencies rapidly because the circuit contains no control-loop time constants.

Figure 14. Logarithmic Shaping Scheme


## 11 Sine Approximation—Voltage Controlled Sine Oscillator

Figure 15 details a modified but extremely powerful version of Figure 14. Here, the input voltage to the LF356 integrator is furnished from a control voltage input instead of the zener diode bridge. The control input is inverted by the LF351. The two complementary voltages are each gated by the 2N4393 FET switches, which are controlled by the LM311 output. The frequency of oscillation will now vary in direct proportion to the control input. In addition, because the amplitude of this circuit is controlled by limiting, rather than a servo loop, response to a control step or ramp input is almost instantaneous. For a 0V–10V input the output will run over 1 Hz to 30 kHz with less than 0.4% distortion. In addition, linearity of control voltage vs output frequency will be within 0.25%. Figure 16 shows the response of this circuit (waveform B) to a 10V ramp (waveform A).

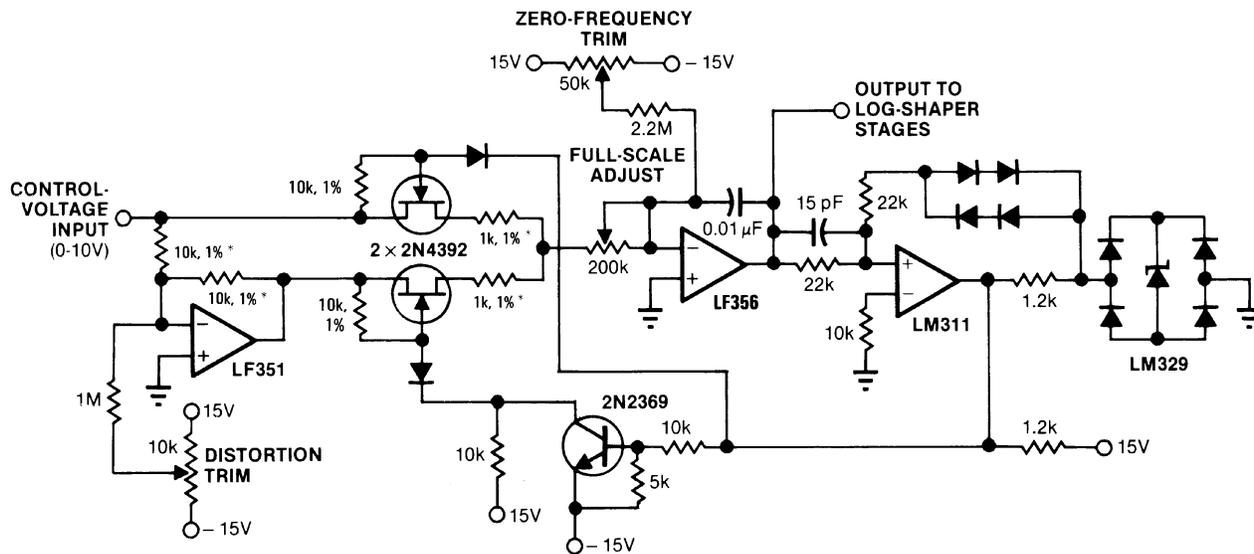

- A Adjust distortion for minimum at 1 Hz to 10 Hz  
Adjust full-scale for 30 kHz at 10V input  
All diodes = 1N4148  
\* Match to 0.1%
- B A voltage-tunable oscillator results when Figure 14's design is modified to include signal-level- controlled feedback. Here, FETs switch the integrator's input so that the resulting summing-junction current is a function of the input control voltage. This scheme realizes a frequency range of 1 Hz to 30 kHz for a 0V to 10V input.

Figure 15. Voltage-Tunable Oscillator

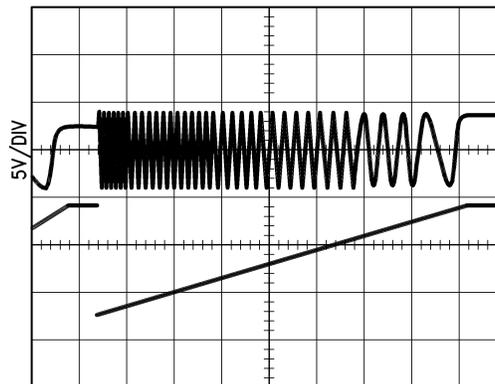


- A Rapid frequency sweeping is an inherent feature of Figure 15's voltage-controlled sine wave oscillator. You can sweep this VCO from 1 Hz to 30 kHz with a 10V input signal; the output settles quickly.

Figure 16. Voltage-Tunable Oscillator Waveforms
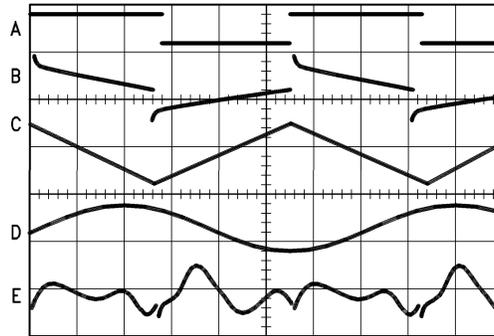
## 12 Sine Approximation—Digital Methods

Digital methods may be used to approximate sine wave operation and offer the greatest flexibility at some increase in complexity. Figure 18 shows a 10-bit IC D/A converter driven from up/down counters to produce an amplitude-stable triangle current into the LF357 FET amplifier. The LF357 is used to drive a shaper circuit of the type shown in Figure 14. The output amplitude of the sine wave is stable and the frequency is solely dependent on the clock used to drive the counters. If the clock is crystal controlled, the output sine wave will reflect the high frequency stability of the crystal. In this example, 10 binary bits are used to drive the DAC so the output frequency will be 1/1024 of the clock frequency. If a sine coded read-


only-memory is placed between the counter outputs and the DAC, the sine shaper may be eliminated and the sine wave output taken directly from the LF357. This constitutes an extremely powerful digital technique for generating sine waves. The amplitude may be voltage controlled by driving the reference terminal of the DAC. The frequency is again established by the clock speed used and both may be varied at high rates of speed without introducing significant lag or distortion. Distortion is low and is related to the number of bits of resolution used. At the 8-bit level only 0.5% distortion is seen (waveforms, [Figure 19](#); graph, [Figure 20](#)) and filtering will drop this below 0.1%. In the photo of [Figure 19](#) the ROM directed steps are clearly visible in the sine waveform and the DAC levels and glitching show up in the distortion analyzer output. Filtering at the output amplifier does an effective job of reducing distortion by taking out these high frequency components.



A Logarithmic shapers can utilize a variety of circuit waveforms. The input to the LF356 integrator ([Figure 14](#)) appears here as trace A. The LM311's input (trace B) is the summed result of the integrator's triangle output (C) and the LM329's clamped waveform. After passing through the 2N3810/LM394 shaper stage, the resulting sine wave is amplified by the LF351 (D). A distortion analyzer's output (E) represents a 0.35% total harmonic distortion.


**Figure 17. Logarithmic Shaper Waveforms**

Trace	Vertical	Horizontal
A	20V/DIV	
B	20V/DIV	20 μs/DIV
C	10V/DIV	
D	10V/DIV	
E	0.5V/DIV	

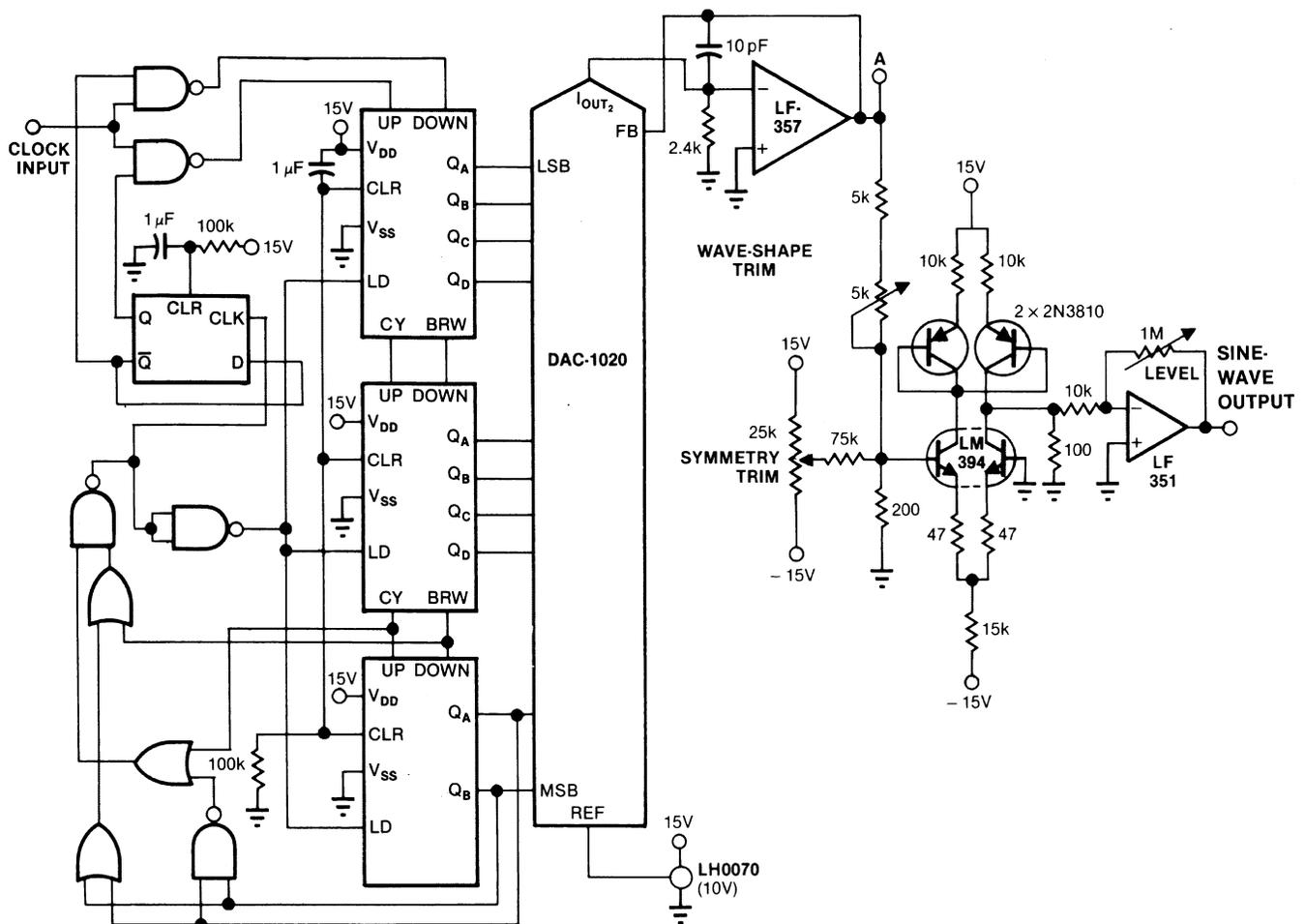

- A MM74C00 = NAND  
MM74C32 = OR  
MM74C74 = D flip-flop  
MM74193 = counters
- B Digital techniques produce triangular waveforms that methods employed in Figure 14 can then easily convert to sine waves. This digital approach divides the input clock frequency by 1024 and uses the resultant 10 bits to drive a DAC. The DAC's triangular output—amplified by the LF357—drives the log shaper stage. You could also eliminate the log shaper and place a sine-coded ROM between the counters' outputs and the DAC, then recover the sine wave at point A.


Figure 18. Log Shaper

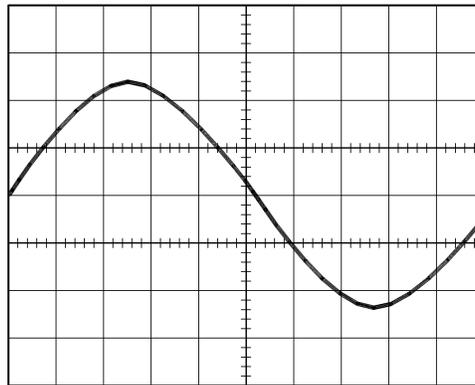

- A An 8-bit sine coded ROM version of Figure 18's circuit produces a distortion level less than 0.5%. Filtering the sine output—shown here with a distortion analyzer's trace—can reduce the distortion to below 0.1%.

**Figure 19. Filtered Sine Output**

Trace	Vertical	Horizontal
Sine Wave	1V/DIV	200 $\mu$ s/DIV
Analyzer	0.2V/DIV	

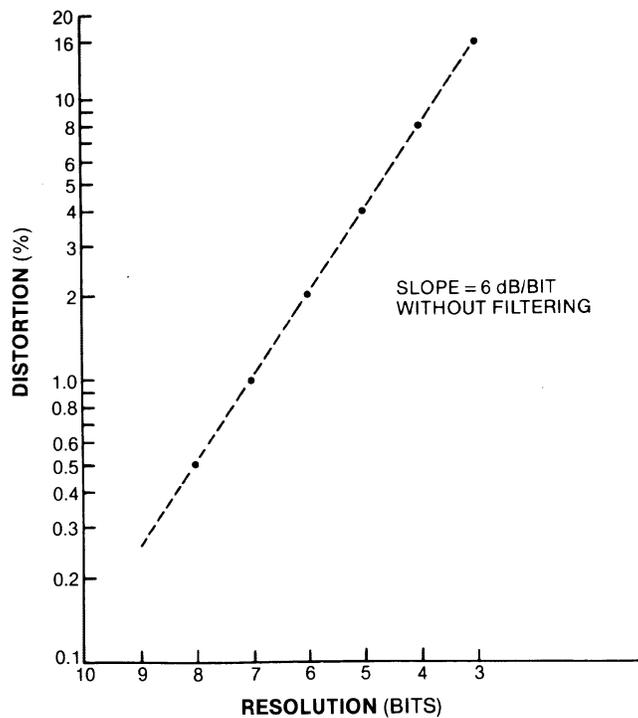

- A Distortion levels decrease with increasing digital word length. Although additional filtering can considerably improve the distortion levels (to 0.1% from 0.5% for the 8-bit case), you're better off using a long digital word.

**Figure 20. Distortion Levels**

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)