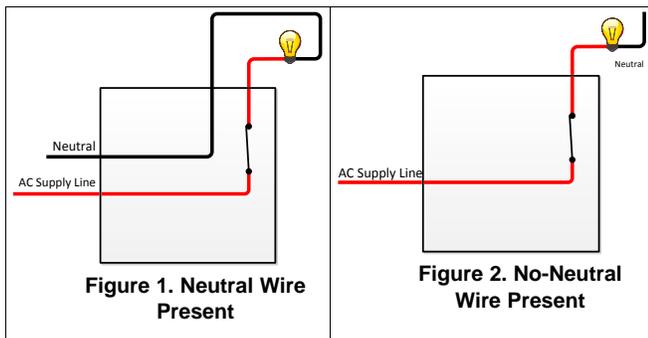


Current Sensing in No-Neutral Light Switches


Adam Althar, Analog Signal Chain



Light switch boxes can be broken down into two major topologies: switch boxes that have a neutral wire run through them, and those which do not. Traditionally in light switches, a switch in the “On” position closes a switch in the line, creating a path for current to flow to a light bulb. In the “Off” position, this switch is opened, thus breaking the current loop. [Figure 1](#) shows a light switch box which has a neutral wire run through it. [Figure 2](#) shows a switch box without a neutral wire running through it.



A problem arises with the introduction of “Smart” switches designed to allow a user to control lighting through various devices like smartphones. For these switches to operate, there are internal components which require constant power, even when the light is turned off. This is necessary so that the switch can still be controlled remotely. In switch boxes with a neutral wire in them, this is not a problem as the neutral wire can be used to create a path for current to flow through even when the switch is in the off position. In switch boxes without a neutral wire, there must be a constant flow of current through the bulb as this is the only path for the current to flow. This challenge means special consideration must be taken when designing a smart switch for no-neutral switch boxes. It is important to use components that require as little current as possible. If the internal components require too much current, it will cause the light bulb to illuminate even when it is turned off. [Figure 3](#) demonstrates the path that is possible in switch boxes with a neutral wire. [Figure 4](#) shows the current path for a switch box without a neutral wire. It is still possible to have a physical switch in a no-neutral setup in the event that the user wants to prevent any current from flowing through the path. However this would also prevent any power from being delivered to the components of the switch as well.

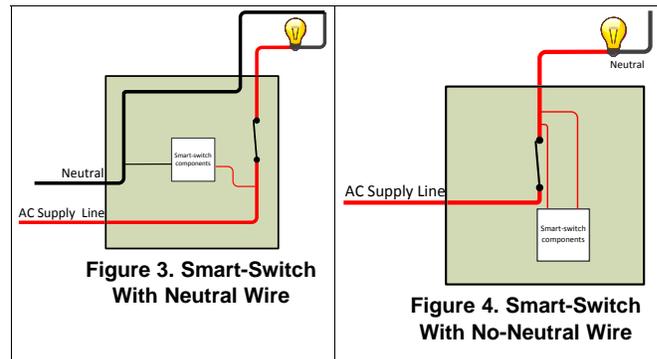

One important internal component of a smart switch is the current-sensing chain. As many smart switches allow the user to set various brightness levels it is important for the microcontroller in the switch to know how much current is being delivered to the bulb to determine its brightness. Current sensing is a technique that is performed by placing an op-amp across a low-resistance shunt resistor that is in series with the bulb. Ohm’s Law tells us that the voltage drop across a resistor is directly related to the current flowing through this resistor. This voltage difference across the resistor is gained up by the op-amp which outputs to an analog to digital converter that is communicating with a microcontroller. The microcontroller uses this input to determine of the current flowing through the bulb.

One very suitable device for this application is the [LPV821](#). The LPV821 is the Industry’s first nanopower zero-drift precision amplifier, with a quiescent current of only 700 nA. The ultra-low current consumption of the LPV821 helps to solve the problem of allowing the internal components of the switch to operate as needed while minimizing current draw. Lower current draw from this device also opens up more overhead for the other components to utilize more current without exceeding a threshold that would cause the bulb to illuminate, or cause the bulb to flicker from the leakage current of the other components.

The zero-drift aspect of the LPV821 also makes it an excellent fit for this application. The LPV821 has an offset voltage of $\pm 20 \mu\text{V}$, allowing the amplifier to have a high accuracy output with only a small voltage drop across the shunt resistor. This means that a very small resistance shunt resistor can be used while still

generating enough of a voltage drop to be detected by the op-amp. As the power dissipated in a resistor is equal to the current squared times the resistance, being able to use a smaller resistor means less power dissipation.

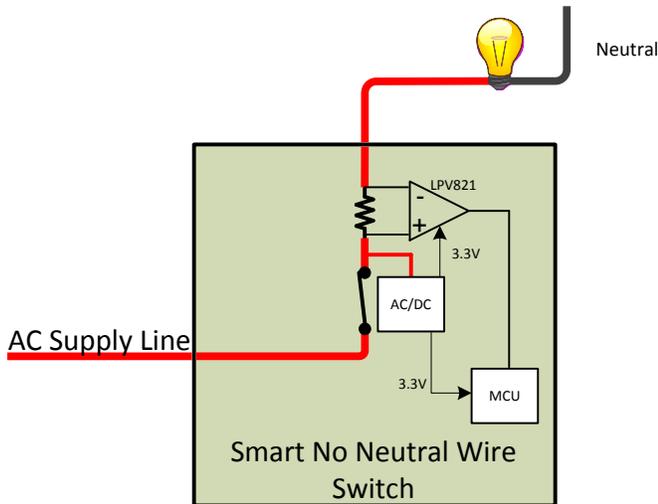


Figure 5. No-Neutral Switch Block Diagram With the LPV821

Figure 5 contains a basic block diagram for using the LPV821 in a Smart No-Neutral switch. Here the LPV821 is placed across a shunt resistor and is feeding information to an analog-to-digital converter that communicates with the microcontroller. There is also an AC to DC converter that steps the 220-V AC down input to a 3.3-V DC signal. This signal is within supply voltage range of the LPV821, and is also used to provide power to the microcontroller.

Another way the LPV821 can be used in a no neutral light switch is as part of a current protection string. By using the output of the LPV821 as the positive input node of a comparator, with a reference voltage on the negative input node the output of the comparator will

shift to the positive rail of the comparator once the voltage on the positive node surpasses the reference voltage. This can be used to raise a flag on the microcontroller to alert of overcurrent as is shown in Figure 6. In this diagram a TLV3691 comparator is used. The TLV3691 is a nanopower comparator making it an ideal fit for low-power applications such as this. The output of the comparator could also be connected to a FET that would create an open circuit if an overcurrent scenario occurs.

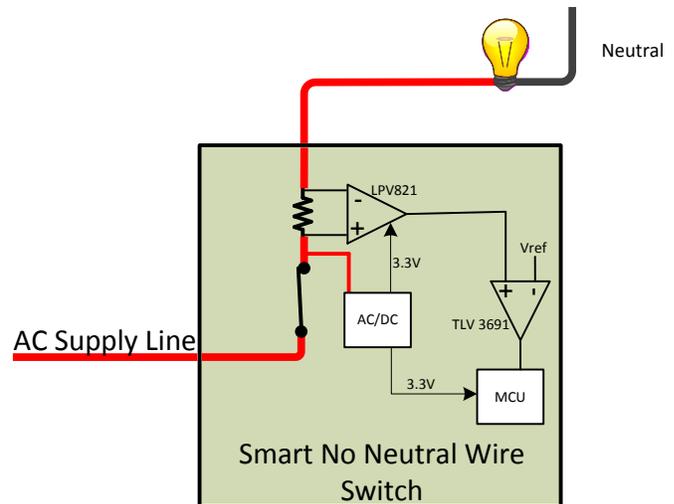


Figure 6. Configuration With TLV3691 Comparator

Alternate Device Recommendations

For applications where quiescent current must be reduced even further the LPV521 is a suitable alternate device offering a quiescent current of only 325 nA, but has a higher offset voltage at 1 mV.

Table 1. Alternate Device Recommendations

DEVICE	OPTIMIZED PARAMETERS	PERFORMANCE TRADE-OFF
OPA333	Supply Voltage Range, Precision	Quiescent Current
LPV811	Quiescent Current	Precision
LPV521	Quiescent Current	Precision

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2017, Texas Instruments Incorporated