

Advantages of Using Nanopower, Zero Drift Amplifiers for Battery Voltage and Current Monitoring in Portable Applications

Jaskaran Atwal, Analog Signal Chain



Lithium Ion batteries have become the chemistry of choice for portable applications such as laptops, cell phones, and cameras. As devices get smaller and lighter, with increased features by the generation, the device battery becomes a critical component of the system. The battery not only determines how long the device can be used before a recharge is needed, it also influences the size, cost, and weight of the device. In addition, these devices need to be efficient while also providing or receiving safe and reliable fast charging. As an example, fast charging in mobile phones provides charge to the battery in the shortest amount of time while still maintaining device performance and battery health. There are many custom methods for providing fast charging to a battery, but each of these requires being able to accurately monitor the voltage and current in and out of the battery.

A typical charging stage of a mobile phone consists of the charger, battery, battery monitoring stage, and MCU as shown in Figure 1. The voltage and current sensing takes place in the battery monitoring stage. The goal of this stage is to accurately monitor the current and voltage of the battery while using the least amount of power possible.

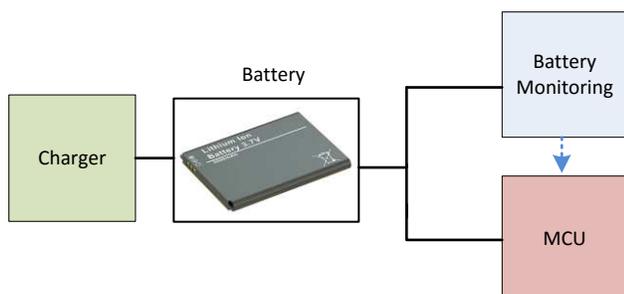


Figure 1. Mobile Phone Charging Stage

Current monitoring is typically done by placing an op-amp across a low resistance shunt resistor that is in series with the battery. In order to ensure the correct current measurement while maximizing the battery life, the op amp needs to be both precise and low power. One suitable op amp for this application is the LPV821. The LPV821 is the industry's first zero-drift nanopower amplifier, with quiescent current of only

650nA. The ultra-low current consumption of the LPV821 ensures the battery life is extended for as long as possible. The zero-drift, self-calibrating architecture of the LPV821 also makes it an excellent choice for this application. The LPV821 has an offset voltage of $\pm 10 \mu\text{V}$, enabling a very low shunt resistor value to be used while minimizing introduced error. Ohm's Law tells us the power dissipated across the resistor is proportional to the resistance value and current flowing through it. With a smaller resistance value, less power will be dissipated across the resistor. This, combined with the LPV821's nanopower consumption, means less power will be drained from the battery itself during the current measurement.

An example of this current measurement is shown in Figure 2. The LPV821 is used to measure the voltage of the shunt resistor through a single ended configuration. In this configuration, the trace resistance to ground in series with the shunt resistor becomes an important factor in introducing error to the measurement.

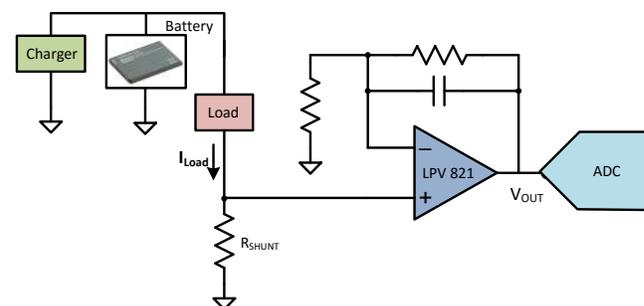


Figure 2. Single Ended Input Configuration

The LPV821 can also be used as a differential amplifier to perform current measurement. The example circuit is shown in Figure 3. This configuration eliminates the inaccuracy due to the trace resistance discussed in the single ended configuration. However, the CMRR of the op amp becomes important in this configuration and must be high, as it is in the LPV821, in order to obtain accurate measurements.

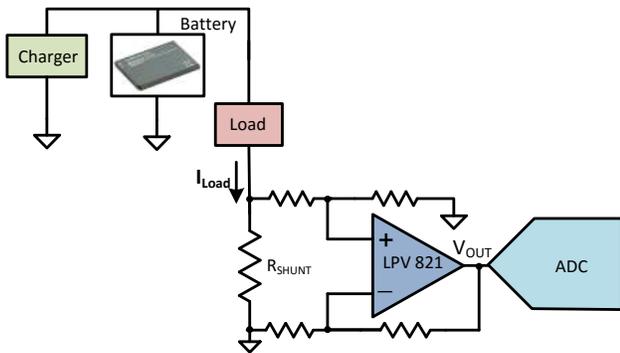


Figure 3. Differential Amplifier Configuration

There are also applications where there is the need to measure both charge and discharge currents. This method is known as bidirectional current sensing and an example circuit of this is shown in Figure 4. When a mobile phone is plugged in to the charging adapter, the adapter supplies power to the mobile phone and charges the battery. In this scenario the battery charging current is monitored to ensure the battery does not overheat and the power drawn from the charging adapter does not exceed limits. This is especially critical during fast charging when the temperature of the device can rise more than normal operation. When the battery is powering the system, the discharge current from the battery is monitored for the purpose of active power management to extend battery life. Based on these measurements actions can be taken to reduce power consumption and improve efficiency of the overall system. Two LPV821s can be used to perform bidirectional current sensing. The low power consumption of the LPV821 ensures the least amount of power is used during this measurement and more power is conserved for other features of the phone.

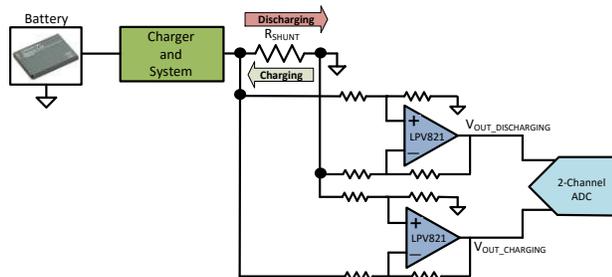


Figure 4. Bidirectional Current Sensing

The battery voltage, along with the current sensing methods described above, also needs to be measured for custom fast charging methods. The battery voltage is monitored in order to determine the stage of the charging profile. The LPV821 is an excellent fit for this application due to its low input offset and allows for accurate battery voltage monitoring. Along with that, the ultra-low power consumption of the LPV821 ensures the least amount of battery drain for this measurement. The measurement can be made by using the LPV821 as a voltage buffer to measure the voltage of the battery over a voltage divider as seen in Figure 5.

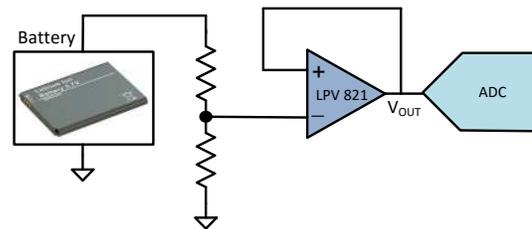


Figure 5. Battery Voltage Monitoring

In order to implement a custom fast charging solution, accurate measurements of charge/discharge currents and cell voltage are necessary. The nanopower, zero-drift LPV821 can be used to make these measurements accurately and does so in a power efficient manner, thus extending battery life.

Table 1. Alternative Device Recommendations

Device	Quiescent Current (Typ.)	GBW	Offset Voltage (Max)
LPV521	350nA	6.2 kHz	1mV
LPV812	425nA	8 kHz	300uV
OPA369	700nA	12 kHz	750uV
OPA333	17uA	350 kHz	10uV

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2017, Texas Instruments Incorporated