

Application Brief

Space-Grade, 100-krad, Discrete, Three Op Amp Instrumentation Amplifier Circuit




Nicholas Butts

Design Goals

Input		Output		Common-mode Voltage	Supply			Total Ionizing Dose	SEL Immunity
V_{d_min}	V_{d_max}	V_{out_min}	V_{out_max}	V_{cm}	V_+	V_-	V_{ref}	$\geq 100\text{krad(Si)}$	$\geq 85\text{ MeV}\cdot\text{cm}^2/\text{mg}$
-50 mV	50 mV	0.2 V	5 V	5 V	10 V	0 V	2.6 V		

Design Description

This design uses discrete op amps to implement an instrumentation amplifier (IA) design using space-grade (SP) components for use in space applications. The circuit converts a differential signal to a single-ended output signal. Linear operation of an instrumentation amplifier depends upon linear operation of its building block: op amps. An op amp operates linearly when the input and output signals are within the respective input common-mode and output swing ranges of the device. The supply voltages used to power the op amps define these ranges.

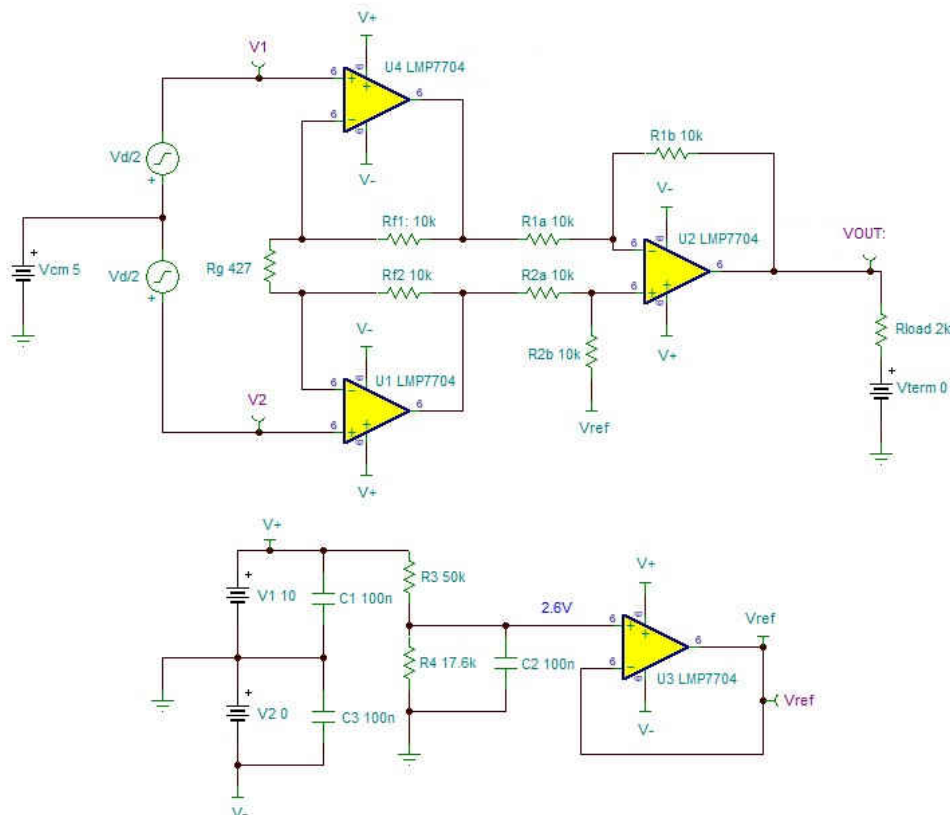

Design Notes

1. Use low-tolerance resistors to achieve high DC CMRR performance. Mismatching of resistors can also lead to errors in gain and output accuracy.
2. All resistors and capacitors must be verified space-grade for this design.
3. R_g sets the gain of the input stage. R_{1a} and R_{1b} can be used to set the gain of the second stage (see [Design Steps](#)).
4. R_{f1} and R_{f2} are nominally matched in this design. In general, R_{f1} and R_{f2} do not need to be matched – it may be desirable in some cases to have R_{f1} and R_{f2} unmatched so that the top amplifier and bottom amplifier in the input stage have different gains. For example, if V_{cm} is not at mid-supply but is closer to one of the rails, R_{f1} and R_{f2} can be tuned so that neither of the input stage amplifiers run out of headroom.
5. Integrated instrumentation amplifiers normally have a fixed minimum gain. In addition to using an IA in high-gain configurations, constructing a discrete IA like this affords the flexibility to achieve any gain less than 1 V/V.
6. High-value resistors can degrade the phase margin of the circuit and introduce additional noise in the circuit.
7. Add an isolation resistor to the output stage to drive large capacitive loads.
8. Linear operation is contingent upon the input common-mode and the output swing ranges of the discrete op amps used. For best performance, choose $V_{cm} = (V_+ + V_-) / 2$ (mid-supply).
9. C_2 along with $R_3 \parallel R_4$ forms a low-pass filter with a corner frequency of 147.16 Hz.
10. The V_{ref} pin must be supplied by a low-impedance reference that can sink and source current, such as a buffer. Using a high-impedance reference, such as a resistor divider with no buffer, may result in a mismatch and degradation of CMRR.
11. V_{out_min} is chosen as 0.2 V for this design to avoid nonlinearities associated with the output of LMP7704-SP swinging too close to the rail. If this design is done with a different op amp, be sure to check the data sheet to determine the minimum and maximum output values allowed.
12. The [LMP7704-SP](#) supply voltage of 10 V was selected according the derating specifications provided by the National Aeronautics and Space Administration (NASA) in document [EEE-INST-002](#) (April 2008) and the European Cooperation for Space Standardization (ECSS) in document [ECSS-Q-ST-30-11C Rev.1](#) (4 October 2011). The documents specify an 80% and 90% derating of the absolute maximum supply voltage for linear ICs, respectively.
13. This design can be implemented with a single 4-channel LMP7704-SP or a similar device. See [Design Alternative Op Amp](#) for a wider supply op amp (36 V). Note that the listed alternative device meets TID = 50 krad(Si).

Design Steps

1. Calculate the output voltage V_{out} for this circuit using the following equation:

$$V_{out} = \left(1 + \frac{R_{f1} + R_{f2}}{R_g} \right) \times \frac{R_{1b}}{R_{1a}} \times V_d + V_{ref}$$

In this equation, $V_d = V_2 - V_1$ is the differential input voltage, V_{ref} is set by R_3 and R_4 to level shift the output, and it is assumed that $R_{1a} = R_{2a}$ and $R_{1b} = R_{2b}$. Integrated instrumentation amplifiers normally fix R_{f1} , R_{f2} , R_{1a} , R_{2a} , R_{1b} , and R_{2b} , leaving only R_g to set the gain of the circuit. In this discrete implementation, the designer has the freedom to alter all of these resistors, but the transfer function can be simplified by using standard values, such as $R_{f1} = R_{f2} = R_{1a} = R_{1b} = R_{2a} = R_{2b} = 10k\Omega$, and using only R_g to set the gain. In this case, R_g can be calculated using the following simplified equation:

$$V_{out} = \left(1 + \frac{20k\Omega}{R_g} \right) \times V_d + V_{ref}$$

2. Set V_{ref} . For this design, V_{ref} has been set as shown in the following equation so that a symmetric input voltage range of $-50mV$ to $+50mV$ results in an output voltage range of $0.2V$ to $5V$.

$$V_{ref} = 2.6V = \frac{V_{out_max} + V_{out_min}}{2} = \frac{5V + 0.2V}{2}$$

$$V_{ref} = 2.6V = V_+ \times \frac{R_4}{R_3 + R_4} = 12V \times \frac{R_4}{50k\Omega + R_4}$$

$$R_4 = 13.83k\Omega \approx 13.8k\Omega \text{ (standard value)}$$

Note

The magnitudes of R_3 and R_4 were chosen such that $R_3 \parallel R_4$ is close to $10k\Omega$ so that the low-pass filter formed by $R_3 \parallel R_4$ and C_2 is close to the common low-pass filter with $R = 10k\Omega$ and $C = 100nF$.

3. Choose R_g to set the required gain using the simplified transfer function.

$$5V = \left(1 + \frac{20k\Omega}{R_g} \right) \times 50mV + 2.6V$$



$$R_g = 425\Omega \approx 427\Omega \text{ (standard value)}$$

This corresponds to a gain of:

$$G = 1 + \frac{20k\Omega}{427\Omega} = 47.84V / V$$


Transient Simulation Results

  With the low-pass filter formed by R_3 , R_4 , and C_2 , V_{ref} takes about 6ms to come up to its target value:



V_{cm} versus V_{out} Limitations

 The following figure shows the allowable output voltage range for a given V_{cm}.



Design References

1. [FAQ](#) - How do Instrumentation Amplifiers (INAs) fit into my design?
2. [TI Precision Labs](#) - Online training course discussing instrumentation amplifier theory and application
3. [Instrumentation Amplifier \$V_{cm}\$ vs. \$V_{out}\$ Plots](#)
4. [Analog Engineer's Calculator](#)

Design Featured Op Amp

LMP7704-SP	
V_{supply}	$\pm 1.35V$ to $\pm 6V$
V_{inCM}	$(V_-) - 0.2V$ to $(V_+) + 0.2V$
V_{out}	$(V_-) - 120mV$ to $(V_+) + 120mV$
V_{os}	$\pm 32\mu V$
I_q	725 μA per channel
I_b	$\pm 200fA$
UGBW	2.5MHz
SR	0.9V/ μs
#Channels	4
Total Ionizing Dose	100krad(Si)
SEL Immunity to LET	85MeV $\cdot cm^2/mg$
www.ti.com/product/LMP7704-SP	

Design Alternate Op Amp

OPA4277-SP	
V_{supply}	$\pm 2V$ to $\pm 18V$
V_{inCM}	$(V_-) + 2V$ to $(V_+) - 2V$
V_{out}	$(V_-) + 1.5V$ to $(V_+) - 1.5V$
V_{os}	$\pm 20\mu V$
I_q	790 μA per channel
I_b	$\pm 17.5nA$
UGBW	1MHz
SR	0.8V/ μs
#Channels	4
Total Ionizing Dose	50krad(Si)
SEL Immunity to LET	85MeV $\cdot cm^2/mg$
www.ti.com/product/OPA4277-SP	

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated