

Design Notes

1. Use low-tolerance resistors to achieve high current gain matching accuracy.
2. All resistors and capacitors must be verified space-grade for this design.
3. In this design, I_{ret} is a local ground, separate from the supply ground, and must be allowed to float.
4. The current through R_3 can be considered a quiescent current. That is, it is a current that should be minimized so as to not use up the current budget. However, as I_3 gets smaller, the matching ratio R_3 / R_4 gets larger, so in practice I_3 cannot be made arbitrarily small.
5. For linear operation, the ratio of the current through R_3 when $V_{in} = V_{in_max}$ and $V_{in} = V_{in_min}$, I_{3_max} / I_{3_min} , must be equal to the ratio of the maximum output current to the minimum output current, $I_{out_max} / I_{out_min}$.
6. This discrete 2-wire current transmitter solution allows the flexibility to set the output current to be different than the standard 4–20 mA or 4–24 mA. This may be necessary because options for space-grade components are relatively limited. For example, if the total quiescent current for the current transmitter plus surrounding peripherals on the same supply loop cannot meet the requirement that they sum to less than I_{out_min} (= 4 mA for this design), the output current range may be shifted to 8–24 mA or something similar.
7. C_1 is a bypass compensation capacitor and is required for the stability of the circuit. Recommended capacitor is 100 nF or greater.
8. R_5 and C_2 are additional components for compensating the circuit. They are not required for stability, but are added for flexibility if additional compensation is required.
9. C_3 is a required output capacitor for the TPS7A4501-SP. Recommended capacitor is 1 μ F to 10 μ F for stability.
10. R_6 linearizes the relationship between the op-amp output and the current through the transistor and limits the current through the transistor.
11. This design can be implemented with a single LMP2012QML-SP or a similar device. See [Design Alternate Op Amp](#) for an alternative device.

Theory of Operation

A 4–20-mA V-to-I current transmitter takes a differential voltage as the input and outputs a current with a linear relationship from input to output. This linear relationship depends on the common-mode range of the op amp and the headroom available for the transistor and LDO. Furthermore, a current transmitter designed with a 2-wire loop requires that the quiescent current drawn from all components on the loop path consume less than the minimum output current $I_{\text{out, min}} - 4 \text{ mA}$ in this design. This includes the op amp, LDO, the current through the R_3 and R_5 branch, and any other peripherals that are on the same supply loop. As long as this requirement is met, the op amp and transistor compensate to supply the remaining current to the loop to output the correct current to the load resistor.

The output current I_{out} is the sum of the currents through R_3 and R_4 , I_3 , and I_4 , respectively:

$$I_{\text{out}} = I_3 + I_4$$

I_3 is set by R_1 and R_2 , along with the input voltage V_{in} and regulated supply V_{reg} . Under ideal operation, the non-inverting terminal of the op amp has a virtual short to the local ground, I_{ret} . Notice also that V_{reg} and V_{in} are referenced to I_{ret} . I_3 is then the following:

$$I_3 = \frac{V_{\text{in}}}{R_1} + \frac{V_{\text{reg}}}{R_2}$$

I_4 is the sum of the local ground return current I_{ret} and the compensating current through the transistor T_1 .

For correct operation of the op amp, the voltages across R_3 and R_4 must be equal, so we have $V_3 = V_4$ and it follows that:

$$I_3 R_3 = I_4 R_4$$

The previous equation is rewritten as:

$$I_4 = I_3 \frac{R_3}{R_4}$$

Combining the first equation, second equation, and previous equation, the transfer function for the circuit is derived as:

$$I_{\text{out}} = \left(\frac{V_{\text{reg}}}{R_2} + \frac{V_{\text{in}}}{R_1} \right) \left(1 + \frac{R_3}{R_4} \right) = I_3 \left(1 + \frac{R_3}{R_4} \right)$$

It is apparent, then, that the current through R_3 that is set by R_1 , R_2 , V_{in} , and V_{reg} is amplified by the factor $1 + R_3 / R_4$.

Design Steps

See the [Design References](#) section for an Excel calculator that calculates the resistor values for the required specifications.

1. Define the input voltage range for the circuit. For this design $V_{in_min} = 0\text{ V}$, $V_{in_max} = 5\text{ V}$ is chosen.
2. Define the output current range for the circuit. For this design $I_{out_min} = 4\text{ mA}$, $I_{out_max} = 20\text{ mA}$ is selected.
3. Calculate R_7 and R_8 to set the output voltage for the TPS7A4501-SP LDO. The equation to set the output voltage for this adjustable LDO follows:

$$V_{reg} = V_{ref} * \left(1 + \frac{R_7}{R_8}\right)$$

In this equation, V_{ref} is the internal bandgap reference voltage for the LDO. TPS7A4501-SP has a nominal reference voltage $V_{ref} = 1.21\text{ V}$ and this design is targeting $V_{reg} = 5\text{ V}$, so the following applies:

$$5\text{V} = 1.21\text{V} * \left(1 + \frac{R_7}{R_8}\right)$$

$$\frac{R_7}{R_8} = 3.13$$

To choose values, the following guideline is used: The current in the feedback resistors from output to ground of an LDO must be at least 100 times the leakage current into the ADJ pin to avoid output accuracy issues. For TPS7A4501-SP, the leakage current of the ADJ pin is $3\text{ }\mu\text{A}$ (typ). This yields the following inequality:

$$\frac{V_{reg}}{R_7 + R_8} \geq 100 * 3\mu\text{A}$$

$$\frac{5\text{V}}{R_7 + R_8} \geq 300\mu\text{A}$$

$$16.67\text{ k}\Omega \geq R_7 + R_8$$

With $R_8 = 3.97\text{ k}\Omega$ (standard value), the following equation is true:

$$R_7 = 3.97\text{ k}\Omega * 3.13 = 12,426\text{ }\Omega \approx 12.4\text{ k}\Omega \text{ (standard value)}$$

With these values for R_7 and R_8 , the following equation is valid:

$$R_7 + R_8 = 3.97\text{ k}\Omega + 12.4\text{ k}\Omega = 16.37\text{ k}\Omega \leq 16.67\text{ k}\Omega$$

Note

Since this design has a current budget limitation, it is desirable to size R_7 and R_8 to be near the limit to minimize this quiescent current contribution.

4. Define the minimum and maximum currents through R_3 . See [Design Note #5](#) before defining these currents. For this design, $I_{3_min} = 20\text{ }\mu\text{A}$, $I_{3_max} = 100\text{ }\mu\text{A}$, is chosen.

5. Calculate the values for R_1 and R_2 to set I_{3_min} and I_{3_max} as defined in [Design Step #4](#). To do this, use the first [equation](#) along with the specifications for V_{reg} , V_{in_min} , V_{in_max} , I_{3_min} and I_{3_max} . When $V_{in} = V_{in_min}$, the following equations occur:

$$I_{3_min} = \frac{V_{in_min}}{R_1} + \frac{V_{reg}}{R_2}$$

$$20\mu A = \frac{0V}{R_1} + \frac{5V}{R_2} = \frac{5V}{R_2}$$

$$R_2 = 250 \text{ k}\Omega \text{ (standard value)}$$

When $V_{in} = V_{in_max}$, the following is true:

$$I_{3_max} = \frac{V_{in_max}}{R_1} + \frac{V_{reg}}{R_2}$$

$$100\mu A = \frac{5V}{R_1} + \frac{5V}{250\text{k}\Omega}$$

$$R_1 = 62.5 \text{ k}\Omega \approx 62 \text{ k}\Omega \text{ (standard value)}$$

6. Calculate R_3 / R_4 to set the required current gain. To do this, use this [equation](#) along with I_{out_min} and I_{3_min} .

$$4\text{mA} = 20\mu A * \left(1 + \frac{R_3}{R_4}\right)$$

$$\frac{R_3}{R_4} = 199$$

Note

Only the minimum values of I_{out} and I_3 are required to calculate R_3 / R_4 because it is assumed that [Design Note #5](#) has been followed.

7. Choose values for R_3 and R_4 . Sizing R_3 is much less important than sizing R_4 because headroom issues can arise if care is not taken when sizing R_3 . To see why, analyze the nodal voltages under the maximum loading condition, $I_{out} = I_{out_max} = 20 \text{ mA}$. The load voltage is the following:

$$V_{load} = I_{out_max} * R_{load} = 20 \text{ mA} * 250 \Omega = 5 \text{ V}$$

Most of the output current comes through R_4 , so with $R_4 = 100 \Omega$, the voltage at I_{ret} is approximately:


$$5 \text{ V} + 100 \Omega * 20 \text{ mA} = 7 \text{ V}$$

V_{reg} is referenced to I_{ret} , so relative to the supply ground, $V_{reg} = 7 \text{ V} + 5 \text{ V} = 12 \text{ V}$, in which case the LDO enters dropout. If the LDO enters dropout, the LDO loses its power supply rejection (PSR) properties, and the op amp has a reduced positive supply and so has a reduced ability to drive the base of the transistor to provide additional output current. Furthermore, if V_{reg} droops, the current through R_3 will be reduced and the circuit begins to exhibit non-linear behavior. Also, if R_6 is too large, the additional voltage drop across R_6 further reduces the available headroom for the transistor.

With these considerations in mind, choose $R_4 = 50 \Omega$ to avoid problems with headroom. It follows that:

$$R_3 = 199 * 50 \Omega = 9.95 \text{ k}\Omega \approx 9.88 \text{ k}\Omega \text{ (standard value)}$$

Transient Simulation Results

 

Design References

1. Texas Instruments, [Excel Calculator Tool](#)
2. Texas Instruments, [TI Precision Labs - Current Loop Transmitters](#)
3. Texas Instruments, [Low Cost Loop-Powered 4-20mA Transmitter EMC/EMI Tested Reference Design](#)

Design Featured Op Amp

LMP2012QML-SP	
V_{supply}	
V_{inCM}	-0.3 V to (V_+) +0.3 V
V_{out}	(V_-) + 40 mV to (V_+) - 22 mV
V_{os}	±120 nV
I_q	930 μ A per channel
I_b	-3 pA
UGBW	3 MHz
SR	4 V/ μ s
#Channels	2
Total Ionizing Dose	50 krad(Si)
SEL Immunity to LET	77.5 MeV·cm ² /mg
https://www.ti.com/product/LMP2012QML-SP	

Design Alternate Op Amp

LMP7704-SP	
V_{supply}	±1.35 V to ±6 V
V_{inCM}	(V_-) - 0.2 V to (V_+) + 0.2 V
V_{out}	(V_-) - 120 mV to (V_+) + 120 mV
V_{os}	±32 μ V
I_q	725 μ A per channel
I_b	±200 fA
UGBW	2.5 MHz
SR	0.9 V/ μ s
#Channels	4
Total Ionizing Dose	100 krad(Si)
SEL Immunity to LET	85 MeV·cm ² /mg
http://www.ti.com/product/LMP7704-SP	

Design Featured LDO

TPS7A4501-SP	
V_{in}	2.3 V to 20 V
V_{out}	1.21 V to 20 V (adjustable output)
I_{out}	750 mA
V_{do} (dropout voltage)	20 mV
I_q	1.1 mA
#Channels	1
Total Ionizing Dose	150 krad(Si)
SEL Immunity to LET	91.9 MeV·cm ² /mg
https://www.ti.com/product/TPS7A4501-SP	

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated