

***AN-557 Optimizing the Ultra-Fast POWERplanar Rectifier Diode for Switching
Power Supplies***



Literature Number: SNVA007

Optimizing the Ultra-Fast POWERplanar™ Rectifier Diode for Switching Power Supplies


National Semiconductor
Application Note 557
Ralph E. Locher
January 1989



Optimizing the Ultra-Fast POWERplanar Rectifier Diode for Switching Power Supplies


INTRODUCTION

A key device in all high voltage AC-DC power supplies is the ultrafast, reverse recovery rectifier diode. These diodes (D1 and D2 in *Figure 1*) not only play a major role in power supply efficiency but also can be major contributors to circuit electromagnetic interference (EMI) and even cause transistor failure if they are not selected correctly. One would assume that by now, this rectifier diode should approximate the behavior of an ideal switch, i.e., zero on-state voltage, no reverse leakage current and instantaneous turn-on. At first glance, the design of this single pn-junction device would appear to be quite straight forward but a review of the device equations reveals that many compromises must be made to optimize its performance. An understanding of these tradeoffs will allow the circuit designer to select the most appropriate rectifier diode.

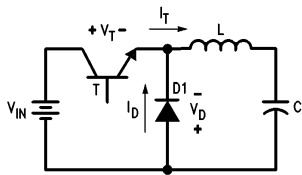

TL/G/10062-1

FIGURE 1a. Buck Regulator to Step-Down Input Voltage V_{IN}

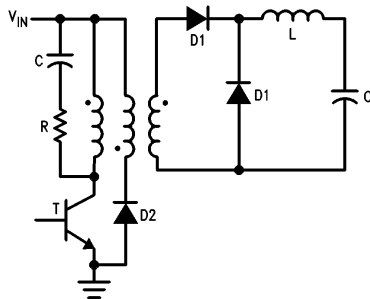

TL/G/10062-2

FIGURE 1b. Forward Converter

Consider how the non-ideal behavior of rectifier D2 affects the circuit performance of the buck regulator in *Figure 1a*. The solid lines in *Figure 2a* depict the switching behavior of the transistor switch and rectifier in comparison to the waveforms (dashed lines) that represent an ideal rectifier. There are four differences between the two cases:

1. The most significant difference is that the peak collector current of the transistor switch (I_T in *Figure 2a*) at the end of turn-on (time t_2) has been increased by the magnitude of the peak reverse recovery current of the rectifier ($I_{R(REC)}$). Correspondingly, the peak power dissipation within the transistor has increased from P_T to P_T as shown in *Figure 2c*.
2. The maximum transistor voltage V_T at turn-off (t_4-t_6 in *Figure 2a*) has been increased by the dynamic voltage drop of the rectifier during turn-on. Since buck regulators generally run at low voltages, this increase has a minimal effect. However, it is more significant in the forward converter circuit of *Figure 1b* and in bridge circuits operating from high bus voltages where the voltage margins cannot be as generous.
3. Since the rectifier is not ideal, its power dissipation consists of the following components:
 - a. Conduction loss ($V_F \times I_F$) during the on-time.
 - b. Turn-off loss during time t_2-t_3 and turn-on loss during time t_5-t_6 (*Figure 2d*).
 - c. Reverse blocking loss ($V_R \times I_R$) during period t_3-t_5 .
4. The rectifier regains its reverse blocking capability at time t_2 . A "snappy" rectifier that quickly turns off $I_{R(REC)}$ will contribute much more EMI than a "soft", fast recovery rectifier.

A better transistor switch will intensify rather than improve the shortcomings of the fast recovery rectifier, so it is necessary to consider more fully the conduction and switching behavior of the rectifier diode.

POWERplanar™ is a trademark of National Semiconductor Corporation.

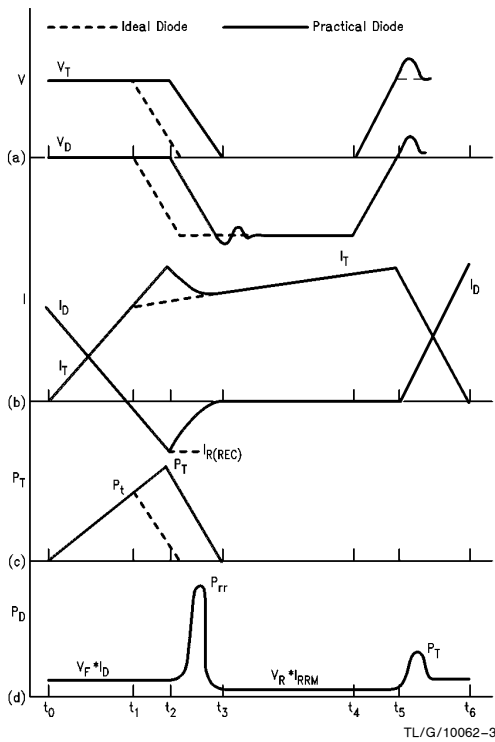


FIGURE 2. Transistor and Rectifier Voltage and Current Waveforms for the Buck Regulator in Figure 1a

- a) Transistor and Rectifier Voltage Waveforms
- b) Transistor and Rectifier Current Waveforms
- c) Transistor Power Dissipation
- d) Rectifier Power Dissipation

POWER LOSSES IN THE ULTRA-FAST RECTIFIER DIODE

Consider the idealized rectifier current and voltage waveforms in Figure 3 for a 50 kHz buck regulator. Power dissipation within the rectifier for a 50% duty factor is:

$$P = P(\text{conduction}) + P(\text{blocking}) + P(\text{reverse recovery})$$

$$P = \frac{1}{2}(V_F I_F + V_R I_R) + V_{RM} I_{R(REC)} t_b f$$

Typical values for a 200V, 8A rectifier are:

- $f = 50 \text{ kHz}$
- $I_R = 1 \text{ mA}$
- $V_F = 0.9 \text{ V}$
- $t_b = 25 \text{ ns}$ (assuming $t_b = t_{rr}/2$)
- $I_F = 8 \text{ A}$
- $V_R = 50 \text{ V}$
- $I_{R(REC)} = 2.0 \text{ A}$
- $V_{RM} = 200 \text{ V}$

$$P = \frac{1}{2}[(8 \text{ A})(0.9 \text{ V}) + (50 \text{ V})(1 \text{ mA})] + (200 \text{ V})(2 \text{ A})(25 \text{ ns})(50 \text{ kHz})$$

$$P = 3.6 \text{ W} + 0.025 \text{ W} + 0.5 \text{ W} = 4.125 \text{ W}$$

CONDUCTION LOSSES

DC conduction or on-state losses occur whenever the rectifier is conducting forward current and consists simply of the integration of $I_F \times V_F$ during the on-time. Literature has dealt extensively with the computation of V_F for many different rectifier structures (Reference 1). The National Semiconductor POWERplanar™ line of fast recovery diodes are planar passivated, P + N - N+ epitaxial type, for which a cross-sectional view can be found in Figure 4. It can be shown that V_F is inversely proportional to minority carrier lifetime and directly proportional to epitaxial thickness (Wi in Figure 4).

Figure 5 plots theoretical curves of normalized V_F vs minority carrier lifetimes for rectifiers with 250V and 500V avalanche voltage breakdown. Since t_{rr} is approximately equal to minority carrier lifetime, it is apparent that high current pn-junction rectifiers are limited to 20 ns-50 ns reverse recovery times because V_F dramatically increases for minority carrier lifetimes less than these. It is also apparent that the V_F curves have a broad minima around 10 ns-30 ns so that another reason to select this value of minority carrier lifetime is that V_F becomes independent of small changes in minority carrier lifetime due to manufacturing tolerances.

It is immediately obvious that the key to maximizing current through the rectifier is to minimize V_F . However at 200 kHz, reverse recovery losses will quadruple to 4W, so that increasing attention must be paid to this parameter as operating frequency is raised.

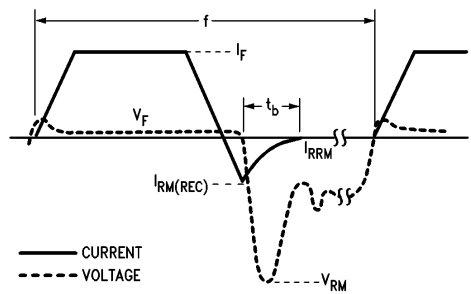


FIGURE 3. Representative Current and Voltage Waveforms for the Rectifier in the Buck Regulator Found in Figure 1a

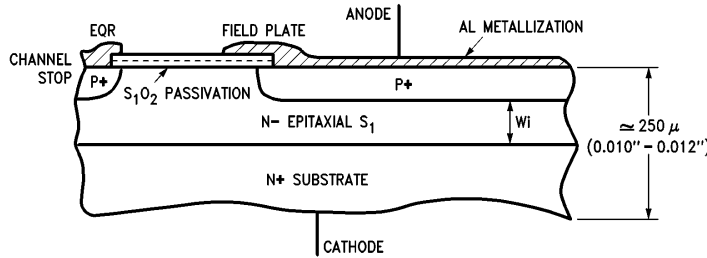


FIGURE 4. Cross-Sectional View of a POWERplanar™
P + N - N +, Fast Recovery Rectifier

TL/G/10062-5

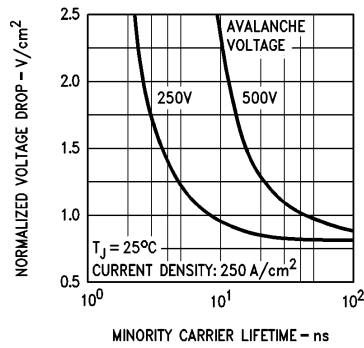


FIGURE 5. Normalized V_F for 250V and 500V Rated Rectifiers as a Function of Minority Carrier Lifetime

TL/G/10062-6

REVERSE BLOCKING LOSSES

Planar passivation techniques have reduced surface leakage currents (I_R) to a negligible amount so that the principle reverse leakage current is recombination current in the space charge region. Some of the many methods to control minority carrier lifetimes are electron or neutron irradiation and gold or platinum diffusion, each with its own advantages and disadvantages. For 200V, ultrafast recovery rectifiers, gold diffusion still represents the best compromise between speed, V_F , I_R and "soft" recovery.

A drawback to gold diffusion is its relatively high reverse leakage current. It should be pointed out that the reliability of the gold-diffused product is the same as other rectifiers (all other factors being equal), since this leakage current is a bulk and not a surface phenomenon. Figure 6 illustrates the dependency of recombination current on junction temperature and minority carrier lifetime, which is inversely proportional to the amount of gold in the depletion region. Experimental leakage test results have been plotted in Figure 6 for the National Semiconductor 8A and 16A series of rectifiers (FRP820 and FRP1620 respectively) at 100°C, 125°C and 150°C. These points indicate that the low current injection level lifetime ranges from 20 ns–30 ns and is relatively independent of T_J . Since reliability design guidelines specify that the rectifiers be operated at one-half their voltage rating and 25°C–50°C below their maximum junction temperature, the expected leakage currents in well designed power supplies will run less than 1 mA.

REVERSE RECOVERY LOSSES

All pn-junction rectifiers, operating in the forward direction, store charge in the form of excess minority carriers. The amount of stored charge is proportional to the magnitude of the forward current. The process by which a rectifier diode is brought out of conduction and returned to its block state is called commutation. Figure 7 shows an expanded view of current commutation, also called reverse recovery. Starting at time t_0 , the rectifier is switched from its forward conducting state at a specified current ramp rate ($-di_F/dt$). The current ramp rate will be determined by the external circuit (E/L) or the turn-on time of a transistor switch. During the time t_1-t_2 , the stored charge within the rectifier is able to supply more current than the circuit requires, so that the rectifier behaves like a short circuit. Stored charge is depleted both by the reverse recovery current and recombination within the rectifier. Eventually the stored charge dwindles to the point that a depletion region around the junction starts to grow, allowing the rectifier to regain its reverse blocking voltage capability (t_2). From a circuit-design standpoint, the most important parameters are the peak reverse recovery current and "S", the softness factor. A "snappy" rectifier will produce a large amplitude voltage transient and contribute significantly to electro-magnetic interference. Figure 8 illustrates the actual reverse recovery of two rectifier diodes. The peak voltage of the snappy rectifier is 175V compared to 142V peak for the FRP820, the higher voltage resulting from both the higher $I_{R(REC)}$ and the fact that the reverse recovery current decays to zero in a shorter time.


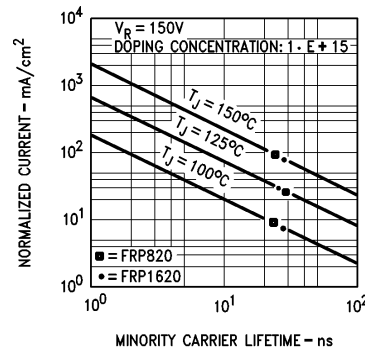


FIGURE 6. Regeneration Current for Gold-Doped, P + N - N + Rectifier Diodes

TL/G/10062-7

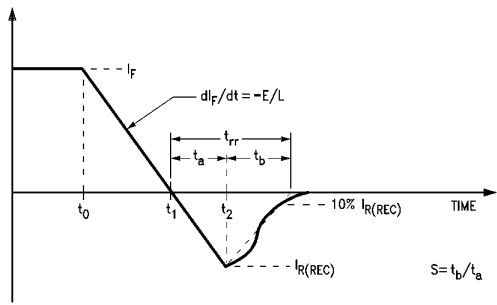

TL/G/10062-8

FIGURE 7. Expanded View of Current Commutation in a Rectifier Diode

The relative snappiness of a rectifier may be defined quantitatively by dividing the reverse recovery time t_{rr} into two subperiods, t_a and t_b , as shown in Figure 7. The softness factor "S" is simply the ratio t_b/t_a . A rectifier with a low value S factor will be more likely to produce dangerous voltage transients, but it will also dissipate less reverse recovery energy than a high S factor rectifier. A reasonable compromise between these two conflicting constraints would be to design a rectifier with $S = 1$ ($t_a = t_b$). The S factors of the FRP820 rectifier and the competitive device in Figure 8 are 0.55 and 0.31 respectively.

Only recently has it become possible to model the ramp recovery in p-i-n rectifiers (References 2, 3) and the following equations have proved useful in predicting reverse recovery parameters.

$$t_{rr} = \frac{W_i \sqrt{\tau / D_a}}{8}$$

$$S = \frac{W_i}{4 \sqrt{D_a \tau}}$$

$$I_{R(REC)} = \left(\frac{dI_F}{dt} \right) \tau \left(1 + \frac{W_i}{8 \sqrt{D_a \tau}} \right) - 1$$

$$Q_{R(REC)} = 0.5 \tau^2 \left(\frac{dI_F}{dt} \right)$$


where:

τ = minority carrier lifetime

W_i = epitaxial thickness

D_a = ambipolar diffusion constant

The blocking voltage rating of the rectifier primarily determines W_i ; but for a given W_i , note that a short minority lifetime not only decreases $I_{R(REC)}$ but happily increases S. These two key parameters are plotted as a function of minority carrier lifetime in Figure 9 for $dI_F/dt = 100 \text{ A}/\mu\text{s}$ and $T_J = 25^\circ\text{C}$. As has been noted before, the minority carrier lifetime had been targeted for 20 ns–30 ns to minimize V_F and this choice has resulted in a typical value of $S = 0.65$ and $I_{R(REC)} = 1.5\text{A}$.

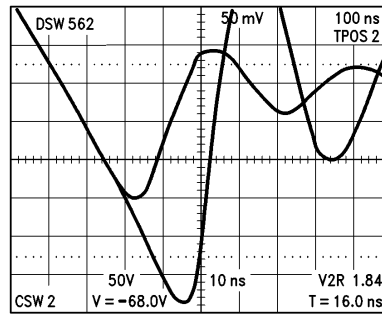

TL/G/10062-9

Test Conditions:


$T_J = 25^\circ\text{C}$

$I = 0.5 \text{ A}/\text{DIV}$

$I_F = 8\text{A}$

$T = 10 \text{ ns}/\text{DIV}$

$dI_F/dt = 100 \text{ A}/\mu\text{s}$

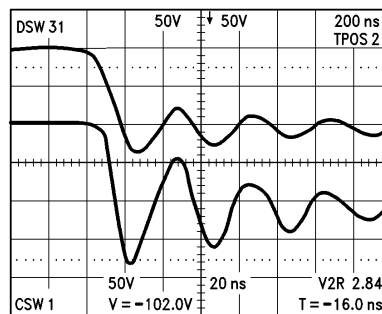

TL/G/10062-10

Test Conditions:

$T_J = 25^\circ\text{C}$

$I = 50 \text{ VA}/\text{DIV}$

$I_F = 8\text{A}$

$T = 10 \text{ ns}/\text{DIV}$

$dI_F/dt = 100 \text{ A}/\mu\text{s}$

FIGURE 8. Comparison of Reverse Recovery of the FRP820 Series Rectifier to a Snappy Rectifier

REVERSE RECOVERY CHARACTERIZATION

Figures 10–13 plot $Q_{R(REC)}$, $I_{R(REC)}$, t_{rr} and S versus dI_F/dt for the FRP1600 series of rectifiers and typical use conditions of $I_F = 16\text{A}$ and $V_R = 200\text{V}$ and for two different junction temperatures of 25°C and 125°C . Theory not only predicts, but it has also been experimentally verified, that these parameters are relatively independent of I_F so only one value of the latter suffices. Any three of the four Figures 10–13 completely specifies the reverse recovery behavior of the rectifier. Since S and T_{rr} vary the least over the plotting dI_F/dt range, it is convenient to formulate reverse recovery energy loss P in microwatts in terms of the circuit parameters V_R and dI_F/dt :

$$P = \frac{V_R \left(\frac{dI_F}{dt} \right) f}{2S} \left(\frac{S t_{rr}}{1 + S} \right)^2 10^{-3} (\mu\text{W})$$

where:

V_R = peak reverse voltage

dI_F/dt = ramp rate ($\text{A}/\mu\text{s}$)

f = operating frequency (kHz)

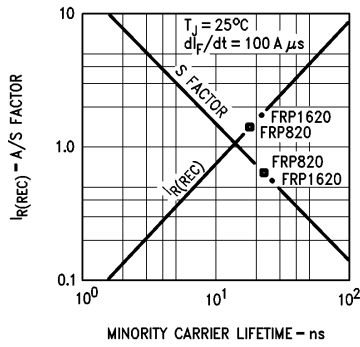


FIGURE 9. Theoretical Plots of $I_{R(REC)}$ and S vs Minority Carrier Lifetime

TL/G/10062-11

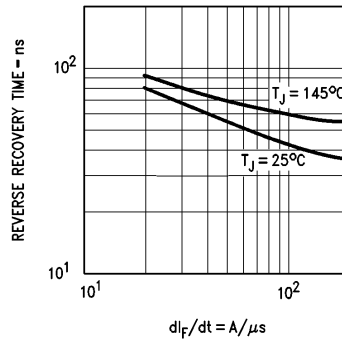


FIGURE 12. Reverse Recovery Time of the FRM/FRP1600 Series Rectifier Diodes

TL/G/10062-14

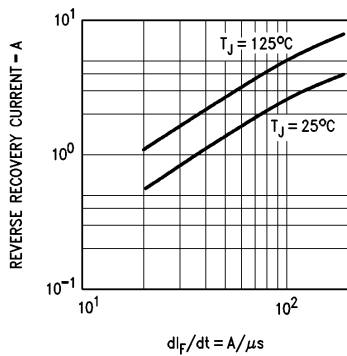


FIGURE 10. Reverse Recovery Current for the FRM/FRP1620 Series Rectifiers

TL/G/10062-12

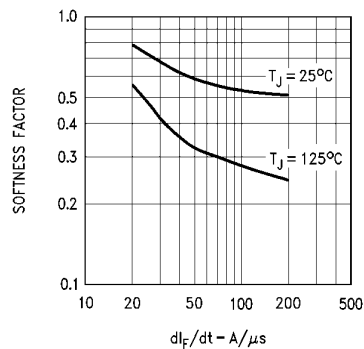


FIGURE 13. Softness Factor S for the FRM/FRP1600 Series Rectifier Diodes

TL/G/10062-15

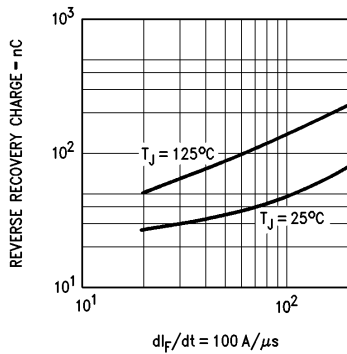


FIGURE 11. Reverse Recovery Charge for the FRM/FRP1600 Series Rectifier Diodes

TL/G/10062-13

Example: Calculate the reverse recovery power loss for the FRP1620 rectifier running at:

$$I_F = 16A \quad V_R = 100V$$

$$dI_F/dt = 100 A/\mu s \quad T_J = 125^\circ C$$

$$f = 75 \text{ kHz}$$

From Figures 12 and 13 $t_{rr} = 56 \text{ ns}$ and $S = 0.29$. Substituting these values in the above equation:

$$P = \frac{(100V)(100 A/\mu s)(75 \text{ kHz})}{(2)(0.29)} \left[\frac{(0.29)(56 \text{ ns})}{1 + 0.29} \right]^2 10^{-3} \mu W$$

$$P = 0.205W$$

There are many ways to shape the reverse recovery voltage spike. The most simple and still most popular is the RC snubber circuit connected across the primary of the transformer in Figure 1b. This serves the dual purpose of suppressing voltage ringing and EMI due to the switching action of both the transistor and rectifier. William McMurray has shown how to design an RC snubber to minimize voltage transients and/or dV/dt ramps just due to the diode reverse recovery current (Reference 4) and also how to de-

sign snubbers to minimize transistor power dissipation (Reference 5). But to date, because the RC snubber plays a major role in reducing EMI, its design tends to be empirical rather than theoretical.

CONCLUSION

This application note has pointed out the major considerations in designing an ultrafast reverse recovery rectifier and shown that the control of minority carrier lifetime is the key in arriving at an optimum device. Because the diode contributes to EMI, its reverse recovery behavior must be carefully controlled and characterized in order to guarantee similar performance from lot to lot.

REFERENCES

1. S. K. Ghandhi, *Semiconductor Power Devices*, (NYC), John Wiley and Sons, p. 110 ff.
2. F. Berz, "Ramp Recovery in p-i-n Diodes", *Solid-State Electronics*, Vol. 23, pp. 783-792.
3. C. M. Hu, Private Communication
4. W. McMurray, "Optimum Snubbers for Power Semiconductors", *IEEE Trans. on Industry Applications*, Vol. 1A-8, No. 5, Sept./Oct. 1972, pp. 593-600.
5. W. McMurray, "Selection of Snubbers and Clamps to Optimize the Design of Transistor Switching Converters", *PESC 1979 Conference Record*, pp. 62-74.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform, when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



National Semiconductor Corporation
 1111 West Bardin Road
 Arlington, TX 76017
 Tel: 1(800) 272-9959
 Fax: 1(800) 737-7018

National Semiconductor Europe
 Fax: (+49) 0-180-530 85 86
 Email: cnjwge@tevm2.nsc.com
 Deutsch Tel: (+49) 0-180-530 85 85
 English Tel: (+49) 0-180-532 78 32
 Français Tel: (+49) 0-180-532 93 58
 Italiano Tel: (+49) 0-180-534 16 80

National Semiconductor Hong Kong Ltd.
 19th Floor, Straight Block,
 Ocean Centre, 5 Canton Rd.
 Tsimshatsui, Kowloon
 Hong Kong
 Tel: (852) 2737-1600
 Fax: (852) 2736-9960

National Semiconductor Japan Ltd.
 Tel: 81-043-299-2309
 Fax: 81-043-299-2408

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated