

Reducing Losses in Your Internal Bootstrap Diode

ABSTRACT

Many half-bridge gate drivers incorporate a bootstrap diode to generate high-side bias, reducing the board space and component count for designers. In high frequency and capacitive load applications, it is often beneficial to add an external bootstrap diode to reduce losses associated with the diode. This report discusses the power dissipation within gate drivers with an integrated bootstrap diode and further discusses the selection of the external bootstrap diode.

Contents

1	Introduction	2
2	Theory of Operation	4
	2.1 Power Dissipation.....	4
3	Recommended External Bootstrap Diodes.....	6
4	Conclusion	6

List of Figures

1	Simplified Schematic of High- and Low-Side Driver	3
2	Gate -Driver Power Dissipation (LO and HO) $V_{CC} = 12\text{ V}$, Neglecting Diode Losses.....	4
3	Internal-Diode Power Dissipation $V_{IN} = 40\text{ V}$	5
4	Internal-Diode Power Dissipation $V_{IN} = 80\text{ V}$	5

List of Tables

1	Recommended External Bootstrap Diodes.....	6
---	--	---

1 Introduction

The gate drive requirements for power MOSFETs, IGBTs, and SiCs used as high-side switches in applications, like half-bridge converters or synchronous buck converters, can be summarized as follows:

- Gate voltage must be 6 to 12 V higher than the source voltage. To fully enhance a high-side switch and reduce switching losses, the gate-to-source voltage must be higher than the threshold voltage, plus the minimum necessary voltage.
- Gate voltage must be controllable from the logic level, which is normally referenced to ground. Thus, the control signals must be level shifted to the source terminal of the high-side MOSFET (HS node), which in most applications, swings between ground and the high voltage rail.
- Power dissipation of the gate driver must remain within the package thermal limitations.

Highly integrated gate-driver ICs include the following blocks:

- Low-side gate driver
- High-side level shifter
- High-side gate driver
- Undervoltage lockout protection for both the high- and low-side drive
- Bootstrap diode

2 Theory of Operation

2.1 Power Dissipation

The total IC power dissipation is the sum of the gate driver losses and the bootstrap diode losses. The gate driver losses are related to the switching frequency (f), output load capacitance (C_L) on LO and HO, and supply voltage (V_{DD}). The power dissipation is roughly calculated as follows in Equation 1:

$$P_{DGATES} = 2 \times f \times C_L \times V_{DD}^2 = 2 \times f \times Qg \times V_{DD}$$

where

- Qg is the total gate charge of the external MOSFET in coulombs. (1)

There are some additional losses in the gate drivers due to the internal CMOS stages used to buffer the LO and HO outputs. Figure 2 shows the measured gate driver power dissipation versus frequency and total gate charge of external MOSFET in coulombs. At higher frequencies and load capacitance values, the power dissipation is dominated by the power losses driving the output loads and agrees with Equation 1. Figure 2 shows the approximate power losses due to the LM510x gate drivers. This data was taken by connecting external capacitive loads on both outputs of the LM510X driver.

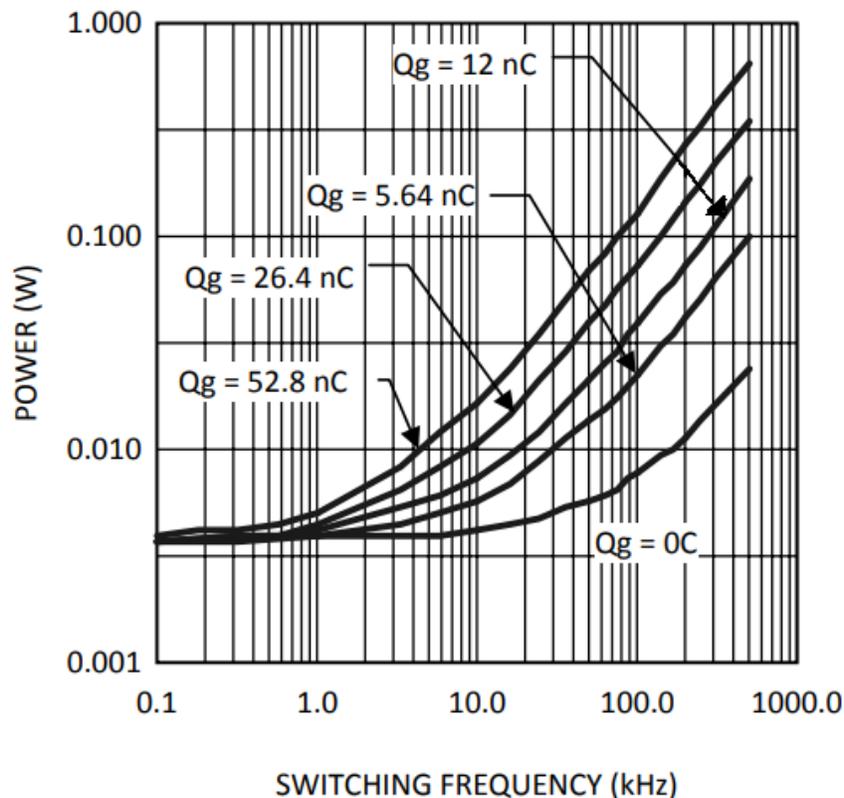


Figure 2. Gate -Driver Power Dissipation (LO and HO)
 $V_{CC} = 12\text{ V}$, Neglecting Diode Losses

The bootstrap diode power loss is the sum of the forward-bias power loss that occurs while charging the bootstrap capacitor and the reverse-bias power loss that occurs during reverse recovery. Because each of these events occurs once per cycle, the diode power loss is proportional to the frequency. Larger capacitive loads require more current to recharge the boot capacitor, resulting in more losses. Higher input voltages (V_{IN}) to the half bridge result in higher reverse-recovery losses. Figure 3 and Figure 4 were generated based on calculations and lab measurements of the diode recovery time and current, under several operating conditions. This method can be useful for approximating the diode power dissipation.

The total IC power dissipation can be estimated from the plots shown in [Figure 2](#), [Figure 3](#), and [Figure 4](#), by summing the gate-drive losses with the bootstrap-diode losses for the intended application. Because the diode losses can be significant, an external diode placed in parallel with the internal bootstrap diode can be helpful in removing power from the IC. For this method to be effective, the external diode must be placed close to the IC, to minimize series inductance and produce a significantly lower forward-voltage drop than the internal diode (see the LM510X data sheet).

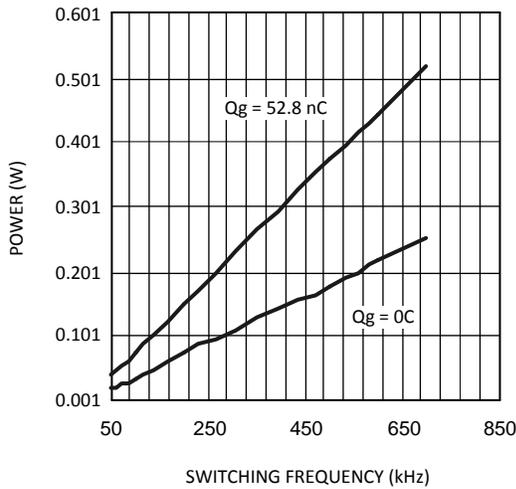


Figure 3. Internal-Diode Power Dissipation
V_{IN} = 40 V

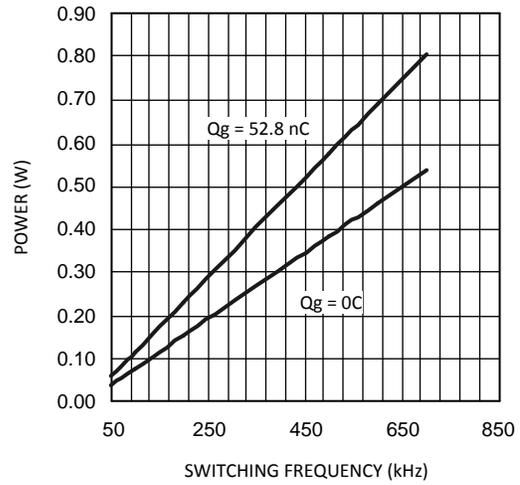


Figure 4. Internal-Diode Power Dissipation
V_{IN} = 80 V

3 Recommended External Bootstrap Diodes

Table 1. Recommended External Bootstrap Diodes

ITEM	DIODE PART NUMBER	MANUFACTURER	REMARKS
1	CRH01	Toshiba	S-FLATTM Package (3.5 mm x 1.6 mm)
2	Mura110T3	ONSEMI	SMA Package. (5.5 mm x 2.9 mm)
3	BYV40E	PHILIPS SEMI	SOT223 Package. (6.7mm x 6.7mm)
4	MA2YD1700L	PANASONIC	Schottky diode. High leakage current at high temperatures. Mini2-F1 package. (3.5mm x 1.6mm)

4 Conclusion

In high frequency and high capacitive load applications, it is beneficial to use an external bootstrap diode to reduce power dissipated within the IC. This application report quantified the losses in the internal bootstrap diode of LM510X high and low side gate driver. This application report is not limited to the LM510X family devices, it extends to other TI half bridge gate drivers with a built-in bootstrap diode.

Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

Changes from A Revision (May 2013) to B Revision	Page
• Changed app note title from AN-1317 Selection of External Bootstrap Diode for LM510X Devices to Selection of External Bootstrap Diode for Half-Bridge Gate Drivers	1
• Added IGBTs and SiCs to Introduction	2
• Deleted Removed approximate cost/unit column from Recommended External Bootstrap Diodes table	6

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2018, Texas Instruments Incorporated