

# LM2788

*Powering Portable Devices: Alternatives To Linear Regulators In Step-Down Conversion*



Literature Number: SNVA527

# Powering Portable Devices: Alternatives To Linear Regulators In Step-Down Conversion

Application Brief 123

William J. McIntyre & John Parry

## Highlights

- High-efficiency Baseband Power at 2.0V, 1.8V, and 1.5V Output
- 120 mA Output Current Capable
- 35  $\mu$ A Typical Supply Current
- No Inductors Required

In portable products such as PDAs and laptop computers—powering the microprocessor from a Li-Ion battery generally means choosing a small and power-efficient step-down DC-DC converter. In terms of efficiency, a switching regulator is the best choice. However, when component height limitations rule out the use of inductors (as sometimes happens in small devices like cell phones), a converter might take the form of a low dropout (LDO) linear regulator. The small and inexpensive LDO works most efficiently when the microprocessor voltage is close to the battery voltage—but the LDOs efficiency can be poor when the voltages are far apart.

Consider the example of a Li-Ion battery charged to 3.6V that powers a microprocessor requiring only 1.8V. Connecting the battery voltage to a 1.8V LDO creates a quiet, stable supply for the microprocessor, but the power loss is significant. The LDO will dissipate power (PD) equal to the load current ( $I_{LOAD}$ ) times the input to output voltage drop ( $PD = I_{LOAD} * (3.6V - 1.8V) = I_{LOAD} * 1.8V$ ). In other words, the LDO as a step-down converter is only 50% efficient in this example. As supply voltages for microprocessors and other logic devices drop, the LDO solution becomes less efficient.

One recent alternative to linear regulators in step-down conversion is the switched capacitor DC-DC converter, also known as a charge pump. The switched capacitor is more efficient than linear regulators due to voltage gain, which is simply the input to output voltage ratio achieved by stacking or paralleling capacitors in two phases (the charging phase and the delivery phase). The gain configuration behaves much like a step-down transformer, delivering power at  $V_{OUT}$  equal to the power supplied at  $V_{IN}$ .

For example, a switched capacitor converter in a gain configuration of 1/2 will transform an input voltage of 3.6V to an output voltage of 1.8V with very little power loss. For a 10 mA load on  $V_{OUT}$ , 5 mA is drawn from  $V_{IN}$ . This high-efficiency, though, holds true only when the target output voltage is close to  $V_{IN}$  multiplied by the gain. Using the previous example, consider the efficiency of the converter in a gain of 1/2, but  $V_{IN}$  is 4.2V. The  $V_{OUT}$  generated by the converter is 2.1V, 300 mV above the desired 1.8V.

The extra 300 mV times the load current is lost power. As  $V_{IN}$  continues to increase, the  $V_{OUT}$  generated by the converter increases, causing more power “leakage” and a decrease in efficiency. Also, note that if the  $V_{IN}$  is less than 3.6V, the converter output is lower than 1.8V. To operate below  $V_{IN}=3.6V$ , a gain greater than 1/2 is needed.

The LM2788 is a buck mode switched capacitor converter that applies three fractional voltage gains to yield an average power conversion efficiency over 84%. An LDO in the same application shows only 45% efficiency. The secret of the new converter’s performance lies in the intelligent selection of the gains equal to 1/2, 2/3 and 1. The proper gain is chosen by dynamically sensing battery voltage and output loading.

Figure 1 charts power efficiency versus the  $V_{IN}$  from the battery. Efficiency is equal to  $V_{OUT}/gain * V_{IN}$ . The efficiency for the gain = 1/2 example is plotted for  $V_{IN} > 3.6V$  and as shown, decreases with  $V_{IN}$ .

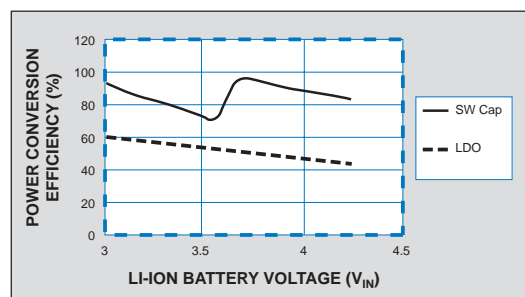


Figure 1: Power Efficiency vs. Battery Voltage

To produce a regulated output voltage, pulse frequency modulation is often used. The output impedance of any switched capacitor converter is proportional to the switching frequency. By modulating the impedance, more or less voltage is dropped across the converter for a given load. Feedback adjusts the frequency to regulate the output voltage. To ensure stability, the output capacitor should be roughly a minimum of 10 times the value of the flying capacitor. The switching frequency and the size of the output capacitor determines the amplitude of the output voltage ripple. If the ripple is too large for a given application, a larger output capacitor can be used. Another option is to add an LDO to the output of the converter. In this case, the converter output voltage is set to the LDO output voltage plus the LDO dropout voltage. This solution provides low noise with the added benefit of higher efficiency.

The LM2788 can be used to drive a microcontroller or other digital device as shown in *Figure 2*. In this case, the power source is a Li-Ion battery. The output voltage is 1.8V and the current required by the micro is 100 mA. With a 10  $\mu\text{F}$  output capacitor, the ripple is typically about 25 mV. The total solution size is about 0.28 in<sup>2</sup>. The average power efficiency over the Li-Ion discharge is about 75% or 45% better than an LDO. This solution only requires one LM2788, two 1.0  $\mu\text{F}$  flying capacitors, two 10  $\mu\text{F}$  hold capacitors, and no inductors.

0.18 $\mu\text{m}$  and smaller geometries have allowed the current requirements for various digital processors to drop to 100 mA and below. At these current levels, switched capacitor DC-DC converters become a viable and efficient alternative to inductive based switchers.

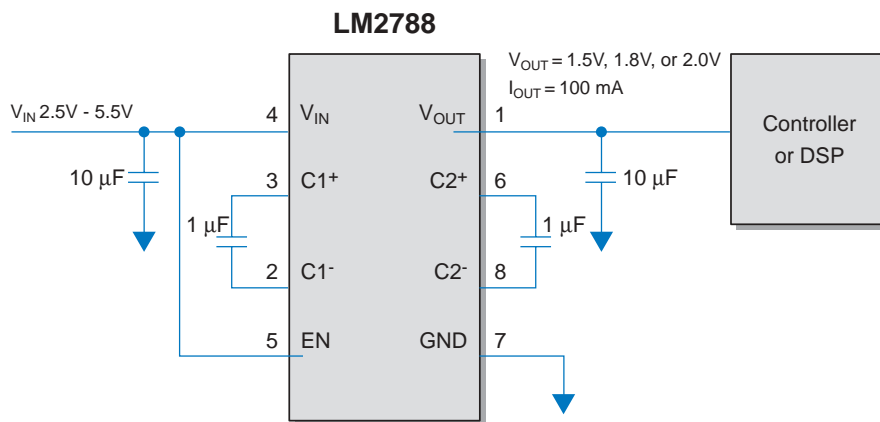


Figure 2: LM2788 Block Diagram

National Semiconductor  
2900 Semiconductor Dr.  
PO Box 58090  
Santa Clara, CA 95052  
1-800-272-9959

Visit our Web site at:  
[www.national.com](http://www.national.com)

For more information,  
send email to:  
[new.feedback@nsc.com](mailto:new.feedback@nsc.com)

 **National**  
Semiconductor  
*The Sight & Sound of Information*

#### Additional Information

[power.national.com](http://power.national.com)  
[www.national.com/pf/LM/LM2788.html](http://www.national.com/pf/LM/LM2788.html)  
[www.national.com/pf/LM/LM2798.html](http://www.national.com/pf/LM/LM2798.html)

Visit **The National Edge**, our online technical journal for an archive of Application Briefs and other interesting information.  
[edge.national.com](http://edge.national.com)

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Mobile Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Transportation and Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

TI E2E Community Home Page

[e2e.ti.com](http://e2e.ti.com)

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2011, Texas Instruments Incorporated