

LM5046

Using a Phase-Shifted Full-Bridge Topology in Small Form Factor Power Converters



Literature Number: SNVA610

Using a Phase-Shifted Full-Bridge Topology in Small Form Factor Power Converters

— By Ajay Hari, Applications Engineer

Introduction

Phase-Shifted Full-Bridge (PSFB) topology has been traditionally used in high input voltage (~400V), high power (>500W) converters that are usually not required to be packed in a small form factor such as the telecom industry standard 1/4th (2.28*1.45 inches) and 1/8th brick format (2.28*0.89 inches). The complexity of the topology, lack of easy-to-use controllers, its perceived benefits only at high input voltages and the use of an additional commutating inductor for resonant transitions are some of the reasons why PSFB topology has not been applied at standard telecom input range of 36V to 75V. The LM5046 is the industry's first PSFB controller with integrated 100V primary drivers. Its high level of integration eases application of PSFB topology into small form factor power converters.

Operation of the Phase-Shifted Full-Bridge Topology

The PSFB topology is a derivative of the classic hard switching full-bridge topology. When tuned appropriately the PSFB topology achieves zero voltage switching (ZVS) of the primary FETs while maintaining constant switching frequency. The ZVS feature is highly desirable as it reduces both the switching losses and the EMI emissions. *Figure 1* illustrates the circuit arrangement for the PSFB topology. The power transfer mode of the PSFB topology is similar to the hard switching full-bridge i.e. When the FETs in the diagonal of the bridge are turned-on (Q1 & Q3 or Q2 & Q4), a power transfer cycle is initiated from the primary to the secondary. At the end of the power transfer cycle, COMP turns-off the switch Q3 or Q4 depending on the phase with a pulse width determined by the input

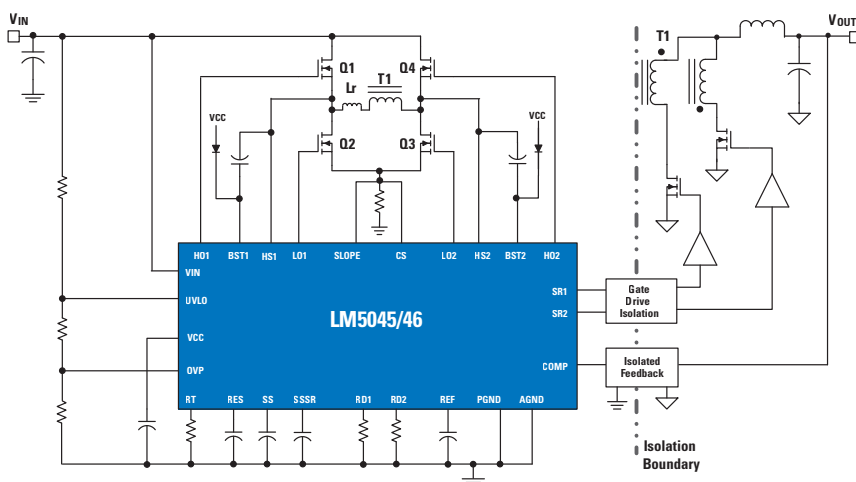


Figure 1. Simplified Schematic of a Phase-Shifted Full-Bridge Converter.

Using a Phase-Shifted Full-Bridge Topology in Small Form Factor Power Converters

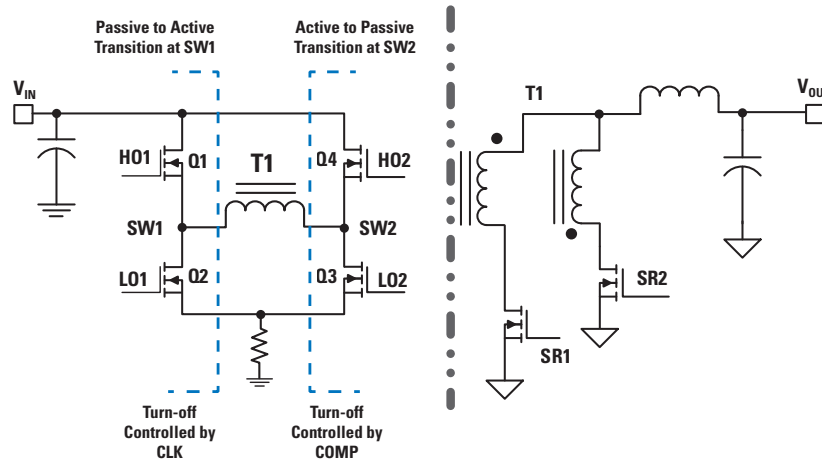


Figure 2. Simplified PSFB Topology Showing the ZVS Mechanism

and output voltages and the transformer turns ratio. In the freewheel mode, unlike the classic full-bridge, where all the four primary FETs are off, in the PSFB topology the primary of the power transformer is shorted by activating either both the top FETs (Q1 and Q4) or both the bottom FETs (Q2 and Q3) alternatively. When turned ON, each diagonal (Q1 and Q3 or Q2 and Q4) applies input voltage to the primary of the transformer. The resulting secondary voltage is then rectified and filtered with an LC filter to provide a smoothed output voltage.

Zero Voltage Switching Mechanism

Active to Passive Transition

As noted, the PSFB differs from the conventional hard-switching full-bridge during the freewheeling period. In the freewheel period, either the top or the bottom FET pairs of the full-bridge are activated. This mechanism facilitates zero voltage switching for all four primary FETs. For example, the power transfer cycle enabled by activating Q1 and Q3 is terminated by turning-off Q3 and the freewheeling cycle is initiated by activating Q4. Once Q3 is terminated, the reflected load current plus the magnetizing current propels the SW2 node towards the V_{IN} and activating Q4 at that instance results

in ZVS. This transition, shown in *Figure 2*, is often called the active to passive transition (power transfer to freewheel transition). The active to passive transition time can be approximated by using the following formula:

Equation A

$$T_{AP} = \frac{C_{\text{parasitic}} \times V_{IN}}{(I_m + \frac{I_{LPEAK}}{N_{TR}})}$$

Where, I_m is the magnetizing current, N_{TR} is the power transformer's turns ratio, I_{LPEAK} is the peak output filter inductor current and $C_{\text{parasitic}}$ is the parasitic capacitance at the node SW2. The LM5046 is setup such that the SW2 node always sees active to passive transition.

Passive to Active Transition

At the end of a freewheeling cycle (and end of one switching period), the primary switch Q1 is turned-off. The voltage at the node SW1 begins to fall towards the GND due to the resonance between leakage inductance of the power transformer plus any additional commutation inductor and the parasitic capacitances at SW1. At this instant, ZVS can be realized by turning on the switch Q2.

The magnetizing inductor is shorted in the freewheel mode and therefore does not play any role in this transition. The LC resonance results in a half-wave sinusoid whose frequency is determined by the leakage inductor and parasitic capacitor. The passive to active transition time can be approximated by using the following formula:

Equation B

$$T_{PA} = \frac{\pi}{2} \sqrt{(L_{leakage} + L_{commutation}) \times C_{parasitic}}$$

Where, $C_{parasitic}$ is the parasitic capacitance at the node SW1.

The peak of the half-wave sinusoid is a function of the load current and the additional commutating inductance and/or leakage inductance and is given by

Equation C

$$V_{PK} = \frac{I_L}{N_{TR}} \sqrt{\frac{(L_{leakage} + L_{commutation})}{C_{parasitic}}}$$

From *Equation A* it is evident that the active to passive transition can always result in ZVS as long as sufficient dead-time is inserted. However, from *Equation B and C*, it can be seen that the passive to active transition can result in ZVS only if there is enough energy stored in the commutating inductor and/or leakage inductance.

Fitting into a Small Form Factor

The power density in small form factor power converters such as the 1/4th and the 1/8th brick format is constantly increasing. With increasing power density new topologies are being pursued, more efficient high power topologies are being employed into lower power applications. Topologies such as the full-bridge and the PSFB used in high power and bulky converters are finding applications in small form factor power converters. To facilitate this

trend, a PWM controller with integrated drivers and a high level of control logic integration that simplifies the use of complex topologies is essential. Further, to meet the height requirements, a PC board integrated planar transformer is also required. The PSFB topology with its ZVS feature can accommodate higher frequencies so that the sizes of bulky passive components are reduced.

Example

A 150W PSFB power converter was built using the LM5046 in the telecom industry standard eighth brick (2.28*0.89 inches). The operating input voltage range is 36V to 75V and the output voltage is 12V. The output current capability is 12A. The converter is configured for current mode control with robust hiccup mode current limiting that initiates at 13A of average load current. The power converter operates at a frequency of 420 kHz. The PCB integrated transformer has 5 turns in the primary and 2 turns in each secondary. The primary and secondary turns were not interleaved and were stacked serially to deliberately increase the leakage inductance to about 1 μH. The efficiency curves for the LM5046 are shown in *Figure 3*. The following are the reasons that made this integration possible:

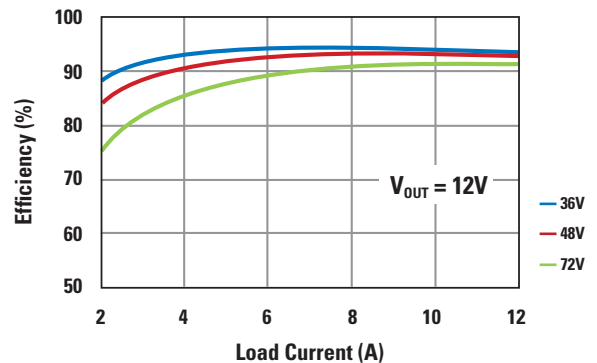


Figure 3. Efficiency Curves for a 150W DC-DC Converter Built Using the PSFB in Eighth Brick Format.

Using a Phase-Shifted Full-Bridge Topology in Small Form Factor Power Converters

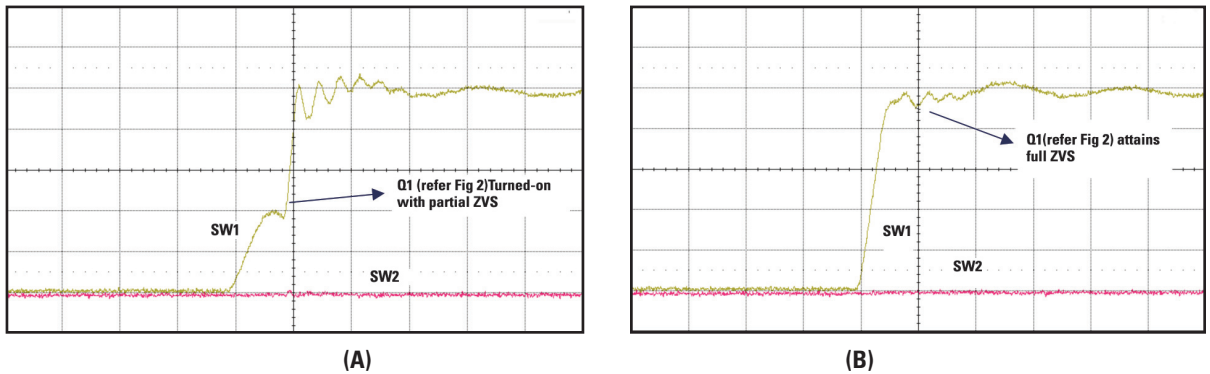


Figure 4. Passive to Active Transition at Partial Load (A) and Full Load (B) Condition

Highly Integrated PWM Controller Driver

The LM5046 is the highest integration controller for small form factor, high density power converters. It features four integrated gate drivers with 2A source and 3A sink capability which saves the use of the two 8-pin half-bridge drivers that are required to implement a PSFB converter. Approximately 50% PCB board area is saved by using one LM5046 in a LLP package over a traditional PSFB controller plus two extra gate drivers in LLP package. This is highly desirable as it frees up lot of valuable PCB real estate.

LM5046 also includes intelligent synchronous rectifier startup to enable linear turn-on into pre-biased loads. LM5046 comes with a 100V startup regulator and other features such as optional hiccup mode, wide-bandwidth opto coupler interface, and integrated UVLO and OVP comparators that avoid discrete circuitry.

Commutating Inductance

From *Equation C*, it can be seen that during the passive to active transition the peak of the half-wave sinusoid depends on both the load current and the commutating inductance. Therefore to enable ZVS at light to medium load conditions considerable commutating inductance is necessary.

The additional commutating inductor needs be selected such that the combined core and copper losses associated with it do not swamp out any gain

in efficiency due to ZVS. This often leads to a physically large inductor. While in high input voltage (~400V) applications it is a common practice to use an additional commutating inductor, due to the real estate challenges in the 1/4th and 1/8th brick format power converters the use of an additional inductor is unattractive.

By deliberately increasing the transformer leakage inductance the available commutating inductance can be increased. This can be achieved by avoiding the primary and secondary interleave and stacking the windings serially. It should be noted that conventionally leakage inductance is kept to a minimum by interleaving the primary and the secondary. Further, one additional advantage of integrated transformers is that by design they reduce the variation of the leakage inductance in mass production compared to wound transformers.

The only drawback of this approach is that depending just on leakage inductance might not be enough to enable ZVS under all the load conditions. In such a situation, the switching losses will occur. However, since the capacitive losses are proportional to V^2 , the losses will reduce considerably even if SW node rises to at least half the input voltage as shown in *Figure 4* and it is still considerably better than hard switching. Even though there is some switching loss at light load conditions, the overall efficiency achieved (as shown in *Figure 3*) by employing PSFB is excellent.

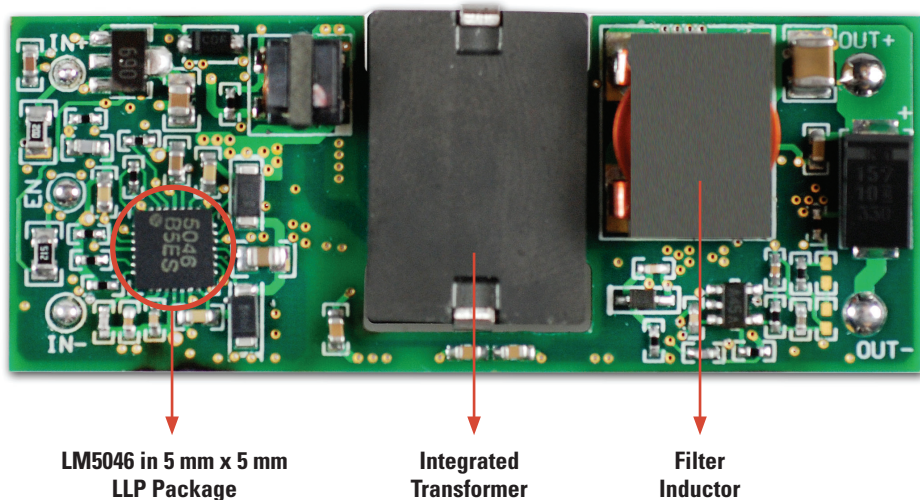


Figure 5. Top Side View of the Eighth Brick

Figure 5 shows the 1/8" brick board with the chief components highlighted.

Conclusion

With ever increasing power density, topologies such as the PSFB which have only been used in the past for high-power and bulky designs, are now finding applications in small form factor power converters. The trend is here to stay. To facilitate this trend, highly integrated PWM controllers are necessary and LM5046 is a big first step in that direction. Intelligent choices need to be made in the transformer design such as integrated transformers and avoiding interleaving the primary and the secondary windings. Increasing frequency of operation to reduce the size of passive components is a must. Further, topologies such as PSFB with ZVS switching will gain more prominence as it enables increasing frequency without incurring major efficiency loss while reducing EMI emissions.

References

- LM5046 Datasheet
- LM5046 Lab Demo Video
- LM5046 Evaluation Board
- AN-2126 App Note for LM5046 1/8 Brick Reference Design

Power Design Tools



Design, build, and test analog circuits in this online design and prototyping environment.
national.com/webench



Expand your knowledge and understanding of analog with our free online educational training tool.
national.com/training



National's monthly analog design technical journal.
national.com/edge

Tools for Energy-Efficient Designs

Access white papers, reference designs, and application notes on PowerWise® products and systems.

national.com/powerwise

National Semiconductor
2900 Semiconductor Drive
Santa Clara, CA 95051
1 800 272 9959

Mailing address:
PO Box 58090
Santa Clara, CA 95052

Visit our website at:
national.com

**For more information,
send email to:**
new.feedback@nsc.com

Don't miss a single issue!

Subscribe now to receive email alerts when new issues of Power Designer are available:

national.com/powerdesigner

Read our Signal Path Designer® online today:

national.com/spdesigner



IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated