

Maintaining Output Voltage Regulation During Automotive Cold-Crank with LM5175 Buck-Boost

Vijay Choudhary

Designing electronics to operate from a 12-V car supply is challenging. The 12-V battery supply voltage can range from 9-16V under normal operation depending on charge and load variation. However, the transient battery voltage range can be much wider. One of these conditions is cold-crank that happens when the battery is trying to energize the starter-motor circuits on the internal combustion engine. Traditionally, only a few critical functions were required to ride through the cold-crank. Increasing car manufacturers are making more features available through cold-cranks for better driver experience and safety.

The cold-crank profile is described by ISO 7637-2 (test pulse 4). Individual car manufacturers have similar cold-crank profiles with the supply rail dropping to 3 V or lower depending on the location of the load. An example cold-crank profile is shown in [Figure 1](#). The actual voltage levels and time intervals are manufacturer specific.

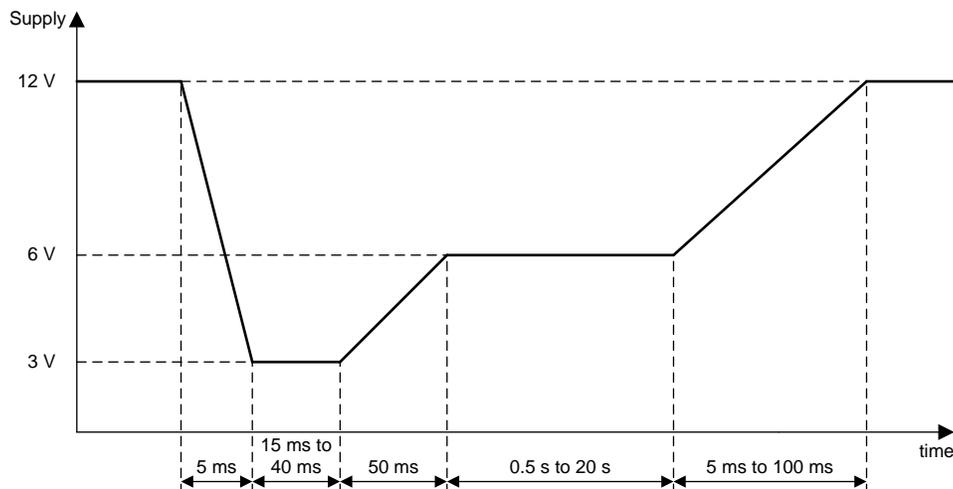


Figure 1. A Representative Startup (Cold-crank) Test Profile for Car Supply with 12-V Battery

To keep the safety and convenience functions such as navigation, entertainment, dashboard, LED brake lights and headlights working through drops in the battery profile, the dc-dc converter supplying these loads must be able to maintain regulation even when the 12-V supply voltage drops below the required output voltage.

The LM5175, a 4-switch buck-boost controller, can maintain regulation even at supply voltages dropping below 3 V. With an absolute maximum voltage rating of 60 V, it can survive load dump transients with ease. In addition, the LM5175 uses a single inductor buck-boost topology to provide small solution size and higher efficiency compared to Flyback or SEPIC. The 4-switch buck-boost solution employs synchronous rectification for both buck and boost modes of operation which results in significant efficiency advantage for high power solutions compared to competing topologies.

A LM5175 based 5 V / 7.5 A buck-boost converter is shown in [Figure 3](#) with an operating input voltage range of 3 V to 20 V with the ability to withstand load dump transients up to 42 V. [Figure 2](#) shows a cold-crank test condition. The converter maintains the output voltage even when the input supply voltage drops below 3 V.

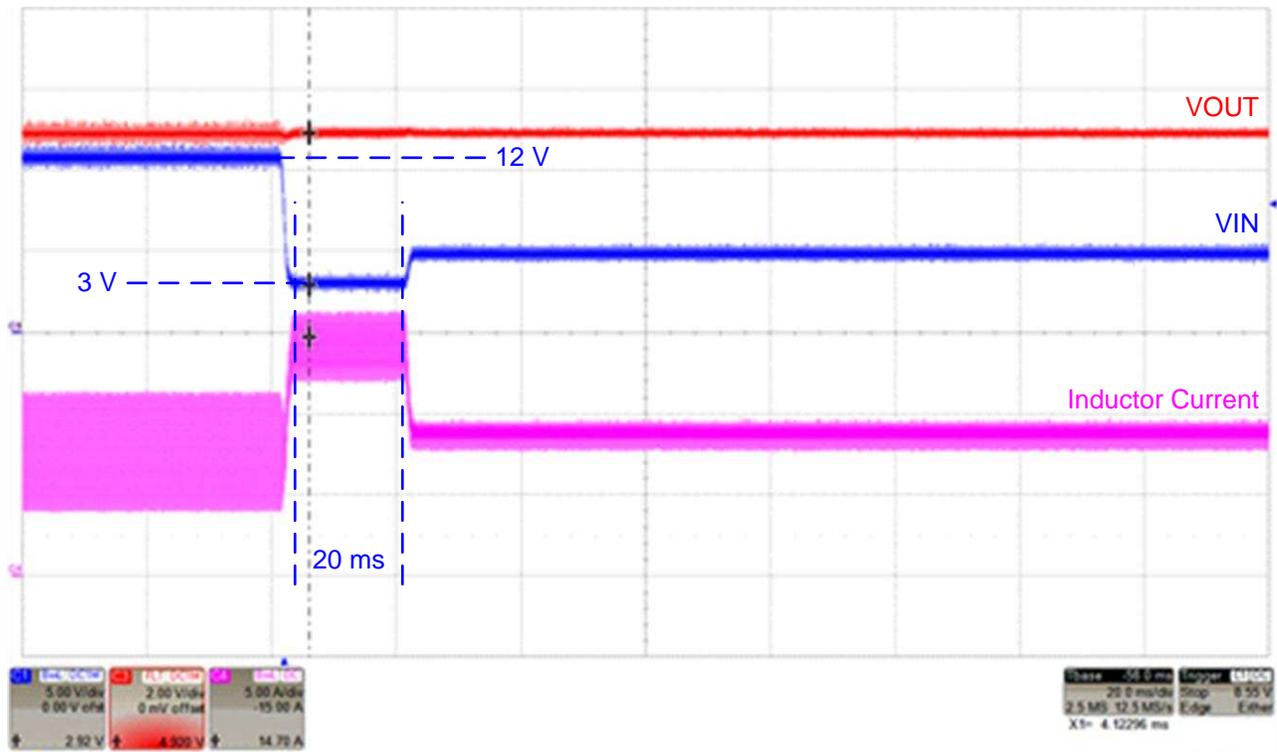


Figure 2. VOUT Regulated to 5 V as the Input Supply Voltage Drops Below 3 V for 20ms (Load=7.5 A)

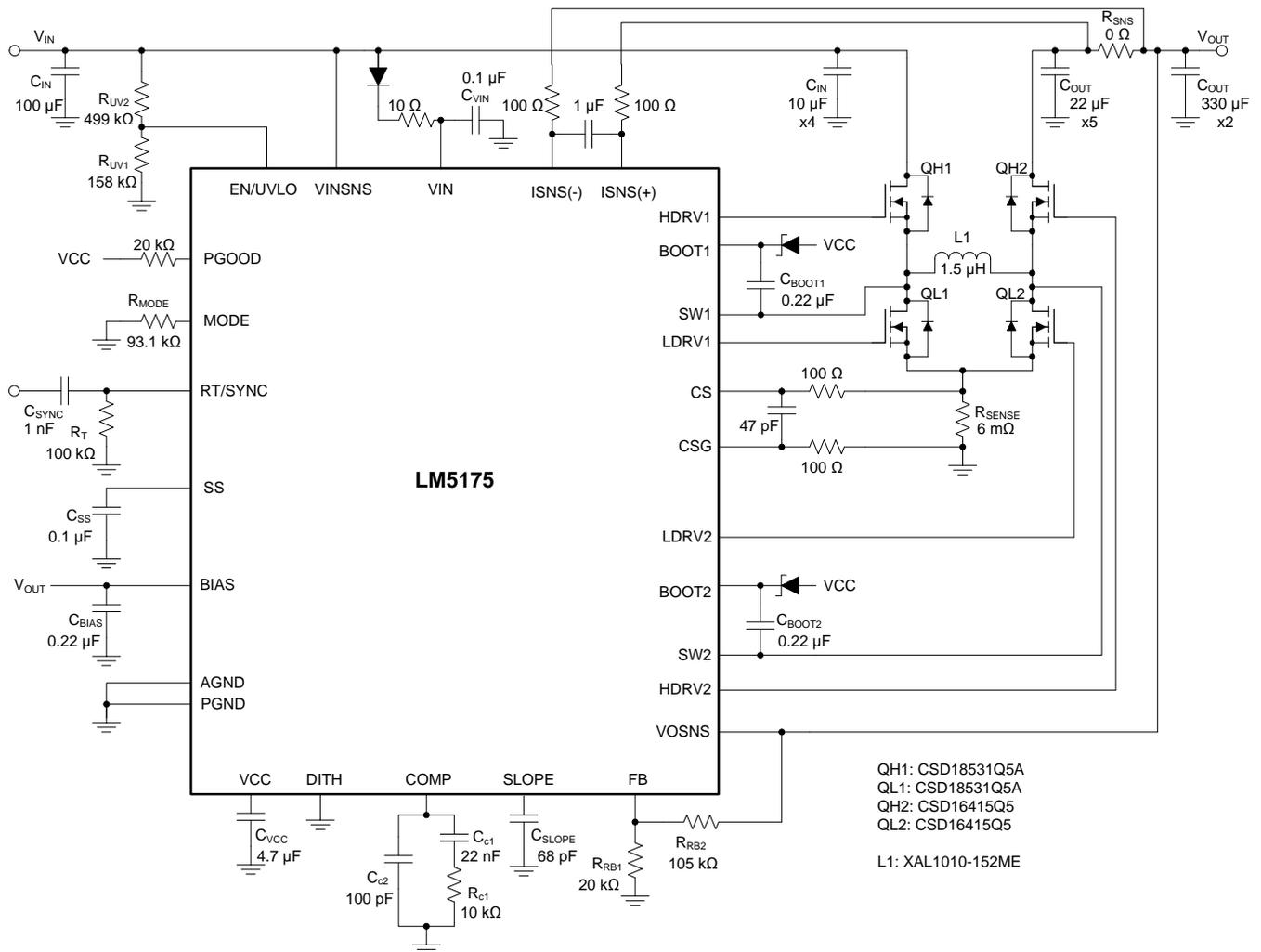


Figure 3. Complete Application Schematic for an Automotive Design For Cold-crank

1 References

ISO 7637-2: Road vehicles - Electrical disturbances from conduction and coupling -Part 2: Electrical transient conduction along with supply lines only.

LM5175 42V Wide VIN 4-Switch Synchronous Buck-Boost Controller ([LM5175](#))

Cranking Simulator Reference Design for Automotive Applications ([PMP7233](#))

Revision History

DATE	REVISION	NOTES
May 2015	*	Initial release.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com