

Soft-start Using Constant Current Approach

Akshay Mehta, Frank De Stasi

ABSTRACT

In many systems backup power is provided either by batteries or simply by a large value capacitor. In these applications the capacitor would only provide the current when the primary power source fails. Further, these applications are usually for light load currents. During normal operation the backup capacitors are kept charged up by a DC/DC converter. The challenge involved in an application like this is how to charge up the large value capacitor without overwhelming the input power supply and/or causing the DC/DC regulator to malfunction. This application note addresses that challenge.

Contents

1	Introduction	1
2	Basic Operation	2
3	External Soft-start.....	4
4	Test Results	5
5	Conclusion	6

List of Figures

1	Design Schematic	3
2	No External Soft-start	5
3	With External Soft-start; $R_{ci} = 0.75\Omega$	5
4	With External Soft-start; $R_{ci} = 1.5\Omega$	6

List of Tables

1	Max Steady state I_{OUT}	6
---	----------------------------------	---

1 Introduction

Charging large capacitors at the output of a DC/DC converter can be a challenge. When the capacitor is completely depleted and is charging up from 0V, it is going to pull large currents from the input power supply which may cause the supply to crash or in some other cases cause the DC/DC regulator to malfunction. To address this issue longer soft start times are added to the charge up of the capacitor. But even then in most devices maximum allowable soft-start times are about 10ms. This time is not going to be enough when you want to charge up a capacitor of more than 1000 μ F up to a few Farads. This is when you would need an external soft-start circuit that can provide a custom soft-start time.

This application note addresses this issue by using the LM2588 in a SEPIC configuration with an external circuit which works as constant current controller. The LM2588 is part of the LM258x family of SIMPLE SWITCHER® boost regulators from Texas Instruments. The internal NPN is capable of handling a voltage of 65V and has a current limit of 6.5A. The maximum input voltage that the device can handle is 40V. Thus this device makes a good candidate for wide V_{IN} solutions. The design shown here is created for a typical input of 5V and an output of 12V.

2 Basic Operation

The LM2588 SEPIC circuit is shown in [Figure 1](#). During the on-time of the internal NPN, the current is flowing from the input through L1 in to the internal power switch. The catch diode would thus be reverse biased and the output capacitor will now be providing the current to the load. The SEPIC cap is now charging up to V_{IN} . During the off-time of the power switch, the polarities on the inductors are reversed to maintain the same current flow through them. The diode is forward biased causing V_{OUT} to be established on L2, and $V_{OUT} + V_{IN}$ at the switch node.

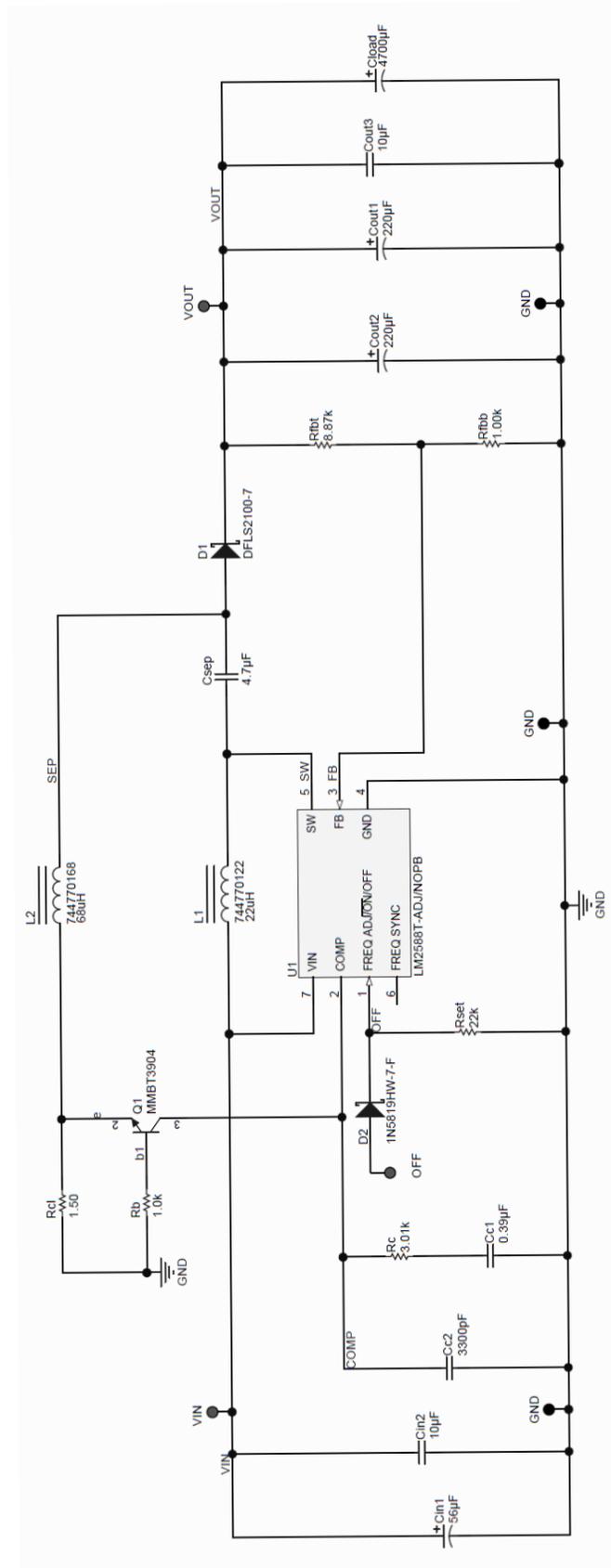


Figure 1. Design Schematic

3 External Soft-start

The SEPIC topology is chosen for this application because of the intended method of adding extra soft-start time. The SEPIC topology allows low side current sense because of the direction of the current flow through L2. Low side current sense is generally preferred because it keeps the sensing circuit simple and doesn't require it to be level shifted.

In normal condition at startup since the output voltage is low, the error generated inside the IC is large. This causes the error amplifier to increase its output in order to increase the duty cycle and help transfer current to the output. A large value capacitor will want to charge immediately to the output voltage and thus require a large current. Due to the large duty cycle, a large current will be drawn from the input source which can cause it to crash. In another situation where the input supply is capable of providing large currents but the DC/DC regulator doesn't have a limited maximum duty cycle, it will cause the device to stay on all the time and consequently the output voltage will never get established. It is therefore important to limit the inrush current and adding extra soft-start time is one way to do it.

In this application the extra soft-start time is added by controlling the COMP pin of the IC during the charging of the large capacitor. A current sense resistor is added in series with the secondary winding to ground. Thus during every switching cycle, the current flowing through the sense resistor and the inductor will cause a slight voltage drop across sense resistor. Consequently the emitter of Q1 will be a bit below ground. The base of Q1 is tied to ground through a resistor. Therefore with every cycle, the NPN turns on and yanks down on the COMP pin. This limits the COMP voltage from railing and forces a maximum duty cycle. This in turn prevents a large inrush current draw from the input power supply.

The sense resistor is part of the steady state circuit too. This means that the steady state current that can be pulled from the output will also be limited. We can use the following equations to estimate the steady state output current that can be delivered. The duty cycle for the SEPIC topology is:

$$D = \frac{V_{OUT}}{V_{OUT} + V_{IN}} \quad (1)$$

The ripple current through L2 can be calculated as shown.

$$I_{PP} = \frac{V_{IN} \cdot D}{L_2 \cdot F_{SW}} \quad (2)$$

The peak current through L2 will be limited because of Q1. It can be estimated as

$$I_{PK} \approx \frac{V_{BE}}{R_{CL}} \quad (3)$$

Now knowing the peak and the ripple current, the average DC current can be estimated as

$$I_{OUT} \approx I_{PK} - \frac{1}{2} \cdot I_{PP} \quad (4)$$

This value will not be exact and will depend on the V_{BE} drop and resistor tolerances. Since the addition of the circuit limits current delivered and also the maximum duty cycle, it increases the time it takes for V_{OUT} to reach regulation. This time is directly proportional to the value of the resistor. Larger resistor values will cause longer soft-start times and vice versa.

4 Test Results

In this example the output capacitor is 4700 μ F. [Figure 2](#) shows the converter starting-up with no external soft-start.

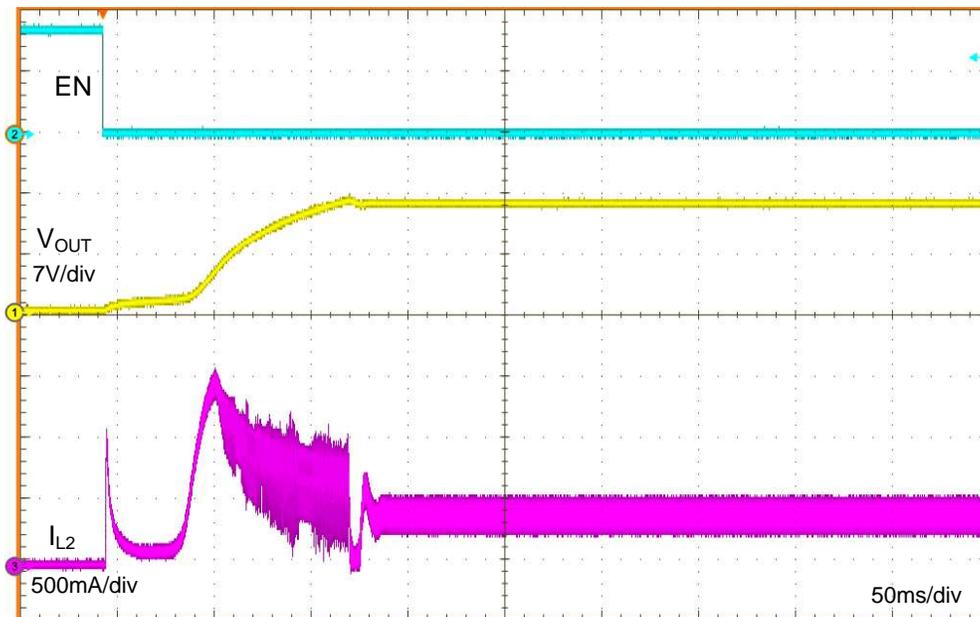


Figure 2. No External Soft-start

With the addition of Q1 and $R_{ci} = 0.75\Omega$, we get the results shown in [Figure 3](#)

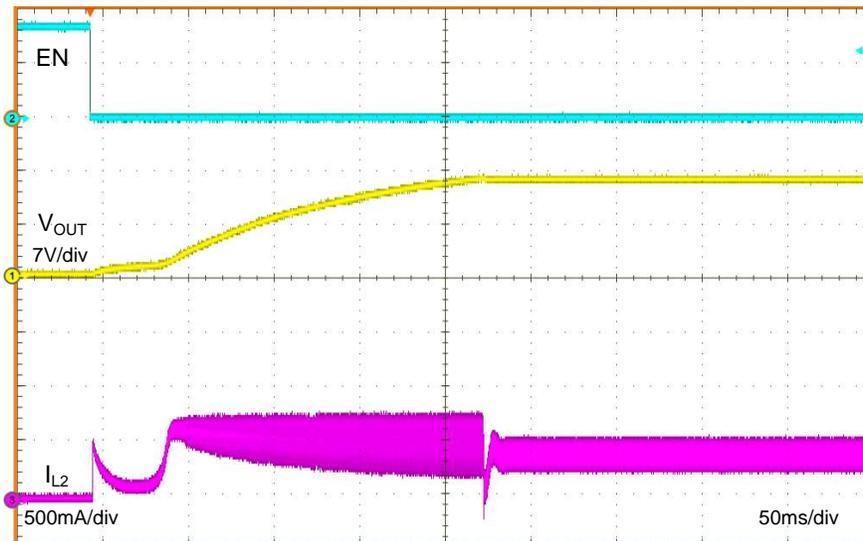


Figure 3. With External Soft-start; $R_{ci} = 0.75\Omega$

Increasing the value of R_{ci} to 1.5 Ω will increase the soft-start time and reduce the inrush current further. This is seen in [Figure 4](#).

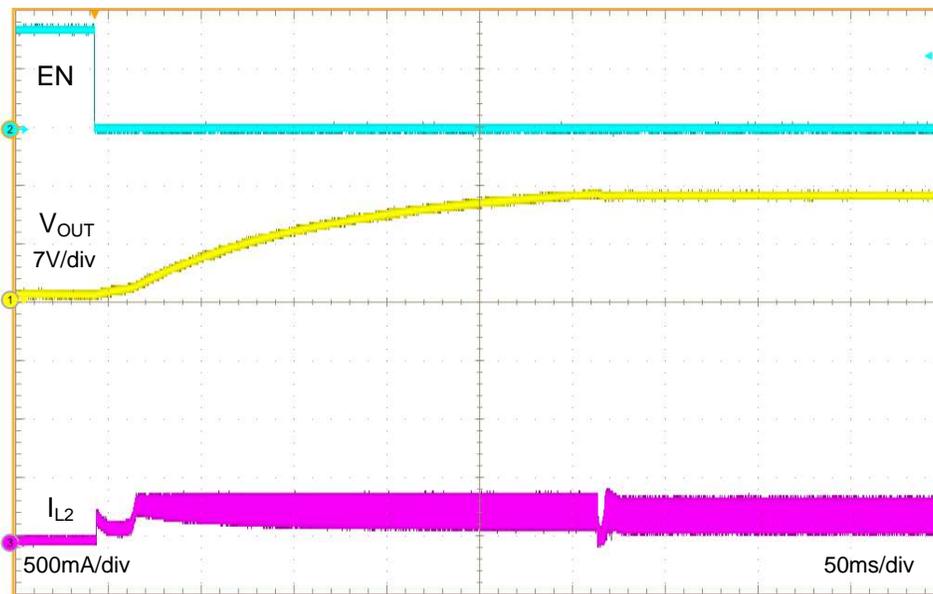


Figure 4. With External Soft-start; $R_{cl} = 1.5\Omega$

Since the external soft-start circuit stays in effect during the steady state operation, this puts a limit on the maximum obtainable load current. [Table 1](#) gives an idea of how the load current will change with change in the value of R_{cl} .

Table 1. Max Steady state I_{OUT}

$R_{cl}(\Omega)$	$I_{OUT}(A)$
1.5	250mA
0.47	540mA

5 Conclusion

Thus we see that in situations where the inrush current needs to be limited and the maximum soft-start time set by the IC is not enough, addition of external soft-start time is needed. The circuit demonstrated does that and is able to limit the inrush currents.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com