

# **Clocking Design Guidelines: Unused Pins**

Carl Wolfe

## **ABSTRACT**

Although every effort is made to provide detailed information in product data sheets to inform the design engineer of the expected performance and assist in the proper application of the device, it is unlikely that every question will be anticipated. An example of this situation is the topic of unused pins. If after reviewing the capabilities of a part, it been determined that a certain feature of a device is not needed, then it is likely there will be remaining unused pins. The design engineer will want to know what the recommendation is for these unused pins. Should they be left open, tied to ground, or pulled high? This paper reviews why these are important questions and uses actual customer questions handled by the TI applications staff as examples.

## **Contents**

1	Summary.....	1
2	Unused Pin Considerations .....	2
3	Unused Pin Examples: Customer Questions and Recommendations.....	4
3.1	CDCE62005: 5/10 Output Clock Generator/Jitter Cleaner with Integrated Dual VCO .....	4
3.2	CDCLVP1212: Low Jitter, 2-Input Selectable 1:12 Universal-to-LVPECL Buffer .....	6
3.3	CDCLVD1204: Low Jitter, 2-Input Selectable 1:4 Universal-to-LVDS Buffer .....	7
3.4	CDCLVP110: 1:10 LVPECL/HSTL to LVPECL Clock Driver .....	8
3.5	CDCV304: General Purpose and PCI-X 1:4 Clock Buffer.....	9
4	Conclusion .....	9
5	References .....	9

## **List of Figures**

1	LVPECL Simplified Drive Circuit Diagram .....	2
2	LVDS Simplified Drive Circuit Diagram .....	3
3	CDCE62005 Functional Block Diagram .....	4
4	CDCE62005 Universal Input Buffer .....	5
5	CDCLVP1212 Simplified Diagram .....	6
6	CDCLVD1204 Simplified Diagram .....	7
7	CDCLVP110 Simplified Diagram .....	8
8	CDCV304 Simplified Diagram .....	9

## **List of Tables**

1	CDCLVP1212 Supply Current .....	2
2	CDCLVP1212 $V_{AC\_REF}$ Pin Description.....	6

## **1 Summary**

This paper is intended as an aid for those engineers who have chosen to use Texas Instruments clocking products in their design, but subsequently discover that the existing data sheet or available documentation does not provide clear guidance for the product operating conditions in the case of unused pins. What is the recommendation when there are unused pins? Should unused pins simply be left open and floating? Or, should they be tied to ground or possibly biased to some voltage level? And why should this matter?

## 2 Unused Pin Considerations

Let's assume that after reviewing the capabilities of a part and comparing to the requirements of the end application, it been determined that a certain feature of a device will not be needed. Given this situation, it is possible that the result may be some pins not being required. Should the design engineer be concerned about unused pins? One might ask, "If it is not being used, then why should it matter?"

The general answer to this question is that it is simply good engineering practice to understand the functionality of the device under consideration and assure that it is applied properly. Part of the process for maximizing first-time success is to account for any unused pins that remain after the application of the product. But, there can be other reasons why one would want to take note if there are unused pins in final design.


One consideration is whether there is any relationship between unused pins and the inherent operation of the device itself. In some cases, the decision on how to handle unused pins can have an effect on the resulting performance of the device. An example of this would be the scenario of having unused output pins for a device that is based on an LVPECL clocking architecture. In this case, terminating an open output pin increases overall power dissipation. This can be seen by reviewing the CDCLVP1212 data sheet ([SCAS886D](#)). This device is a low additive jitter LVPECL buffer that can create 12 LVPECL output pairs. The supply current specifications provided in the data sheet are shown in [Table 1](#).

**Table 1. CDCLVP1212 Supply Current**

Parameter		Test Conditions	CDCLVP1212			Unit
			MIN	TYP	MAX	
$I_{EE}$	Supply internal current	Outputs unterminated			88	mA
$I_{CC}$	Output and internal supply current	All outputs terminated, $50\ \Omega$ to $V_{CC} - 2$			468	mA

As can be seen, the supply current is specified for the case of all outputs terminated, as well as the case of all outputs unterminated. If the intended application of this product is to utilize the full 12 output capability, then the power dissipation is represented by both the internal and external current under an all output load termination condition ( $468\ \text{mA} \times 3.3\ \text{V} = 1500\ \text{mW}$ ).


Note that under the operating condition where all outputs are un-terminated, the supply current is given as a much lower value of 88 mA. The maximum power dissipation will be a combination of the inherent internal dissipation of the part + the external load dissipation. The overall external load dissipation will be a function of the number of terminated outputs. As shown in [Figure 1](#), an LVPECL output stage is an open-emitter transistor. The power dissipated in this stage is a function of the current established when the external termination resistors are connected. <sup>(6)</sup> So, if there are unused LVPECL outputs in a given application and those unused outputs are terminated, they will be contributing to the overall power dissipation. A rough approximation is about 20 mW per LVPECL output pair.

 

**Figure 1. LVPECL Simplified Drive Circuit Diagram**

If you are using an LVPECL clocking buffer and not utilizing the full fanout capability, be aware that the overall power dissipation can be reduced by not terminating the unused outputs.

A similar recommendation applies for LVDS outputs, but the reduction is not as significant. The reason being that LVDS is a lower power architecture and power dissipation contribution of the load is much lower. This can be seen in [Figure 2](#), where the simplified diagram illustrates that the LVDS drive is a 3.5-mA current source. So, when terminated in a 100-Ω termination, the resulting power dissipation represented by the load is  $P = I^2R = (0.0035)^2 \times 100 = 1.2 \text{ mW}$ .

 


**Figure 2. LVDS Simplified Drive Circuit Diagram**

Device power dissipation is an example of a “general” unused pin design consideration that the engineer should keep in mind, but sometimes there will be questions regarding unused pin scenarios for a particular device. The following information provides responses to common customer questions for specific products.

### 3 Unused Pin Examples: Customer Questions and Recommendations

#### 3.1 CDCE62005: 5/10 Output Clock Generator/Jitter Cleaner with Integrated Dual VCO

**Question #1:** “What do I do with the SEC\_REF+ and SEC\_REF– pins, if I’m not using this input? Should both of these unused inputs be grounded (see Figure 3)?”

 

**Figure 3. CDCE62005 Functional Block Diagram**

**Response:** The decision for how to handle unused PRI\_REF/SEC\_REF inputs depends on the input buffer selection. These unused input pins should be connected depending on the buffer type selected, as described as follows:

- If input buffer selection is LVCMOS (internal termination is turned off), the unused inputs should be connected to ground through 1-k $\Omega$  resistors.
- If input buffer selection is differential (LVDS/LVPECL), then connect one input of the differential pair to  $V_{DD}$  and other input to ground through 1-k $\Omega$  pullup and pulldown resistors.

**Question #2:** “Is there a preference to select internal termination vs external termination? For example, in the case of the SEC REF +/- inputs, if PRI REF +/- is CMOS, it is suggested to tie the unused SEC REF +/- to gnd via a 1-k $\Omega$  external resistor. But, there is also the option to set internal termination resistors for these pins via internal register settings. What are the considerations for whether to use external or internal termination?”

**Response:** When you choose PRI\_REF as LVCMOS input, the SEC\_REF will also be selected as LVCMOS input. The reason is that the same register bit selects the buffer type, so both input buffers are selected as the same type. So, in the case of the LVCMOS buffer selection, the recommendation is to ground both input pins to ground through 1-k $\Omega$  resistors.

Regarding the internal input termination resistors, these are an option as part of the universal buffer input stage, although they are not intended for terminating unused pins. Rather, they are intended for providing receiver input termination for LVPECL (50-Ω termination) or LVDS (100-Ω termination) drivers. These internal termination values can be configured for the appropriate termination based on the PN, PP, and PINV switch setting selections made in register 5 (see Figure 4). The basic consideration on whether to use external or internal termination will be performance. External termination is usually more accurate since it will exhibit tighter tolerance and has less temperature variation vs integrated silicon-based internal resistors.


 


Figure 4. CDCE62005 Universal Input Buffer

**Question #3:** “What do I do with the unused AUX\_IN?”

**Response:** If the AUX\_IN pin is not used, it is recommended to connect this pin to ground through a 1-kΩ resistor. In addition, the VCC\_AUX power supply pin, intended for powering the internal 3.3-V crystal oscillator circuitry, can be left open/not connected.

### 3.2 CDCLVP1212: Low Jitter, 2-Input Selectable 1:12 Universal-to-LVPECL Buffer

 

**Figure 5. CDCLVP1212 Simplified Diagram**

**Question #4:** “What should I do with the V<sub>AC\_REF</sub>, pin 7, if unused? Do I still put a 0.1- $\mu$ F capacitor to ground as it recommends in the pin description table on page 5 of the data sheet (see [Figure 5](#))?”

**Table 2. CDCLVP1212 V<sub>AC\_REF</sub> Pin Description**

Terminal Name	Terminal Number	Type	Pullup/Pulldown	Description
V <sub>AC_REF</sub>	7	Output	—	Bias voltage output for capacitive coupled inputs. If used, it is recommended to use a 0.1- $\mu$ F capacitor to GND on this pin. The output current is limited to 2 mA.

**Response:** If the internal biasing/ V<sub>AC\_REF</sub> function is not used (assuming external biasing and termination is used), then connection of that capacitor to the V<sub>AC\_REF</sub> pin is not required.

### 3.3 CDCLVD1204: Low Jitter, 2-Input Selectable 1:4 Universal-to-LVDS Buffer


 


Figure 6. CDCLVD1204 Simplified Diagram

**Question #5:** “What are the recommendations for unused inputs and outputs (see Figure 6)?”

**Response:** Unused outputs can be left open, although it is recommended to not connect any traces to unused output pins. But, for unused inputs, it is recommended to connect both unused input pins, INPx, INNx, to ground thru using 1-kΩ resistors. Open outputs can conserve power, while terminating the inputs will help minimize the receiver stage from picking up noise.

### 3.4 CDCLVP110: 1:10 LVPECL/HSTL to LVPECL Clock Driver

 

**Figure 7. CDCLVP110 Simplified Diagram**

**Question #6:** “We are using the CDCLVP110 for differential signaling, but we do not know what to do with the VBB pin then. Do we tie it high, or low, or leave it open (see [Figure 7](#))?”

**Response:** Yes, you can leave VBB floating if you do not use that. You can use this VBB biasing voltage if you use ac-coupled differential input.

**Question #7:** “I am only using six of the 10 outputs of the CDCLVP110. How do I calculate power dissipation savings when 4 outputs are unused?”

**Response:** From CDCLVP110 data sheet ([SCAS683D](#)):

IEE - Max internal supply current = 82 mA

ICC - Max output + internal supply current (with all outputs terminated in 50 Ω) = 370 mA


Therefore, Max current due to load (20 terminations) = ICC – IEE = 370 mA – 82 mA = 288 mA.

So, output current due to load/channel = 288/20 = 14.4 mA.

Power dissipation per load =  $I^2R = (.0144)^2 \times 50 \Omega = 10 \text{ mW/load termination (or } 20 \text{ mW per differential output pair)}$ .

Therefore, expected power dissipation savings associated with 4 unused outputs is 80 mW.

### 3.5 CDCV304: General Purpose and PCI-X 1:4 Clock Buffer

 

**Figure 8. CDCV304 Simplified Diagram**

**Question #7:** “Do the unused outputs need to be terminated? If so, what is the recommended termination (see [Figure 8](#))?”

**Response:** TI recommends leaving the unused outputs floating without connecting any traces to the output pin.

## 4 Conclusion

Do not ignore unused pins as you finalize your design. If the available product documentation does not specifically provide recommendations regarding the status of unused pins, then the manufacturer’s local or factory applications staff should be contacted for further guidance.

## 5 References

1. *Power Consumption of LVPECL and LVDS* ([SLYT127](#))
2. *LVDS Handbook* ([www.ti.com/LVDS](http://www.ti.com/LVDS))
3. *CDCE62005 Data Sheet* ([SCAS862F](#))
4. *CDCLVP1212 Data Sheet* ([SCAS886D](#))
5. *CDCLVD1204 Data Sheet* ([SCAS898A](#))
6. *CDCLVP110 Data Sheet* ([SCAS683D](#))
7. *PCB Layout Guidelines for the CDCLVP110* ([SCAA057](#))
8. *CDCV304 Data Sheet* ([SCAS643H](#))

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)