

Analysis and Design of Input Filter for DC-DC Circuit

Charles Zhang

ABSTRACT

When designing DC-DC circuits, it is common to add the input filter circuit before the power stage. An LC filter is one of most frequently used input filter circuit. However, if a design is not optimal, input filter circuit may cause large output noise instead of suppressing the noise, and may even cause loop stability problems. This application report analyzes the influence of the input filter on the DC-DC control loop transfer function, and the influence of a closed loop on the input filter, explains why input filter causes unexpected problem, and suggests how to eliminate the side effect of the input filter.

Contents

1	Function of Input Filter Circuit.....	2
2	Loop Gain of Buck With Input LC Filter	2
2.1	Open Loop Small Signal Model	2
2.2	Closed Loop of the Buck Converter	4
2.3	Loop Gain With Input LC Filter.....	5
3	Closed-Loop Input Impedance	7
3.1	Closed-Loop Input Impedance Calculation.....	7
3.2	Influence of the Input Impedance on Input Filter	8
4	Designing the Input Filter Circuit.....	9
4.1	Stability Criteria With Input Filter.....	9
4.2	Damping the Input Filter.....	10
5	Conclusion	11
6	References	11

Trademarks

All trademarks are the property of their respective owners.

1 Function of Input Filter Circuit

Input filters are widely used in power design. They have two main purposes: one is to suppress the noise and surge from the front stage power supply, another is to decrease the interference signal at switching frequency and its harmonic frequency to go back to the power supply and interfere other devices which uses the power supply. The input filter design is very important to pass the electromagnetic compatibility (EMC) test.

Simple LC passive filters are among the common filters for DC-DC converters. They can attenuate the high frequency noise from the power supply and can also suppress the switching noise to go back to the power supply.

If LC filter is not well damped, the frequency response will peak near resonant frequency, which means the LC actually is amplifying the noise signal. Apart from the amplification, sometimes, LC filter design also has effect on the control loop of the DC-DC converter, some poor LC filter will decrease the phase margin and degrade the transient response performance, some even cause stability problem. This is discussed in [Section 2](#) based on a buck converter.

2 Loop Gain of Buck With Input LC Filter

2.1 Open Loop Small Signal Model

[Figure 1](#) is a traditional synchronous buck converter. During the on and off status of one switching cycle, FET shows non-linear characteristic. According to the average model, the small signal of input current and switching node voltage can be calculated as [Equation 1](#), and the open loop small signal model of the buck can be expressed as [Figure 2](#).

$$\begin{aligned}\hat{i}_{in} &= I_L \hat{d} + D \hat{i}_L \\ \hat{u}_{CP} &= U_{in} \hat{d} + D \hat{u}_{in}\end{aligned}\quad (1)$$

 


Figure 1. Buck Circuit Topology

 


Figure 2. Buck Circuit Small Signal Model

It is normal that input voltage and output current may change, which influences the output voltage and inductor current. When adopting closed loop control, duty cycle may change to maintain the output voltage, at the same time, the inductor current will change. So we can build the open loop control block diagram as [Figure 3](#).

 


Figure 3. Open-Loop Buck Controller Block Diagram

For simplicity, ignore the inductor DCR and output capacitor ESR when calculated the transfer function. Then the six transfer functions in Figure 3 are calculated as Equation 2 to Equation 7. All the six transfer functions will be used in following sections, especially at Section 3.1.

$$G_{ud}(s) = \frac{\hat{u}_o(s)}{\hat{d}(s)} \Big|_{\hat{u}_i(s), \hat{i}_o(s)} = \frac{U_i}{LCs^2 + \frac{L}{R}s + 1} \quad (2)$$

$$G_{uu}(s) = \frac{\hat{u}_o(s)}{\hat{u}_i(s)} \Big|_{\hat{d}(s), \hat{i}_o(s)} = \frac{D}{LCs^2 + \frac{L}{R}s + 1} \quad (3)$$

$$Z_{out}(s) = \frac{\hat{u}_o(s)}{\hat{i}_o(s)} \Big|_{\hat{d}(s), \hat{u}_i(s)} = \frac{Ls}{LCs^2 + \frac{L}{R}s + 1} \quad (4)$$

$$G_{id}(s) = \frac{\hat{i}_L(s)}{\hat{d}(s)} \Big|_{\hat{u}_i(s), \hat{i}_o(s)} = \frac{\frac{U_i}{R}(1 + RCs)}{LCs^2 + \frac{L}{R}s + 1} \quad (5)$$

$$G_{iu}(s) = \frac{\hat{i}_L(s)}{\hat{u}_i(s)} \Big|_{\hat{d}(s), \hat{i}_o(s)} = \frac{\frac{D}{R}(1 + RCs)}{LCs^2 + \frac{L}{R}s + 1} \quad (6)$$

$$G_{ii}(s) = \frac{\hat{i}_L(s)}{\hat{i}_o(s)} \Big|_{\hat{d}(s), \hat{u}_i(s)} = \frac{1}{LCs^2 + \frac{L}{R}s + 1} \quad (7)$$

Input impedance is a key parameter in this paper, which is not obvious to draw in Figure 3; nevertheless, open loop input impedance can be defined and calculated as Equation 8 using a similar method.

$$Z_{in}(s) = \frac{\hat{u}_i(s)}{\hat{i}_{in}(s)} \Big|_{\hat{d}(s), \hat{i}_o(s)} = \frac{\hat{u}_i(s)}{\hat{i}_L(s)} \Big|_{\hat{d}(s), \hat{i}_o(s)} = \frac{R}{D^2} \frac{LCs^2 + \frac{L}{R}s + 1}{(1 + RCs)} \quad (8)$$

2.2 Closed Loop of the Buck Converter

For a buck converter, it is normally desired that the output voltage is constant. Feedback topology is used to close the control loop, it automatically changes the duty cycle to decrease or even eliminate the influence from the input voltage or output current. A typical closed loop of VMC buck converter is as Figure 4. H is the feedback resistor network, G_c represents the error amplifier, and G_m is for the modulator gain.

 


Figure 4. VMC Closed Loop Buck Controller Block Diagram

By adopting closed loop topology, loop gain is defined as the product of the gains in feedforward path and feedback path in the closed loop as [Equation 9](#). Take the VMC plus type III compensator as example, the frequency response of T_{loop} can be plotted as [Figure 5](#).

$$T_{loop}(s) = HG_cG_mG_{ud} \quad (9)$$

 


Figure 5. Loop Gain Frequency Response

Under the effect of the closed loop, the transfer function from the perturbation to the output voltage is multiplied by a factor $1/(1 + T(s))$. The closed loop audio susceptibility and output impedance can be expressed as [Equation 10](#) and [Equation 11](#). And the open loop and closed loop frequency response can be drawn as [Figure 6](#) and [Figure 7](#), it can be seen from the picture, low frequency perturbation can be well suppressed by closing the control loop.

$$G_{uu_CL}(s) = \frac{G_{uu}(s)}{1 + T_{loop}(s)} = \frac{D}{(1 + T_{loop}(s)) \cdot (LCs^2 + \frac{L}{R}s + 1)} \quad (10)$$

$$Z_{out_CL}(s) = \frac{Z_{out}(s)}{1 + T_{loop}(s)} = \frac{Ls}{(1 + T_{loop}(s)) \cdot (LCs^2 + \frac{L}{R}s + 1)} \quad (11)$$

 


Figure 6. Closed Loop Audio Susceptibility

 


Figure 7. Closed Loop Output Impedance

2.3 Loop Gain With Input LC Filter

Even though closed loop suppresses the audio susceptibility a lot at low frequency, but it doesn't change too much for the middle and high frequency. The designer should also consider the interference from the DC-DC back to the power bus. Thus, a LC filter is often used for DC-DC circuit to pass EMI test.

When adopting LC filter to solve an EMI problem, another problem may arise, when the load transient performance changes, audio stability becomes worse at some frequency, some even cause the stability problem. These problems can be explained as that input filter circuit modifies the transfer function of the buck converter, including the control to output transfer function G_{ud} , which then changes the loop gain, phase margin, etc.

According to Middlebrook's extra element theorem, adding the filter circuit to the buck converter adds a correction factor to the original transfer function.

 


Figure 8. Buck Control Block Diagram With LC Filter

$$G_{ud_f}(s) = \left(G_{ud}(s) \Big|_{Z_{filter}(s)=0} \right) \frac{\left(1 + \frac{Z_{filter}(s)}{Z_N(s)} \right)}{\left(1 + \frac{Z_{filter}(s)}{Z_D(s)} \right)}$$

where

- $G_{ud}(s) \Big|_{Z_{filter}(s)=0}$ is the original transfer function before addition of input filter. (12)

$Z_{filter}(s) = (sL_f + R_{DCR}) \parallel \left(\frac{1}{sC_f} + R_{ESR} \right)$ is the output impedance of the LC filter, looking from DC-DC side.

$Z_D(s) = Z_{in}(s) \Big|_{\hat{d}(s)=0} = \frac{R}{D^2} \frac{LCs^2 + \frac{L}{R}s + 1}{1 + RCs}$ is the converter input impedance, with $\hat{d}(s)$ set to zero.

$Z_N(s) = Z_{in}(s) \Big|_{\hat{u}_o(s) \rightarrow 0} = -\frac{R}{D^2}$ is the converter input impedance, with the output nulled to zero.

Using a poorly designed LC filter as an example, after addition of correct factor, the new loop gain transfer function can be calculated from [Equation 13](#). The frequency response can be calculated as [Figure 9](#), simulated as [Figure 10](#) using Simplis, the two waveforms show good consistency of the LC resonant frequency.

$$T_{loop}(s) = HG_c G_m G_{ud_f} \quad (13)$$

 


Figure 9. Mathcad Calculation Loop Gain

 


Figure 10. Simplis Simulation Loop Gain

Comparing the new frequency response waveform with original one, it can be easily found that the LC filter brings a dip to the original frequency response, the magnitude-frequency curve drops to close to 0 db in this case, and the phase-frequency curve also drops near that point, which makes the loop gain performance worse.

3 Closed-Loop Input Impedance

3.1 Closed-Loop Input Impedance Calculation

The open loop input impedance is defined as [Equation 8](#), after applying the closed loop, the closed loop changes the input impedance, because when input voltage change, duty cycle changes to maintain the output voltage, which also brings additional change to the input current.

To calculate the closed loop input impedance, combined with [Equation 1](#), the block diagram can be draw as [Figure 11](#). By changing the feedback and feed-forward position, a simplified block diagram can be drawn as in [Figure 12](#). By comparing [Equation 2](#) through [Equation 8](#), it can be calculated that

$$\frac{G_{uu}}{G_{ud}} = \frac{D}{U_I}, D G_{iu} = \frac{1}{Z_{in}}, G_{uu} G_{id} = \frac{G_{ud}}{D Z_{in}} \quad (14)$$

combined with [Figure 12](#), a single block from input voltage to input current can be expressed as [Figure 13](#).

 


Figure 11. Closed Loop Input Impedance Calculation Block Diagram

 


Figure 12. Simplified Closed Loop Input Impedance Calculation Block Diagram

$$\hat{u}_i \rightarrow \frac{1}{(1+T_{loop})Z_{in}} - \frac{D}{U_I} \times \frac{T_{loop}}{1+T_{loop}} \times I_L \rightarrow \hat{i}_{in}$$

Figure 13. Single Block From Input Voltage to Input Current

So the closed loop input impedance can be calculated as [Equation 15](#):

$$Z_{in_CL}(s) = \frac{\hat{u}_{i_CL}(s)}{\hat{i}_{in_CL}(s)} = Z_{in} \frac{(1+T_{loop})}{1 - \frac{DI_L T_{loop} Z_{in}}{U_I}} \quad (15)$$

The frequency response of closed loop input impedance is plotted as [Figure 14](#) in comparison with open loop input impedance. It can be seen that closed loop impedance and open loop impedance shows similar characteristic when frequency goes high; during middle frequency, the closed loop makes the impedance amplitude larger, which means that same input voltage change will bring smaller input current variation. At low frequency, they show same amplitude characteristic, but closed loop makes the phase characteristic changes, the phase at low frequency is close to -180° , it functions as negative incremental input impedance. For example, the output voltage and current are fixed, if input voltage increases, the input current decreases, it looks like negative resistor.

 


Figure 14. Open-Loop and Closed-Loop Input Impedance

3.2 Influence of the Input Impedance on Input Filter

For a DC-DC circuit, if the input filter is utilized, this negative incremental input impedance also has some influence on the input filter circuit. From [Figure 14](#) it can also be seen, when loop is open, the input impedance is very low at middle frequency, and the low impedance brings more damping to the LC filter circuit, but when adopting closed loop, the impedance becomes negative, this is decreasing the damping to the LC filter. Define the transfer function from input voltage to the output of the LC filter as $G_{fv}(s)$. Use Mathcad to draw the frequency response of $G_{fv}(s)$ as [Figure 15](#). It can be seen, when loop is open, the peak value of the amplitude is very small, much less than 20 dB. But when adopting the closed loop, the peak value is close to 20 dB, which means very small damping of the LC circuit.

 


Figure 15. Input Filter Frequency Response With Closed Loop

When the damping ratio is too small, normally there will be large amplitude oscillation in time-domain waveform. [Figure 16](#) is the test result based on the TPS40040EVM by adding a 3.5- μ H inductor as filter circuit. Taking the de-rating of the inductor and MLCC into consideration, a Simplis simulation result is plotted as [Figure 17](#), which shows good consistence with the EVM test result.

 


Figure 16. Load Transient Test on EVM

 


Figure 17. Load Transient Test of Simplis Simulation

4 Designing the Input Filter Circuit

4.1 Stability Criteria With Input Filter

From above load transient test, it can be seen that when the load is heavy, the oscillation is much larger than light load, because larger load current brings smaller negative incremental input impedance, which means much smaller damping ratio, or even brings stability problem. Capacitor ESR, Inductor DCR and power source output impedance R_O are also very critical for stability, because they also bring damping to the LC filter. To analyze the stability of a buck circuit with an LC filter, use a pure resistor $-R_{in} = Z_{in}(s)|_{s=0}$ as input impedance, then equivalent circuit is [Figure 18](#).

 


Figure 18. Equivalent Circuit for Stability Analysis

R_{ESR} is normally much smaller than $-R_{in}$, so the paralleled impedance of the capacitor, and the input impedance can be expressed as [Equation 16](#) and $G_{fv}(s)$ can be expressed as [Equation 17](#).

$$-R_{in} // \left(\frac{1}{sC} + R_{ESR} \right) \approx \frac{-R_{in} (1 + sCR_{ESR})}{1 - sCR_{ESR}} \quad (16)$$

$$G_{fv}(s) = \frac{\hat{u}_f(s)}{\hat{u}_in(s)} = \frac{R_{in} (1 + sCR_{ESR})}{s^2 L C R_{in} + s [R_{in} C (R_O + R_{DCR} + R_{ESR}) - L] + (R_{in} - R_O - R_{DCR})} \quad (17)$$

For stability, there should be no positive pole for $G_{fv}(s)$, then

$$\begin{aligned} LCR_{in} &> 0 \\ R_{in}C(R_O + R_{DCR} + R_{ESR}) - L &> 0 \\ R_{in} - R_O - R_{DCR} &> 0 \end{aligned} \quad (18)$$

So the stability requirement is as [Equation 19](#) and [Equation 20](#), and the damping ratio is as [Equation 21](#).

$$R_{in} > \frac{L}{C(R_O + R_{DCR} + R_{ESR})} \quad (19)$$

$$R_{in} > R_O + R_{DCR} \quad (20)$$

$$\zeta = \frac{[R_{in}C(R_O + R_{DCR} + R_{ESR}) - L]}{2\sqrt{LCR_{in}} \times (R_{in} - R_O - R_{DCR})} \quad (21)$$

Normally it is not very hard to meet [Equation 19](#) and [Equation 20](#). But in some cases, even though meets [Equation 19](#) and [Equation 20](#), if R_{in} is too small, according to [Equation 21](#), the damping ratio of the system is also small, which brings large oscillation. Normally this happens with the condition of large output current and large duty cycle, and the input cap is using MLCC which has smaller ESR. That's why in [Figure 9](#) and [Figure 10](#), when load is heavy, the oscillation amplitude is large.

4.2 Damping the Input Filter

If oscillation happens after adding a LC filter circuit, normally decreasing the inductor value or increasing the capacitor value may increase the damping ratio and remove the oscillation, but this will also change the target LC filter characteristic. Sometimes replacing MLCC with electrolytic capacitor may also solve the problem. But the large ESR of the electrolytic capacitor will also bring large input voltage ripple when the MOSFET is switching. Another way is to add an additional damping circuit after the LC filter circuit like [Figure 19](#). The resistor is to damp the filter, and because we only want to damp the middle frequency amplitude peak value, there is no need to use a pure resistor as the damping circuit. Rather, a series capacitor C_d can be used to avoid large power dissipation on the resistor. A capacitor much larger than C is required for the LC filter to detect R_d at the middle frequency, $C_d \geq 4C$ may be an acceptable value, and there is no need to use good-quality capacitor like C to saving cost.

 


Figure 19. LC Filter With Damping Circuit

 


Figure 20. Equivalent Circuit at Middle Frequency

By applying the damping circuit, the approximate circuit at middle frequency is as [Figure 20](#), the equivalent input impedance is shown in [Equation 22](#): by adding the damping circuit, the absolute value of the equivalent input impedance value will increase, which increases the damping ratio of the LC filter.

$$-R_{in}' = \frac{(-R_{in}) \cdot R_d}{-R_{in} + R_d} = -R_{in} \left(\frac{1}{1 - R_d/R_{in}} \right) \quad (22)$$

By adding additional damping circuit, EVM test result and the Simplis simulation result are as [Figure 21](#) and [Figure 22](#), which shows good consistency.

 


Figure 21. Load Transient Test on EVM

 


Figure 22. Load Transient Test of Simplis Simulation

5 Conclusion

An LC filter is widely used to optimize the EMC during DC-DC design, but improper design of the LC filter may cause the stability problem. This paper analyzes the influence of the input filter on the closed-loop gain, also explains how the closed loop brings the negative incremental input impedance and influence the LC filter. At the end, this paper describes stability criteria for LC filter design and also suggests some methods to solve oscillation problem when adopting LC filter.

6 References

1. R.D. Middlebrook, "Input filter considerations, in design and application of switching regulators" 1976 IEEE
2. Texas Instruments, *Input Filter Design for Switching Power Supplies* application note
3. Texas Instruments, *Low Pin Count, Low VIN (2.5V to 5.5V Synchronous Buck DC-to-DC Controller TPS40040/1* data sheet
4. Texas Instruments, *AN-2162 Simple Success With Conducted EMI From DCDC Converters* application report
5. R. Ahmadi, D. Paschedag, and M. Ferdousi, "Closed-loop input and output impedances of DC-DC switching converters operating in voltage and current mode control," *Proc. IECON '10*, 2010, pp. 2311–2316.
6. R. W. Erickson and D. Maksimovic, *Fundamentals of Power Electronics*, 2nd ed. New York: Kluwer, 2001.
7. Marian K. Kazimierczuk, *Pulse Width Modulated DC-DC Power Converters*, 2nd ed. Ohio: Wiley, 2016.

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), evaluation modules, and samples (<http://www.ti.com/sc/docs/samptersms.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2017, Texas Instruments Incorporated