

# Implementing Analog Thermal Foldback with the LP8867-Q1 and TMP61-Q1



Jalen Tate

## ABSTRACT

As technology increases in this digital age, visualization technologies are the most vital components of in-vehicle interactions, with overall automotive navigation and connectivity characterizing the cars of this generation. The incorporation of interactive displays have become a key feature of manufacturing processes deployed by prominent automakers. As demand for interactive operations and experiences get stronger, more and more products provide an LCD screen.

---

## Table of Contents

<b>1 Introduction</b> .....	2
<b>2 Conventional Backlighting vs. Local-Dimming backlighting</b> .....	2
<b>3 LP886x-Q1 TSET Implementation</b> .....	3
<b>4 LP886x-Q1 ISET Implementation</b> .....	5
<b>5 Summary</b> .....	7

## List of Figures

Figure 2-1. LCD Panel Architecture.....	2
Figure 2-2. Local Dimming vs. Conventional Backlight zones.....	3
Figure 3-1. Temperature-Based LED Current Dimming Functionality.....	3
Figure 3-2. TSET Temperature-Based LED Current Dimming Schematic.....	4
Figure 3-3. Current Foldback Profile with TMP61.....	5
Figure 4-1. ISET Temperature-Based LED Current Dimming Schematic.....	6
Figure 4-2. Simulation Results.....	6

## List of Tables

## Trademarks


All trademarks are the property of their respective owners.

## 1 Introduction

The LED backlight driver is a key part of this LCD panel system and some engineers may encounter various problems when choosing the right devices and designing such circuits. These LED drivers regulate the output current to the LED's on the panel. In automotive environments the LED's on the display panel can get very hot. Temperature sensors are often used to monitor the LED temperature and provide brightness regulation. Additionally, temperature sensors are also used to monitor the LED Driver thermals. With the remote thermistor embedded in the backlight enclosure/panel there are a couple ways to achieve thermal sensing and foldback with an LED Driver. The integrated thermistor can be used with the foldback pin of an LED Driver or provide thermal foldback in a discrete implementation to the LED Driver. This application report shows how to implement TI's TMP6 family of thermistors with TI's LP886x family of low EMI Automotive LED Drivers, specifically the LP8867-Q1.

## 2 Conventional Backlighting vs. Local-Dimming backlighting

There are two types of technologies for controlling the dimming and brightness of an LCD screen, conventional and local dimming. In conventional backlighting black is reproduced as dark gray and details are lost in the shadows. With local dimming techniques, backlighting is optimized for specific areas of the image, resulting in deeper blacks. A local-dimming backlight technology is a direct-lit architecture where the LEDs are directly behind the LCD panel as shown in [Figure 2-1](#).

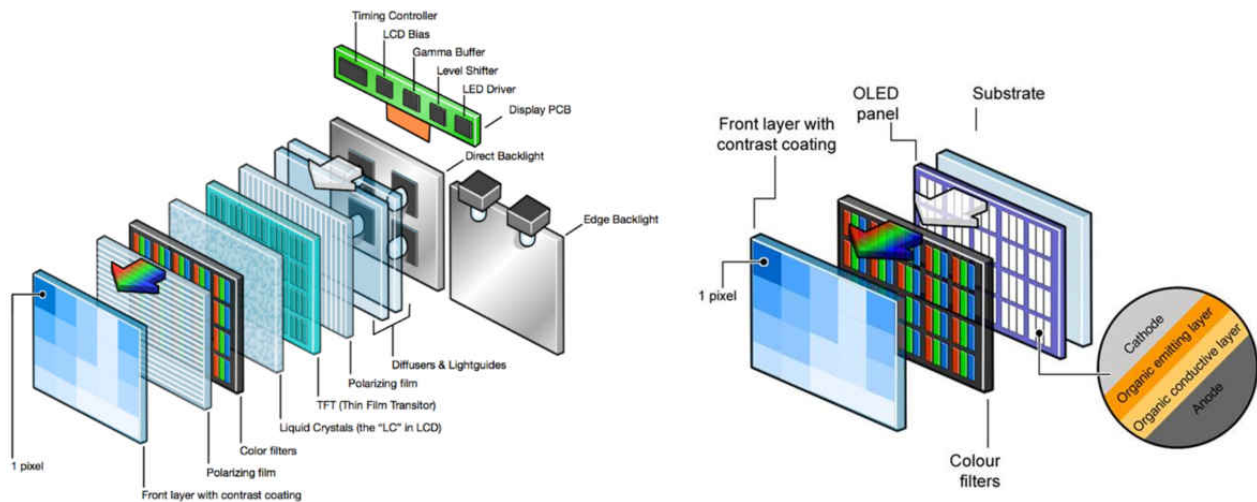

**Figure 2-1. LCD Panel Architecture**

In local dimming backlight, the LCD panel is divided into many small “zones”. The brightness of each zone is adjusted according to different display content. A local dimming backlight allows the display to have “darker blacks” and “brighter whites”.

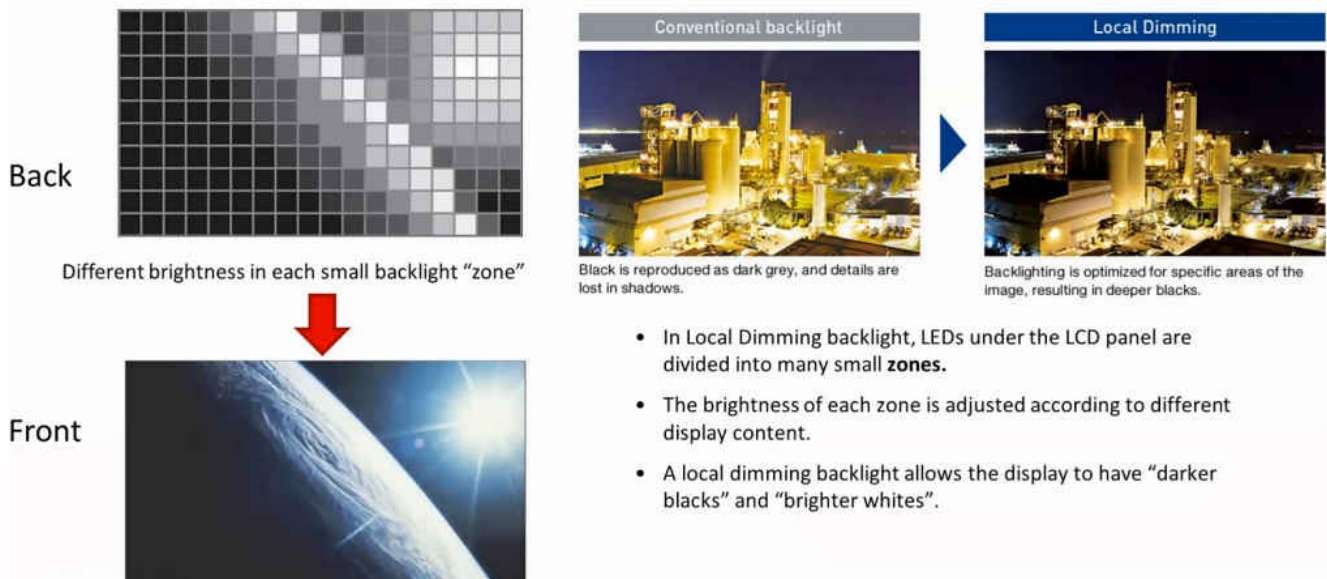


Figure 2-2. Local Dimming vs. Conventional Backlight zones

To optimize the control of the brightness of these small zones, temperature feedback is critical to provide to the system. The LP8869-Q1 has two pins  $T_{SET}$  and  $I_{SET}$  that can be used in concert with thermistor divider circuits to provide thermal information to the system and allowing for a thermal foldback profile for the LED's, limiting the amount of current after a certain temperature threshold thus protecting them.

### 3 LP886x-Q1 TSET Implementation

The LP886x-Q1 has an optional feature to decrease automatically LED current when LED overheating is detected with an external PTC sensor. An example of the behavior is shown in Figure 3-1. When the PTC temperature reaches  $T_1$ , the LP886x-Q1 starts to decrease the LED current. When the LED current has reduced to 17.5% of the nominal value, current turns off until temperature returns to the operation range.

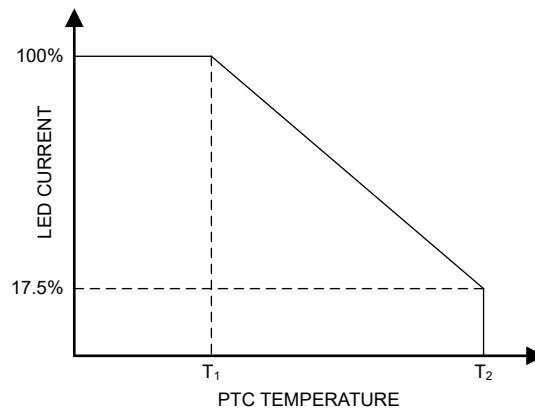
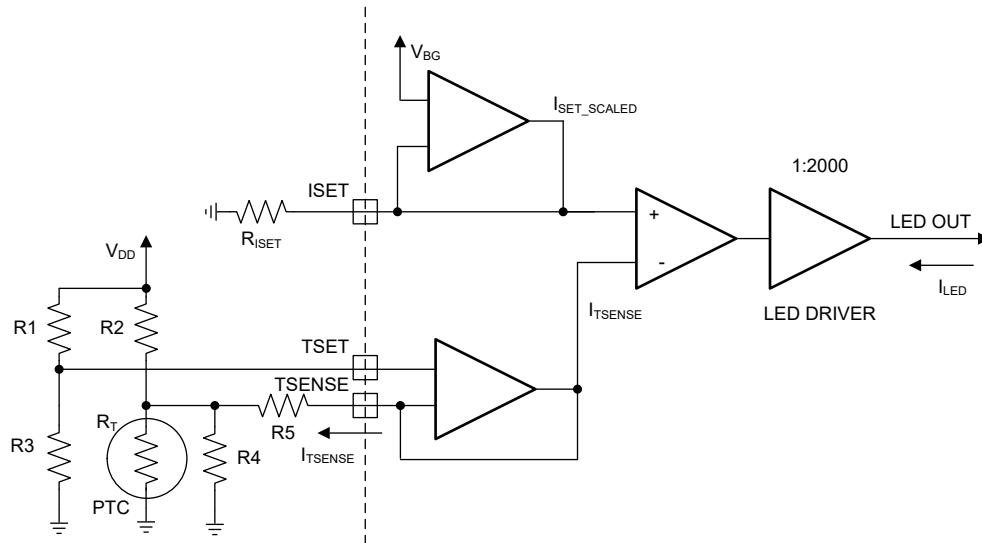


Figure 3-1. Temperature-Based LED Current Dimming Functionality

When external NTC (PTC) is connected, the  $T_{SENSE}$  pin current decreases LED output current. Temperature  $T_1$  and de-rate slope are defined by external resistors as explained below.


**Figure 3-2. TSET Temperature-Based LED Current Dimming Schematic**

Parallel resistance of the PTC sensor  $R_T$  and resistor  $R_4$  is calculated by formula:

$$R_{||} = \frac{R_T \times R_4}{R_T + R_4} \quad (1)$$

$T_{SET}$  voltage can be calculated with [Equation 2](#).

$$V_{TSET} = V_{DD} \times \frac{R_3}{R_1 + R_3} \quad (2)$$

$T_{SENSE}$  pin current is calculated by [Equation 3](#).

$$I_{TSENSE} = \frac{V_{TSET} - V_{DD} \times \frac{R_{||}}{R_{||} + R_2}}{R_{||} + R_5 - \frac{R_{||}^2}{R_{||} + R_2}} \quad (3)$$

where

- $V_{DD}$  is the bias voltage of the resistor group. It is recommended to connect with chip's internal LDO output (pin 2)

$I_{SET}$  pin current designed by  $R_{ISET}$  is:

$$I_{SET\_SCALED} = \frac{V_{BG}}{R_{ISET}} \quad (4)$$

Using:

R1	5kΩ
RT	6.5kΩ
R2	10kΩ
R3	PTC
R4	DNP
R5	1kΩ
$R_{ISET}$	2.4kΩ

The output current thermal foldback profile in [Figure 3-3](#) is achieved:

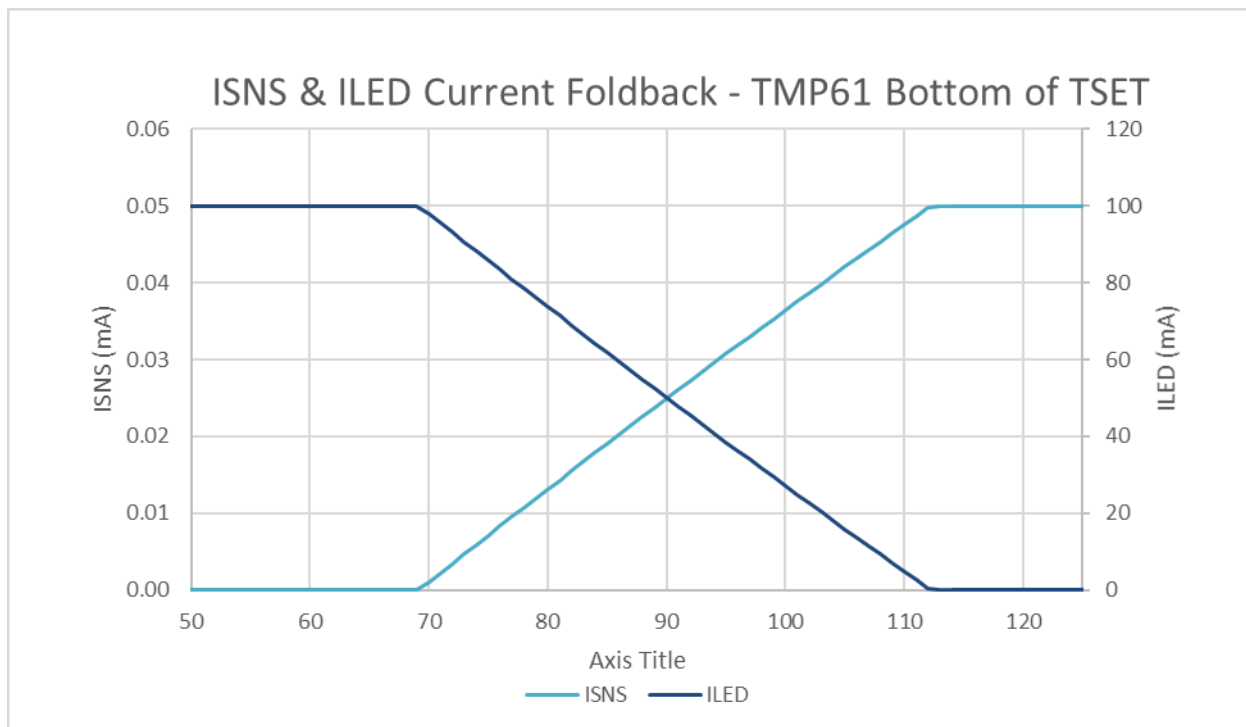


Figure 3-3. Current Foldback Profile with TMP61

#### 4 LP886x-Q1 ISET Implementation

Some LED Drivers don't have a built  $T_{SET}$  pin to allow for easy connection of a thermistor divider for the temperature sensing. The circuit below provides a discrete solution for using a current sensing pin with LED Drivers that don't have the  $T_{SET}$  option. The output current of the LED outputs is controlled with external  $R_{ISET}$  resistor.  $R_{ISET}$  value for the target LED current per channel can be calculated using Equation 5 .

$$I_{LED} = 2000 \times \frac{V_{BG}}{R_{ISET}} \quad (5)$$

where

- $V_{BG} = 1.2 \text{ V}$
- $R_{ISET}$  is current setting resistor,  $k\Omega$
- $I_{LED}$  is output current OUTx pin, mA

For example, if  $R_{ISET}$  is set to  $20k\Omega$ ,  $I_{LED}$  will be 120 mA per channel. (6)

The simulation in Figure 4-1 shows a discrete circuit that performs a derating current from 70°C to 85°C on the LED Low Side Current Limit.

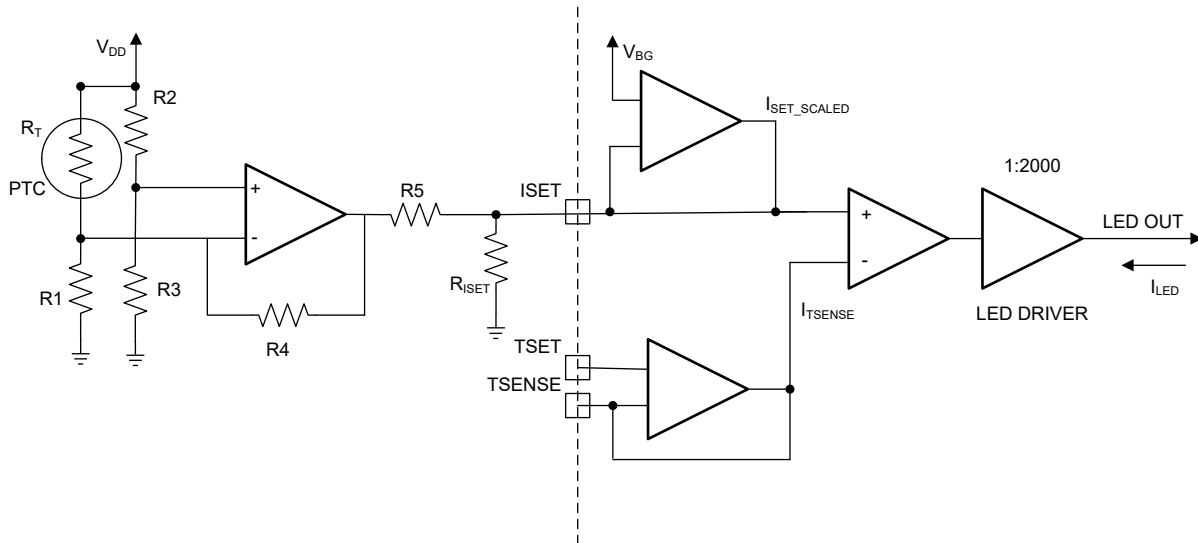


Figure 4-1. ISET Temperature-Based LED Current Dimming Schematic

Simulation results are shown in Figure 4-2:

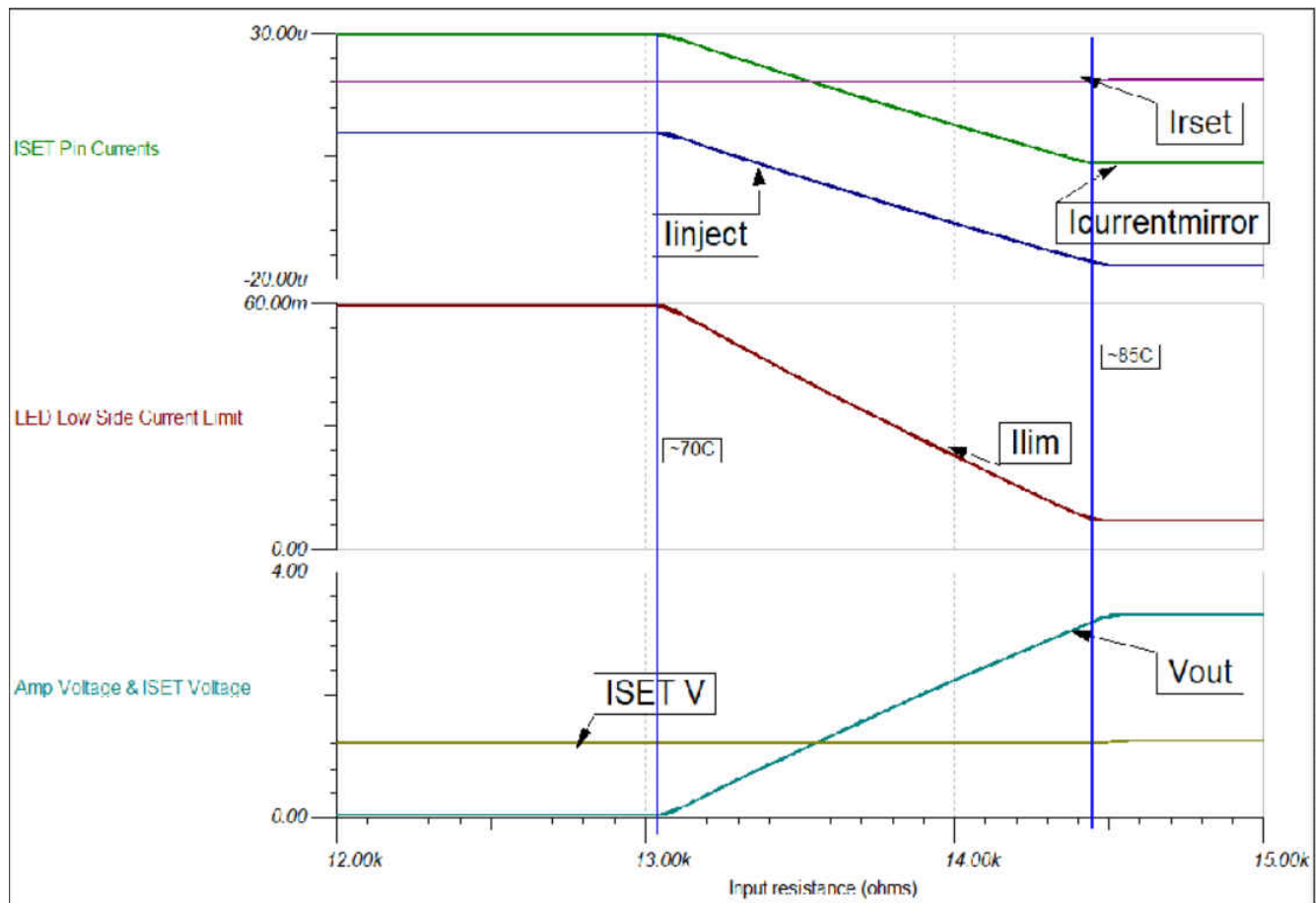


Figure 4-2. Simulation Results

The discrete implementation gives complete control of the output current to the LED Driver. The current derates from 60mA to 15mA from 70 to 85°C. The linearity of the TMP61-Q1 ensures a reliable solution for accurate current output profiles.

## 5 Summary

In conclusion designers can use the TMP61-Q1 linear thermistor with a LED Driver such as the LP886x-Q1 to monitor the LED temperature and provide brightness regulation or to monitor the LED Driver thermals through implementation with either the  $T_{SET}$  or  $I_{SET}$  approach. All in all, this provides a simple yet effective way of protecting LEDs from thermal damage in critical Automotive Lighting applications.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated