

PR426  
TMS320VC550x Design 9

**FEATURES:**

- Provides sequenced core and I/O voltages from an input source between 3.6 and 5.0 V.
- /RESET delay fixed at 65 ms minimum, 130 ms typical.
- All switching regulators for high efficiency operation.
- Small solution size.

**IMPORTANT WEB LINKS:**

- Link to the TI power management home page at <http://power.ti.com> then select the TI DSP Solutions link for more information and other reference designs.
- Link to datasheets at:
  - o <http://focus.ti.com/lit/ds/symlink/tps62300.pdf>
  - o <http://focus.ti.com/lit/ds/symlink/tps3103k33.pdf>
  - o <http://focus.ti.com/lit/ds/symlink/tps76933.pdf>


**THEORY OF OPERATION:**

PR426 consists of a TPS62300 buck regulator to regulate the core voltage and a TPS76933 linear regulator for the I/O voltage.

**CIRCUIT LIMITATIONS AND CAPABILITIES:**

The TPS62300 is capable of supplying 500 mA of core current. The TPS76933 is capable of 100 mA of I/O current.


**POWER UP SEQUENCING:**

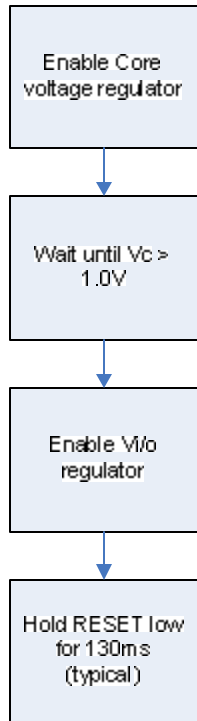

The circuit will start to ramp up the I/O voltage immediately after the core voltage is above about 1.0V. The 1.0V threshold value will vary with the characteristics of the transistor being used in the sequencing circuit. Some systems may require a longer time delay between the core and I/O voltage applications. A capacitor can be added between the base of Q1 and ground to slow the turn on of the I/O voltage. The turn on time is delayed by the RC time constant created by R4 and the added capacitor.

Since the enables of the two IC's are opposite logic polarities, the sequencing circuit (R3, R4 and Q1) of this design forms an inverter. If sequencing is not required, components R3, R4, and Q1 can be removed. However, each IC's enable will need to be tied to its respective logic 'on' state.

#### **WAVEFORMS:**

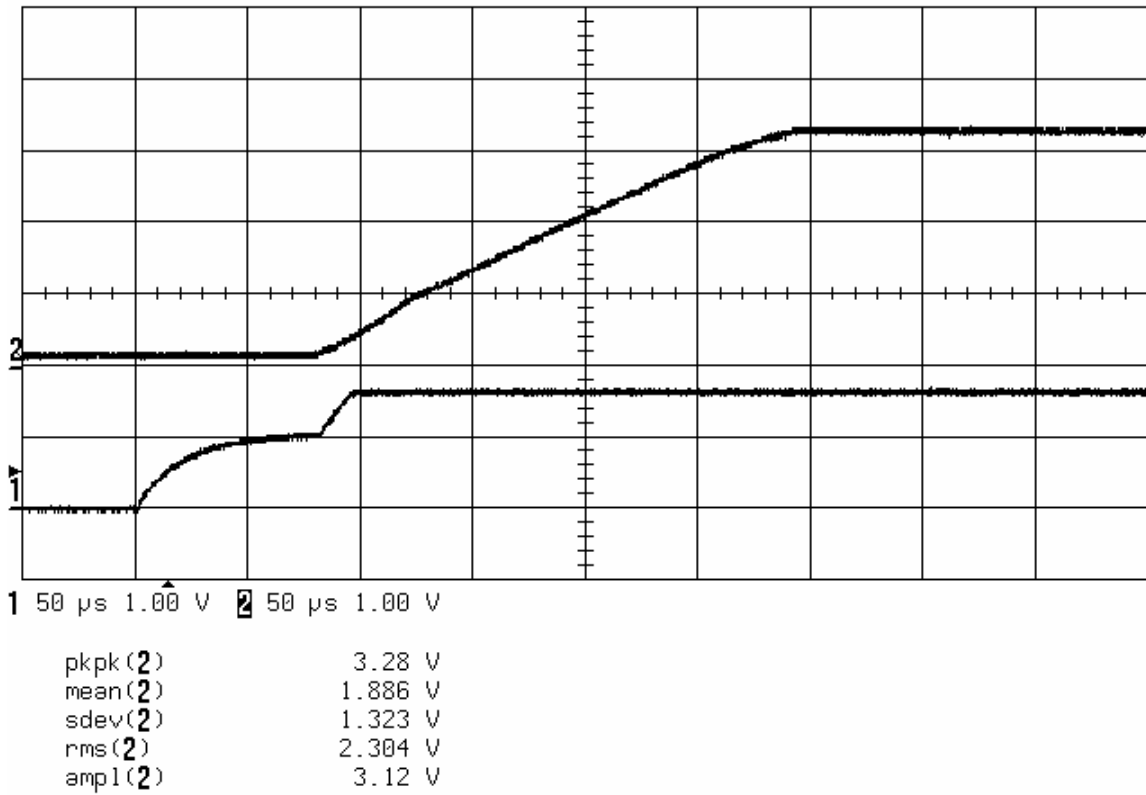

□ NORMAL

Figure 1 - Power up with  $V_{IN} = 3.6\text{ V}$ ,  $V_{core} = 1.6\text{ V @ } 267\text{ mA}$ ,  $V_{i/o} = 3.3\text{ V @ } 70\text{ mA}$

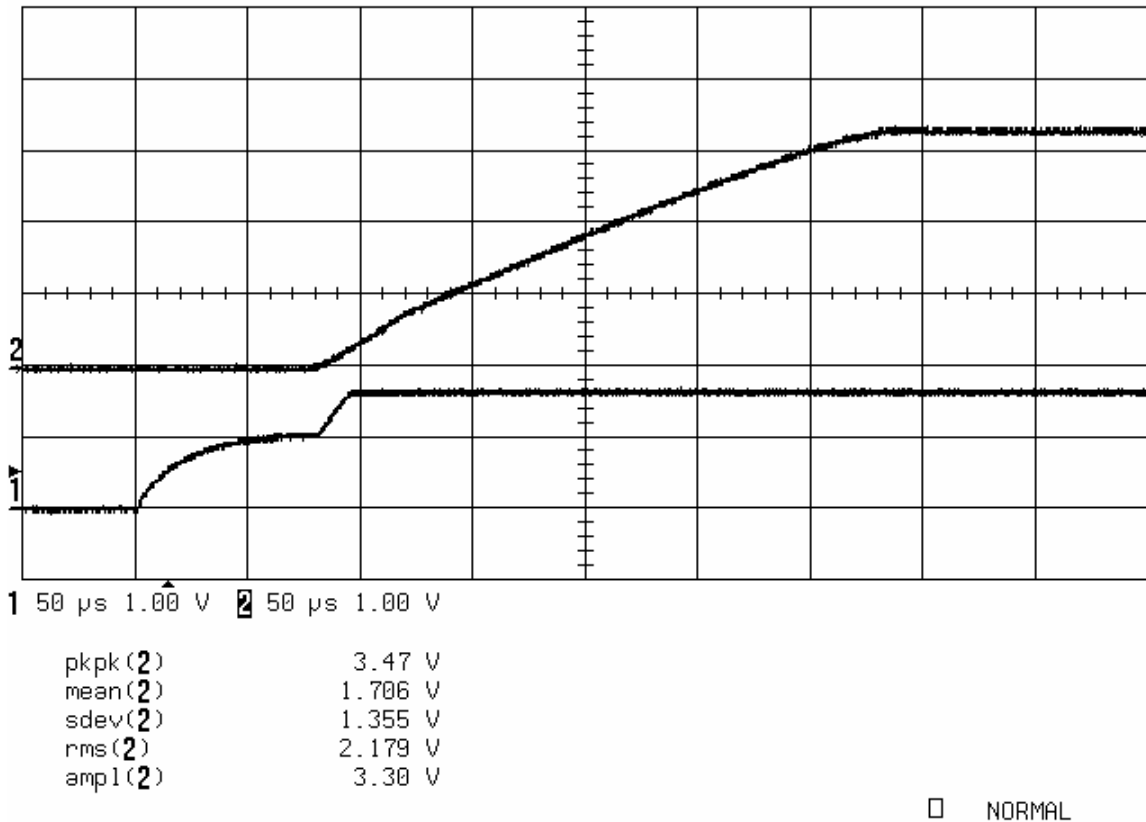



Figure 2 - Power up from Enable when  $V_{IN} = 3.6\text{ V}$ ,  $V_{core}=1.6\text{ V @ }267\text{ mA}$ ,  $V_{i/o} = 3.3\text{ V @ }70\text{ mA}$


**TESTING METHOD:**

The solution was tested on the bench and in an actual DSP circuit. Bench testing included start up into full DSP load, switched load from no load to full DSP load, and power up sequencing. The full DSP load is defined as the current draw a C550x DSP would present to the power supply under worst operating conditions. This full DSP load current is heavily dependent on board layout, firmware configurations, DSP clock speed, and core voltage. For testing purposes, the following values were assumed to be the full DSP load current.

Voltage (V)	Function	Full load current (mA)
1.2	Core	110
1.6	Core	256
3.3	I/O	70

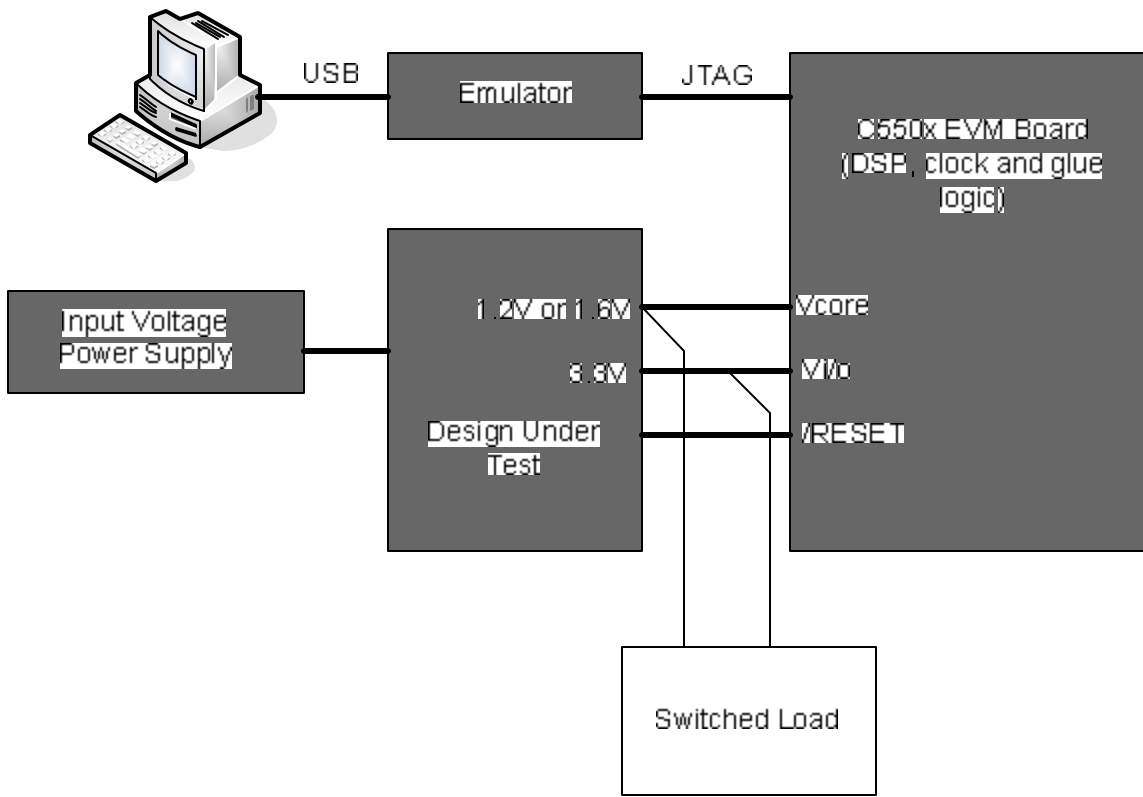The solution was also tested in an active DSP board. The following test setup was used for this testing:



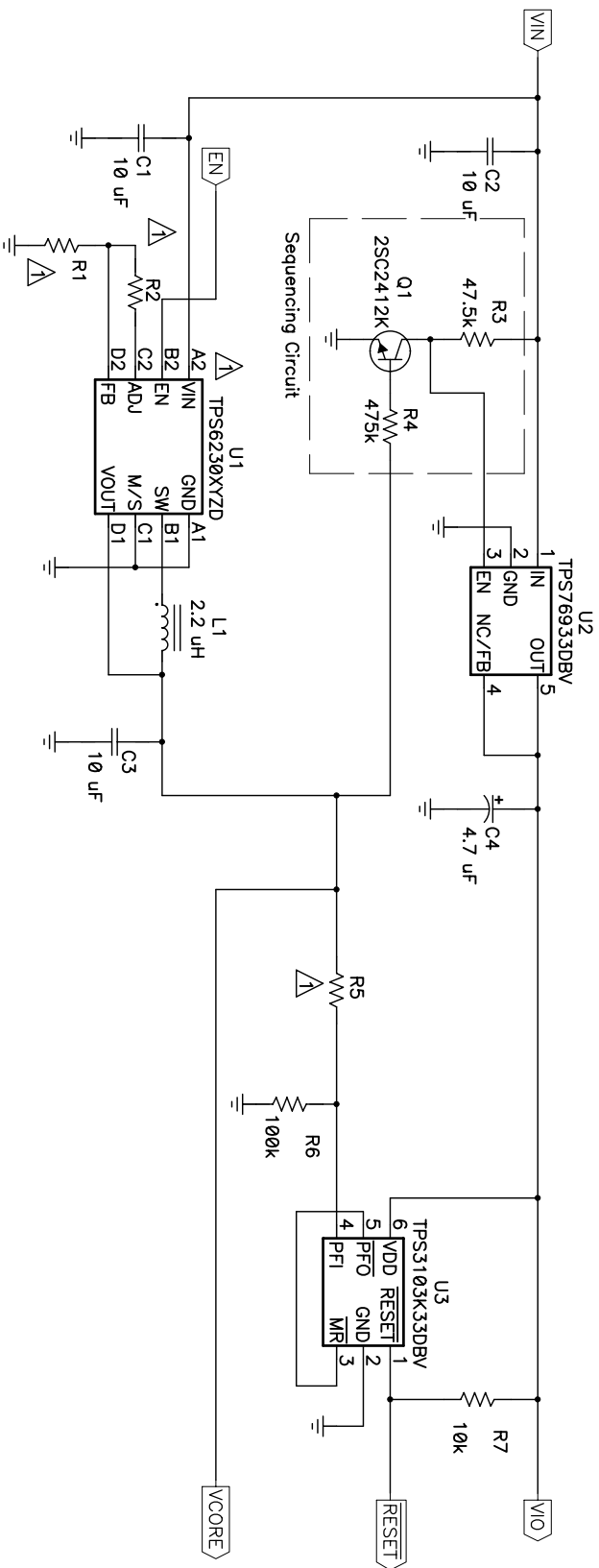

Voltage	U1	R1	R2	R5
1.2V	TPS62300	332k	332k	97.6k
1.6V	TPS62302	Open	Open	162k

Title		C5000 DSP Attach Design 9	
Size		for 3.6 < Vin < 5.0V	
B	Number	PR426	Rev
Date	02/14/05	Drawn by	of
Filename	pr426.sch	Sheet	of

Filename: PR426_bom.xls						
Date: 02/14/2005						
<b>PR426 BOM</b>						
<b>COUNT</b>						
<b>-001</b>	<b>-002</b>	<b>RefDes</b>	<b>Description</b>	<b>Size</b>	<b>Part Number</b>	<b>MFR</b>
2	2	C1, C2	Capacitor, Ceramic, 10-uF, 6.3-V, X5R, 10%	0805	GRM21BR60J106KE01	muRata
1	1	C3	Capacitor, Ceramic, 10-uF, 4-V, X5R, 10%	0603	C1608X5R0G106KT	TDK
1	1	C4	Capacitor, Tantalum, 4.7-uF, 20-V, 0.95-Ohm, 20%	3528(B)	595D475X020B2T	Vishay
1	1	L1	Inductor, SMT, 2.2-uH, 770-mA, 230-milliohms	0805	CB2016T2R2M	Taiyo Yuden
1	1	Q1	Transistor, NPN General Purpose, VCE 50V, VCB 60V, VEB 7V, IC 0.15A	SOT-23	2SC2412K	ROHM
1	0	R1	Resistor, Chip, 332k-Ohms, 1/16-W, 1%	0603	Std	Std
0	0		Resistor, Chip, xx-Ohms, 1/16-W, 1%	0603		
1	0	R2	Resistor, Chip, 332k-Ohms, 1/16-W, 1%	0603	Std	Std
0	0		Resistor, Chip, xx-Ohms, 1/16-W, 1%	0603		
1	1	R3	Resistor, Chip, 47.5k-Ohms, 1/16-W, 1%	0603	Std	Std
1	1	R4	Resistor, Chip, 475k-Ohms, 1/16-W, 1%	0603	Std	Std
1	0	R5	Resistor, Chip, 97.6k-Ohms, 1/16-W, 1%	0603	Std	Std
0	1		Resistor, Chip, 162k-Ohms, 1/16-W, 1%	0603	Std	Std
1	1	R6	Resistor, Chip, 100k-Ohms, 1/16-W, 1%	0603	Std	Std
1	1	R7	Resistor, Chip, 10k-Ohms, 1/16-W, 1%	0603	Std	Std
1	0	U1	IC, 3MHz Synchronous Step-Down Converter, 400mA	CSP-8	TPS62300YDZ	TI
0	1		IC, 3MHz Synchronous Step-Down Converter, 400mA	CSP-8	TPS62302YDZ	TI
1	1	U2	IC, Micro-Power 150 mA LDO Regulator	SOT23-5	TPS76933DBV	TI
1	1	U3	IC, Ultra Low Current/Supply, Voltage Supervisor	SOT23-6	TPS3103K33DBV	TI

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

<b>Products</b>		<b>Applications</b>	
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>	Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>	Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>	Broadband	<a href="http://www.ti.com/broadband">www.ti.com/broadband</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>	Digital Control	<a href="http://www.ti.com/digitalcontrol">www.ti.com/digitalcontrol</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>	Military	<a href="http://www.ti.com/military">www.ti.com/military</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>	Optical Networking	<a href="http://www.ti.com/opticalnetwork">www.ti.com/opticalnetwork</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>	Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
		Telephony	<a href="http://www.ti.com/telephony">www.ti.com/telephony</a>
		Video & Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
		Wireless	<a href="http://www.ti.com/wireless">www.ti.com/wireless</a>

Mailing Address: Texas Instruments  
Post Office Box 655303 Dallas, Texas 75265