

PR450
Virtex™-4 Design 6
TPS75003 Power Management Solution Providing Up to 3A from $V_{IN} = 5\text{ V}$

FEATURES:

- Recommended only for all SX, FX100 and smaller, and LX80 and smaller Virtex-4 FPGAs with no more than 300 mA of $I_{CCAUXMIN}$ power on currents
- Flexible dual buck controller design allows for optimization of the solution for output power, size, power dissipation and/or cost

IMPORTANT WEB LINKS:

- Link to the TI home page for Xilinx FPGA power management solutions at <http://www.ti.com/xilinuxfpga> for more information and other reference designs.
- Link to the datasheets at <http://focus.ti.com/lit/ds/symlink/TPS75003.pdf>
- Link to the TPS75003 design spreadsheet at <http://www-s.ti.com/sc/psheets/sbvc002a/sbvc002a.zip> to assist further optimization/customization of design.


IMPLEMENTATION NOTES:

- **Thermal Considerations:** Diode D2 in the SMC package has limited power dissipation capabilities. So, this design is not recommended for ambient temperatures above 55 C without additional airflow.
- **Sequencing:** Per Xilinx DS302 v1.3, Virtex-4 power rails can be turned on in any sequence, though V_{CCAUX} must power on before or with V_{CCO} for the minimum power-on current specifications shown in the Xilinx datasheet to apply. For this reason and to reduce the risk that large currents for charging bulk capacitance forces the point of load converter into current limit and/or pulls down the input supply at power up, the following recommended design techniques were used:
 - o Integrated soft-start configured with a capacitor to provide a current controlled, monotonic rise time for V_{CCINT} , V_{CCAUX} and V_{CCO}
 - o Starting V_{CCINT} and V_{CCAUX} simultaneously then starting V_{CCO} using the ENABLE pins of the TPS75003
- **Additional Capacitance:** The TPS75003 buck controller outputs use a current controlled soft start, thus the soft start timing is dependent on the startup load current. If the amount of bulk capacitance changes from the values in the table below, the startup load current may increase and so the soft-start timing may need to change to ensure monotonic startup of the voltage rails.

Capacitor (uF)	V _{CCO} QTY	V _{CCAUX} QTY	V _{CCINT} QTY
0.047	51	14	38
0.22	39	7	19
0.68	15	4	10
2.2	15	3	7
330 (0.15 Ω ESR)	15	1	3

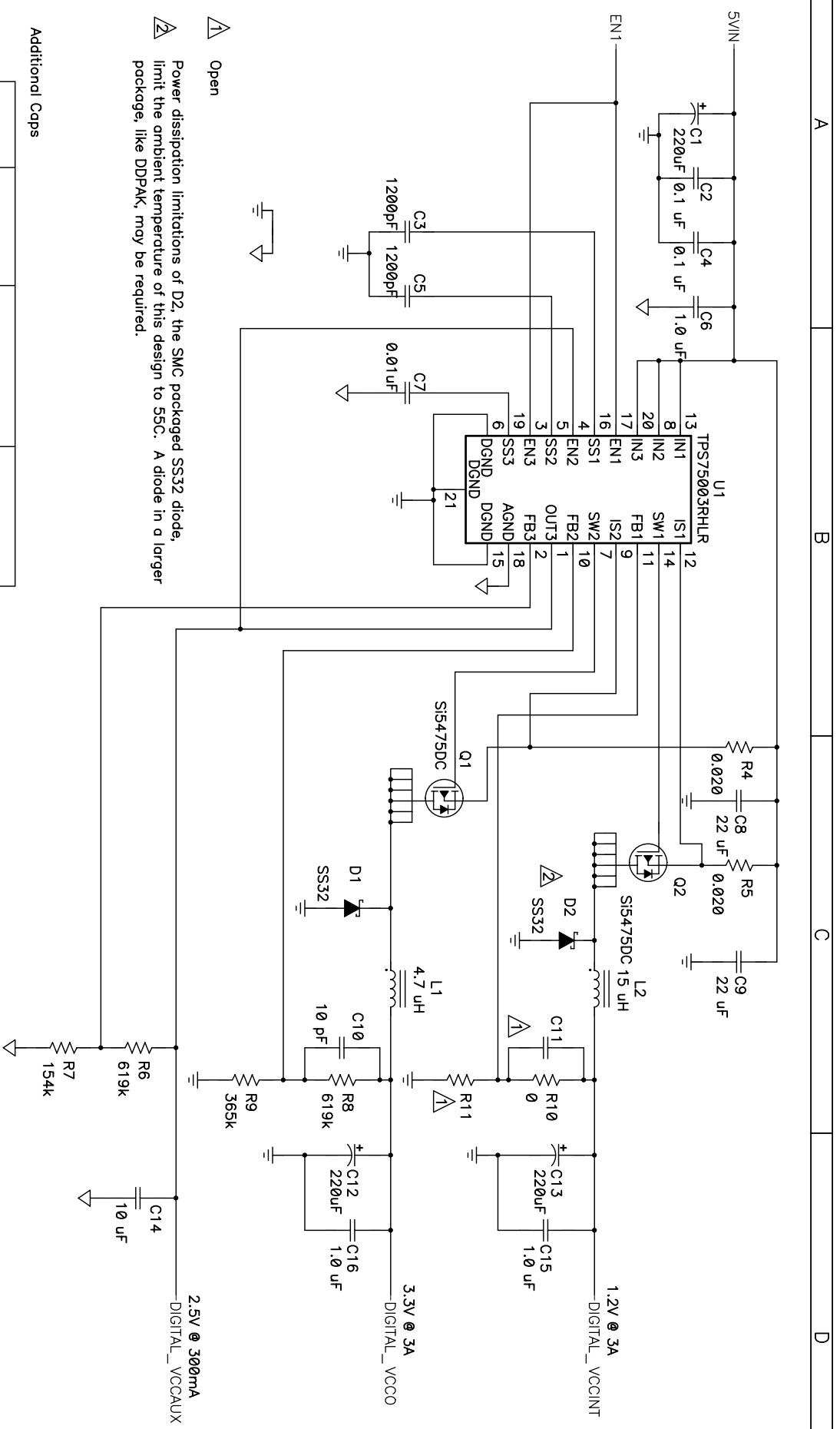QUESTIONS?

- Send an email to <mailto:fpgasupport@list.ti.com>



⚠ Open

⚠ Power dissipation limitations of D2, the SMC packaged SS32 diode, limit the ambient temperature of this design to 55C. A diode in a larger package, like DDP4K, may be required.

Additional Caps

VALUE	DIGITAL_VCCO QTY	DIGITAL_VCCAUX QTY	DIGITAL_VCCINT QTY
0.047 uF	51	14	38
0.22 uF	39	7	19
0.68 uF	15	4	10
2.2 uF	15	3	7
330 uF	15	1	3

Title Vrtex-4 TPS75003 Based for Vin=5V			
Size B	Number PR450	Rev	
Date 2/21/05	Drawn by		of
Filename pr450.sch	Sheet		of

Filename: PR450_bom.xls					
Date: 02/22/2005					
PR450 BOM					
COUNT	RefDes	Description	Size	Part Number	MFR
1	C1	Capacitor, POSCAP, 220-uF, 6.3-V, 40-milliohm, 20%	7343(D)	6TPB220ML	Sanyo
1	C10	Capacitor, Ceramic, 10-pF, 50-V, C0G, 5%	0603	C1608C0G1H100D	TDK
0	C11	Capacitor, Ceramic, xx-uF, xx-V	0603		
2	C12, C13	Capacitor, POSCAP, 220-uF, 4-V, 55-milliohm, 20%	7343(D)	4TPB220ML	Sanyo
1	C14	Capacitor, Ceramic, 10-uF, 10-V, X5R, 20%	0805	C2012X5R1A106MT	TDK
2	C2, C4	Capacitor, Ceramic, 0.1-uF, 16-V, X7R, 10%	0603	C1608X7R1C104K	TDK
2	C3, C5	Capacitor, Ceramic, 1200-pF, 50-V, X7R, 10%	0603	C1608X7R1H122K	TDK
3	C6, C15, C16	Capacitor, Ceramic, 1.0-uF, 6.3-V, X5R, 10%	0603	C1608X5R0J105K	TDK
1	C7	Capacitor, Ceramic, 0.01-uF, 50-V, X7R, 10%	0603	C1608X7R1H103K	TDK
2	C8, C9	Capacitor, Ceramic, 22-uF, 6.3-V, X5R, 20%	0805	C2012X5R0J226MT	TDK
2	D1, D2	Diode, Schottky, 3.0-A, 20-V	SMC	SS32	Vishay
1	L1	Inductor, SMT, 4.7-uH, 4.6-A, 2.9-milliohm	0.327 X 0.327	CDRH8D38-4R7	Sumida
1	L2	Inductor, SMT, 15-uH, 4.5-A, 27-milliohm	0.472 sq	CDRH127-150	Sumida
2	Q1, Q2	MOSFET, P-ch, -12V,-7.6-A, 31-milliohm	1206-8	Si5475DC	Vishay
1	R10	Resistor, Chip, 0-Ohms, 1/16W, 5%	0603	Std	Std
0	R11	Resistor, Chip, xx-Ohms, 1/16-W, 1%	0603		
2	R4, R5	Resistor, Chip, 0.020-Ohms, ¼ W, 1%	1210	Std	Std
2	R6, R8	Resistor, Chip, 619k-Ohms, 1/16-W, 1%	0603	Std	Std
1	R7	Resistor, Chip, 154k-Ohms, 1/16-W, 1%	0603	Std	Std
1	R9	Resistor, Chip, 365k-Ohms, 1/16-W, 1%	0603	Std	Std
1	U1	IC, Triple Channel DC/DC Converter	QFN-20	TPS75003RHRLR	TI

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
		Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265