

ESD Protection for HDMI Applications

Matthew Xiong



Since its creation in 2002, High-Definition Multimedia Interface (HDMI) has remained one of the most popular interfaces for transmitting video and audio data. With each HDMI standard update, improvements in process technology have allowed manufacturers to increase data bandwidth and add additional features in smaller and smaller chipsets. However, with this decrease in size, HDMI components have become more sensitive to transient voltages such as electrostatic discharge. This has created a need for ESD protection that clamp at very low voltages without compromising high speed signal integrity.

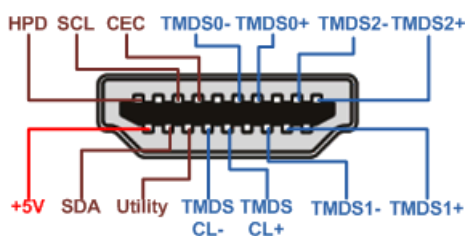


Figure 1. Pinout of the HDMI Receptacle

In the HDMI connector (figure 1), there are four differential pairs of transmission minimized digital signaling (TMDS) channels. For HDMI 2.0, three TMDS pairs (TMDS0, TMDS1 and TMDS2) are responsible for transferring millions of pixels of data per second while the TMDS CL pair provides the clocking signal to synchronize this information.

Apart from the four TMDS pairs, the HDMI connector also has six other channels: The hot plug detect (HPD) channel senses when a connection is established, the consumer electronic control (CEC) channel allows users to control devices through HDMI, the utility channel can be used for HDMI Ethernet or an audio return channel, the SDA and SCL channels provide I2C control, and the final channel provides 5V of power.

To protect against ESD failure, a 5V [working voltage](#), 6-channel TVS diode such as the [TPD6E05U06](#) can be placed on the non-TMDS channels by the HDMI connector (5V power, SDA, SCL, HPD, CEC and utility). 5V working voltage, 1-channel TVS diodes ([TPD1E05U06](#)) can also be used here for layout flexibility. Since these non-TMDS channels do not pass high speed data, minimizing the [capacitance](#) of the diodes is usually not a concern.

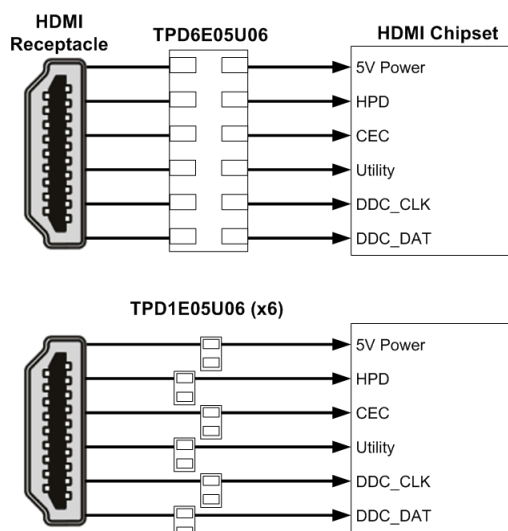


Figure 2. 6-channel TVS diode array (top) vs. 1-channel TVS diodes (bottom) for non-TMDS protection

On the other hand, the TMDS channels pass differential data that can reach 18Gbps (6Gbps for each pair) for HDMI 2.0, with a maximum single-ended operating voltage of 3.3V on each differential line. As a result, the ESD protection diodes that are placed on these high speed traces must have low enough capacitance to maintain signal integrity and meet the HDMI compliance standard.

Due to the sensitive nature of the TMDS I/O pins, [clamping voltage](#) must also be minimized for TMDS ESD protection. This is accomplished by selecting an ESD diode that has an ultra low dynamic resistance (R_{DYN}) so when an ESD strike is present, the diode provides a low impedance path to steer current away from sensitive circuitry downstream.

However, ESD R_{DYN} and capacitance have an inverse relationship. Increasing the diode junction area would decrease the R_{DYN} but increase the diode capacitance which may degrade signal integrity. As a result, selecting TVS diodes that protect the TMDS channels without compromising the data transfer is challenging. In spite of this, the [ESD224](#) is a 4-channel ESD protection device that is able to clamp $\pm 8kV$ IEC ESD events to sufficient levels while maintaining an ultra-low capacitance by employing TI's proprietary ESD

process technology. Since there are four pairs of TMDS channels, two ESD224 protection diodes would provide the necessary protection on TMDS traces while passing the signal integrity eye diagram mask test (Figure 3).

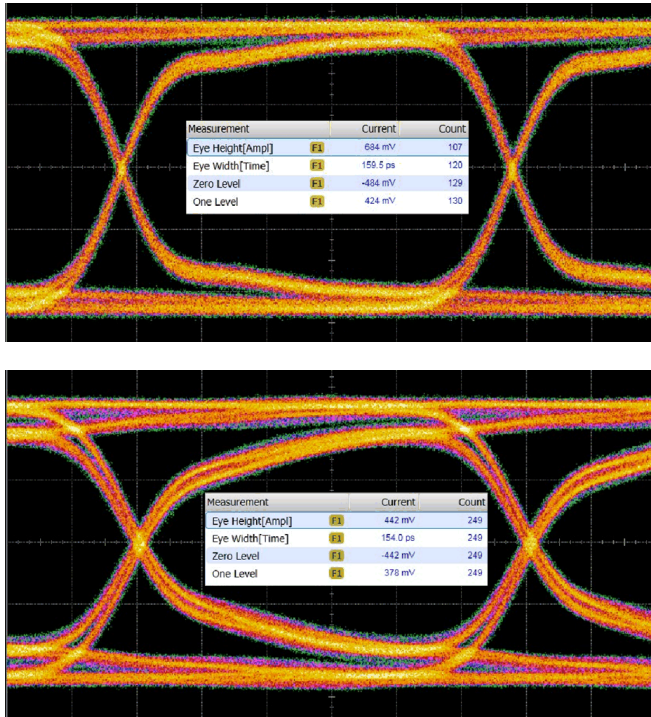


Figure 3. 6Gbps HDMI 2.0 Eye Diagram Without (top) and With (bottom) ESD224 Protection

The ESD224 is also able to provide the necessary ESD clamping protection for sensitive HDMI 2.0 redrivers, retimers and chipsets. For example, the BCM7250 is a Broadcom HDMI 2.0 SoC that fails at a low transient voltages: 9.15V and -5.71V. In Figure 4, a 100ns transmission line pulse (TLP) is used to determine the ESD failure voltage since 100ns is approximately the length of an IEC ESD pulse.

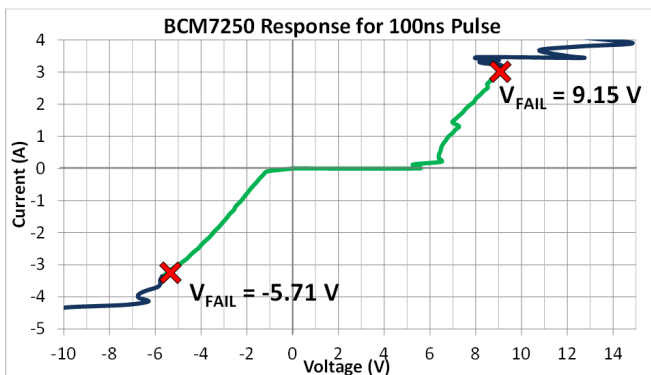


Figure 4. BCM7250 Fails at 9.15V and -5.71V During ESD Events

To protect sensitive HDMI 2.0 SoCs such as the BCM7250 against ESD strikes, the TVS diode must ensure that the positive clamping voltage does not exceed 9.15V and the negative clamping voltage does not exceed -5.71V. Figure 5 shows that the ESD224 provides this protection by clamping an 8kV IEC ESD strike to 8.1V and a -8kV IEC ESD strike to -5V.

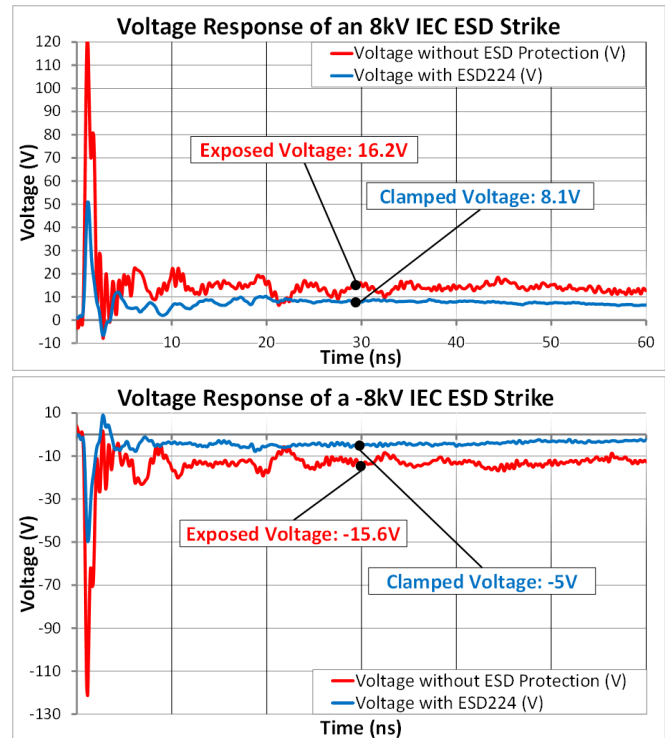


Figure 5. ESD224 Clamps +8kV ESD Voltage to 8.1V and -8kV ESD to -5V

For a complete HDMI 2.0 solution, 2x ESD224 can be used to protect the TMDS channels and 6x TPD1E05U06 can be used to protect the other channels. If the ultra low clamping performance of the ESD224 is not required, the TPD4E02B04 can be used to protect the TMDS channels.

Table 1. Alternative Device Recommendations

Device	Optimized Parameters	Performance Trade-Off
TPD4E02B04	0.25pF capacitance, flow through routing	Higher clamping voltage
TPD4E05U06	5V working voltage, flow through routing	Higher clamping voltage
ESD204	30kV/30kV IEC rating, 5.5A surge protection, flow through routing	Higher capacitance

Related Documentation

- [System Level ESD Selection Guide](#)
- [ESD224 HDMI 2.0 Compliance AppNote](#)
- [ESD Essentials Video Series](#)

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2018, Texas Instruments Incorporated