

TI-RSLK

Texas Instruments Robotics System Learning Kit



Module 8

Activity: Interfacing Input and Output




Activity: Interfacing input and output devices using LEDs and Switches

Question 1

You are given a double-pole switch that has three pins, labeled 1, 2, and 3. If the switch is not pressed, pins 1 and 2 are connected (0Ω resistance) and pins 2 and 3 are not connected (infinite resistance). If the switch is pressed, pins 2 and 3 are connected (0Ω resistance) and pins 1 and 2 are not connected (infinite resistance). Pins 1 and 3 are never connected (it is a break-before-make switch). Interface this switch to the microcontroller, such that input pin is high (3.3V) if the switch is pressed and input pin is low (0V) if the switch is not pressed.

You do not need to debounce the switch. Label all chip numbers and resistor values. No software is required. The best solution will not require any resistors.

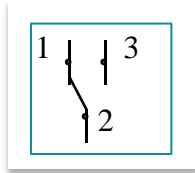

Question 2

Interface a positive logic switch to P1.5 without an external resistor. Write code to configure Port 1 bit 5 as needed. Write code that waits for the switch to be touched, and then released.

- Part a) Develop a solution assuming the switch does not bounce.
- Part b) Develop a solution assuming there is 2ms of switch bounce

Question 3

Interface a negative logic switch to P2.6 without an external resistor. Write code to configure Port 2 bit 6 as needed. Write code that waits for the switch to be touched, and then released.

- Part a) Develop a solution assuming the switch does not bounce.
- Part b) Develop a solution assuming there is 2ms of switch bounce.

Question 4

Interface an LED that requires 1 mA at 2.5 V. A digital output high on the microcontroller turns on the LED. Assume $V_{OH} = 3.2V$. I.e., this interface is positive logic.

Question 5

Interface an LED that requires 2 mA at 2.0 V. A digital output low on the microcontroller turns on the LED. I.e., this interface is negative logic. Because of the direct connection to the microcontroller, you should use 3.3V to power the LED (and not 5V). Assume $V_{OL} = 0.3V$.

Question 6

Interface an LED that requires 15 mA at 2.5 V. Use a LM7405 driver and a current limiting resistor. A digital output high on the microcontroller turns on the LED as this interface is positive logic. The LM7405 output voltage V_{OL} is 0.5V. At this current you can safely use either 3.3V or 5V to power the LED.

ti.com/rslk



IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2019, Texas Instruments Incorporated