

MSP430 Advanced Technical Conference 2006



Hands-On: Using MSP430 Embedded Op Amps

Steve Underwood
MSP430 FAE Asia
Texas Instruments

An outline of this session

- **Provides hands on experience of setting up the MSP430's built in op-amp modules**
- **Look at the construction of the op-amp module, and the topologies it can offer**
 - Inverting mode, non inverting mode etc
- **Experiment with the different op-amp topologies**
 - A software signal generator is provided, to simulate the amplifiers
 - PC oscilloscope program is provided to observe the output

Current devices with op-amps

- **FG43x**
 - Three op-amps
 - Rail-to-rail input capability
- **FG461x**
 - Three op-amps
 - Rail-to-rail input capability
- **F22x4**
 - Two op-amps

Key op-amp features


- **Three independent op-amps on-chip**
- **Selectable GBW product**
 - 500kHz, 1.4MHz, or 2.2MHz
 - The 500kHz GBW mode takes ~50uA
- **Class AB output for mA range drive**
- **Integrated charge pump for rail-to-rail input range & superior offset behavior (FG only)**
- **User-configurable feedback and interconnect**
 - Most designs need no external passive components
 - Internal connections to the ADC and DAC
 - Saves pins

Amplifier performance


Amplifier Speed Setting	slow	medium	fast
Technology	0.35 um CMOS		
min. Supply Voltage	2.2 V		
DC gain	> 100 dB		
GBW @ 50 pF load	500 kHz	1.4 MHz	2.2 MHz
Phase margin @ 50 pF load	>= 60 °		
Slew Rate	0.5 V/us	1.2 V/us	2 V/us
Current consumption @ Charge Pump off	42 µA	110 µA	190 µA
Current consumption @ Charge Pump on	90 µA	200 µA	320 µA
CMRR	~ 80 dB		
PSRR	~ 80 dB		
Offset voltage	+/- 1 mV		
Input voltage noise (white noise) [nV/sqrt(Hz)]	60	35	28
Input voltage noise @ 1 kHz [nV/sqrt(Hz)]	75	55	45

Internal structure of each op-amp

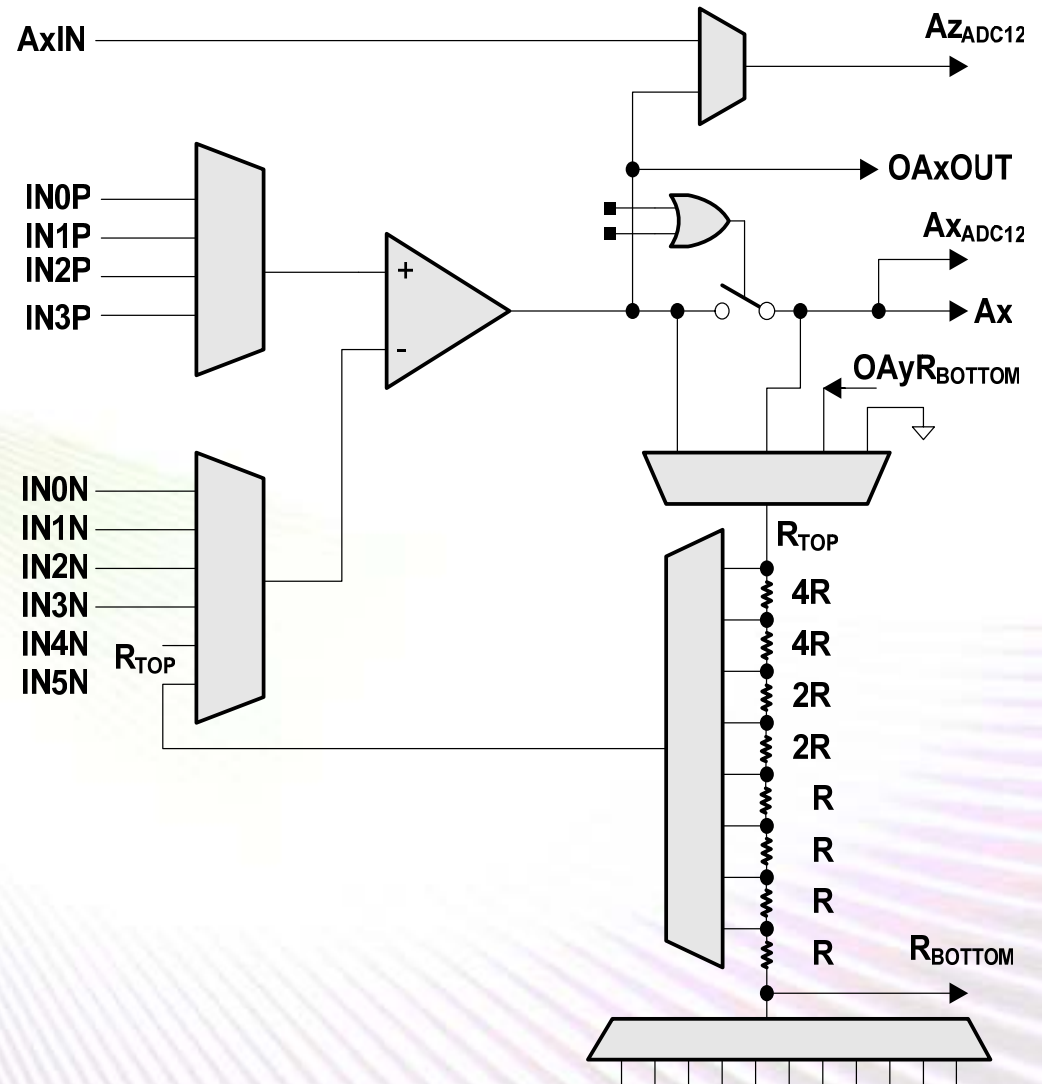- Flexible feedback network
- Internal R ladder
- Internally chainable
- Internal ADC and DAC connections




General purpose op-amp

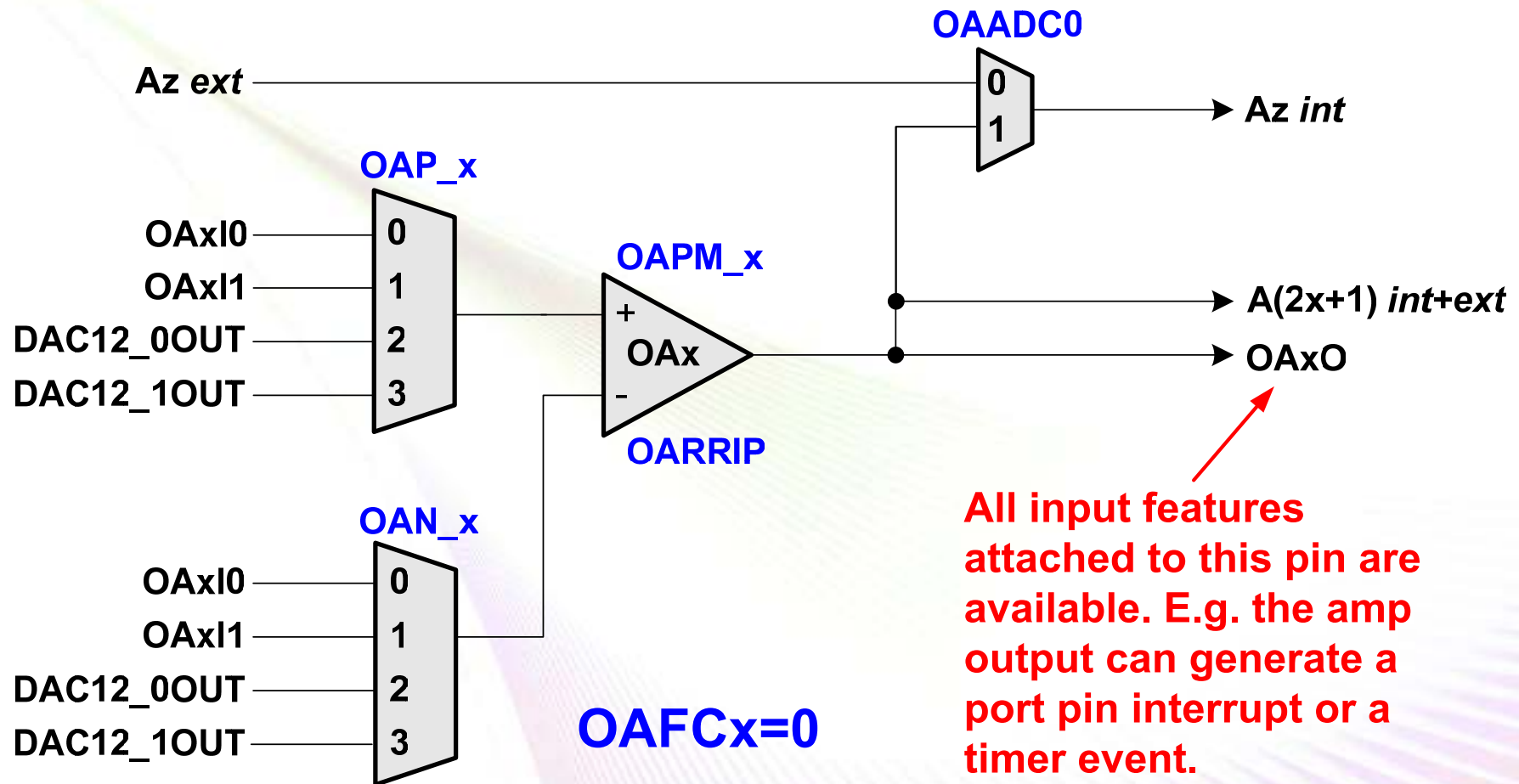

```
OA0CTL1 | = OAFc_0;
OA0CTL0 | = OAP_1 | OAN_0 | OAPM_3;
```

Test setup

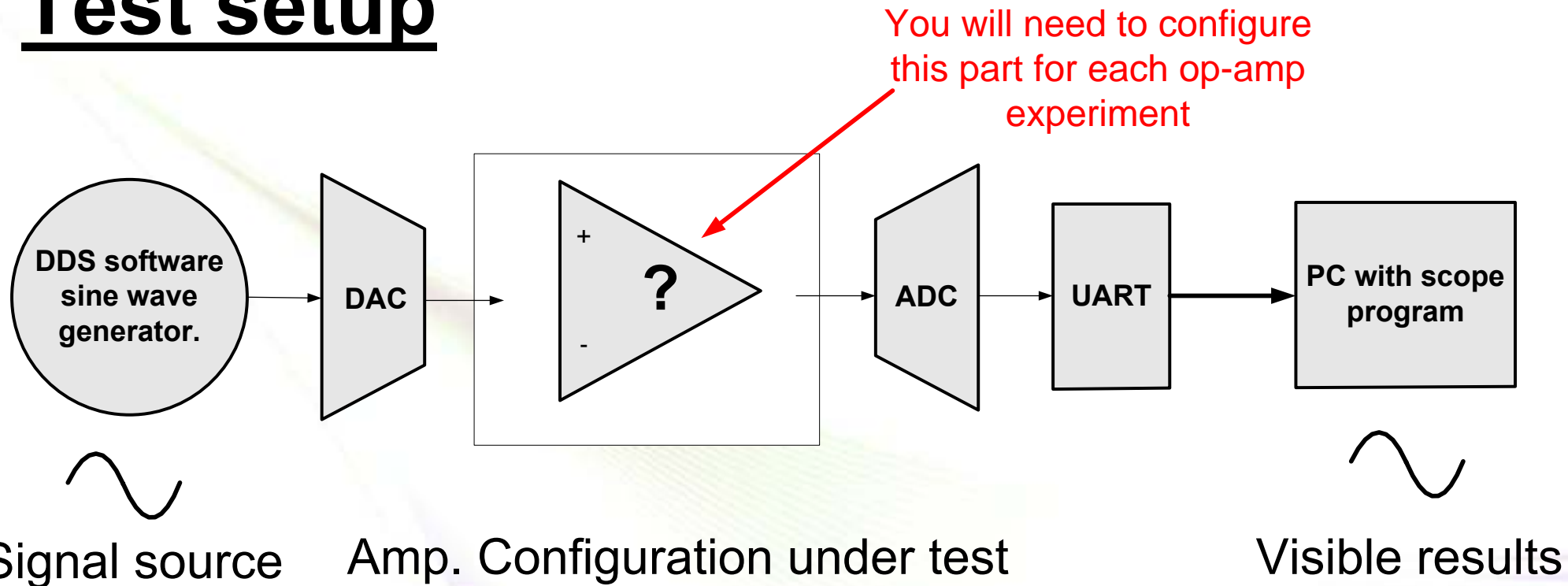

- **DDS sine wave generator software**
- **DAC12 > amplifier under test > ADC12**
- **Through isolated serial interface to PC**
- **Simple PC “scope” program to display output**

Let's get started.....

- Find the project “op_amp_lab”, open it, build it, and load it into the MSP430FG4619 on your board.
- Connect the board's RS232C port on your PC.
- Find the program “scope.exe”, and run it on your PC.
 - If you are using COM1, just click and run the program
 - If you are using another COM port (e.g. a USB→serial interface) find the port number, and use the Windows “run” option to run “scope <com port name>”

....Let's get started....

- You should now have a sine wave on your PC, directly from the signal generator
- Comment out the following line with “//”


```
UCA0TXBUF = DAC12_0DAT >> 4;
```

- Uncomment the following line

```
//UCA0TXBUF = x;
```


- You should now be seeing the output of the ADC12 – there's no signal right now.

Amplifying the microphone

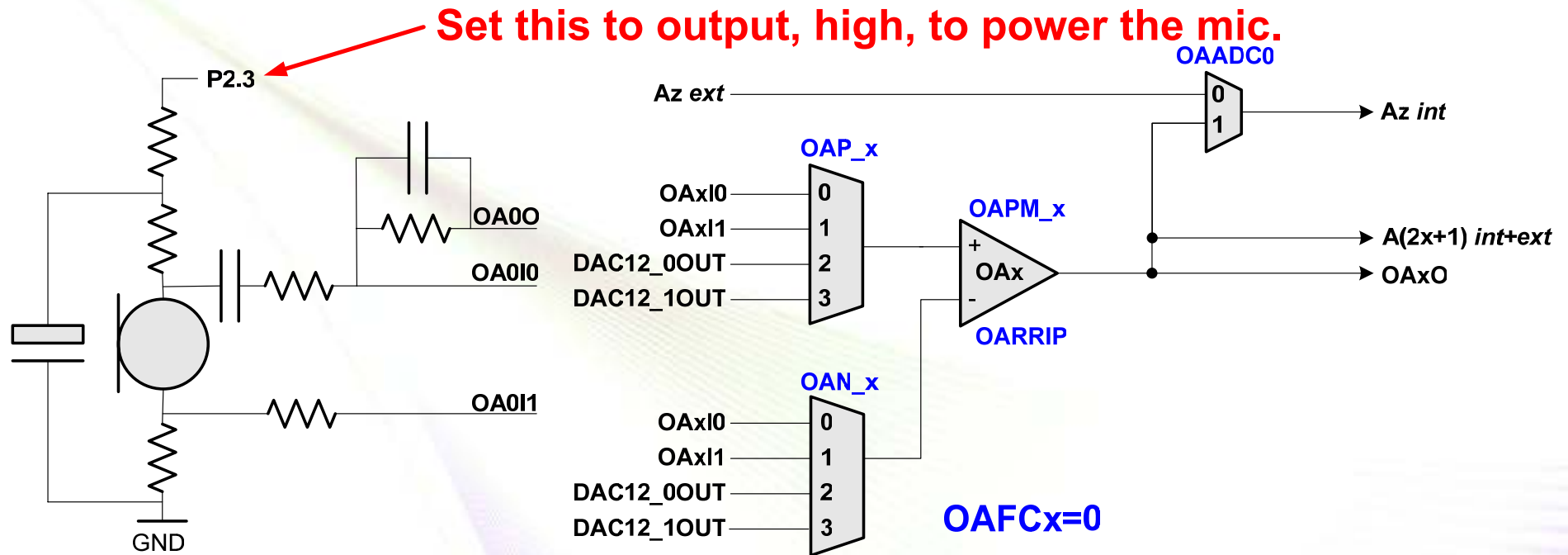

```
OA0CTL1 | = OAFC_0;
OA0CTL0 | = OAP_1 | OAN_0 | OAPM_3;
```

Unity gain, voltage follower

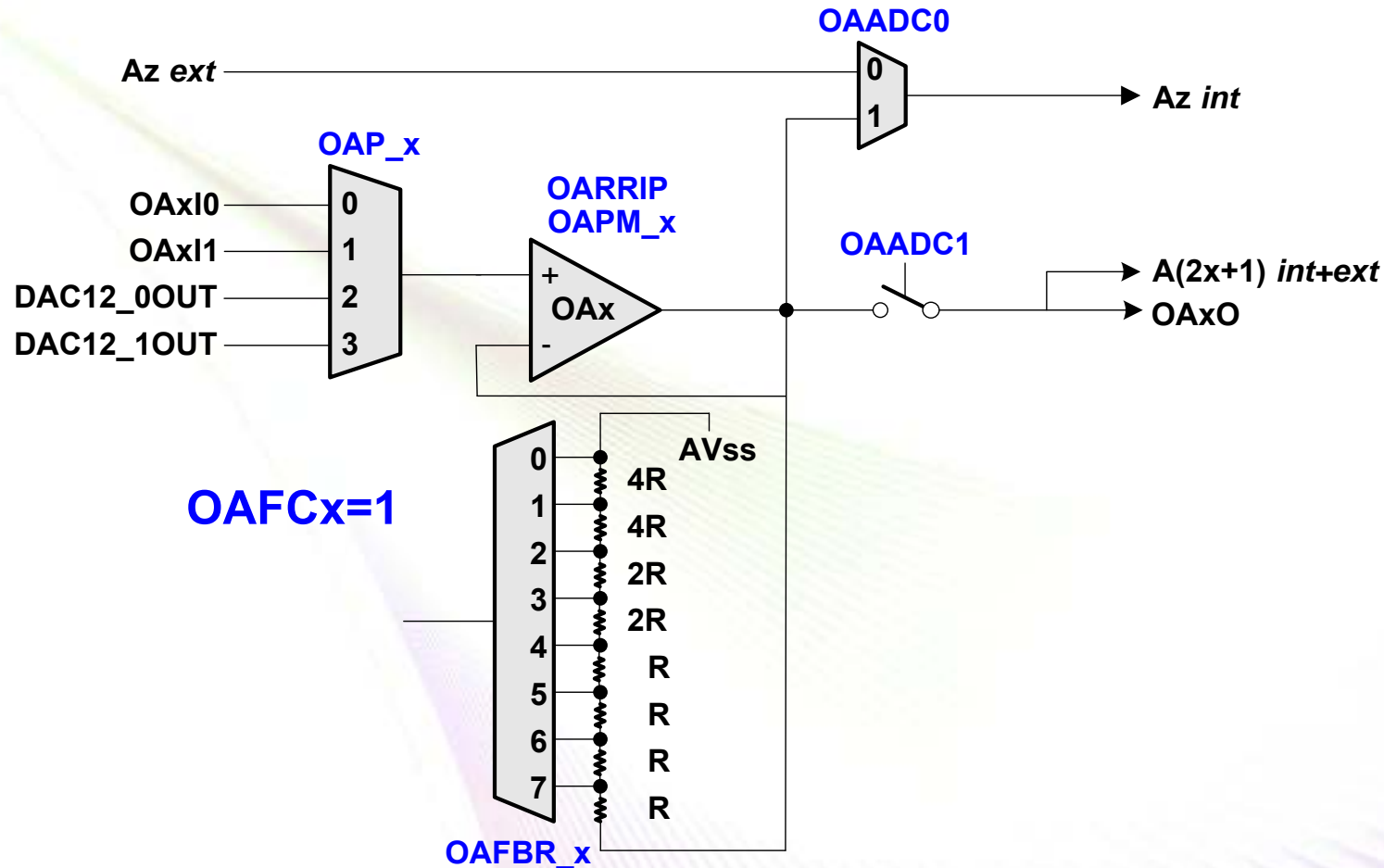


```
/* High performance buffering of DAC12_0 to the output */
```

```
OA0CTL1 |= OAF_C_1;
```


```
OA0CTL0 |= OAP_2 | OAPM_3 | OAADC1;
```

Comparator

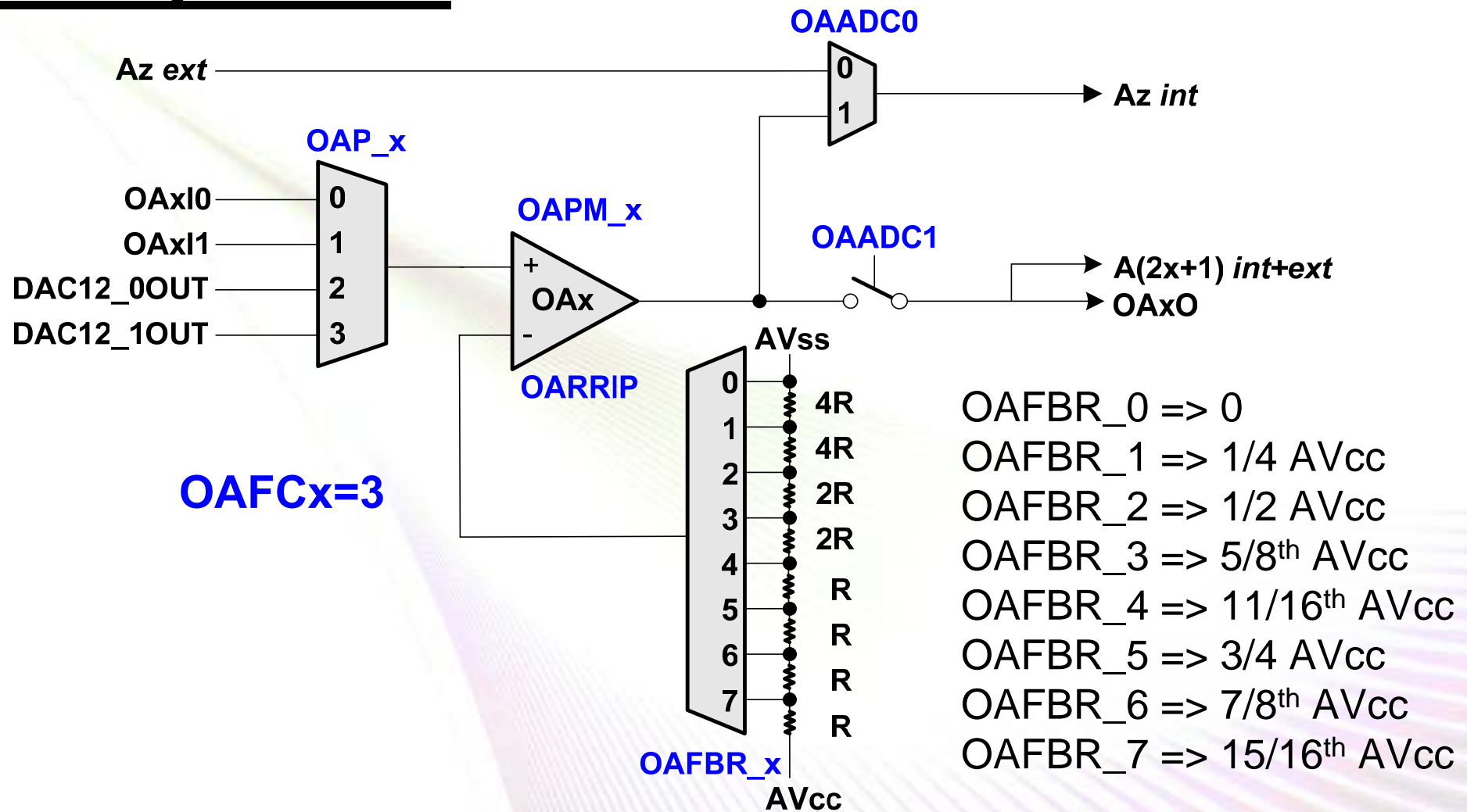


```
OA0CTL1 | = OAFc_3 | OAFBR_2;
OA0CTL0 | = OAP_2 | OAPM_3 | OAADC1;
```

Non-inverting PGA

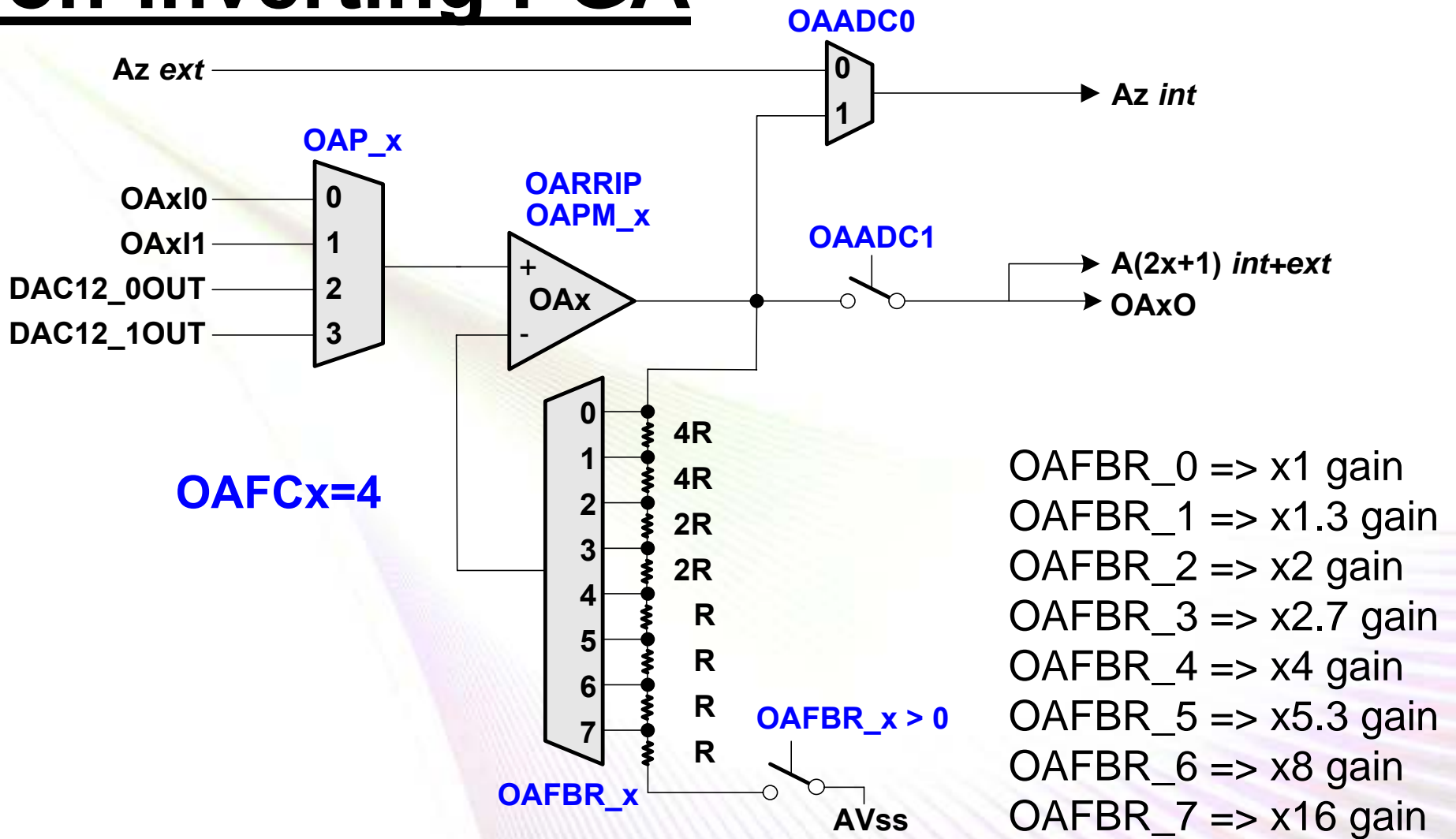

```
OA0CTL1 | = OAFB_4 | OAFBR_2;
OA0CTL0 | = OAP_2 | OAPM_3 | OAADC1;
```


Inverting PGA

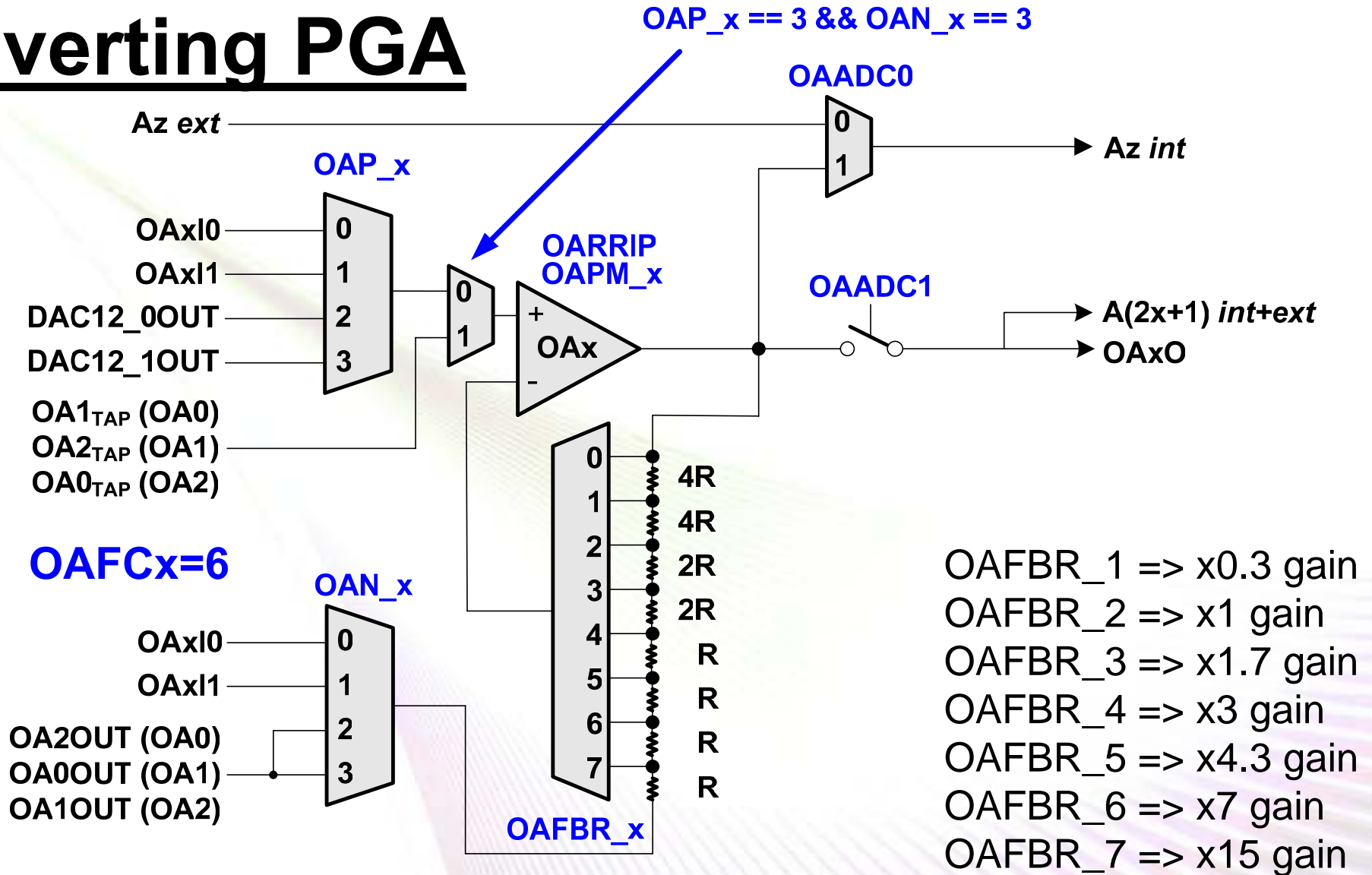

```


OA0CTL1 | = OAF6 | OAFBR7;
OA0CTL0 | = OAP3 | OAN2 | OAPM3 | OAADC1;
    
```

Differential mode

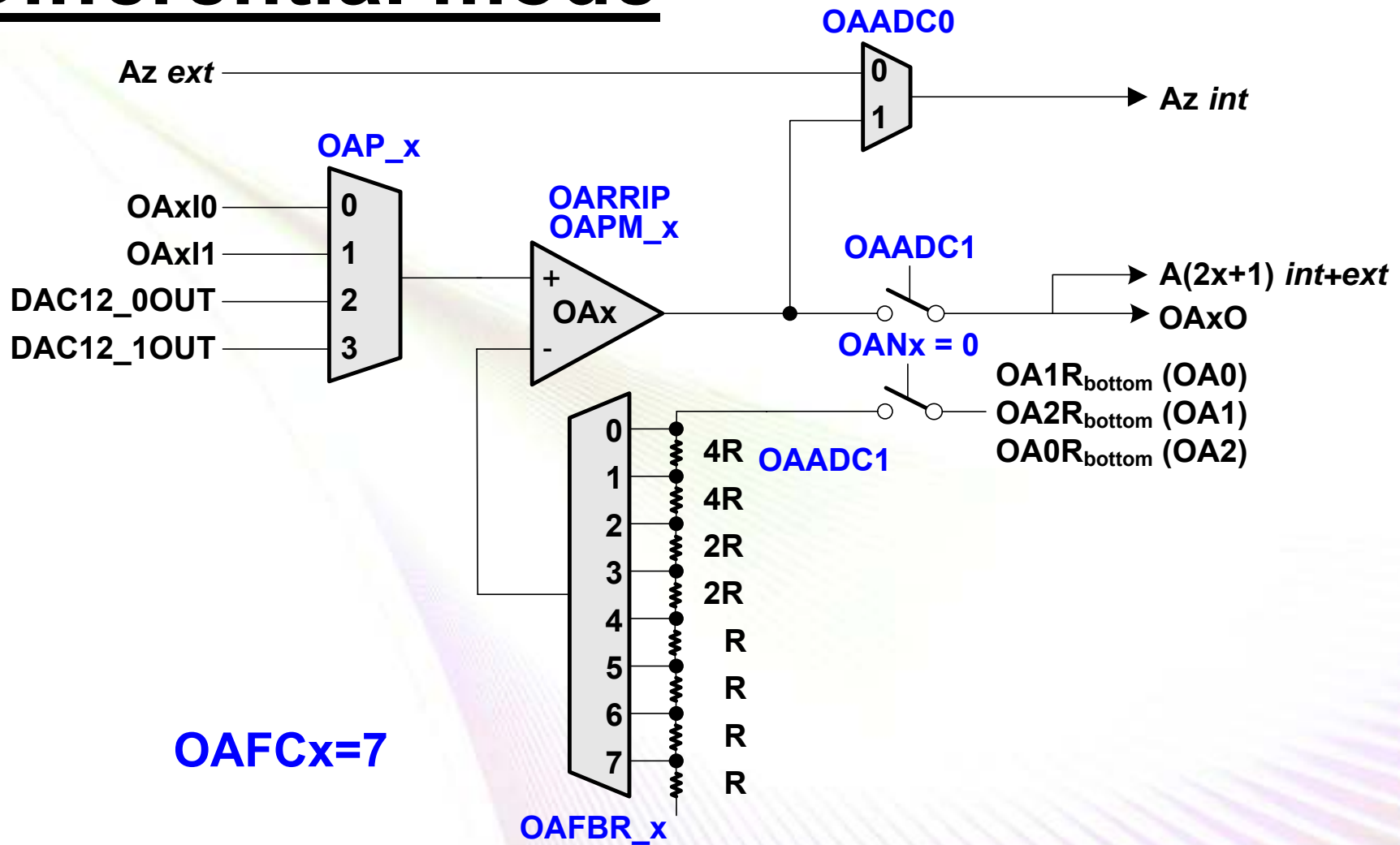

```
OA0CTL1 | = OAFC_7;
OA0CTL0 | = OAP_0 | OAN_0 | OAPM_3 | OAADC1;
```



2-amp microphone amplifier

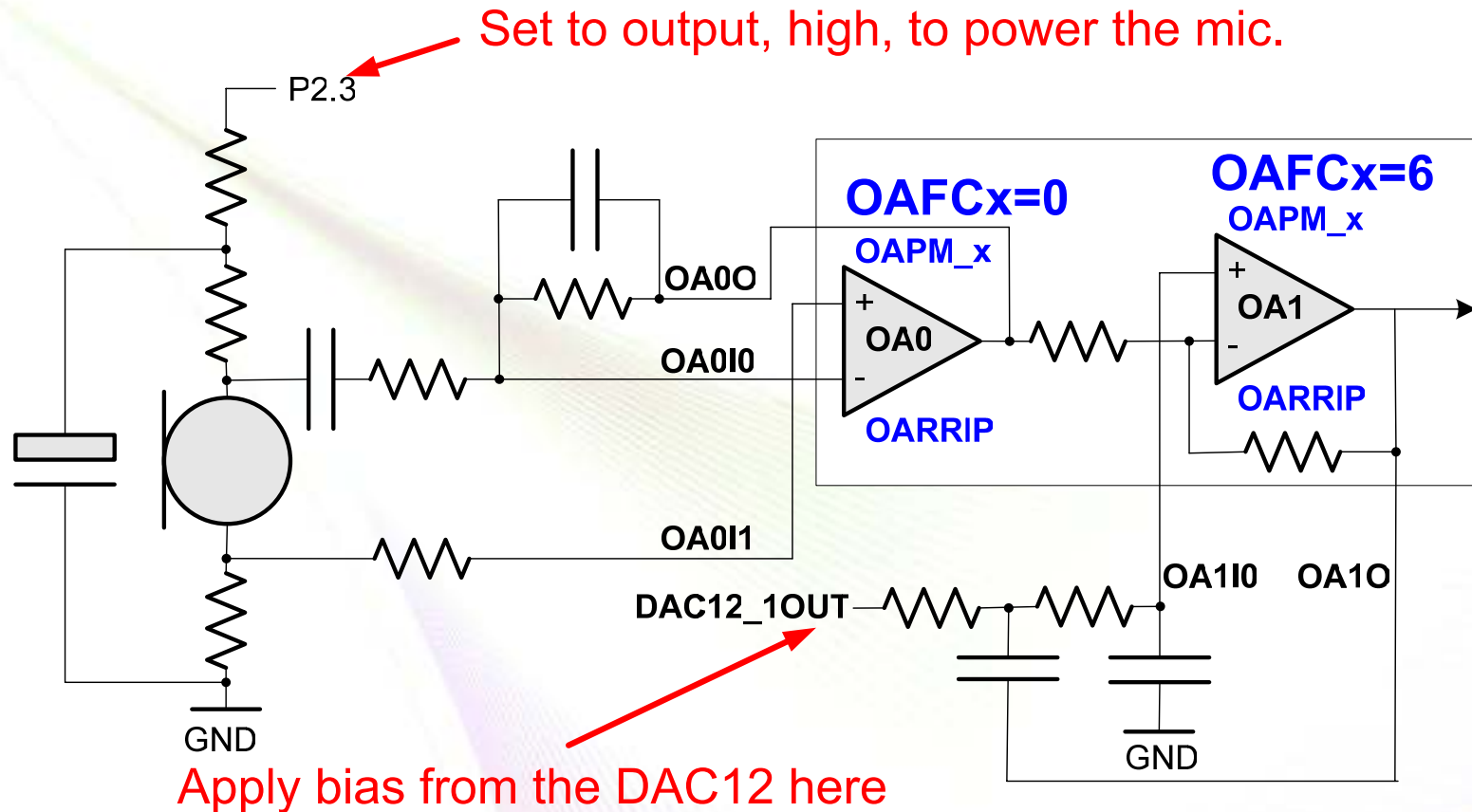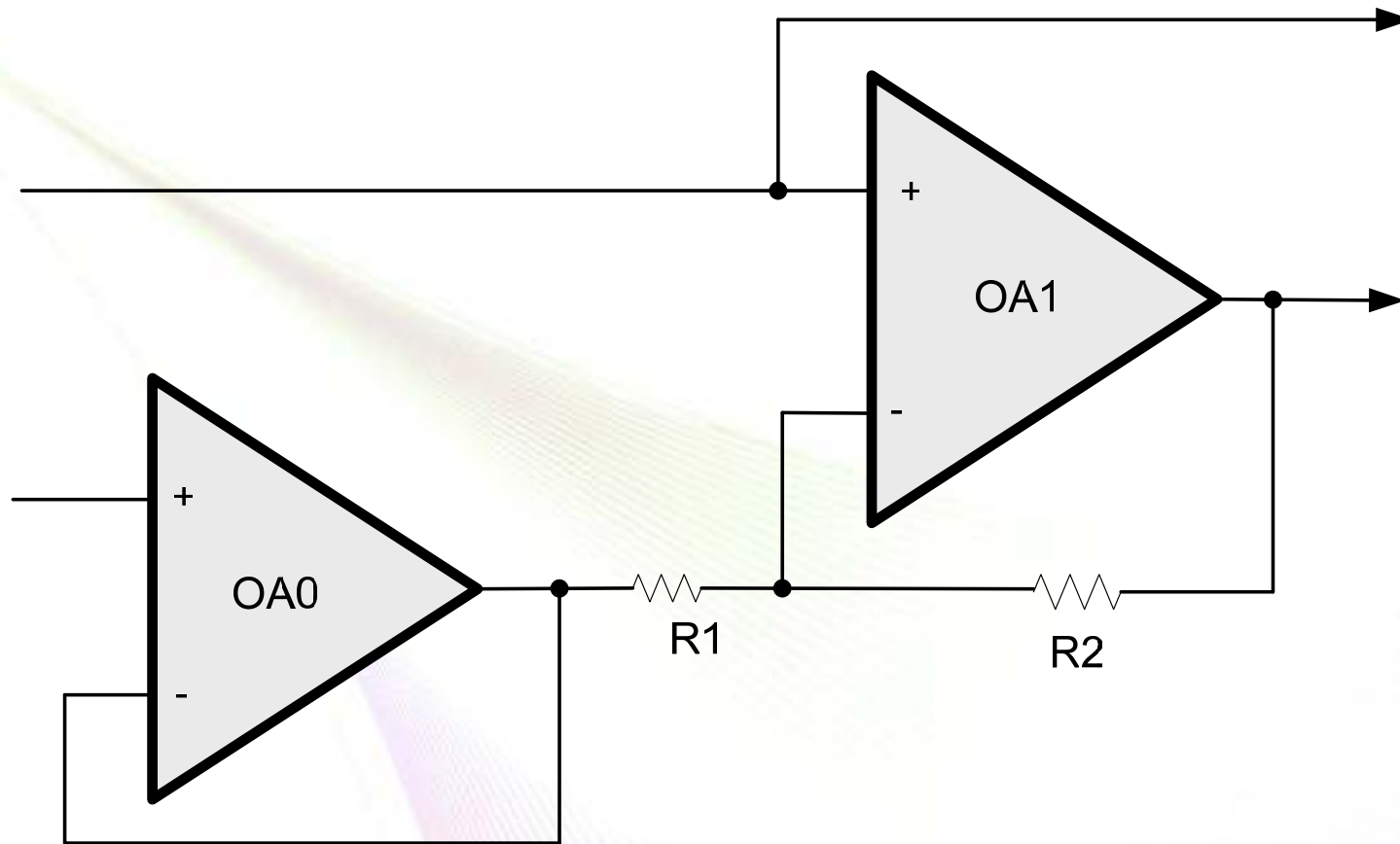

```


OA0CTL1 = OAFc_0;
OA0CTL0 = OAN_0 | OAP_1 | OAPM_3;
OA1CTL1 = OAFc_6 | OAFBR_2;
OA1CTL0 = OAN_2 | OAP_0 | OAPM_3 | OAADC1;
    
```

2-amp differential amplifier



```
OA0CTL1 | = OAF7C_7 | OAFBR_0; /* Differential mode */  
OA0CTL0 | = OAP_2 | OAPM_3;  
OA1CTL1 | = OAF6C_6 | OAFBR_2; /* Inverting PGA mode */  
OA1CTL0 | = OAP_3 | OAN_2 | OAPM_3 | OAADC1;
```

3-amp differential amplifier

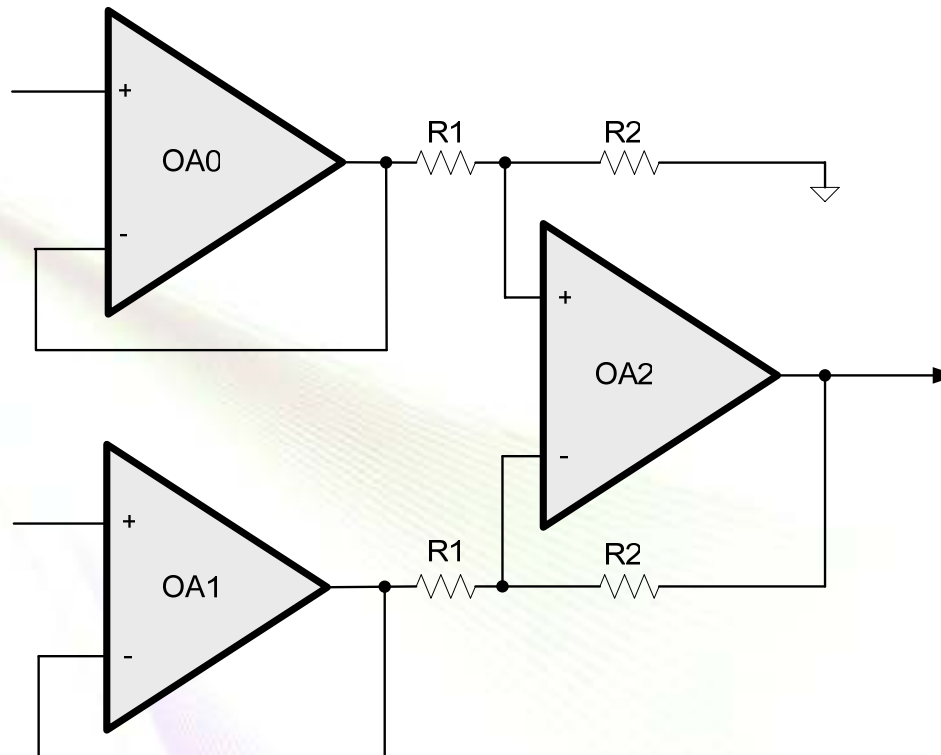

```
OA0CTL1 | = OAFc_1 | OAFBR_2; /* Unity gain mode */  
OA0CTL0 | = OAP_2 | OAPM_3;  
OA1CTL1 | = OAFc_7 | OAFBR_0; /* Differential mode */  
OA1CTL0 | = OAP_3 | OAPM_3;  
OA2CTL1 | = OAFc_6 | OAFBR_2; /* Inverting PGA mode */  
OA2CTL0 | = OAP_3 | OAN_3 | OAPM_3 | OAADC1;
```

In conclusion...

- **Flexible modes, to optimize current consumption & performance**
- **User configurable as general purpose, unity gain, voltage comparator, inverting & non-inverting PGA, differential**
- **Internally connected to ADC and DAC**
- **Highly configurable & suitable for portable medical system requirements**

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
RFID	www.ti-rfid.com	Telephony	www.ti.com/telephony
Low Power Wireless	www.ti.com/lpw	Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2007, Texas Instruments Incorporated