

TI *Live!* BATTERY MANAGEMENT SYSTEMS SEMINAR

LUIS HERNANDEZ SALOMON





OPTIMIZING MONITOR USAGE WITH MULTIPLE
PARALLEL FETS FOR HIGH POWER
APPLICATIONS

Agenda

- Electronic switching
- Battery protection switching
- High-side vs. low-side switching
- Battery protection FET topologies
- Parallel FET considerations



Electronic switching

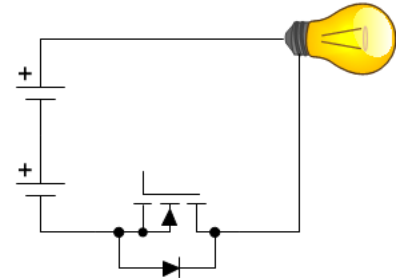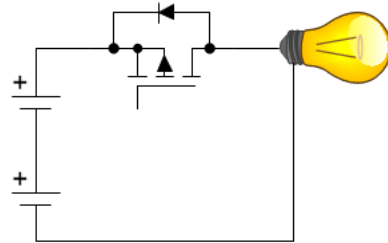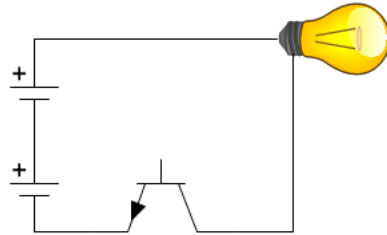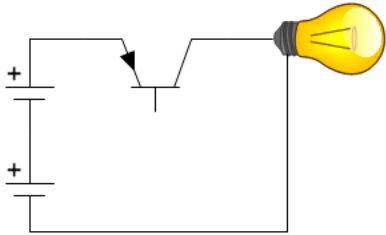- Electronic switches (simple) will have a polarity
 - BJT is a current-controlled switch
 - FET is a voltage-controlled switch
- FET most commonly used in switching
 - Low drive current
 - Low on-resistance





FET switching

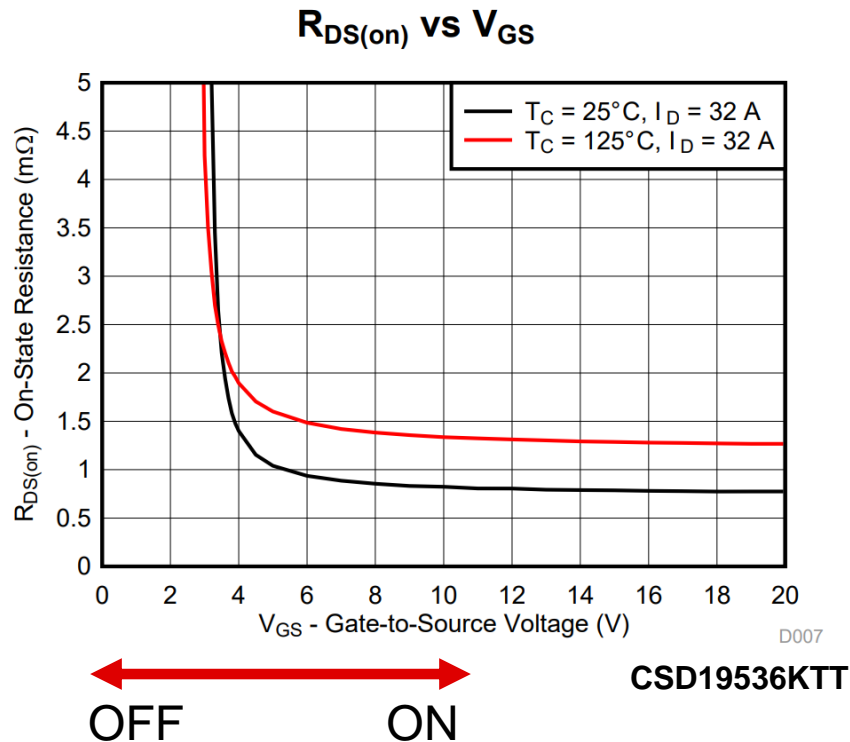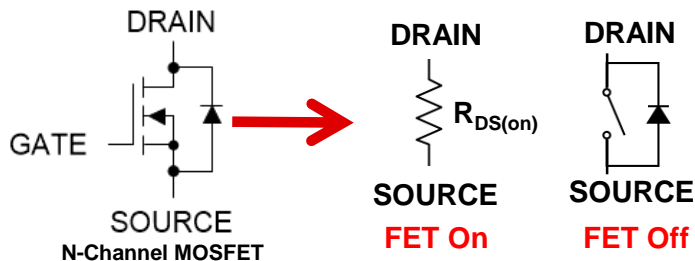- Want high drive voltage for low $R_{DS(on)}$
- Must slew through the transition voltage to turn off
- MOSFET blocks current in one direction
 - Behaves as a diode in the other



FET drive

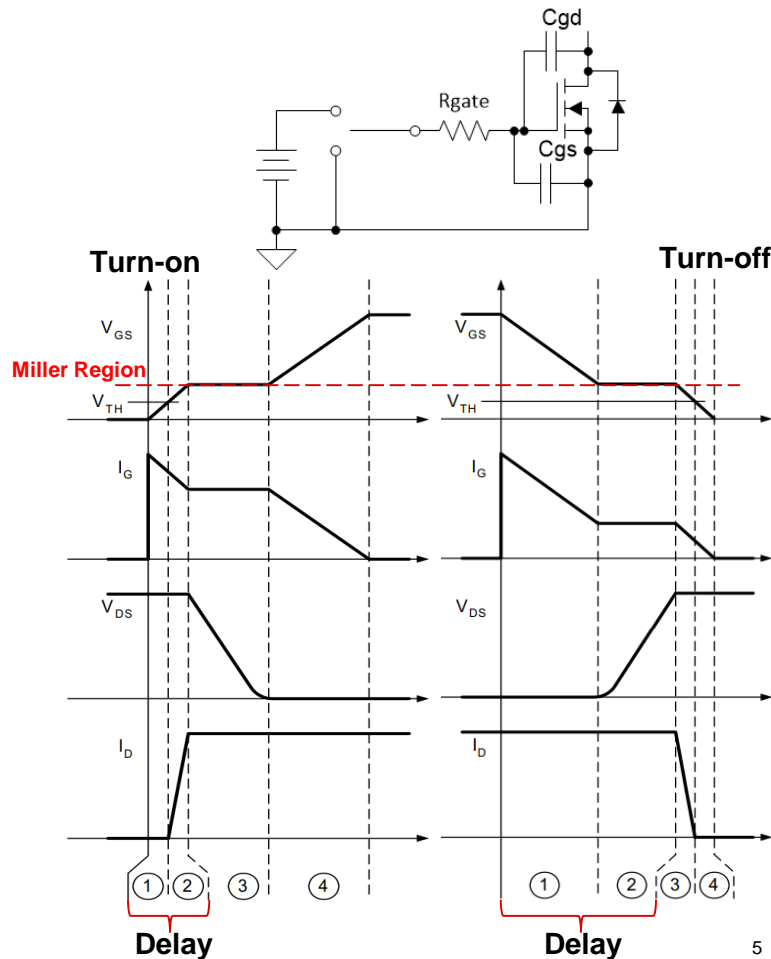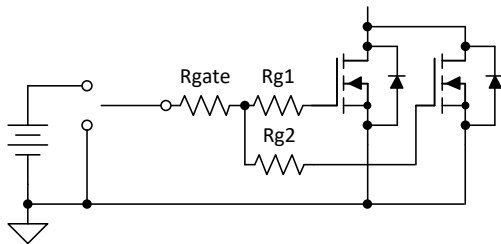- FET gate is capacitive
 - More input capacitance leads to longer switching
- Miller plateau/region at switching
- Generally parallel well
 - FETs “self-correct” current shared due to $R_{ds(on)}$ temperature dependency
 - Current distributed evenly across FETs
 - May need individual gate resistor or ferrite bead



FET drive voltage


- FETs will vary on-resistance at a specified drive voltage
 - $R_{DS(ON)}$ at V_{GS}
- Want lowest $R_{DS(ON)}$ for load switching
- Cannot exceed absolute maximum V_{GS}

$R_{DS(on)}$	Drain-to-Source On Resistance	$V_{GS} = 4.5\text{ V}$	1.2	m Ω
		$V_{GS} = 10\text{ V}$	0.79	
$V_{GS(th)}$	Threshold Voltage	1.7		V

Absolute Maximum Ratings



$T_A = 25^\circ\text{C}$		VALUE	UNIT
V_{DS}	Drain-to-Source Voltage	40	V
V_{GS}	Gate-to-Source Voltage	± 20	V

CSD18510Q5B

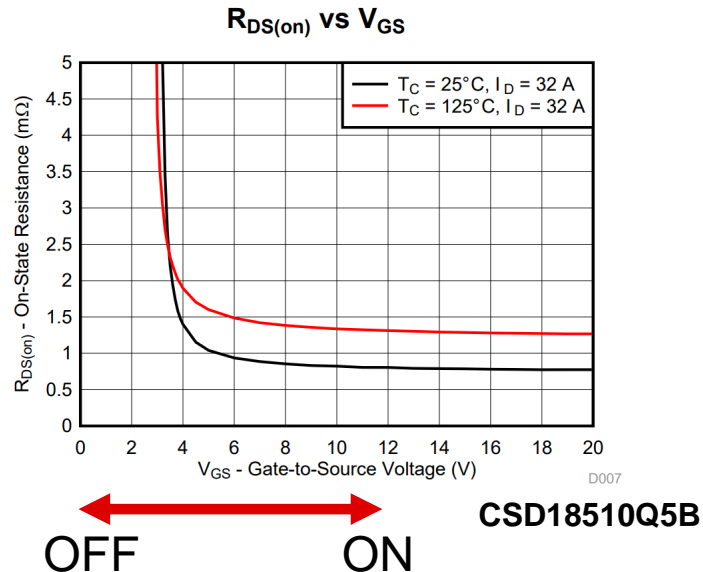


Types of FET switching

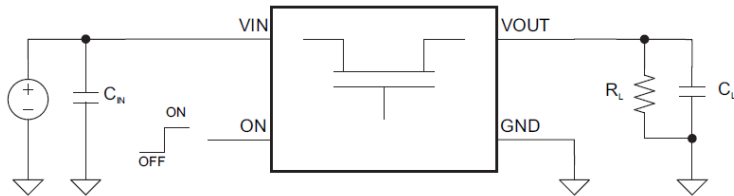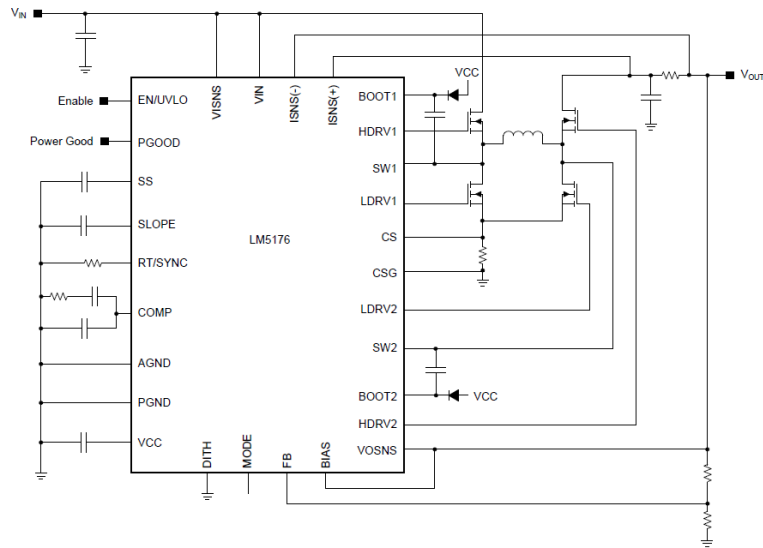- Power conversion
 - Fast switching
 - kHz to MHz
 - Low on-resistance
 - Want high efficiency
 - Fast switching, high drive currents
- Load switching
 - Infrequent switching
 - Low on-resistance
 - Prefer small loop, may be dictated by physical size
 - Slow switching to avoid exciting system inductance




Protecting a battery with FETs

- Lithium-Ion batteries need to be operated within specified limits
 - Do not over-charge & Do not over-discharge
 - MOSFETs commonly used for protection
- MOSFET is an unidirectional switch
 - Want to drive FETs gate-source voltage to minimize $R_{DS(on)}$
- Two MOSFETs in series controlled independently to avoid a latch
 - At high battery charge, allow discharge
 - At low battery charge, allow charge

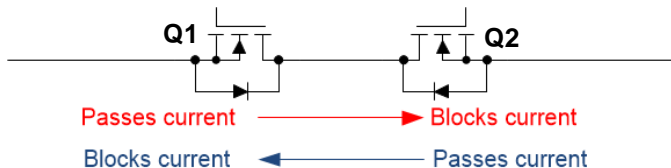


Low-side switching with N-channel FETs

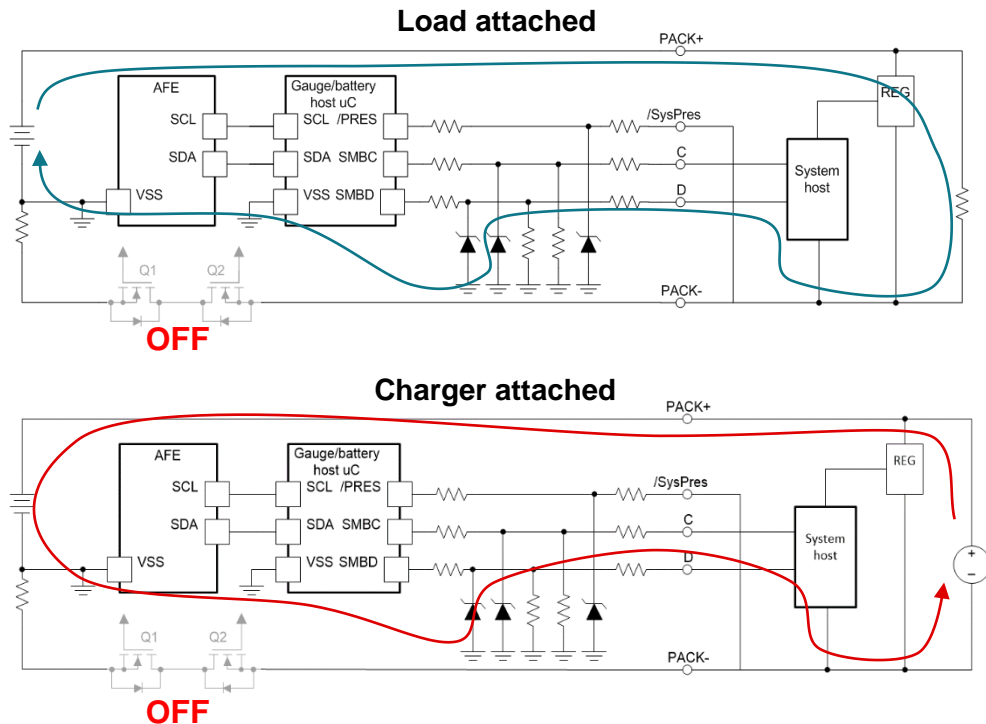- Low-side switching can be achieved with gate-drive within the battery's voltage
 - Easier to implement
- With direct coupled communication to the battery, low-side switching has some challenges
 - Loss of signal reference
 - Leakage past protection FETs




Mitigating comm & low-side switching issues

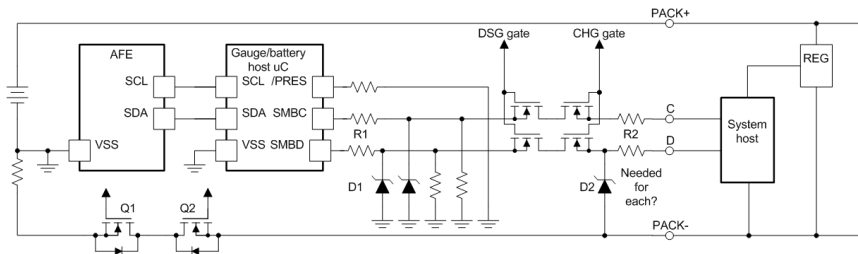
- Switch communications
 - Can't talk to system host



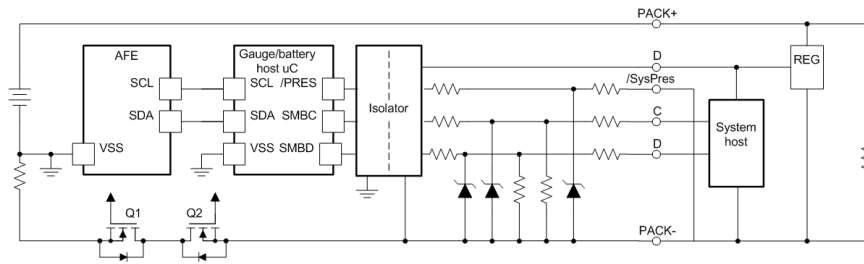- Isolate communications
 - May be included in some interfaces




- High-side switching

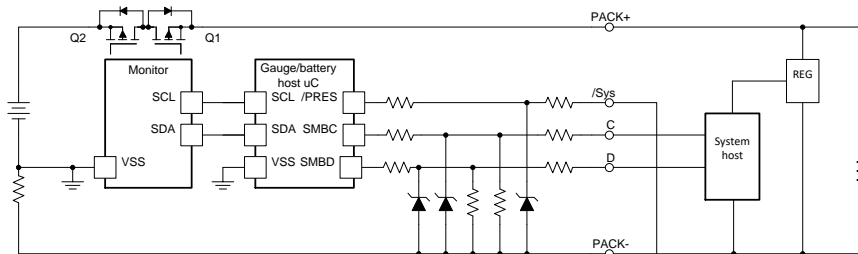


High-side switching with N-channel FETs

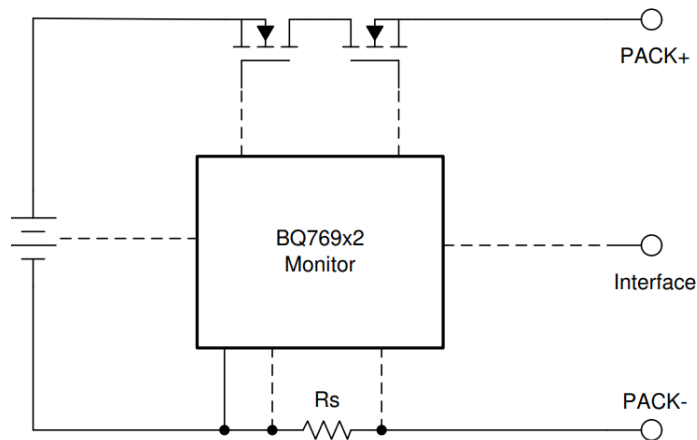- High-side switching avoids ground disconnection during protection faults.
- Gate driver voltage requires voltage above the battery voltage.
- Charge-pump is needed to drive FETs above battery voltage.
 - BQ769x2 family implements high-side switching with integrated charge-pump




Changing drive level of the part

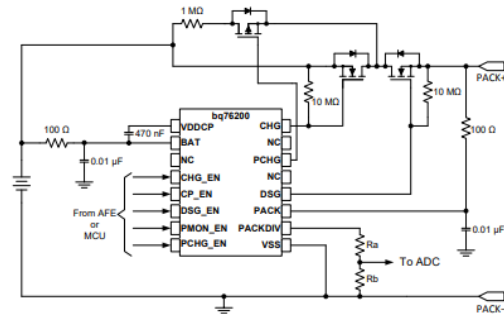- Sometimes part features may not match the drive level required by the system
- High-side BMS output – but low-side switch desired
 - Create level shift to low level
 - Use low-side driver
- Low-side BMS output – but high-side switch desired
 - Use high-side N-channel FET driver
 - High side P-channel
 - Isolated gate driver
 - Requires power supply for both sides




High side N-channel gate driver BQ76200

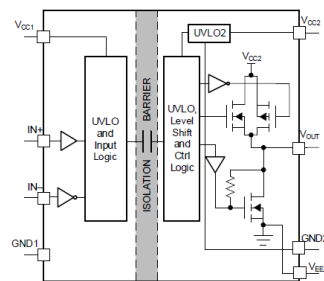

Isolated gate driver UCC53x0


Pre-charge & pre-discharge FET switching

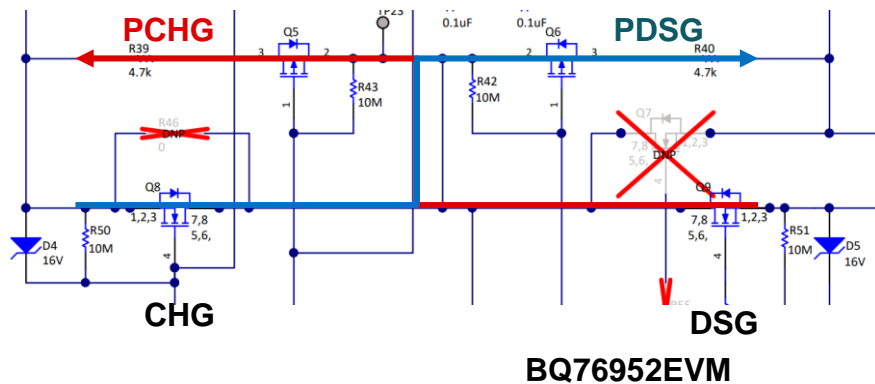- Depending on the application, reducing current in power path may be desired
 - Reduce inrush current on load during initial power-up
 - Reduce charge current on discharged battery cells
- FETs with added resistance on path used to reduce current in path
- Integrated high-side PCHG and PDSG drivers implemented in BQ769x2 family
 - P-Channel FET drive



Separate charging and discharge paths

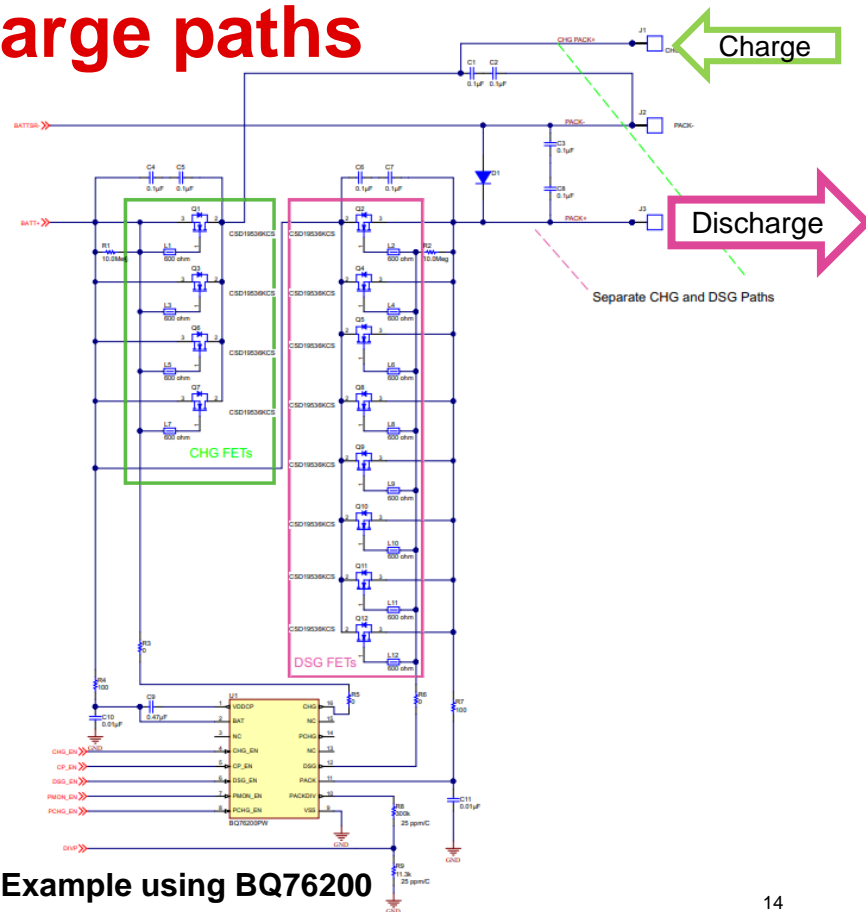
- In some applications there is a large difference between charging and discharge currents
 - Cost savings
 - Architecture
- It may be desired to use small charge FETs and large discharge FETs
 - Body-diode protection can cause unintended FETs to turn-on
 - Additional circuitry may be required to prevent leakage currents in parallel paths



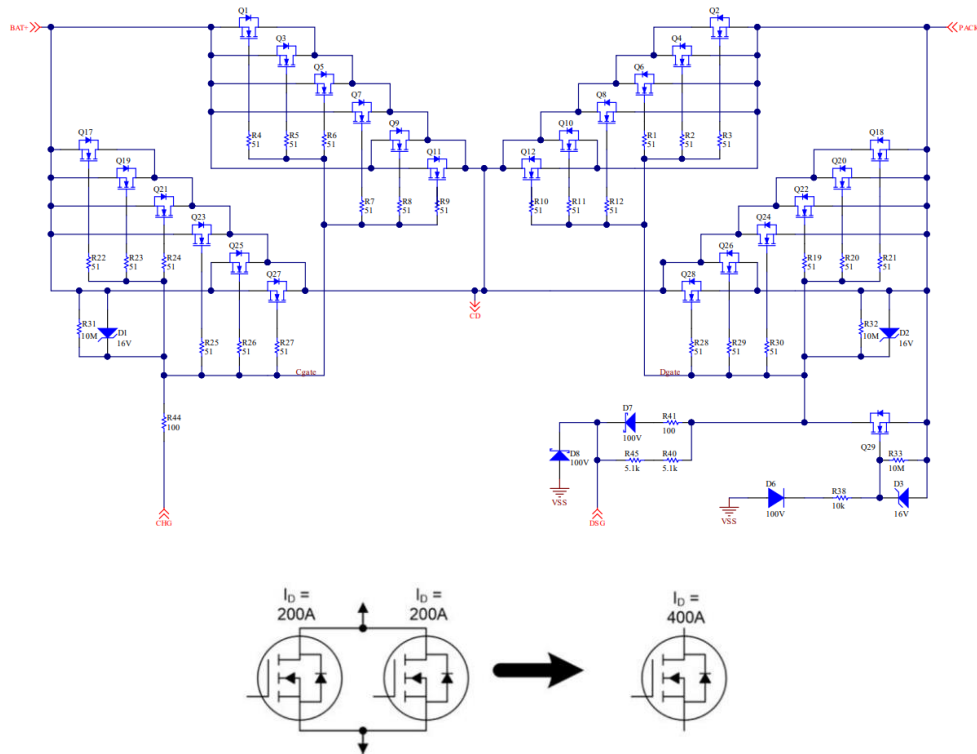Example using BQ76200



High-current with multiple parallel FETs

- In high-current cases, parallel FETs can be implemented
 - Allow higher charge/discharge currents
 - Better heat dissipation
- FETs in parallel increase gate capacitance
 - Slower switching
- Parasitic oscillations can occur at the gate of the FETs during switching
 - Individual gate resistance or ferrite bead may need to be added




Parallel FETs effect on switching speed

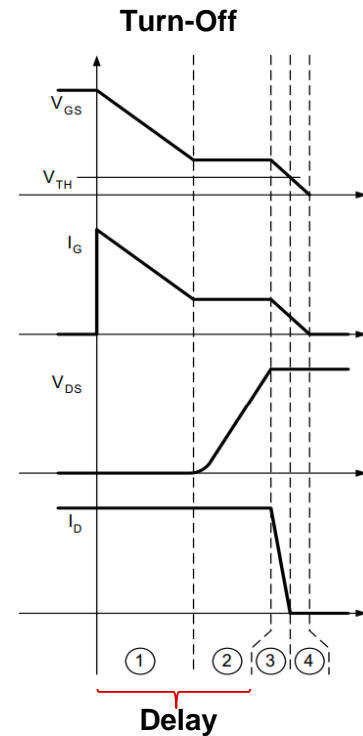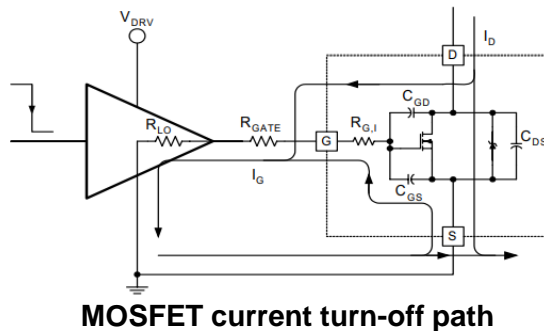
- Gate capacitance is increased in parallel FET implementations
 - Slower switching
 - Turn-off may be too slow
- Gate resistance can slow switching
- BMS gate drive may be limited by the device's design specifications
 - External circuitry can be added to speed switching speed



External local turn-off circuits

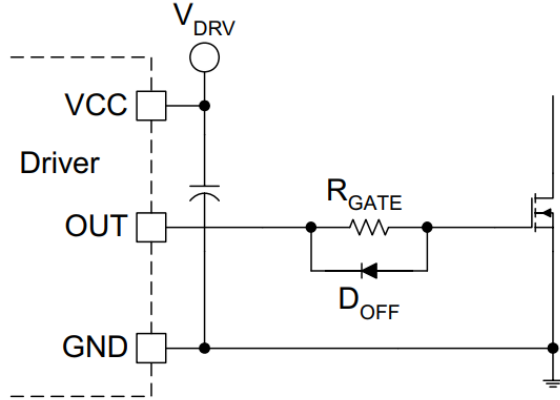

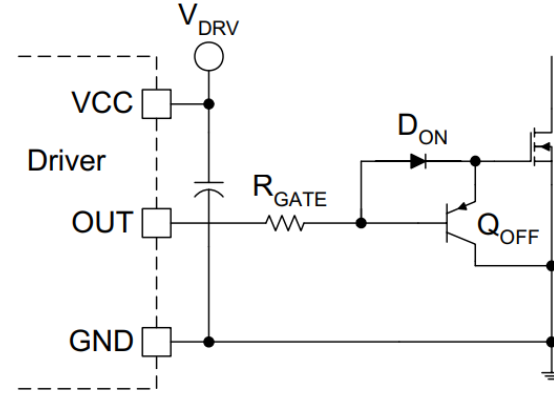
- Add diode that will be forward-biased during turn-off
 - Limited by driver speed



- Current pulled by driver during turn-off will turn-on PNP transistor, giving a faster discharge on MOSFET

Parasitic oscillations during turn-off

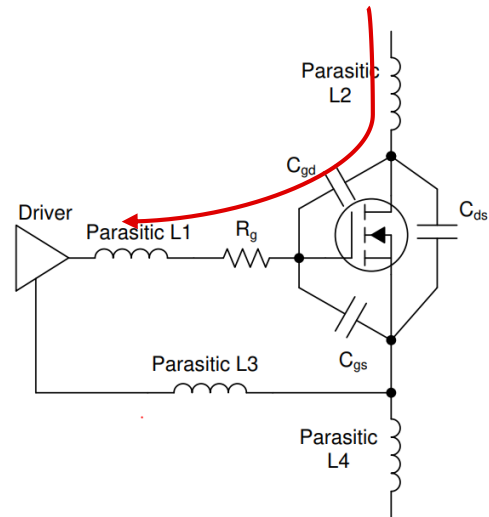
- Power MOSFETs are susceptible to parasitic oscillation
 - Generally have larger gain and capacitances
 - Layout could introduce stray inductances
- During events of fast transients at switching, inverse current can rush through C_{gd} into stray gate inductance
 - Generating RLC resonant circuit
 - Creates a positive feedback loop, which generates oscillations



Parasitics in gate drive circuit


Parasitic oscillations in parallel FETs

- Variation in electrical characteristics, particularly V_{TH} can lead to different switching timings
 - Lower V_{th} leads to faster turn-on, slower turn-off
 - Higher V_{th} leads to slower turn-on, faster turn-off
- One MOSFET will ultimately carry more current due to uneven switching behavior
- During turn-off FETs can cause voltage swing that can couple through parasitic C_{gd} into the shared gate connection causing oscillations

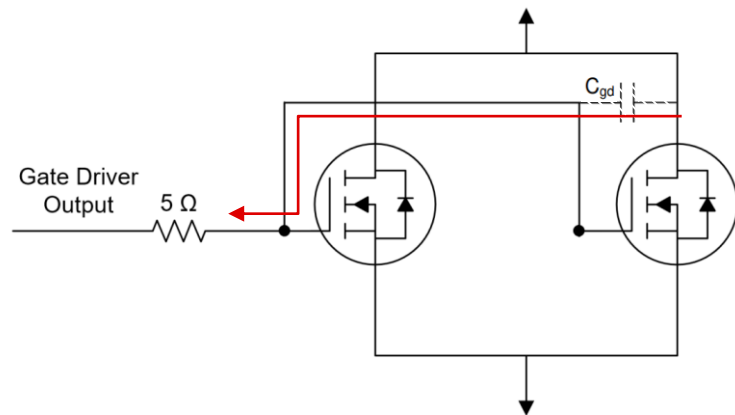


Mitigating oscillations during turn-off

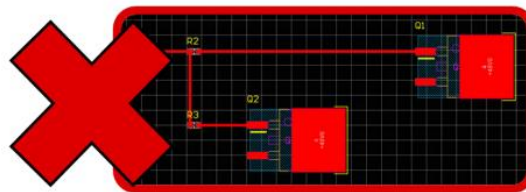- Good PCB layout practices
 - Matched gate traces
 - Small turn-off current loops
 - Reduce PCB trace inductances




Bad gate layout

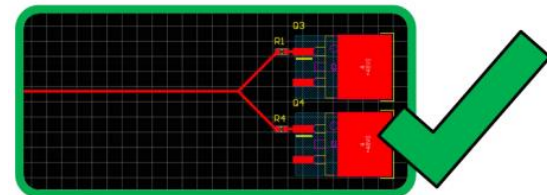

Good gate layout

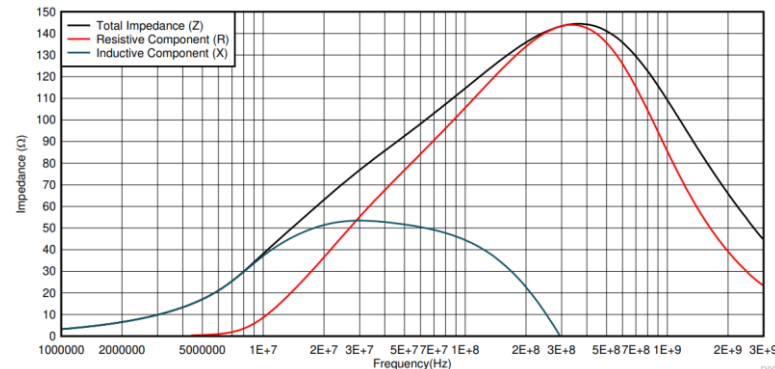- Add individual gate resistance/ferrite bead
 - Dampens oscillations
 - Gate resistor can slow switching speed
 - Bead have frequency-dependent impedances
 - Low impedance at low frequency
 - High impedances at high frequencies.
- Choose closely matched FETs
 - Contact FET provider for parallel recommendations.



Ferrite bead impedance vs frequency

Summary

- What drives the BMS requirement?
- FET Topologies for battery protection
 - High-Side
 - Simple Communication
 - Low-Side
 - Simple implementation
 - Pre-charge/pre-discharge
 - Separate discharge/charge paths
- Parallel FETs need additional considerations
 - Individual gate resistor/ferrite beads
 - Good layout practices
 - Select FETs with low difference in electrical characteristics

Resources

- [Multiple FETs with the BQ76952, BQ76942 Battery Monitors](#)
- [Parallel Paths with the BQ769x2 Battery Monitor](#)
- [FET Configurations for the bq76200 High-Side N-Channel FET Driver](#)
- [Fundamentals of MOSFET and IGBT Gate Driver Circuits](#)
- [The Use and Benefits of Ferrite Beads in Gate Drive Circuits](#)
- [Driving Parallel MOSFETs Using the DRV3255-Q1](#)
- [External Gate Resistor Selection Guide](#)



© Copyright 2022 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated