

# New Product Update

## Buck Converter vs. Power Module Performance Comparison

**Harrison Overturf**

Systems Engineer

**Adam Grula**




Product Marketing Engineer, Wide-VIN Buck  
Switching Regulators

# Agenda

- Overview of controllers, converters and modules
- Tradeoffs when selecting a converter vs. a module
- Key considerations when designing with modules
- Performance comparison between LMR36506 and TPSM365R6

Please feel free to “chat” Adam Grula, Product Marketing Engineer who is available to answer any questions you have throughout this presentation.

# Step-down (buck) switching regulators

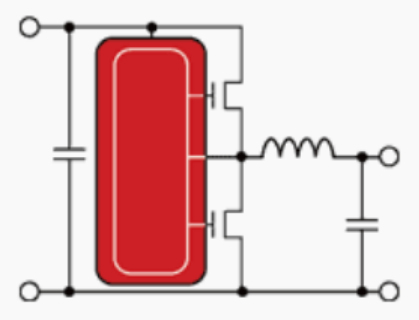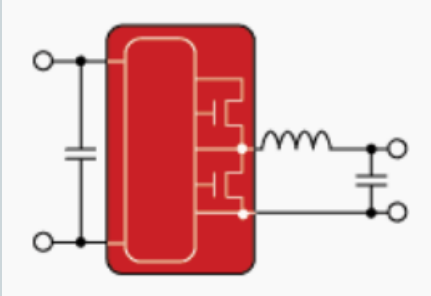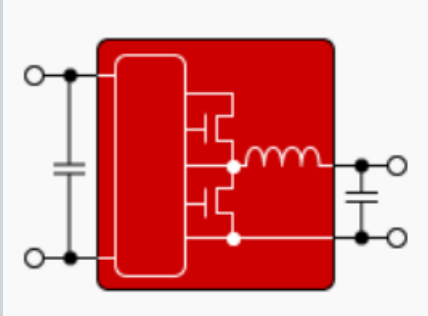Controller	Converter	Power module
 <ul style="list-style-type: none"><li>- External FETs</li><li>- External inductor</li></ul>	 <ul style="list-style-type: none"><li>- Internal FETs</li><li>- External inductor</li></ul>	 <ul style="list-style-type: none"><li>- Internal FETs</li><li>- Internal inductor</li><li>- Internal caps and resistors*</li></ul>

# LMR36506/03

Industry's smallest, highest power density & lowest Iq 65V, 600mA/300mA synchronous Step-down DC-DC converter

## Features




- Wide VIN range: 3.6V – 65V (Abs. Max = 70V)
- 2mm x 2mm HotRod™ package; -40C to 150C T<sub>J</sub> operation**
- <6μA Low Iq (Standby) with VOUT/BIAS
- Adjustable Fsw with RT variant(200kHz – 2.2MHz)
  - PFM and FPWM versions available
- Peak current mode control with internal compensation
- Precision EN/UVLO and PGOOD with delay
- Fixed (3.3V/5V) and Adj. VOUT options available
- Module option: TPSM365R6/R3

## Applications

- PLC
- Position sensor
- Analog I/O module
- Digital I/O module
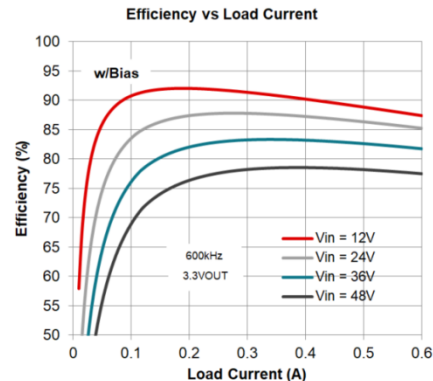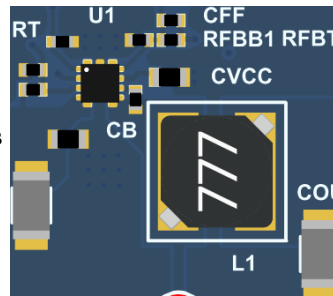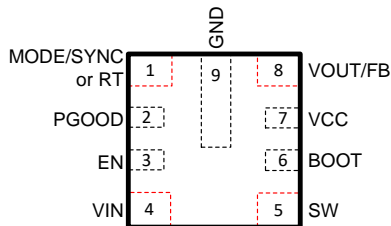
## Benefits

- Allows ultra small solution size suitable for space constrained applications
- Capable of handling **input transients up to 70V**
- Fixed frequency** (with adjustable option) and ultra low output voltage ripple over entire load range
- Best in class Wide-V<sub>IN</sub> TI solution for <10uA standby current requirements
  - Typ. Industrial (~**87%**@24Vin, 3.3VOUT @300mA 600KHz)



# TPSM365R6/3

65V, 600mA/300mA synchronous step-down DC-DC power module

## Features


- Adj. output voltage range of **1V to 13V** and **Fixed 3.3V, 5V** variants
- **Low Iq solution** - 4 $\mu$ A at 24Vin to 3.3Vout (fixed output option)
- **SYNC/MODE with fixed output.**
  - FPWM (Fixed frequency operation at no load)
  - PFM (Improved light load efficiency at light load)
- **BIAS input with fixed VOUT** to enable high efficiency for wide vin operation
- **RT pin** for adjustable output. Configurations:
  - RT -> GND = 1MHz, RT -> VCC = 2.2MHz, Resistor program = 400kHz-2.2MHz
- **Low EMI solution** with PSRR spread spectrum and FCOL package
- Pin spacing complies with IPC2221A(L)
- **FCOL package 4.5mmx3.5mmx2.0mm**

## Applications

- Control/field transmitters
- Application specific test equipment
- PLC, DCS
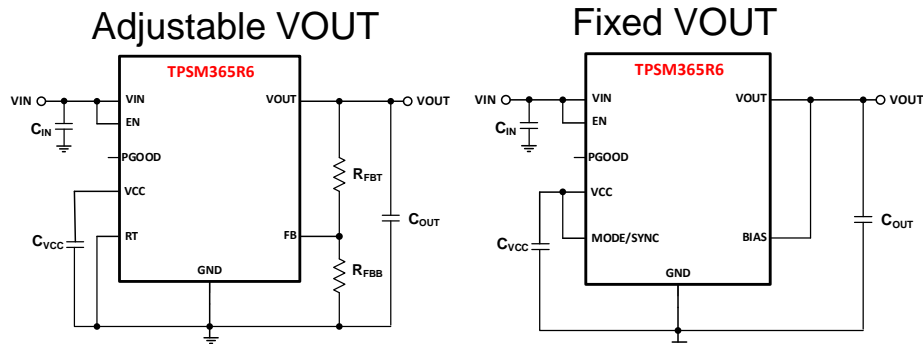
## Benefits

- Wide input for applications with unregulated 24V bus. No input protection needed.
- Mode pin to enable fixed frequency and ultra low ripple over entire load range. PFM mode for applications which require high efficiency at light loads
- Adjustable frequency to enable a wide VOUT range.
- Bias input for fixed VOUT options to improve efficiency over load
- Ease of power sequencing with PGOOD



# Scalable **converter/module** solution

2mm × 2mm pin-to-pin compatible VQFN-HR 9-pin package solution from 50mA to 2A

65Vin  
**0.05A**

65Vin  
**0.15A**

65Vin  
**0.6A**



36Vin  
**2A**

**LMR36500**

**LMR36501/02**

**LMR36503/06**

**LMR43610/20**

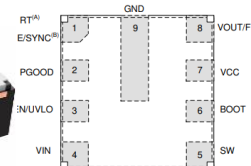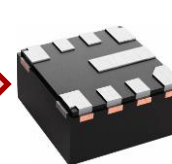

4.5mm × 3.5mm × 2mm pin-to-pin compatible HR-QFN 11-pin package solution from 50mA to 2.5A

65Vin  
**0.15A**


65Vin  
**0.6A**

36Vin  
**2.5A**

**TPSM365R0/R1**

**TPSM365R3/R6**

**TPSM33615/25**

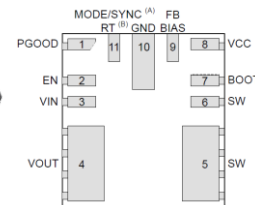

# Tradeoffs between LMR36506 & TPSM365R6

LMR36506	TPSM365R6
<ul style="list-style-type: none"><li>• Higher efficiency is possible<ul style="list-style-type: none"><li>• Better thermal performance</li></ul></li><li>• Greater flexibility when designing<ul style="list-style-type: none"><li>• Wider output voltage range</li></ul></li><li>• More precise control over switching frequency</li></ul>	<ul style="list-style-type: none"><li>• Integrated Passives reduce component count<ul style="list-style-type: none"><li>• Inductor (10<math>\mu</math>H)</li><li>• Boot capacitor</li></ul></li><li>• Smaller solution size<ul style="list-style-type: none"><li>• Easier layout – no need to route SW node</li></ul></li><li>• Includes MODE/SYNC variant</li><li>• Includes spread spectrum</li></ul>

# How to decide between converter and module?

1. What are my desired operating conditions? [VIN, VOUT, IOUT, TA, fsw]
2. Do my operating conditions violate the recommended operating conditions of the converter or the module?
  1. See Table 8.3 and Table 9.6 in TPSM365R6 datasheet
  2. See Table 7.3 in LMR36506 datasheet
3. Does my design have special requirements?
  1. Is solution size a big concern?
  2. Is there a frequency band of interest I need to avoid?
  3. Do I need to synchronize to an external clock frequency?
  4. What's my maximum ambient frequency?
  5. Do I plan to reuse this device for future designs?




# Key considerations for power modules


Benefits	Tradeoffs
<ul style="list-style-type: none"><li>• BoM count reduction</li><li>• Ease of design<ul style="list-style-type: none"><li>• Don't need to worry about sizing of SW node layout</li><li>• No need for Boot cap placement</li><li>• No need to select inductor</li></ul></li><li>• Smaller solution size</li></ul>	<ul style="list-style-type: none"><li>• Fixed inductor<ul style="list-style-type: none"><li>• Output voltage range is limited(usually to &lt;16V)</li><li>• Slightly lower efficiency due to fixed inductor</li><li>• Less control over switching frequency</li></ul></li></ul>

# LMR36506 vs. TPSM365R6 package

**LMR36506**

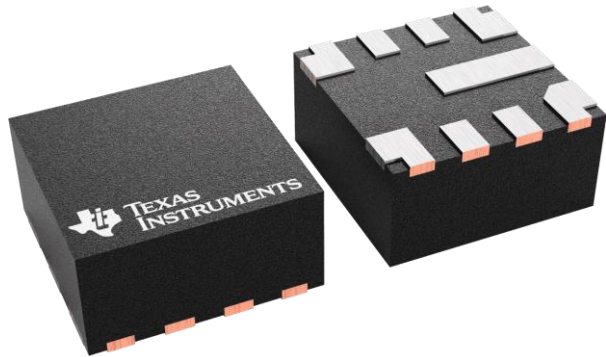


**TPSM365R6**

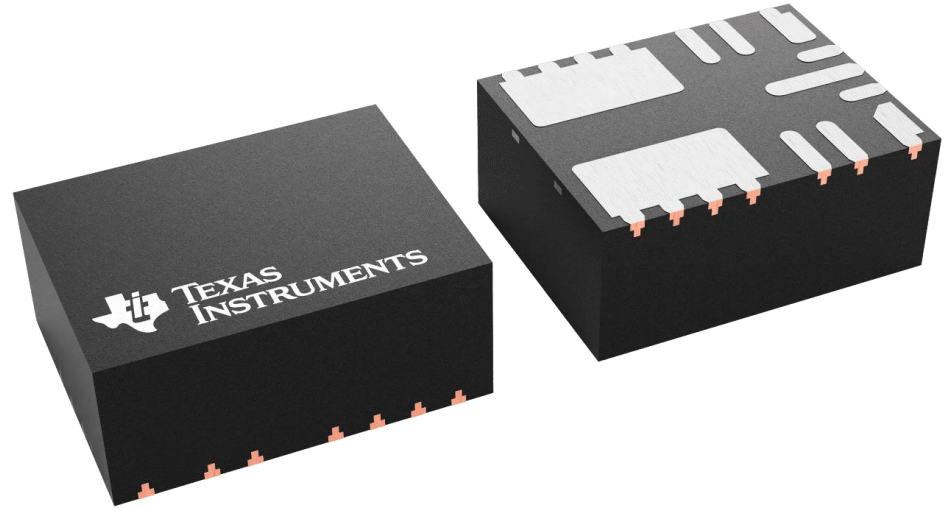


# TPSM365R6 solution size

Module (TPSM365R6)

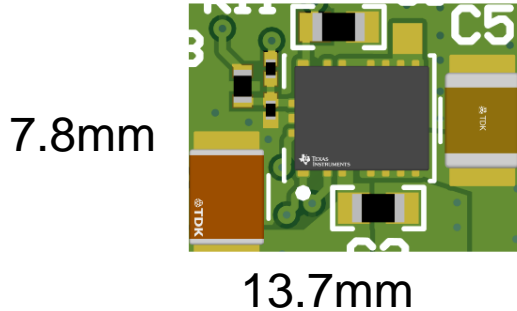


IC (LMR36506)

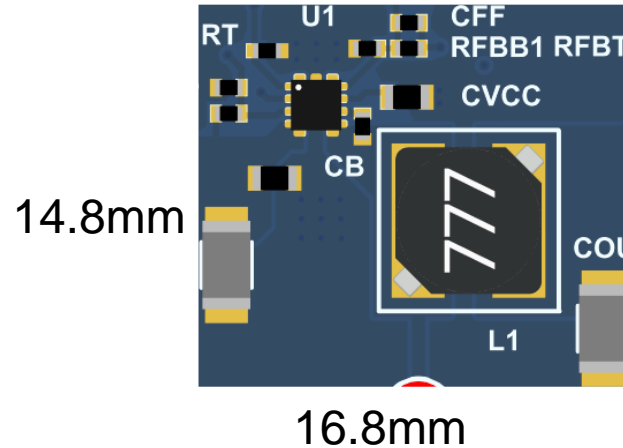


Smaller footprint. Tradeoff is usually lower efficiency vs IC.

# TPSM365R6 electrical performance

## Efficiency 12V input 5V output

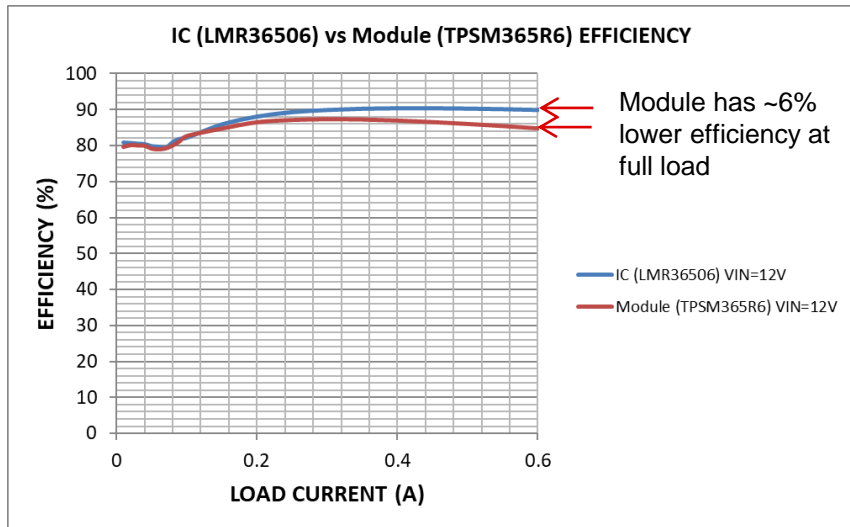

## Efficiency 24V input 5V output

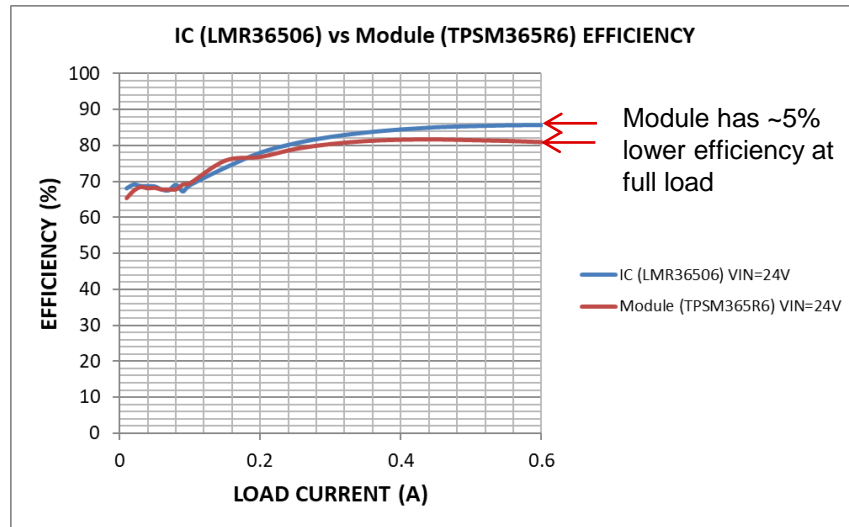


Efficiency tradeoff is understood, but what about thermal performance?

# TPSM365R6 thermal performance


## Module (TPSM365R6)

VIN=24V VOUT=5V IOU=0.5A, standard EVM

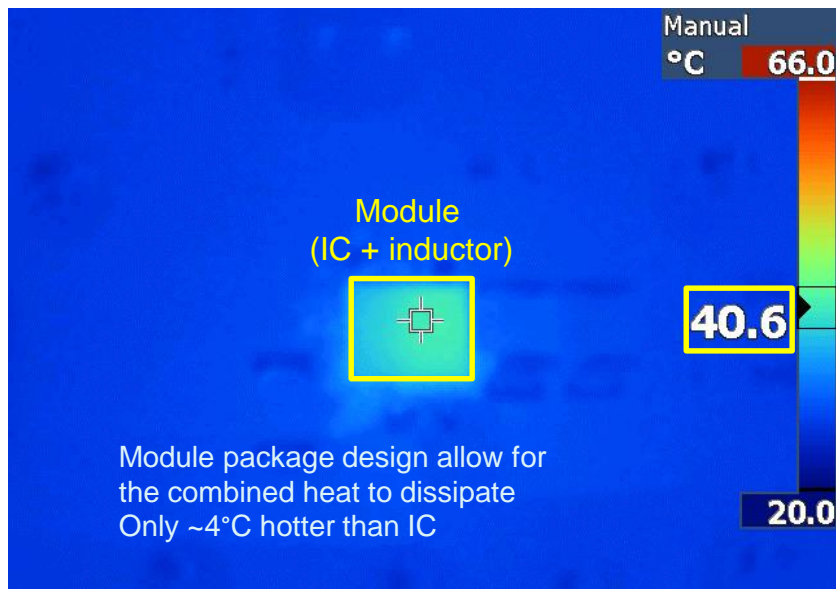


## IC (LMR36506)

VIN=24V VOUT=5V IOU=0.5A, standard EVM

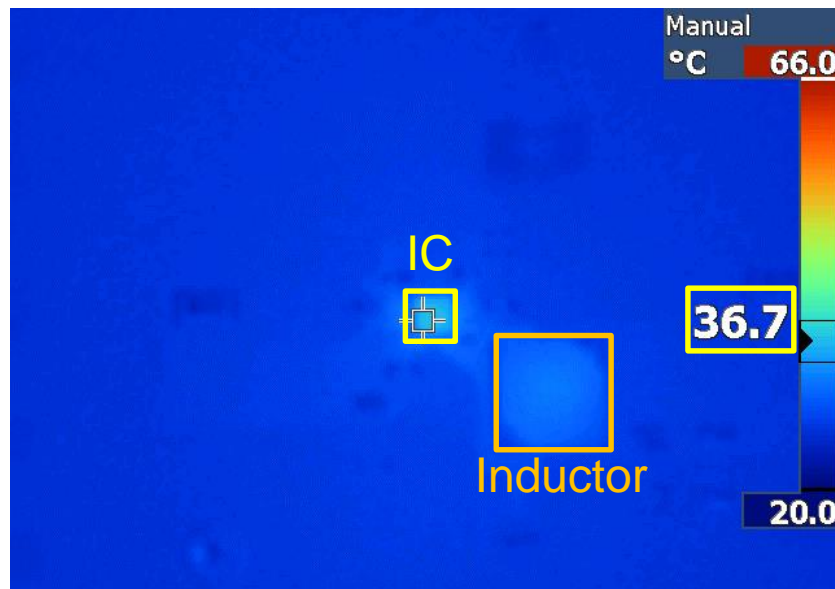

# Derating curve (VIN=24V)

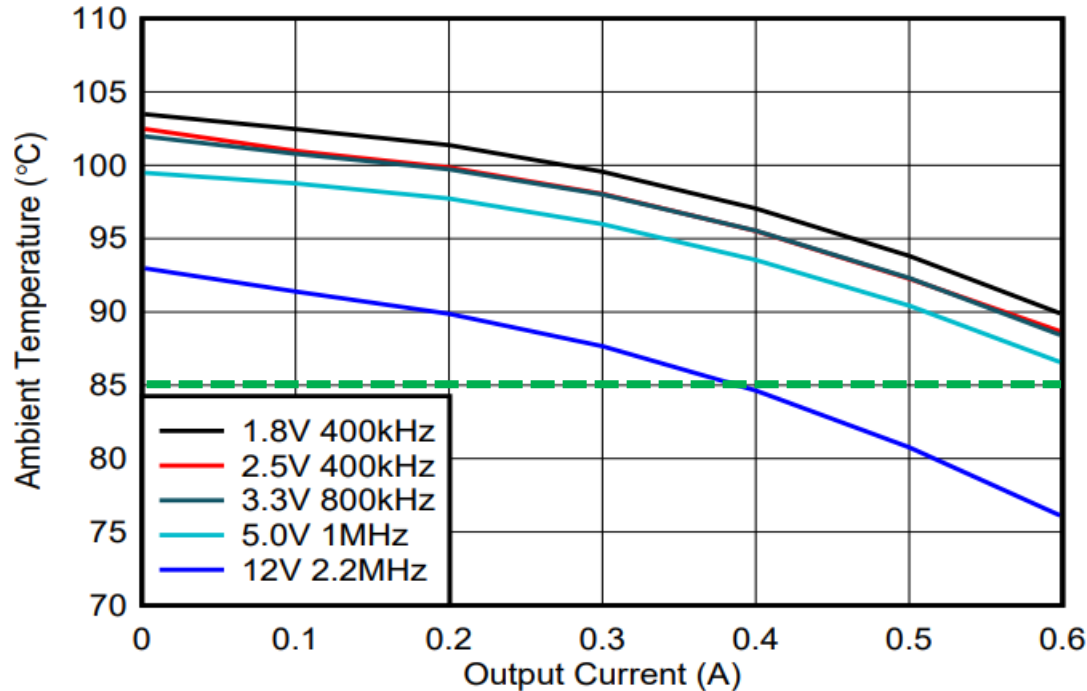


Suitable for most industrial applications without current derating


Figure 8-11. Safe Operating Area (Standard EVM Layout and Board Size)

# TPSM365R6 EMI performance (with same setup)

## Horizontal

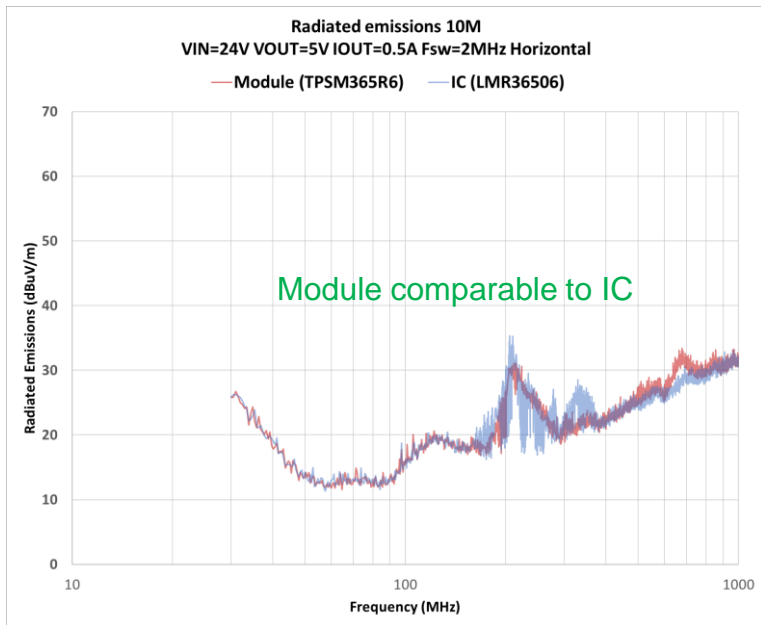

## Vertical

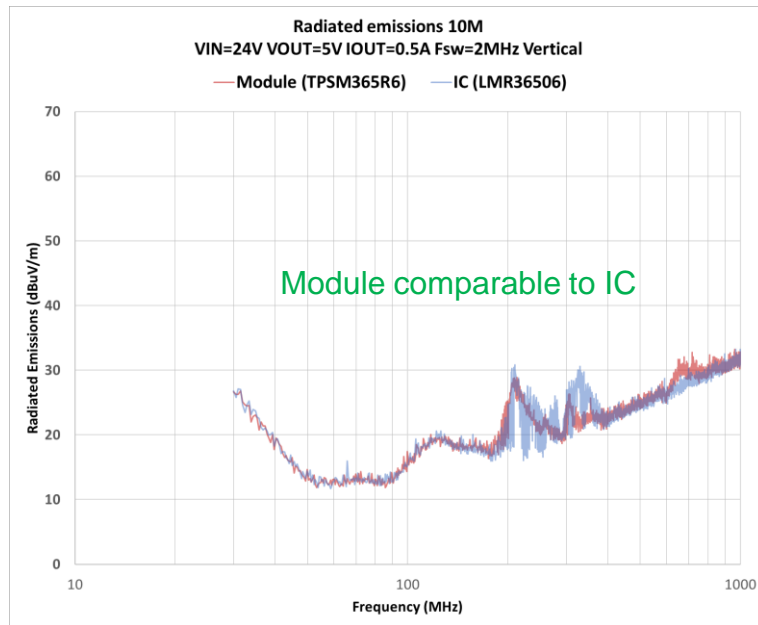

# Getting started

You can start evaluating this device leveraging the following:

Content type	Content title	Link to content or more details
Product folder	TPSM365R6 LMR36506	<a href="https://www.ti.com/product/TPSM365R6">https://www.ti.com/product/TPSM365R6</a> <a href="https://www.ti.com/product/LMR36506">https://www.ti.com/product/LMR36506</a>
Reference design	400W GaN-based MPPT charger controller and power optimizer reference design	<a href="https://www.ti.com/tool/TIDA-010042">https://www.ti.com/tool/TIDA-010042</a>
Technical blog content or white paper	Bi-polar Fly-buck-Boost Solution for Analog Output Modules	<a href="https://www.ti.com/lit/an/snvaa84/snvaa84.pdf">https://www.ti.com/lit/an/snvaa84/snvaa84.pdf</a>
Selection and design tools and models	TPSM365R6 Design Tools LMR36506 Design Tools	<a href="https://www.ti.com/product/TPSM365R6#design-tools-simulation">https://www.ti.com/product/TPSM365R6#design-tools-simulation</a> <a href="https://www.ti.com/product/LMR36506#design-tools-simulation">https://www.ti.com/product/LMR36506#design-tools-simulation</a>
Development tool or evaluation kit	TPSM365R6EVM LMR36506RREVM	<a href="https://www.ti.com/tool/TPSM365R6EVM">https://www.ti.com/tool/TPSM365R6EVM</a> <a href="https://www.ti.com/tool/LMR36506RREVM">https://www.ti.com/tool/LMR36506RREVM</a>





© Copyright 2024 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.  
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2024, Texas Instruments Incorporated