



Module 8


Quiz: Interfacing Input and Output



Quiz: Interfacing input and output devices using LEDs and Switches

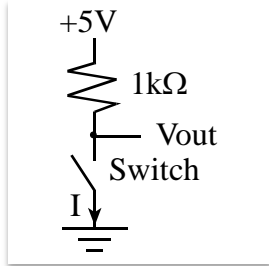Q1 Switch Interfacing

Consider this negative logic switch circuit used in a +5V digital system. Do not consider the switch to be ideal. Rather, assume the resistance of the switch when the switch is open is $1\text{ M}\Omega$, and the resistance of the switch when the switch is closed is $1\ \Omega$. How much current flows in mA through the switch when the switch is not pressed?




How much current in mA flows through the switch when the switch is pressed?

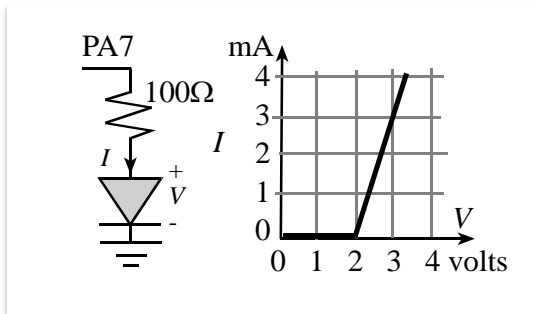Q2 LED Interfacing

The output on P1.7 controls this LED. For LED voltages less than 2 volts, the LED current is 0. Assume the output high voltage of P1.7 is 3.3V. For voltages above 2 volts, the LED current is

$$I = 3 * (V - 2), \text{ where } I \text{ is in mA, } V \text{ is in volts.}$$




What are the current, voltage, and power to the LED when it is on?

Q3 LED Interfacing.

Consider an LED with a desired operating point of (I_d, V_d) . Let V_{OL} , V_{OH} , I_{OL} and I_{OH} be the operating parameters of the digital output on P1.1. What is the design equation needed to calculate the desired resistance R for this circuit?

P1

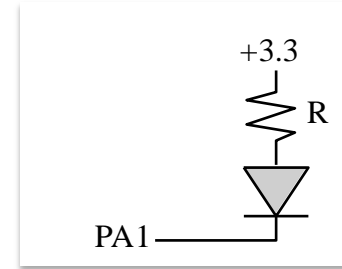





Quiz: Interfacing input and output devices using LEDs and Switches

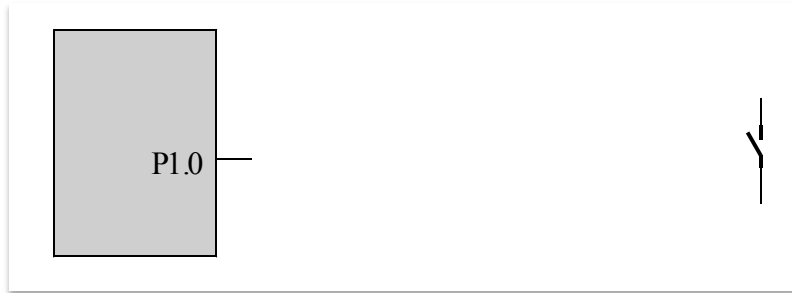Q4 Switch Interfacing

Interface a switch to P1.0. Implement the interface in negative logic. Assume the port pin is initialized as an input with internal pull-up. Minimize cost of the interface. Show hardware connections; no software is required.



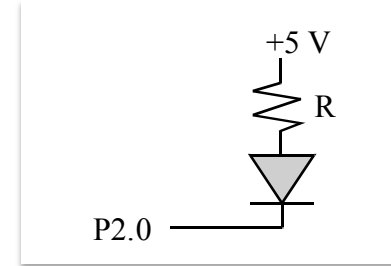Q6 This is not an MSP432, but rather assume this is another microcontroller running at 5V power. The following interface is used to interface a low current LED. Assume the LED voltage drop is 2 V. The resistor is 1000 Ω. When the software outputs a high, the voltage on P2.0 becomes 4.9 V. When the software outputs a low, the voltage on P2.0 becomes 0.5 V. What is the LED current when the LED is on? Is this positive or negative logic?



Q5 LED Interfacing

Interface a multicolor LED to the microcontroller. Each color is controlled by a separate diode with an operating point of 2V, 25mA. You can use any number of 7406 inverters, and any number of resistors. Assume the V_{OL} of the 7406 is 0.5V. Assume the microcontroller output voltages are $V_{OH} = 3.0V$ and $V_{OL} = 0.1V$. Specify values for any resistors needed. Show equations of your calculations used to select resistor values. Make each output control one color, positive logic.



IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2018, Texas Instruments Incorporated