

Understanding the Difference between Switched Capacitor and Fully Differential Amplifier (FDA) Inputs for Isolated Data Converters



Introduction

Isolated delta-sigma modulators are a common solution for current measurement in high-voltage systems such as motor drives, inverters, and power conversion stages. By digitizing the analog input on the high-voltage side and transmitting a bitstream across a galvanic isolation barrier, these devices protect low-voltage signal circuitry while rejecting large common-mode voltages inherent to switching power stages.

Two input architectures are present in today's isolated modulator solutions: the fully differential amplifier (FDA) front-end, which actively buffers and conditions the analog signal before it reaches the modulator, and the direct switched-capacitor input, which connects the modulator directly to the analog inputs without an intermediate amplifier stage. This document compares the two types of inputs and how to properly design an input filter for each type.

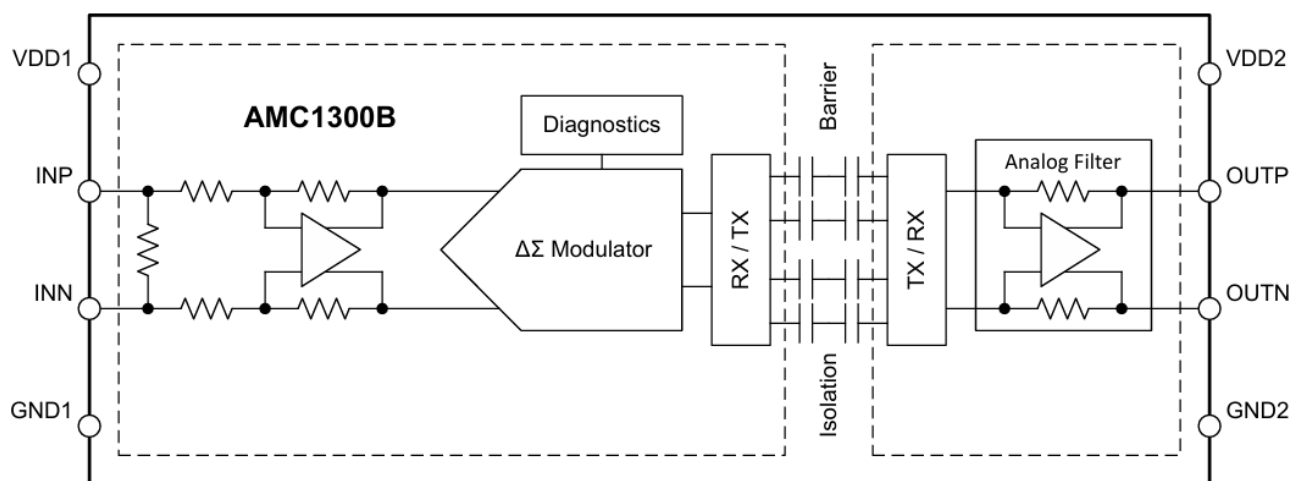


Figure 1. Fully Differential Amplifier Input

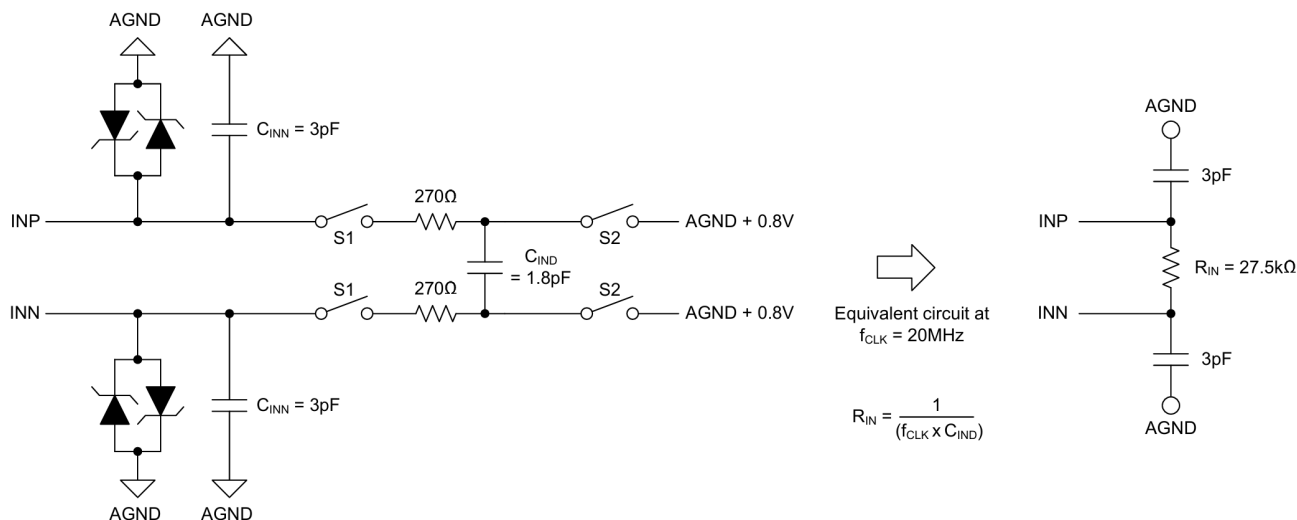


Figure 2. Switched-Capacitor Input

The main difference between the switched-capacitor input and the FDA is the op-amp input stage on the input of the delta-sigma modulator on the FDA architecture. Omitting this amplifier on the input allows for more cost-effective solutions for designers. The layout of the input filtering also looks different between the two inputs.

Both input architectures should have a differential capacitor between the inputs. Due to the switched capacitors' higher peak current draw, common-mode capacitors should also be placed between both inputs to ground. These capacitors should be 10 to 20 times smaller than the differential capacitor between the inputs. The design of the differential input filter does not change between the two input structures; namely, it should follow these guidelines:

- The cutoff frequency of the differential filter is at least one order of magnitude lower than the sampling frequency (20MHz) of the $\Delta\Sigma$ modulator
- The input bias current does not generate significant voltage drop across the DC impedance of the input filter
- The impedances measured from the analog inputs are equal

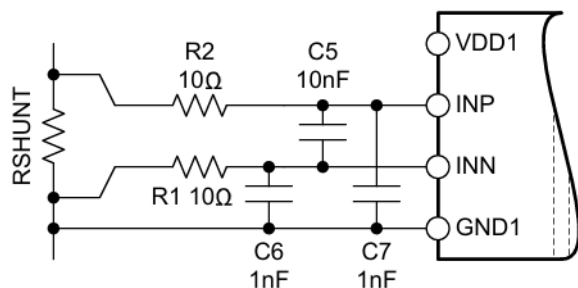


Figure 3. Input Filter for a Switched-Cap Input

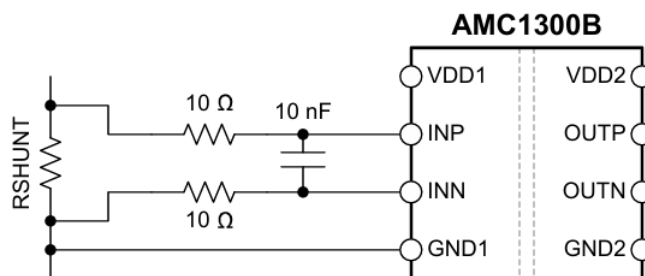


Figure 4. Input Filter for an FDA Input

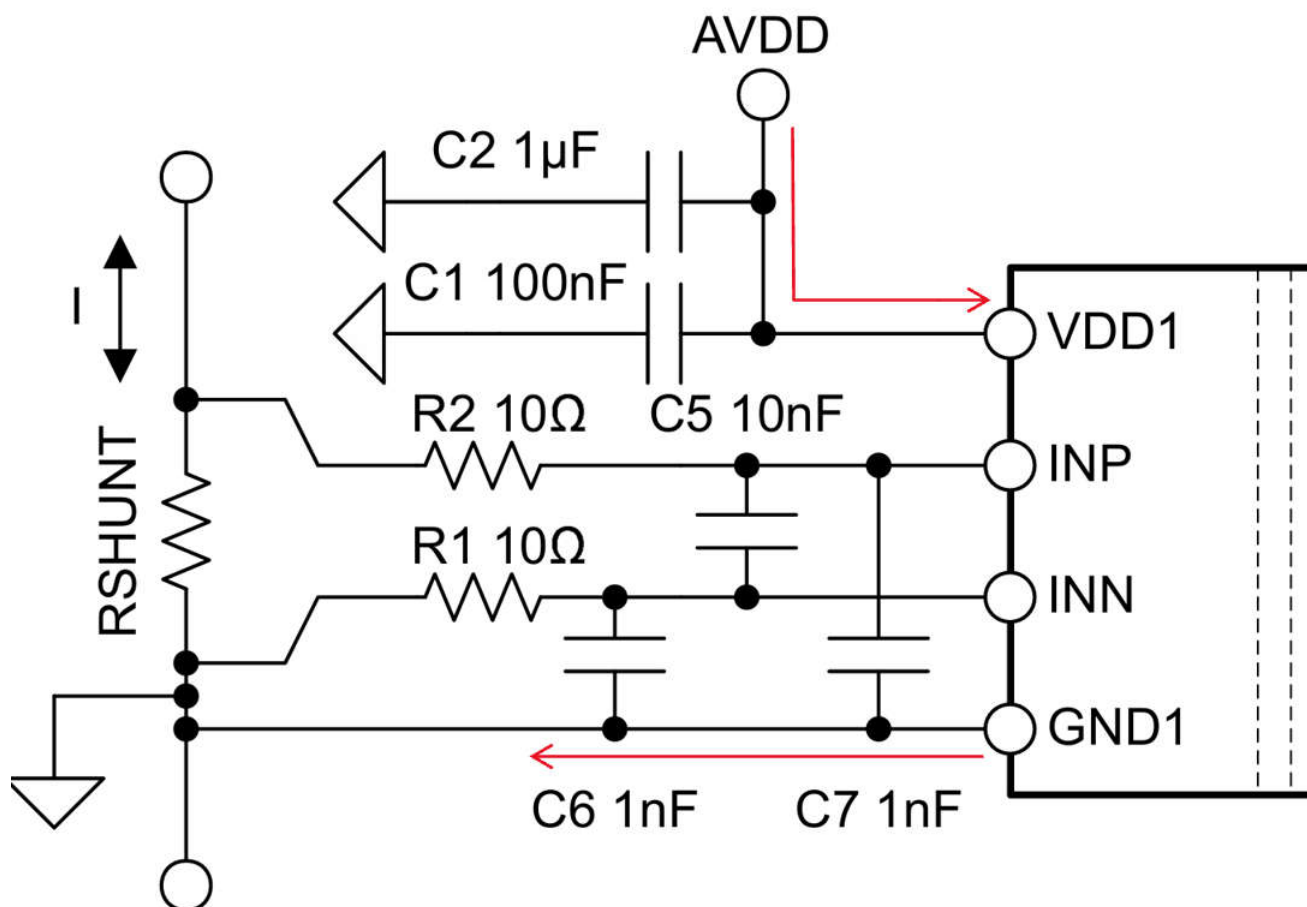


Figure 5. Example High-Side Current Path

It must be noted that a separate trace path should run from the shunt resistor to INN and to GND1. Do not short INN and GND1 together. GND1 is the return path for current flowing into the device, primarily from VDD1. This return current will cause a small but measurable voltage drop on the return path trace. If this voltage drop is coupled onto the INN pin, it will cause errors in the current sense measurements.

This diagram shows an example of the current path on the high side of the circuit. A large current runs into the device at VDD1 and out of the device at GND1. This induces a small voltage across the GND1 trace. If GND1 were shorted to INN, this voltage would be measured and lead to inaccuracies in measurements.

References

- [AMC1306 to AMC0306 Migration Guide](#)

Trademarks

All trademarks are the property of their respective owners.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you fully indemnify TI and its representatives against any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#), [TI's General Quality Guidelines](#), or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products. Unless TI explicitly designates a product as custom or customer-specified, TI products are standard, catalog, general purpose devices.

TI objects to and rejects any additional or different terms you may propose.

Copyright © 2026, Texas Instruments Incorporated

Last updated 10/2025