

Application Brief

Current Sensing in Mobile Robots



Kyle Stone

Current Sensing

Introduction

Mobile robots are widely used in warehouse settings. These mobile robots help to increase efficiency within warehouses by moving quickly around a facility and collecting items that are needed to fulfill orders in a timely manner. By using these mobile robots, warehouse operators can have reduced overhead cost, a continuous faster output, and warehouses can potentially be organized in more efficient configurations, as these mobile robots can reach places humans cannot easily access.

Mobile robots start at their home base where robots are charged and are stored. When the robot is called upon, the robot can move around the warehouse to pick up the requested items, and bring those items to a desired location, where either a human or another robot such as industrial robot can take the items to an assembly line or shipping line. The mobile robot typically uses brushless DC motors to move. An accurate phase current sensing is critical in motor control. A poor current sensing can lead to large torque ripple, audible noise, and inefficiency. [Figure 1](#) illustrates where current sensing plays a role in motor-drive applications.

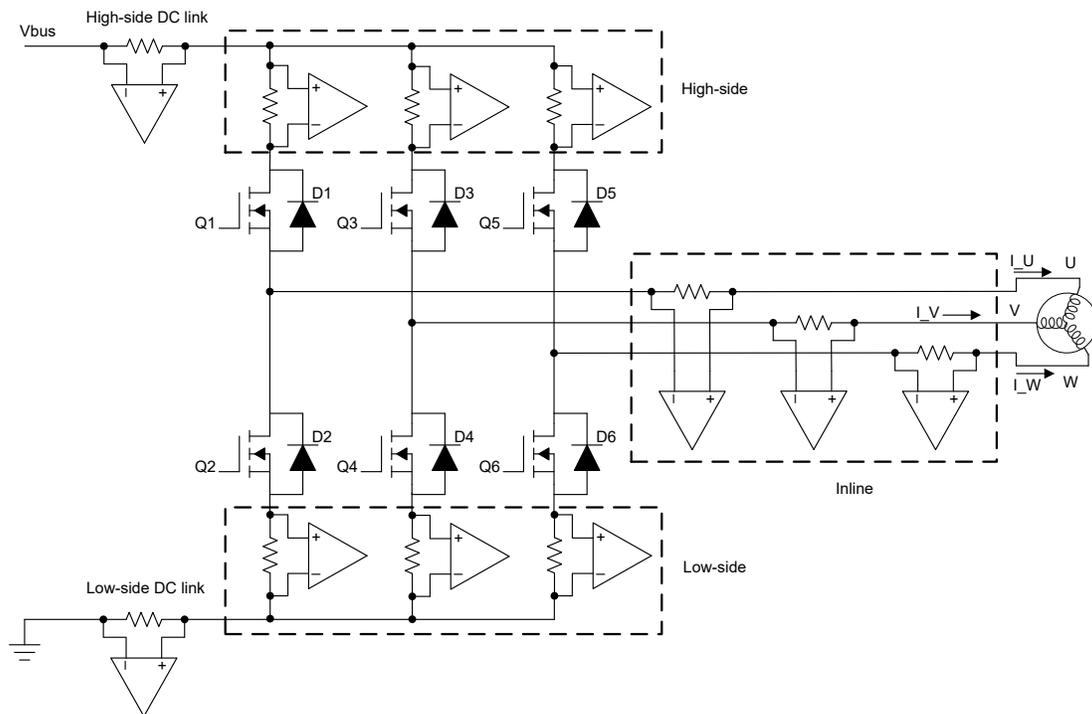


Figure 1. Methods of Motor Current Sensing in Mobile Robots

There are three methods of motor current sensing with their own positives and negatives as shown in [Table 1](#). The best location to measure the motor current is directly in-line with each phase due to continuity of signal measurement and direct correlation to the phase currents. In-line current sensing comes with the challenge where each motor phase is subjected to common-mode voltage transitions that can switch between large voltage levels over very short time periods. Current measurement in other locations, such as the low-side of each phase, requires recombination and processing before meaningful data can be utilized by the control

algorithm. [INA241A](#) is designed for in-line motor current sensing. [INA241A](#) offers high CMRR of 166 dB and enhanced PWM rejection allowing for minimal error at the output in switching systems.

Table 1. Current Sensing in an H-Bridge

Current Measurement	Positives	Negatives
High-side	Detect shorted load from battery for diagnostics	High voltage common-mode amplifier
Inline	Direct motor current measurement, low bandwidth amplifier	High dv/dt signals. PWM settling time.
Low-side	Low cost, low common-mode voltage	Unable to detect shorted load.

The mobile robots typically have onboard 48-V lithium-ion batteries, and can be charged wirelessly or wired. Charging currents and discharging currents can be monitored through Texas Instruments' line of digital power monitors such as the [INA228](#) and [INA238](#). The [INA228](#) can monitor current, voltage, power, energy, or charge up to 85-V common-mode input range with 20-bit resolution through an I2C output. This allows for the robot to monitor the battery levels to the onboard computer. [INA228](#) can monitor battery level and when the battery level runs low, the mobile robot can report back to the home base to be re-charged.

There are several other subsystems within the mobile robot, such as DC/DC converters, onboard computers, lighting systems, radars, and so forth, that can use current sensing. DC/DC converters can use current monitors in the system such as the [INA296A](#) to monitor the safe level of current and to make the system more efficient. The onboard computer is the brain of the mobile robot, and typically operates on a 5-V rail. The onboard computer can leverage current sensing with a digital power monitor such as the [INA219](#), to monitor current and voltage into the system to report back health or power usage in the system. Current monitors can also be used to monitor various peripherals on the robot such as the lighting and radar systems.

Using current monitors can verify these subsystems are operating correctly for safely preventing an incident with a human or physical structure. Monitoring current through the peripheral systems can enable the system to detect a malfunction and can have the robot return to home base for maintenance. The [INA281](#) or [INA296A](#) can be used to monitor the current flow in these peripherals. [Figure 2](#) shows one possible way current sensing can be used in point-of-load (POL) applications where understanding the current going to a specific load in the system is important. This can be used for diagnostics, safety, and protection.

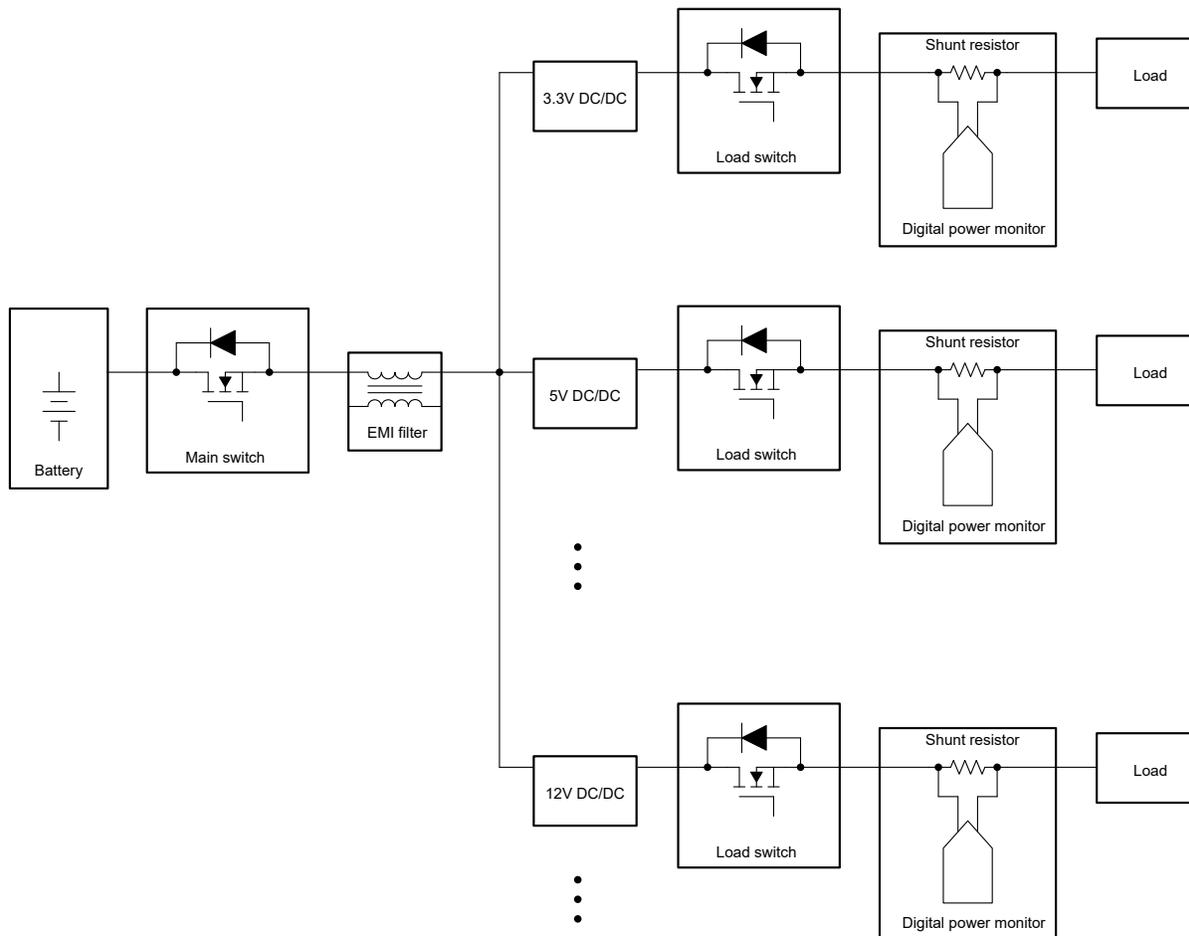


Figure 2. Power Monitoring at POL for Power System in Robotics

Conclusion

In conclusion, mobile robots are generally used in warehousing settings to reduce human involvement and speed up the movement of goods within the facility. Safety and efficiency are critical components of mobile robots. Leveraging various current-sensing techniques within the subsystems in motors, batteries, onboard computers, and peripheral systems can help these robots to operate safely and efficiently.

Alternate Device Recommendations

The [INA241B](#) is a high-precision, accurate analog current-sense amplifier. [INA241B](#) can be used in high-voltage bidirectional applications paired with 1.1-MHz bandwidth to offer fast response time with precise control for in-line control within H-bridge applications. The [INA241B](#) can measure currents at common-mode voltages of -5 V to 110 V and survive voltages between -20 V to 120 V, making the [INA241B](#) device an excellent choice for many systems.

The [INA253](#) is an ultra-precise current-sense amplifier with an integrated low-inductive, precision 2-m Ω shunt with an accuracy of 0.1% and a temperature drift of < 15 ppm/ $^{\circ}$ C. The [INA253](#) is limited to applications that need $< \pm 15$ A of continuous current at $T_A = 85^{\circ}$ C. The [INA253](#) integrated shunt is internally Kelvin-connected to the [INA240](#) amplifier. The [INA253](#) provides the performance benefits of the [INA240](#) amplifier with the inclusion of a precision shunt providing a total uncalibrated system gain accuracy of $< 0.2\%$.

The [INA281](#) can be used in high-voltage applications such as high-side current sensing in a motor. The [INA281](#) can measure currents at common-mode voltages of -4 V to 110 V and survive voltages between -20 V to 120 V, making the device versatile for a variety of applications where voltage can swing negative.

An option for low-side sensing is the [INA381](#) which is a cost-optimized current-sense amplifier with an integrated comparator which serves to reduce PCB footprint size and simplifies design.

Table 2. Alternate Device Recommendations

Device	Optimized Parameter	Performance Trade-Off
INA241B	V_{cm} range: -5 V to 110 V Bidirectional	Slightly lower accuracy compared to INA241A
INA281	V_{cm} range: -4 V to 110 V	Unidirectional
INA381	Integrated Comparator	V_{cm} limited to 26 V
INA253	Integrated shunt 2 m Ω , V_{CM} range: -4 V to 80 V	± 15 -A maximum continuous current

Table 3. Related TI Application Briefs

Literature Number	Description
SBOA160	Low-Drift, Precision, In-Line Motor Current Measurements With PWM Rejection
SBOA176	Switching Power Supply Current Measurements
SBOA163	High-Side Current Overcurrent Protection Monitoring
SBOA555	Current Sensing in Collaborative and Industrial Robotic Arms

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2022, Texas Instruments Incorporated