TI-RSLKMAX

Texas Instruments Robotics System Learning Kit





Module 2

Introduction: Voltage, Current and Power

Introduction: Voltage, Current and Power

Educational Objectives:

REVIEW Electric circuits with resistors, capacitors and inductors **UNDERSTAND** Voltage, current, and power **EXPLORE** Behavior of resistors, capacitors, and LEDs **LEARN** How to use an oscilloscope **MEASURE** Voltage and current in resistors, capacitors and LED

Prerequisites (Module 1)

Running code on the LaunchPad (Module 1)

Recommended reading materials for students:

 Chapter 4, Embedded Systems: Introduction to Robotics, Jonathan W. Valvano, ISBN: 9781074544300, copyright © 2019

This module serves as a brief overview of the electrical engineering terms used in the circuits of this class. As a prerequisite of this course, we expect the students to have basic understanding of resistors, capacitors, and inductors. The electrical circuits for the robot explorer are either given or very simple, so this course does not entail circuit design. However, students will need to understand voltage, current, and power as they apply to these circuits. This module presents formal definitions of voltage, current, and power. The lab provides a simple means to discover these parameters for resistors, capacitors, and LEDs.

A **circuit** is mechanism we use to describe electrical systems, which include a power source (e.g., battery), the electrical components (e.g., resistors, LEDs, capacitors, sensors, transistors, motors etc.) and the interconnection of the components (e.g., wires or printed circuit board). **Voltage** (V) is an electrical term representing the potential difference between two points. The units of voltage are volts (V), and it is always measured as a difference. Voltage is the electromotive force or potential to produce current.

Another important parameter occurring when current flows through a device is **power**. The power (P in watts) dissipated in a device can be calculated as the product of voltage (V in volts) times current (I in amps). Interestingly, although voltage has a polarity (+ and –) and current has a direction, power has neither a polarity nor a direction. Resistors, capacitors, LEDs, and motors dissipate power in different ways.

The **energy** (E in joules) stored in a battery can be calculated from voltage (V in volts), current (I in amps), and time (t in seconds). Energy has neither polarity nor direction.

An **oscilloscope**, or scope, graphically displays information about an electronic circuit, where the voltage amplitude versus time is displayed. A scope has one or more channels, with many ways to trigger or capture data. A scope is particularly useful when interfacing sensors and actuators to the robot explorer.

A **signal generator** is a device that creates a voltage versus time output. Example waveform shapes are square waves, pulses and sine waves. Some generators allow you to control frequency and voltages of these waves.

In the lab associated with this module, you will build some simple circuit with resistors, capacitors, and LEDs. Using a voltmeter and current meter, you will study the steady state response (direct current, **DC**) of resistor and LED circuits. In this way, you can discover voltage, current and power. Using a signal generator and an oscilloscope, you will study the transient response (alternating current, **AC**) of the resistor/capacitor circuits.

Current (I) is defined as the movement of electrons. Current is directional and measured at one point as the number of electrons travelling per second. Current has amplitude and a direction. Because electrons are negatively charged, if the electrons are moving to the left, we define current as flowing to the right.

ti.com/rslk



IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2019, Texas Instruments Incorporated