

Optimizing Transient Response of Internally Compensated dc-dc Converters With Feedforward Capacitor



Brian Butterfield

PMP- Portable Power

Abstract

This application report describes how to choose the feedforward capacitor value (C_{ff}) of internally compensated dc-dc power supplies to achieve optimum transient response. The described procedure in this application report provides guidance in optimizing transient response by increasing converter bandwidth while retaining acceptable phase margin. This document is intended for all power supply designers who want to optimize the transient response of a working, internally compensated dc-dc converter.

Table of Contents

1 Introduction	2
2 Feedback Network With and Without the Feedforward Capacitor	3
2.1 Feedforward Capacitor Value Optimization Process	5
2.2 Determining the Crossover Frequency	5
2.3 Determining the Crossover Frequency Using Frequency Analysis	7
2.4 Calculating the Feedforward Capacitor for Optimum Loop Response	8
2.5 Improvement	9
2.6 Optimizing Toward a Faster Loop At the Expense of Less Phase Margin	9
2.7 Optimizing Toward Greater Phase Margin for Less Ringing	10
3 Conclusion	12
4 References	12
5 Revision History	12

List of Figures

Figure 2-1. Feedback Network Consisting of Two Bias Resistors Used to Set Output Voltage	3
Figure 2-2. Standard Feedback Divider Transfer Function	3
Figure 2-3. Feedback Network With Addition of Feedforward Capacitor	3
Figure 2-4. Standard Feedback Divider With Feedforward Capacitor Transfer Function	4
Figure 2-5. Internally Compensated Converter Without Feedforward Capacitor	5
Figure 2-6. Tip and Barrel Measurement Technique	6
Figure 2-7. Voltage Transient in Response to Load Transient Without Feedforward Capacitor	6
Figure 2-8. Step Response vs Loop Phase Margin	7
Figure 2-9. Loop Gain and Phase Plot of TPS61081 Circuit Without Feedforward Capacitor	7
Figure 2-10. Voltage Transient in Response to a Load Transient With 82-pF Feedforward Capacitor	9
Figure 2-11. Loop Gain and Phase Plot of TPS61081 Circuit With 82-pF Feedforward Capacitor	9
Figure 2-12. Voltage Transient in Response to a 0 to 100% Load Transient With 1000-pF Feedforward Capacitor	10
Figure 2-13. Loop Gain and Phase Plot of TPS61081 Circuit With 1000-pF Feedforward Capacitor	10
Figure 2-14. Voltage Transient in Response to Load Transient With 33-pF Feedforward Capacitor	11
Figure 2-15. Loop Gain and Phase Plot of TPS61081 Circuit With 33-pF Feedforward Capacitor	11

1 Introduction

Internally compensated dc-dc converters allow designers to save time in the design and in debug processes by minimizing the number of external components that they must select. This simplification inherently narrows a designer's ability to optimize the transient response of the converter. However, with some internally compensated converters, the use of a feedforward capacitor in the feedback network is recommended, but only general guidance is provided for choosing this capacitor value to improve transient response. With measured transient or loop characteristics of a working dc-dc converter, a feedforward capacitor value can be chosen such that the converter bandwidth is significantly improved while still maintaining adequate phase margin. Furthermore, with a better understanding of the feedforward capacitor, the designer can go one step further to optimize either higher bandwidth or greater phase margin to meet specific performance requirements.

2 Feedback Network With and Without the Feedforward Capacitor

Without a feedforward capacitor, the feedback network of an internally compensated dc-dc converter consists of two feedback resistors used to set the output voltage of the converter, as shown in Figure 2-1. Figure 2-2 shows the corresponding gain and phase plot.

 


Figure 2-1. Feedback Network Consisting of Two Bias Resistors Used to Set Output Voltage

 


Figure 2-2. Standard Feedback Divider Transfer Function

Figure 2-3 shows the addition of the feedforward capacitor, C1 (C_{ff}), in the feedback network and Figure 2-4 shows the corresponding gain and phase plot. With the addition of the feedforward capacitor network, the converter can more effectively respond to high-frequency disturbances on the output voltage rail. The bode plots in Figure 2-2 and Figure 2-4 show that the responses of each feedback network are identical at lower frequencies. At mid-to-higher frequencies, disturbances on the output rail are attenuated less as the impedance path through C1 decreases and effectively provides a boost in gain and phase. In a working power supply, the increased gain and phase correlates to the converter responding faster to transient loads because the voltage deviation, sensed at the feedback node, is attenuated less at higher frequencies. The converter reacts by adjusting the duty cycle to more quickly correct the output voltage deviation.

 


Figure 2-3. Feedback Network With Addition of Feedforward Capacitor

Although C_{ff} introduces a gain boost after its zero frequency, loop phase boost is at a maximum between the zero and pole frequencies; see the following Equation 1 and Equation 2. Increasing the value of C_{ff} shifts the

zero and pole in Equation 1 to lower frequencies, and decreasing the value C_{ff} shifts the zero and pole to higher frequencies. The gain at dc is set by R_1 and R_2 . The following equations calculate the pole, zero, and the dc gain of the feedback network as is shown in Figure 2-4.

$$f_z = \frac{1}{2\pi \times R_1 \times C_{ff}} \quad (1)$$

Equation 1 calculates the zero frequency based on the feedforward capacitor value and the top bias resistor, R_1 . f_z is shown on the plot in Figure 2-4.

$$f_p = \frac{1}{2\pi \times C_{ff} \left(\frac{1}{R_2} + \frac{1}{R_1} \right)} \quad (2)$$

Equation 2 calculates the pole frequency based on the feedforward capacitor value and both top and bottom bias resistors, R_1 and R_2 . f_p is shown in on the plot in Figure 2-4.

The transfer function is plotted as:

 


Figure 2-4. Standard Feedback Divider With Feedforward Capacitor Transfer Function

To optimize transient response, a C_{ff} value is chosen such that the gain and phase boost of the feedback increases the bandwidth of the converter, while still maintaining an acceptable phase margin. In general, larger values of C_{ff} provide greater bandwidth improvements. However, if C_{ff} is too large, the feedforward capacitor causes the loop gain to crossover too high in frequency and the C_{ff} phase boost contribution is insufficient, resulting in unacceptable phase margin or instability. Recommended limitations of C_{ff} is discussed later in this document.

2.1 Feedforward Capacitor Value Optimization Process

The following process outlines a step-by-step procedure for optimizing the feedforward capacitor.

1. Determine the crossover frequency of an internally compensated dc-dc converter with an unpopulated feedforward capacitor (f_{nocff}). In certain circumstance, this can be calculated, but for this application report, this optimization procedure is based on measured converter characteristics. You can determine the crossover frequency (converter bandwidth) with transient analysis or by using a network analyzer. Both methods are shown.
2. Once the crossover frequency is known, a few equations allow calculation of a feedforward capacitor value which prompts a good compromise between bandwidth improvement and acceptable phase margin. Improvement in transient and loop response is shown with transient analysis and frequency analysis to confirm the design.
3. If the designer chooses to optimize for higher bandwidth or increased phase margin (more damping), guidance is provided.

2.2 Determining the Crossover Frequency

The TPS61081 is used in this example to determine the crossover frequency. This example can be applied to other internally compensated dc-dc converters which recommend external feedforward capacitors in the feedback network.

After using the data sheet guidelines to choose all appropriate external components, remove the feedforward capacitor, and measure the converters crossover frequency by using transient analysis or a network analyzer. Note that to determine the crossover frequency, f_{nocff} , the feedforward capacitor must be left open as shown in Figure 2-5.

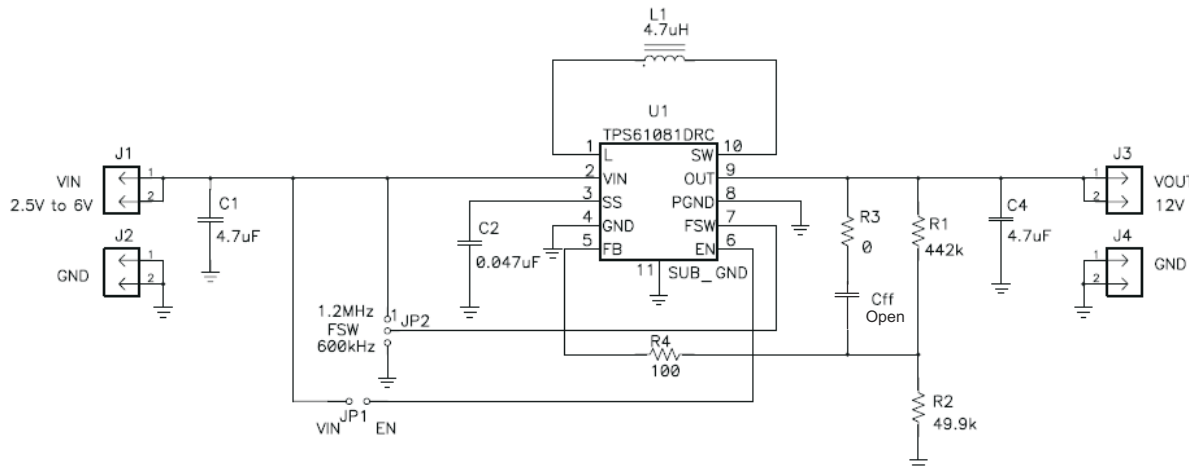


Figure 2-5. Internally Compensated Converter Without Feedforward Capacitor

Figure 2-6 shows the tip and barrel measurement method set up for transient analysis. A transient load is connected to the output of the power supply circuit, while a current probe measures the transient load current, and a tip and barrel voltage probe measures the voltage deviation during transient load conditions on the output.

 


Figure 2-6. Tip and Barrel Measurement Technique

The tip and barrel measurement technique in [Figure 2-6](#) is used to minimize coupling magnetic fields and obtain a more accurate voltage waveform during transient load transitions. TP14 is connected to the measured signal whereas TP15 is connected to ground. TP14 and TP15 are not shown in [Figure 2-5](#). If the power supply does not include the appropriate test points, the test points can be strategically placed using bus wire. It is recommended that the bus wire test points be tacked onto the converter output capacitor closest to the load. [Figure 2-7](#) shows the TPS61081 transient response as measured with the tip and barrel technique. The plots are taken using the TPS61081EVM-147 with $V_{in} = 5\text{ V}$, $V_{out} = 12\text{ V}$, and a load transient from 0 mA to 160 mA.

 


Figure 2-7. Voltage Transient in Response to Load Transient Without Feedforward Capacitor

About 0.9 V of output voltage deviation from the dc voltage set point is observed. The voltage waveform in [Figure 2-7](#) provides insight to the converter crossover frequency as described in [Evaluation and Performance Optimization of Fully Integrated DC/DC Converters](#) (Topic 7 of the 2006 Portable Power Design Seminar). The frequency of the voltage deviation waveform in response to a load transient is related to the crossover frequency of the converter. Using the oscilloscope's cursors, the crossover frequency is approximated. The frequency of the transient ripple in this example is approximately 15 kHz. Note that the voltage deviation begins to correct 30 μs after the transient occurs. As the crossover frequency of the converter is increased, it is confirmed that the converter response is improved as the voltage deviation begins to correct in less time, resulting in less voltage deviation.

 


Figure 2-8. Step Response vs Loop Phase Margin

Using [Figure 2-8](#) from the 2006 Portable Power Design Seminar topic paper *Evaluation and Performance Optimization of Fully Integrated DC/DC Converters*, the phase margin of the loop can be adequately approximated. Comparing the two plots, the TPS61081 measured the transient response most resembling the number of oscillations of the blue trace with just slightly more oscillation. This means that the measured loop has just slightly less than 30° of phase margin.

2.3 Determining the Crossover Frequency Using Frequency Analysis

Because frequency analysis equipment is costly, using such equipment is not always an option. However, when such equipment is available, the crossover frequency can be quickly measured. This method is more accurate than the transient analysis approximation and should be used when possible. [Figure 2-9](#) shows the frequency analysis of the control loop for the example circuit in [Figure 2-5](#).

 


Figure 2-9. Loop Gain and Phase Plot of TPS61081 Circuit Without Feedforward Capacitor

Once the loop gain and phase plot is obtained with a network analyzer, the crossover frequency is quickly noted. The phase margin is 28° which confirms the transient analysis approximation of being just less than 30°. The crossover frequency also is measured at 16 kHz which is close to the 15-kHz approximation.

2.4 Calculating the Feedforward Capacitor for Optimum Loop Response

With the crossover frequency with no Cff identified (f_{nocff}), the value of Cff can be calculated for optimum transient response by choosing Cff such that the zero and pole frequency geometrically straddle f_{nocff} .

$f_{\text{nocff}} = 16 \text{ kHz}$ Converter crossover frequency with no Cff
 $R1 = 442 \text{ k}\Omega$ $R2 = 49.9 \text{ k}\Omega$

R1 and R2 are the feedback bias resistors used to set the output voltage of the converter as shown in [Figure 2-5](#).

[Equation 3](#) calculates the geometric mean of the feedback network's zero and pole frequencies. The geometric mean frequency equation is used to calculate the frequency where the phase boost from the zero and pole is at a maximum. However, because Cff is currently unknown, equations f_z and f_p are left in variable form.

$$F_{\text{geometric_mean}} = \sqrt{(f_z \times f_p)} \quad (3)$$

[Equation 4](#) sets the geometric mean frequency equal to the converter crossover frequency with no Cff.

$$f_{\text{noCff}} = \sqrt{(f_z \times f_p)} \quad (4)$$

Setting the geometric mean frequency equal to the converter crossover frequency with no Cff positions the maximum phase boost of Cff at f_{nocff} . However, because Cff introduces a boost in phase and in gain, the new crossover frequency occurs at a frequency greater than the geometric mean frequency. Therefore, the new converter crossover frequency does not occur at the maximum phase boost frequency due to Cff, but crosses over at a higher frequency facilitating a faster converter response time, while still benefitting from additional phase boost. The following plots confirm that the converter response time does indeed improve, and as a result, less transient voltage deviation is observed.

Substituting [Equation 1](#) and [Equation 2](#) into [Equation 4](#) results in [Equation 5](#), which is now a function of R1, R2, and Cff.

$$f_{\text{noCff}} = \sqrt{\left(\frac{1}{2\pi \times R1 \times Cff}\right) \left[\frac{1}{2\pi \times Cff} \left(\frac{1}{R2} + \frac{1}{R1}\right)\right]} \quad (5)$$

Solving for Cff results in a feedforward capacitor value for optimum transient response, Cff_op.

$$Cff_{\text{op}} = \frac{1}{2\pi \times f_{\text{nocff}}} \times \sqrt{\frac{1}{R1} \times \left(\frac{1}{R1} + \frac{1}{R2}\right)}$$

$$Cff_{\text{op}} = 7.066 \times 10^{-11} \quad (6)$$

Where $f_{\text{nocff}} = 16 \text{ kHz}$, $R1 = 442 \text{ k}\Omega$, and $R2 = 49.9 \text{ k}\Omega$. Rounding the calculated Cff value up to the next nearest standard capacitor value, rounds to 82 pF.

Cff_std = 82 pF

2.5 Improvement

Figure 2-10 shows the improved transient response with the addition of the 82-pF Cff capacitor. The converter responds in 14 μ s with Cff = 82 pF compared to 30 μ s without Cff. The maximum transient voltage deviation is 377 mV with Cff compared to 900 mV without Cff.

 


Figure 2-10. Voltage Transient in Response to a Load Transient With 82-pF Feedforward Capacitor

 


Figure 2-11. Loop Gain and Phase Plot of TPS61081 Circuit With 82-pF Feedforward Capacitor

Figure 2-11 shows that the network analyzer also confirms the improved bandwidth with adequate phase margin. For this example, the addition of the Cff capacitor increased the bandwidth by a factor of 3, from 16 kHz to 48 kHz, and increased the phase margin to an acceptable 55°.

For most applications, this is an optimum placement of the feedforward capacitor response. Increasing the feedforward capacitance value pushes both the zero and pole frequencies closer to the origin which increases the crossover frequency but can result in lower overall phase margin. This corresponds to a faster loop at the expense of lower phase margin. Decreasing the Cff value results in the opposite result until a certain point where the feedforward capacitor gain and phase boost contribution diminishes and approaches the response of having no Cff. Having too small a Cff value injects a zero and pole at frequencies too high and effectively too late in loop response, resulting in little or no performance improvement

2.6 Optimizing Toward a Faster Loop At the Expense of Less Phase Margin

To reduce transient ripple even more, the feedforward capacitor value can be increased to push the crossover to higher frequencies. Although this can decrease the voltage deviation even more and speed up loop response, more ringing is observed because less phase boost is added from the feedforward capacitor at

the new crossover frequency. Larger C_{ff} values provide less phase boost because increasing C_{ff} causes the converter to cross over at higher frequencies while the maximum phase boost moves to lower frequencies. It is recommended to keep the feedforward capacitor value smaller than the value which corresponds to 30° of phase margin, so that a phase margin $\geq 30^\circ$ is the minimum phase margin target. This corresponding C_{ff} value limit must be determined empirically, if required. It is generally not recommended to increase C_{ff} significantly greater than the calculated optimized C_{ff} .

Figure 2-12 and Figure 2-13 show the same converter using a 1000-pF feedforward capacitor which is much larger than the initially optimized capacitor value in an attempt to speed up the loop response. It is seen that the converter begins to correct the deviation from dc faster and results in less voltage deviation, at 258 mV. Using the network analyzer, the resulting crossover frequency is improved from 48 kHz to 73 kHz at the expense of lower phase margin, now at 22° , which is lower than that generally recommended. In this transient response, the voltage deviation begins to correct in 9 μ s as opposed to the optimized 14- μ s response.

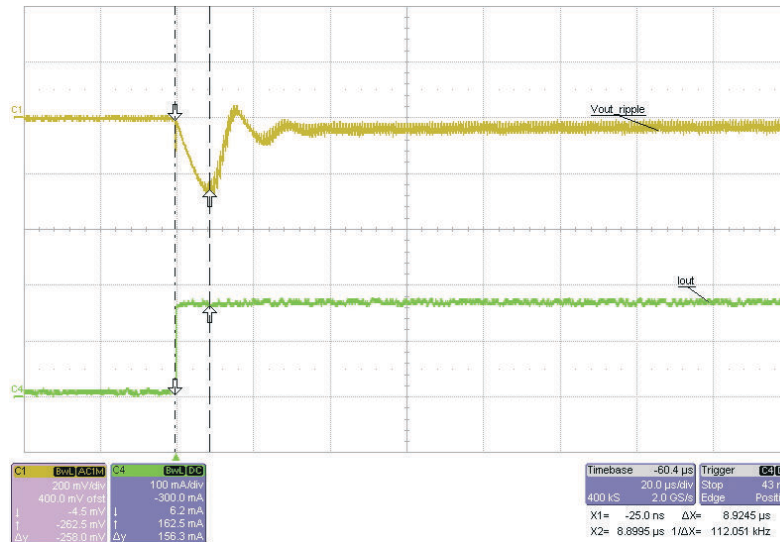


Figure 2-12. Voltage Transient in Response to a 0 to 100% Load Transient With 1000-pF Feedforward Capacitor

 


Figure 2-13. Loop Gain and Phase Plot of TPS61081 Circuit With 1000-pF Feedforward Capacitor

2.7 Optimizing Toward Greater Phase Margin for Less Ringing

Conversely, if more phase margin is desired, a smaller feedforward capacitor allows the loop to crossover at a lower frequency and position the maximum phase boost from the feedforward capacitor closer to the new

crossover frequency, with the tradeoff of lower bandwidth. As the C_{ff} capacitor value is reduced, the bandwidth of the converter approaches the bandwidth of the converter without the feedforward capacitor. Figure 2-14 and Figure 2-15 show the transient and loop response of a converter with the 82-pF C_{ff} replaced with a 33-pF C_{ff} . With only 33 pF, the converters response time has increased to 22 μ s, resulting in a larger transient voltage deviation of 613 mV. This, however, is still better than the 30- μ s response, 900-mV voltage deviation of the converter without the feedforward capacitor. Also, note that a 0-A to full-load transient is very aggressive testing and was used to show more clearly the optimization throughout this application report.

 


Figure 2-14. Voltage Transient in Response to Load Transient With 33-pF Feedforward Capacitor

 


Figure 2-15. Loop Gain and Phase Plot of TPS61081 Circuit With 33-pF Feedforward Capacitor

3 Conclusion

The feedforward capacitor used in the feedback network improves the performance of internally compensated dc-dc converters. The respective data sheet describes how to generally size the feedforward capacitor for improved loop response. However, with measured response characteristics of a working design, the feedforward capacitor can be sized to facilitate an improved transient response. The calculated optimal Cff value can be increased or decreased to optimize the converters transient response for minimum voltage deviation or higher phase margin.

4 References

1. *Evaluation and Performance Optimization of Fully Integrated DC/DC Converters* (Topic 7 of [2006 Portable Power Design Seminar](#))
2. *Using the TPS40040EVM-001: A 12-V Input, 1.8-V Output, 10-A Synchronous Buck Converter User's Guide* (SLUU266)
3. *TPS6108xEVM-147 User's Guide* (SLVU144)
4. *TPS61080/81, High Voltage DC/DC Boost Converter With 0.5-A/1.3-A Integrated Switch* data sheet (SLVS644)

5 Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

Changes from Revision B (November 2017) to Revision C (October, 2026)	Page
• Updated the numbering format for tables, figures, and cross-references throughout the document	1

Changes from Revision A (May 2015) to Revision B (November 2017)	Page
• Changed Figure 2-8	5

Changes from Revision * (January 2008) to Revision A (May 2015)	Page
• Changed From: $[R2/(R1 \times R2)]$ To: $[R2/R1 + R2]$ in Figure 2-2	3

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you fully indemnify TI and its representatives against any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#), [TI's General Quality Guidelines](#), or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products. Unless TI explicitly designates a product as custom or customer-specified, TI products are standard, catalog, general purpose devices.

TI objects to and rejects any additional or different terms you may propose.

Copyright © 2026, Texas Instruments Incorporated

Last updated 10/2025