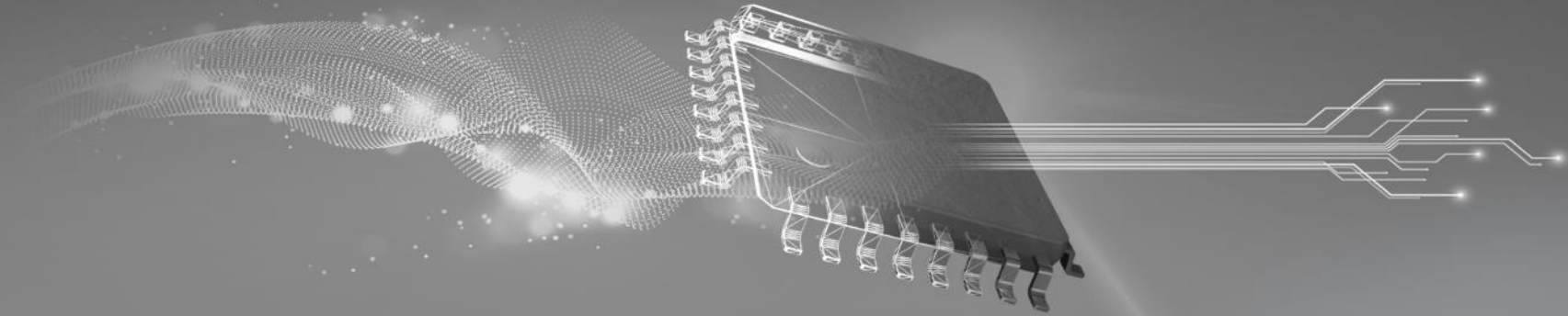


TI TECH DAYS



Calculating and simulating error in current sensing systems


Mubina Toa and Peter Iliya

Current and Position Sensing


Agenda

- Current sensing architectures (5-7min)
- Error analysis (3 min)
- PSPICE simulation (9 min)
- Key current sensing applications (4 min)
- TI current sensing portfolio (4 min)


Current sensing architectures: types

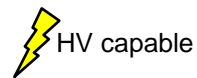


Operational amplifier

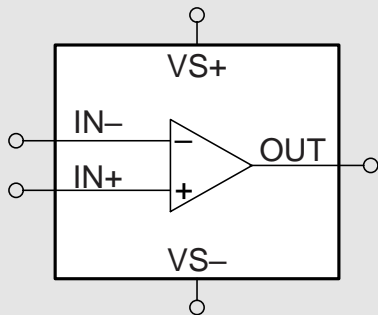


Difference amplifier

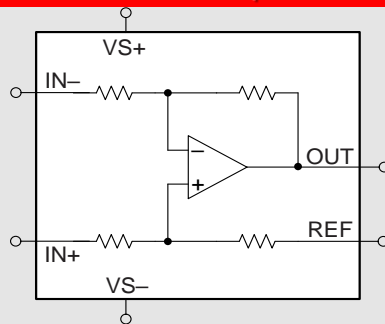


Isolated current sense

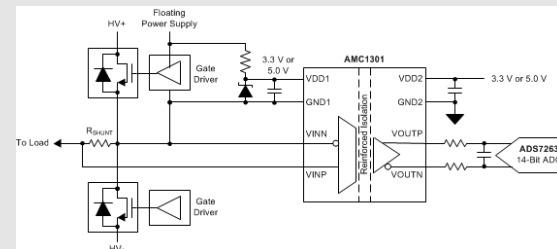


Instrumentation amplifier

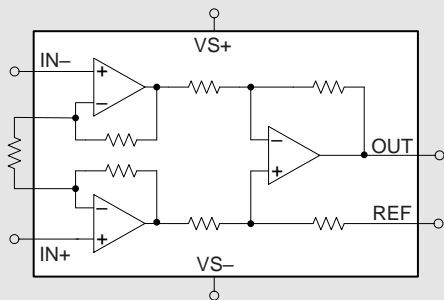


Current sense amplifier

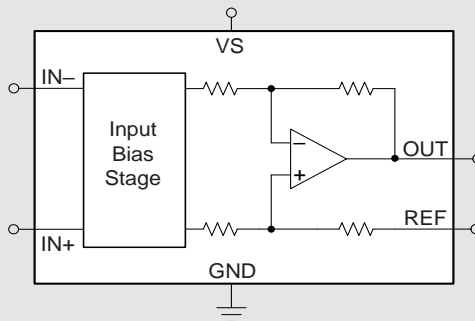

In-package Hall-effect current sensor

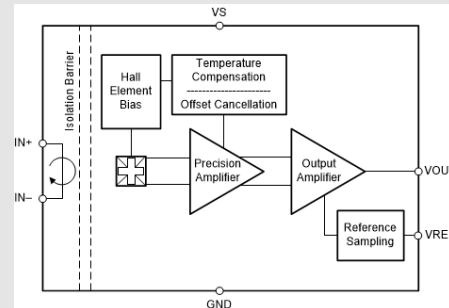

Current sensing architectures: pros and cons

 HV capable

Operational amplifier

Pros

- Large open-loop gain
- Often very low cost

Cons

- Accuracy is set by external components
- Low-side only: $V_{CM} \approx GND$
- With a single-ended input, PCB parasitics will create additional error

Difference amplifier

Pros

- Can tolerate very large common-mode voltages (up to $\pm 275V$ with $\pm 15V$ supply)

Cons

- System impedance < than diff amp input impedances; Resistor network loads sys.
- Low gain requires additional amplifier stage to keep P_{DIS} in shunt reasonable
- Output must be managed to limit output dynamic range to protect downstream circuitry when supporting high V_{CM}

Isolated current sense

Pros

- Extends CM capability by galvanically isolating the input stage from the output
- Enables galvanic isolation even in low voltage (< 100V) apps w/ transients
- Low offset & integrated precision gain network on input enable high accuracy

Cons

- Limited gain options limit shunt resistor options

Instrumentation amplifier

Pros

- Large input impedance allows for measuring very small currents
- Change gain with external resistor

Cons

- Common-mode voltage must remain within supply voltage, $V_{CM} \leq V_S$
- Usually used for low-side sensing, but can be used for high-side depending on common-mode voltage

Current sense amplifier

Pros

- Unique floating input stage topology; V_{CM} can exceed and be independent of V_S
- Precision integrated gain network maximizes accuracy and minimizes drift
- Low offset enables use of low ohmic shunt resistors enabling higher current measurements & minimizing power loss

Cons

- Typically only fixed gain

In-package Hall-effect current sensor


Pros

- Extends common mode capability by galvanically isolating the input stage from the output
- Enables galvanic isolation even in low voltage (< 100V) applications where transients exist that may require isolation

Cons

- Current limited to 30A at 25°C
- Sensitive to stray magnetic fields that can degrade measurement accuracy

TI TECH DAYS

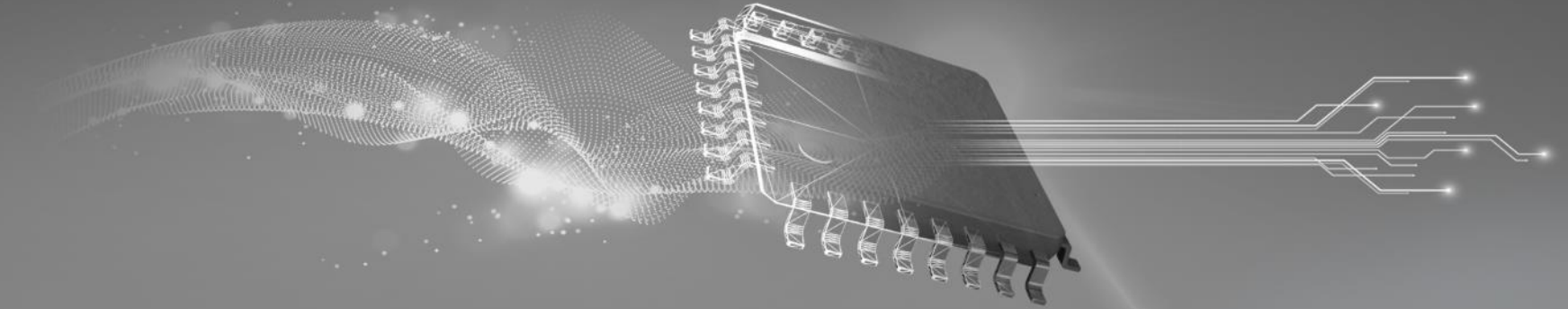

Error analysis (INA228)

Different types of error in current sensing circuits

1. Offset error $\longrightarrow e_{Offset} (\%) \approx e_{Vos} + e_{CMRR} + e_{PSRR}$
2. Gain error $\longrightarrow e_{Gain} (\%) \approx e_{Gain_error} + e_{Linearity} + e_{Shunt_tolerance}$
3. Application error $\longrightarrow e_{Application} (\%) \approx e_{Bias_current} + e_{Other}$

Worst-case total error – more conservative

$$\zeta_{Worst}(\%) \approx e_{Vos} + e_{CMRR} + e_{PSRR} + e_{Gain_error} + e_{Linearity} + e_{Shunt_tolerance} + e_{Bias_current} + e_{Other}$$


Root-sum-square (RSS) total error – more realistic

$$\zeta_{RSS}(\%) \approx \sqrt{e_{Vos}^2 + e_{CMRR}^2 + e_{PSRR}^2 + e_{Gain_error}^2 + e_{Linearity}^2 + e_{Shunt_tolerance}^2 + e_{Bias_current}^2 + e_{Other}^2}$$

INA228 error analysis

Conditions

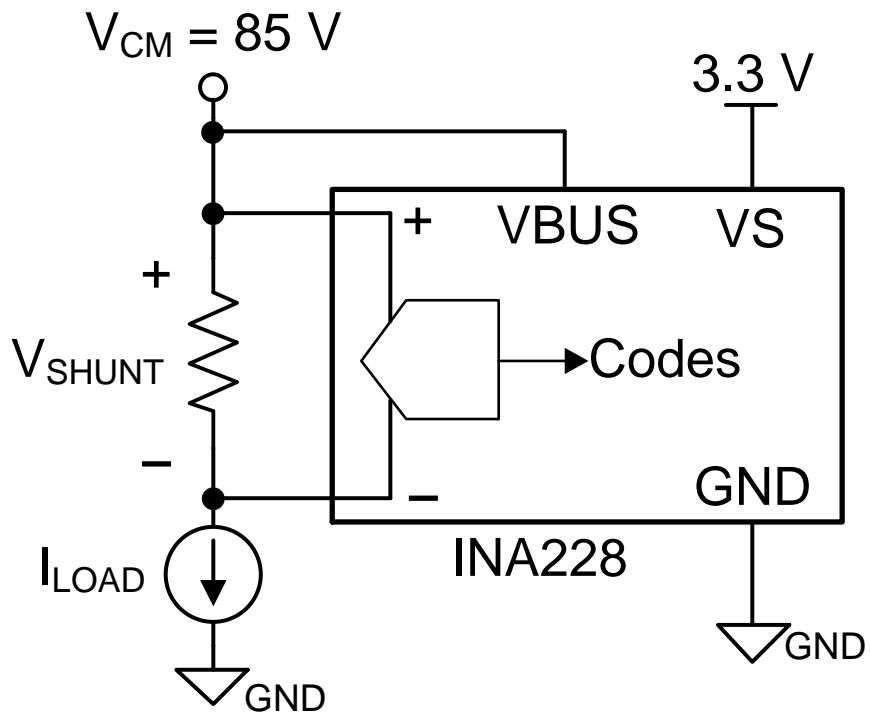- $V_{CM} = 85\text{ V}$
- $V_S = 3.3\text{ V}$
- $T_A = 25^\circ\text{C}$ to 120°C ($\Delta 95^\circ\text{C}$)
- Load = 1 mA to 1 A
- $R_{SHUNT} = 100\text{ m}\Omega$
 - $V_{SHUNT} = 100\text{ }\mu\text{V}$ to 163 mV
- $LSB_{V_{SHUNT}} = 312\text{ nV}$ (ADCRANGE=0)
- ADC conversion time = 4.12 ms
- ADC number of averages = 512



Note: R_{SHUNT} has perfect 0% tolerance in this example

INA228 error analysis example

- Determine the maximum offset for V_{SHUNT} measurement

$$V_{OSI} = \pm 2 \mu V$$

$$V_{OS_CMRR} = |V_{CM} - 48V| * 10^{-\frac{CMRR_{min}}{20dB}} = |85V - 48V| * 10^{-\frac{146}{20dB}} = \pm 1.85 \mu V$$

$$V_{OS_PSRR} = |V_S - 3.3V| * PSRR_{min} = 0$$

$$V_{OS_drift} = |\Delta TA| * \frac{dV_{OS}}{dT} = |95^{\circ}C| * 0.01 \frac{\mu V}{^{\circ}C} = \pm 0.95 \mu V$$

$$V_{OS_Total} = V_{OSI} + V_{OS_CMRR} + V_{OS_PSRR} + V_{OS_drift} = \pm 4.8 \mu V$$

- Determine the maximum ADC gain error for V_{SHUNT} measurement

$$G_{Error_25C} = \pm 0.1\% = \pm 0.001$$

$$G_{Error_drift} = |\Delta TA| * 20ppm = 95^{\circ}C * 20ppm * 10^{-6} = \pm 0.0019$$

$$G_{Error_total} = G_{Error_25C} + G_{Error_drift} = \pm 0.0029$$

INA228 error analysis example

- Convert to digital codes and calculate total error at 1 mA load


$$G_{IDEAL} = \frac{1}{LSB_VSHUNT} = \frac{1}{312\text{ nV}} = 3,076,923 \frac{\text{codes}}{V}$$

$$Codes_{IDEAL_1mA} = V_{SHUNT} * G_{IDEAL} = 1mA * 100m\Omega * 3,076,923 = 307.7\text{ codes}$$


$$Codes_{MAX_1mA} = ROUND[(V_{SHUNT} + VOS) * G_{IDEAL} * (1 + G_{Error_total})] = 323\text{ codes}$$

$$\text{Total Error at 1mA} = 100 * (Codes_{MAX_1mA} - Codes_{IDEAL_1mA}) / Codes_{IDEAL_1mA} = 4.98\%$$

INA228 error analysis example

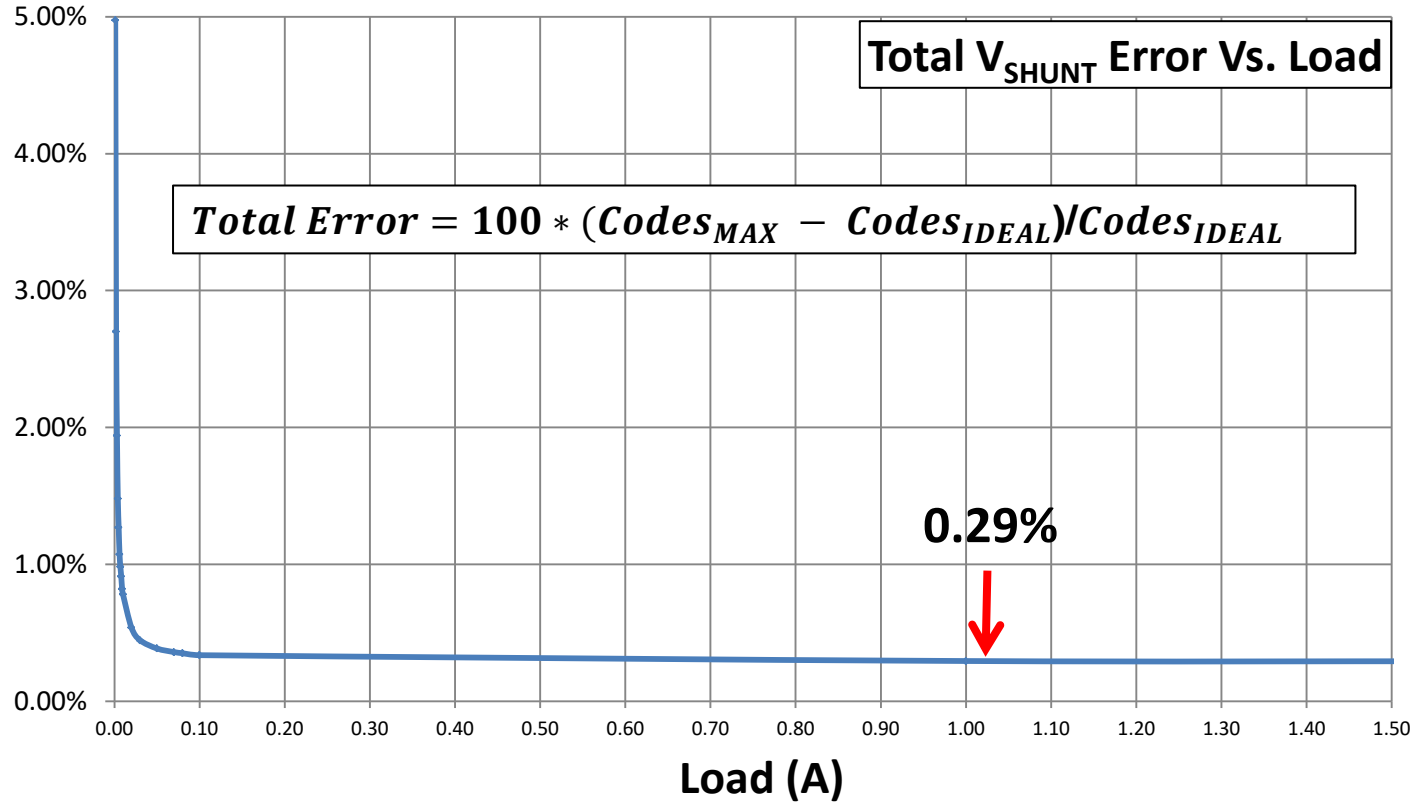

TI TECH DAYS

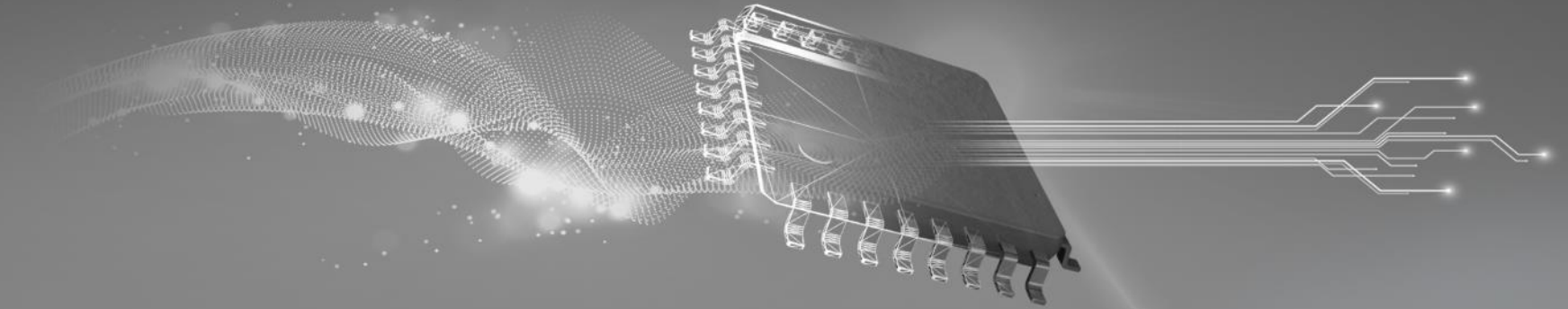

PSPICE simulation with INA293

Simulation models for current sense amplifiers (CSA)

- SPICE models include the following behaviors from datasheet:
 - V_{OS} , gain error, and drift over temperature
 - Input bias and input offset currents
 - Noise density
 - Bandwidth, slew rate
 - Claw curve (Swing-to-rail Versus Output current)
 - AC and DC CMR
 - AC and DC PSR
 - Output impedance (Z_{OUT})
- Most models are behavioral based and not transistor based.
- Models work best for small-signal analyses.



PSPice® for TI

- *In addition to the free TINA-TI software, TI now offers a free simulation and design environment using PSPICE from Cadence.*
- *Includes mixed-signal simulation capability and a full library of pre-loaded models along with links to technical documentation.*

Simulation example - charge bucket filter for ADC

Problem: Solve for R and C to yield $<1/2$ LSB error with SAR ADC.

Advantages:

- Reduce design time.
- Remove need for high-speed buffer amplifier.

CSA model needs:
→ BW & Z_{OUT}

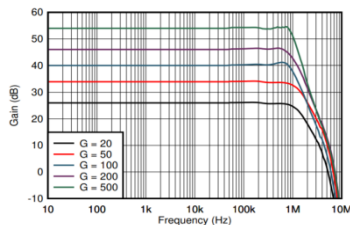


Figure 6-9. Gain vs Frequency



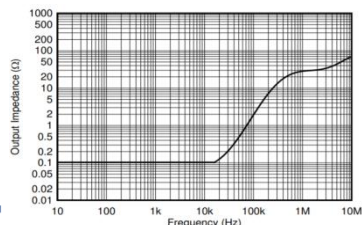


Figure 6-21. Output Impedance vs Frequency

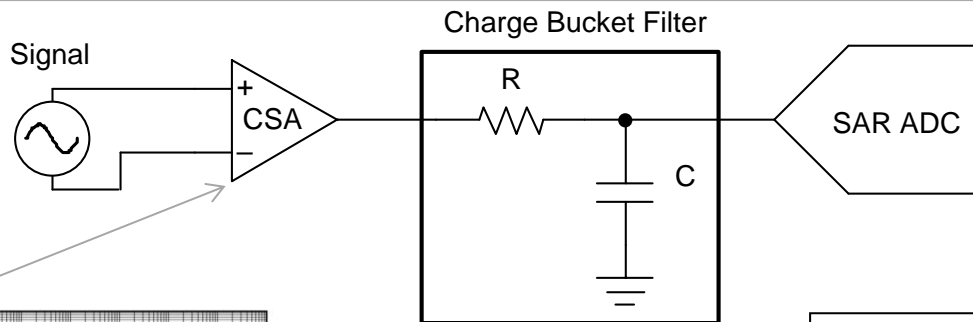

ADC model needs:
→ Input impedance

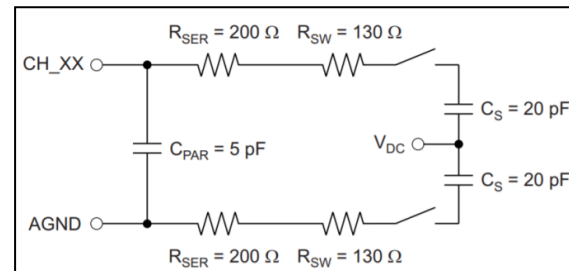

Verify INA293A1 model behavior

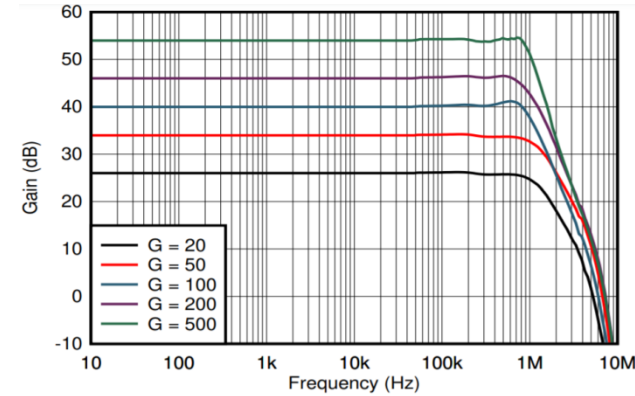
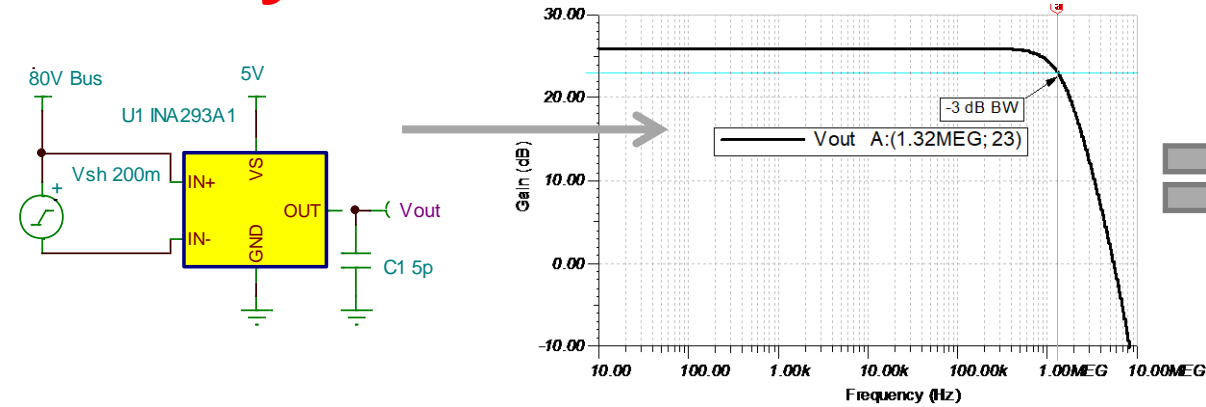


Figure 6-9. Gain vs Frequency



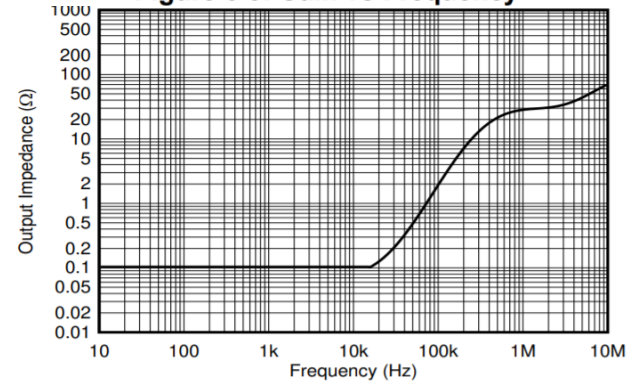
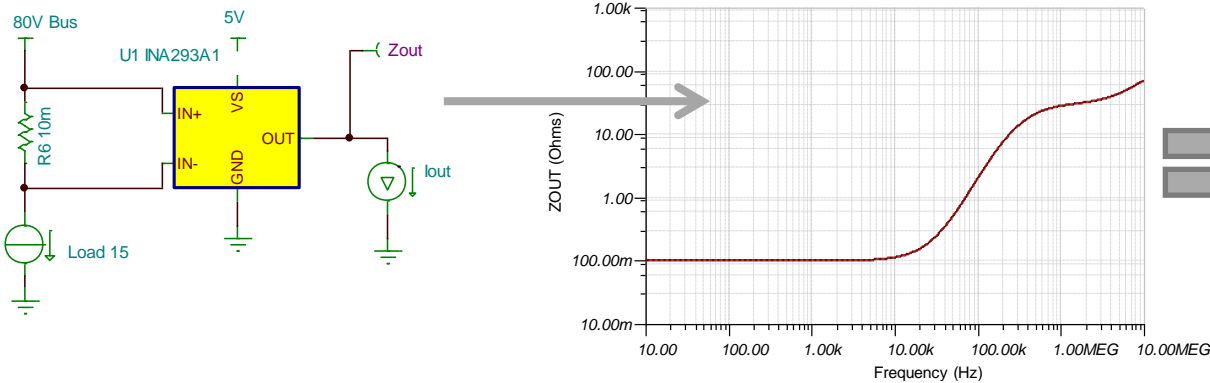


Figure 6-21. Output Impedance vs Frequency

INA293 + ADS8528 with charge bucket

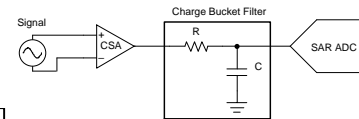

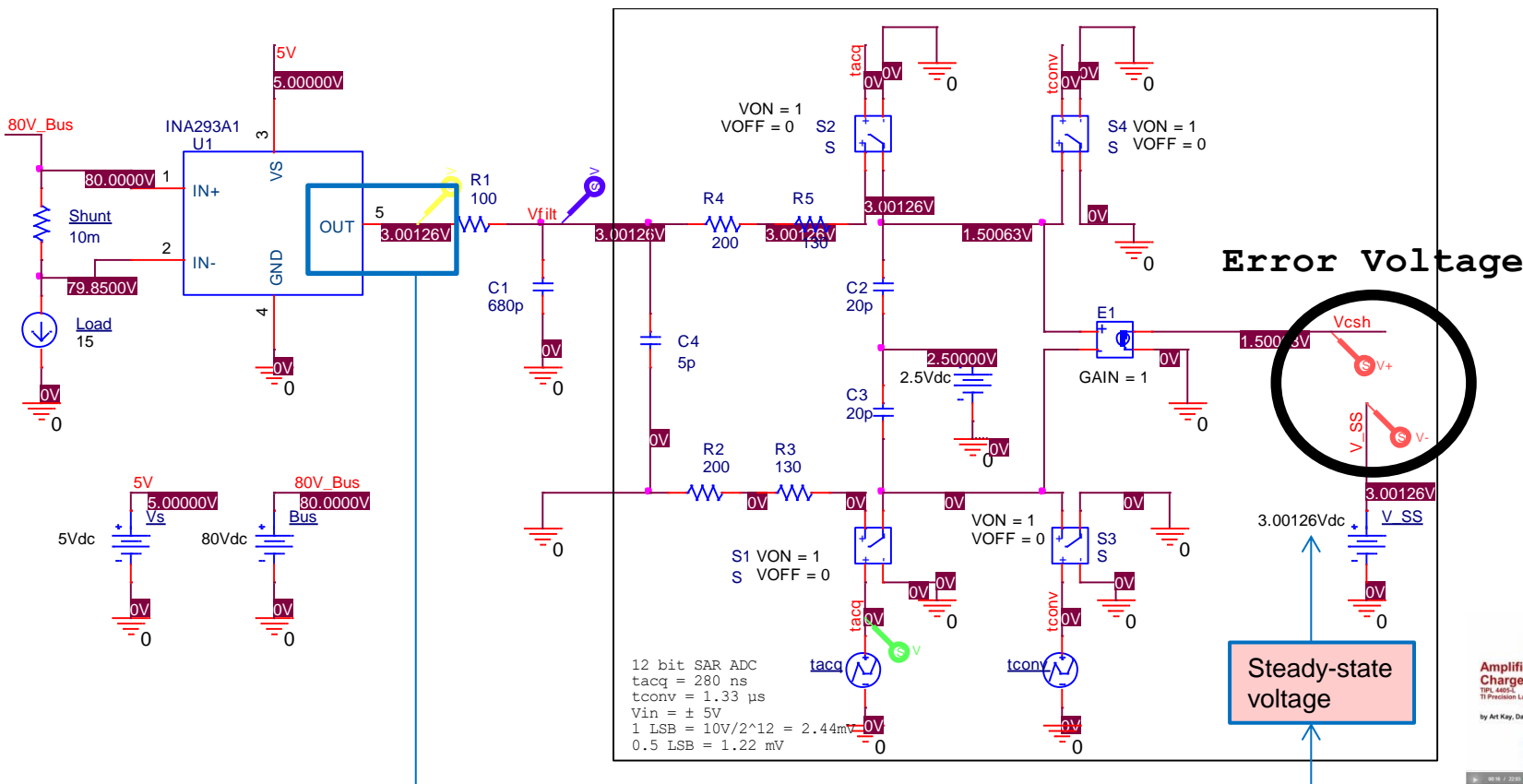
Solve for R and C to yield <1/2 LSB error.



Watch our [training videos](#) for more information.



Transient simulation result

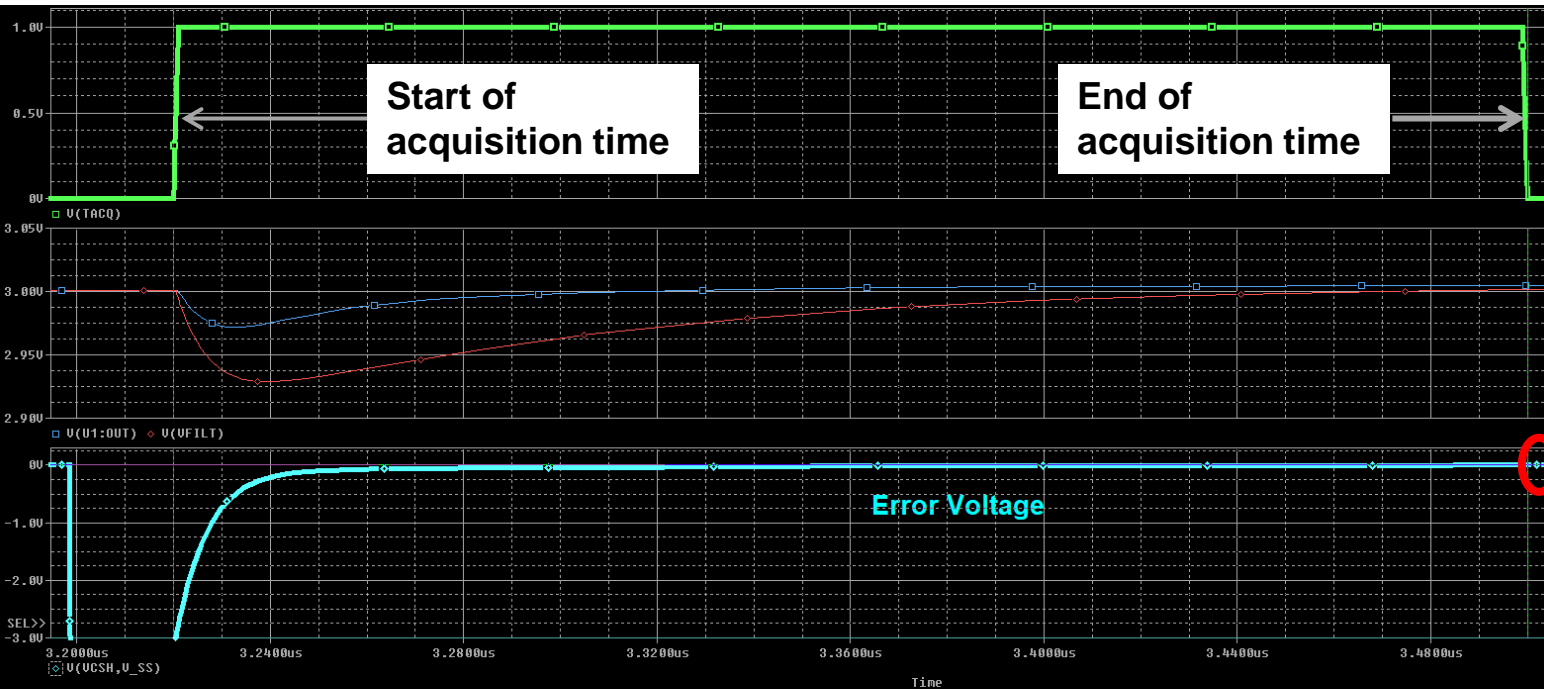


Does the error voltage settle to $< 1.22 \text{ mV}$ at the end of the acquisition time?

150 μV .
Yes, error voltage settles to $< 0.5 \text{ LSB}$.


Trace Color	Trace Name	Y1	Y2	Y1 - Y2	Y1(Cursor1) - Y2(Cursor2)	Max Y	Min Y	Avg Y
	X Values	3.2200u	3.4000u	-280.042n	Y1 - Y1(Cursor1) Y2 - Y2(Cursor2)			
CURSOR 1,2	V(VCSH,V_SS)	-3.0013	150.587u	-3.0014	0.000	150.587u	-3.0013	-1.5006
	V(U1:OUT)	3.0010	3.0045	-3.4834m	6.0023	3.0044	3.0010	3.0028
	V(VFILT)	3.0010	3.0017	-692.992u	6.0023	3.0016	3.0017	3.0014
	V(TACQ)	0.000	-120.000n	120.000n	3.0013	-150.707u	0.000	-120.000n

Comparison to TINA-TI

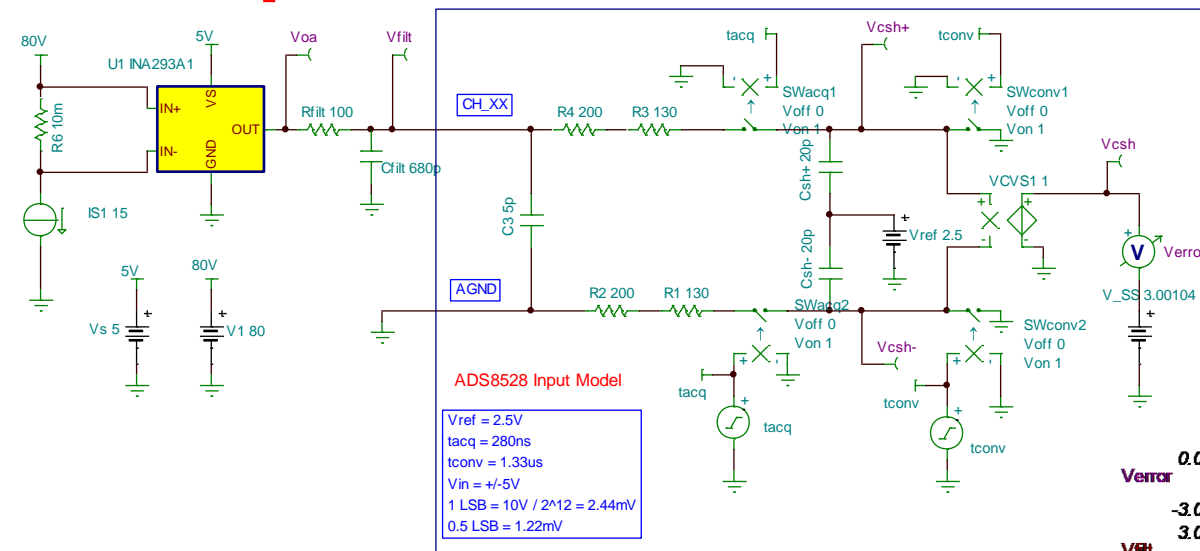Differences between TINA and PSPICE can arise due to simulation parameter settings.




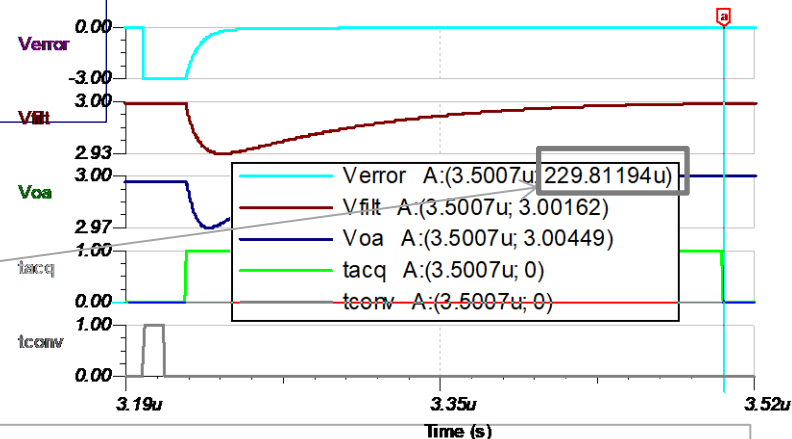Error is 229.8 μ V at the end of acquisition time, which satisfies the goal.



Current & power measurement use cases

Solutions customers seek

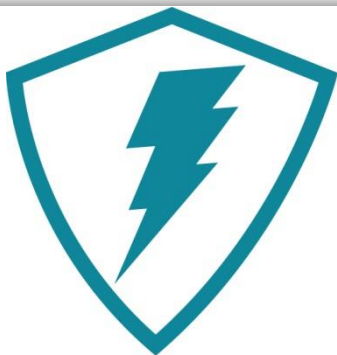


Real-time overcurrent protection (OCP)

Current-level detection exceeding a predetermined threshold as system fluctuations occur due to loads and transients



Current and power monitoring for system optimization

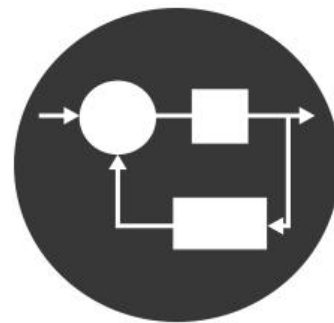Modeling of system performance and energy to maximize efficiency and/or battery life




Current measurement for closed loop circuits

Infer diagnostic and/or operational system information from the current measurement


Current sensing portfolio

Analog output

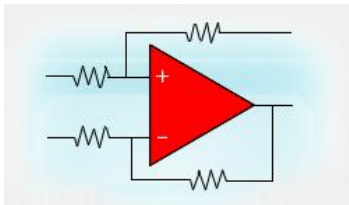


Integrate the full analog signal processing and provide a voltage or current output

Digital monitor

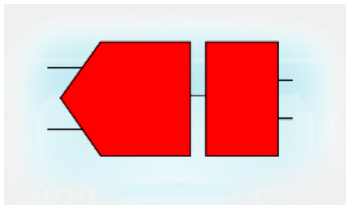


Integrate the full signal conditioning path and utilize standard digital interfaces

Int. comparator

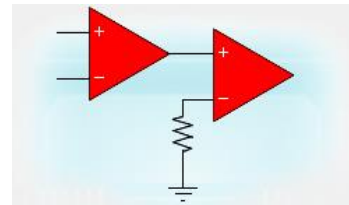


Provides a simple ALERT signal when the load current exceeds a threshold along with analog or digital out

In-package shunt

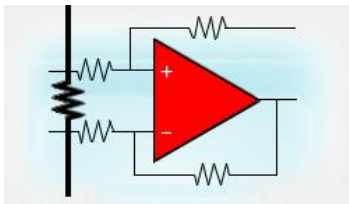


Offers a low-drift, precision shunt resistor element in-package with either analog or digital out

In-package Hall-effect current sensors

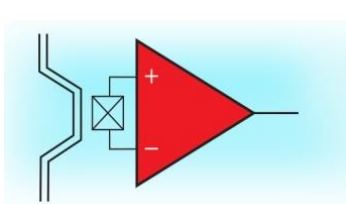

Offers precision isolated Hall through-package current measurement.

Ambient magnetic field current sensors

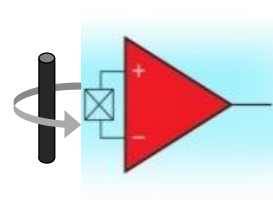


On-chip sensors measures the magnetic field flux density and generates a voltage output proportional to the current

Current sensing use-cases in industrial

Analog current sense amplifier use-cases


Brushless DC motor commutation

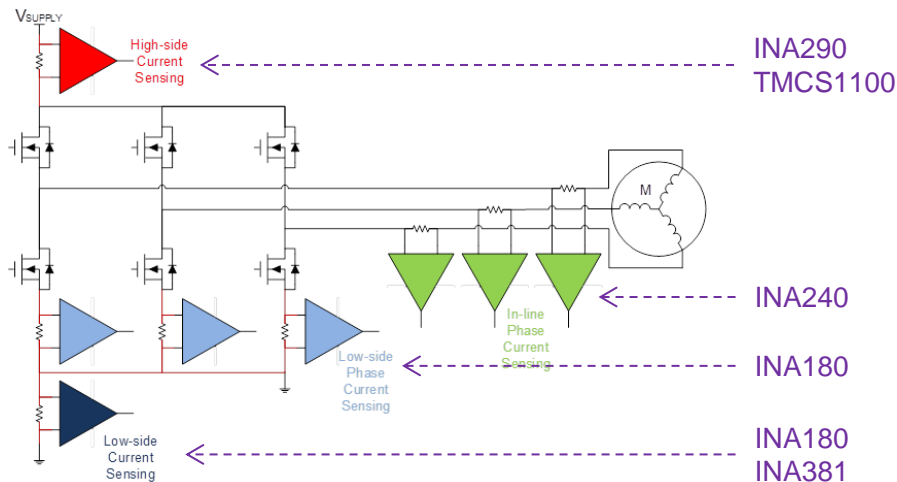Uses up to three current sense amplifiers in low-side of high-side configurations for torque measurement.




Power supplies

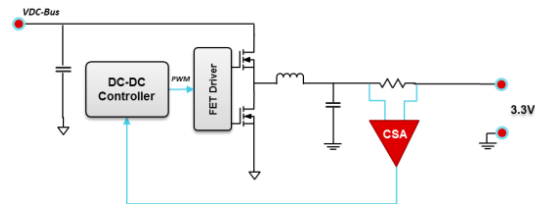Current sensing in power supplies for accurate current measurement for control loops and quick over-current detection.



PLCs

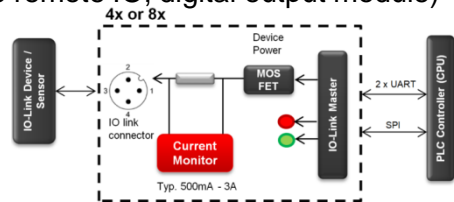To avoid that a sensor could create problems for the system, each port monitors the current to ensure proper operation. (Stand-alone remote IO, digital output module)



Low-cost hero devices

Existing

New Release

In Preview

Q100 Option
Available

Q100 in
Development

Analog output

<48V



INA180/2180/4180

-0.3V to 26V CMR
150 μ V Offset, 1% Gain Error
Gains: 20, 50, 100, 200 V/V
Op-amp footprint compatible
Single/Dual/Quad options

\geq 48V



INA281

-4V to 110V CMR
-20V to 120V Survivability
150 μ V Offset, 0.5% Gain Error
1.3MHz BW & 2.5V/ μ s slow rate
Gains: 20, 50, 100, 200, 500V/V
SOT-23 Dual Pinouts



INA280

2.7V to 120V CMR
-20V to 122V Survivability
150 μ V Offset, 0.5% Gain Error
1.1MHz BW & 3V/ μ s slow rate
Gains: 20, 50, 100, 200, 500V/V
SC-70

Digital monitor



INA237

-0.3V to 85V CMR
50 μ V Offset & 0.3% Gain Error
16-bit ADC
I²C Output

Integrated comparator



INA381

-0.3V to 26V CMR
500 μ V Offset, 1% Gain Error
5 μ s Response Time



TEXAS INSTRUMENTS

High performance hero devices

Existing

New Release

In Preview

Q100 Option
Available

Q100 in
Development

Analog output

<48V



INA190

-0.1V to 40V CMR
15 μ V Offset, 0.2% Gain Error
Gains: 25, 50, 100, 200, 500 V/V
Disable Pin (QFN & SOT23-8)
SC70-6, QFN-10, & SOT23-8

\geq 48V

In-line



INA240

-4.0V to 80V CMR
25 μ V Offset, 0.2% Gain Error
Gains: 20, 50, 100 V/V
Enhanced PWM Rejection
AEC-Q100 Grade 0 in SOIC
TSSOP & SOIC

High-side



INA290

2.7V to 120V CMR
-20V to 122V Survivability
12 μ V Offset, 0.1% Gain Error
1.1MHz BW & 3V/ μ s slew rate
Gains: 20, 50, 100, 200, 500V/V
SC-70

Digital monitor

<48V



INA226

0V to +36V CMR
10 μ V Offset & 0.1% Gain Error
MSOP-10

\geq 48V



INA228


0V to +85V CMR
1 μ V Offset & 0.1% Gain Error
20-bit ADC
I2C Output



INA229

0V to +85V CMR
1 μ V Offset & 0.1% Gain Error
20-bit ADC
SPI Output

Integrated shunt

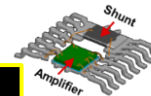

INA250

0.75% total gain error over temp
-0.3V to 36V CMR
Available Gains: 200, 500, 800,
1000 mV/A
TSSOP-16



INA253

0.75% total gain error over temp
-4.0V to +80V CMR
Gains Options: 200, 500, 1000
mV/A
TSSOP-16

TMCS1100

Precision, bi-directional, galvanically isolated current sensor with external reference


Features

- 80 kHz signal bandwidth.
- 1% accuracy (-40 to 125°C).
- ± 600 V working voltage, 3 kV dielectric isolation (IEC 60950-1).
- Operating voltage: 3.0 V to 5.5 V.
- 20 A max continuous DC/RMS current (thermally limited).
- Multiple sensitivities for wide linear measurement ranges:
 - TMCS1100A1: 50 mV/A – TMCS1100A2: 100 mV/A
 - TMCS1100A3: 200 mV/A – TMCS1100A4: 400 mV/A
- 8-pin SOIC package.
- **AEC-Q100 Grade 1 Option.**

Applications

- Motor control
- PV string inverters
- Switching converters
- Overcurrent protection
- Power monitoring
- On-board charger PFC


Tools & Resources

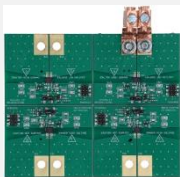


- [TMCS1100EVM](#)
- TINA-TI SPICE Model

Benefits

- Ability to measure an isolated ac or dc current.
- In-package sensing simplifies PCB and application design.
- Highest accuracy Hall current sensing device in the industry.
- Highest working voltage isolation (600 V) in 8-pin SOIC.
- Ability to precisely set the reference voltage (VREF) independent of Vcc enables higher accuracy.
- VREF can be shared with ADC for increased system accuracy.
- Fixed sensitivity eliminates ratiometry errors and improves supply noise rejection.

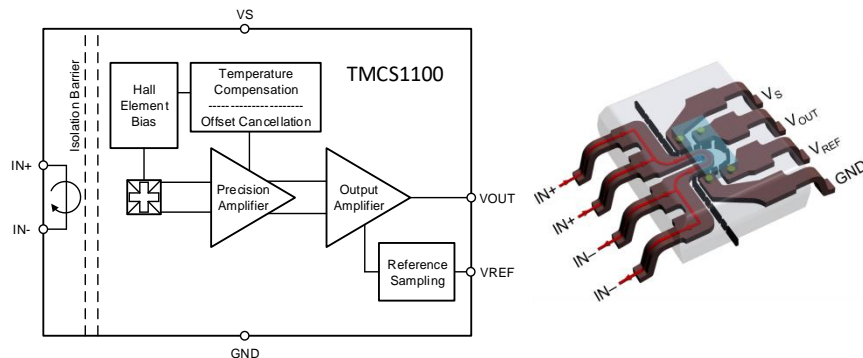

Key Resources

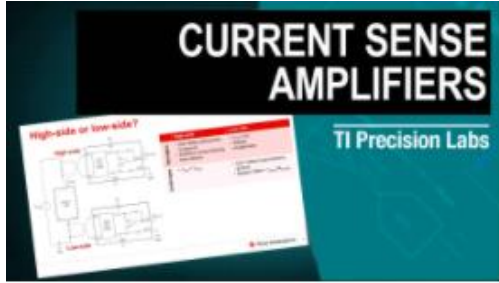

TI Precision Labs

Cross reference search


Enter a partial or full part number

Enter a part number

Add unlimited part numbers to view equivalent TI cross reference part information, TI datasheets, instant inventory, and price data for each part number.

Upload your BOM (Bill of Materials) to view equivalent TI cross reference part information, TI datasheets, instant inventory, and price data for your entire list, up to 5000 parts (.csv, .tsv, .xls, .xlsx, Eagle .sch, KiCad.sch, .SchDoc)

Cross-reference search

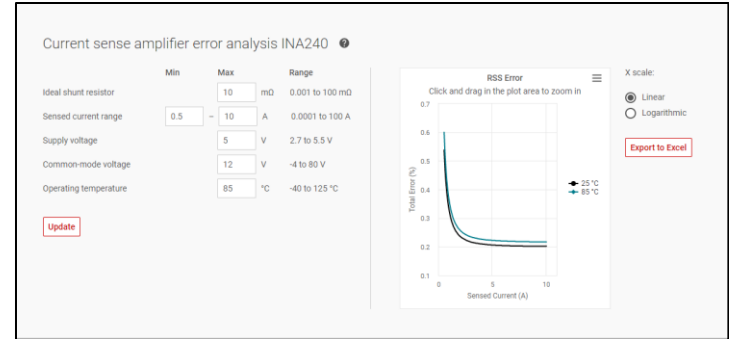

Web-based error tool



©2020 Texas Instruments Incorporated. All rights reserved.

The material is provided strictly "as-is" for informational purposes only and without any warranty.
Use of this material is subject to TI's **Terms of Use**, viewable at [TI.com](https://www.ti.com)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2020, Texas Instruments Incorporated