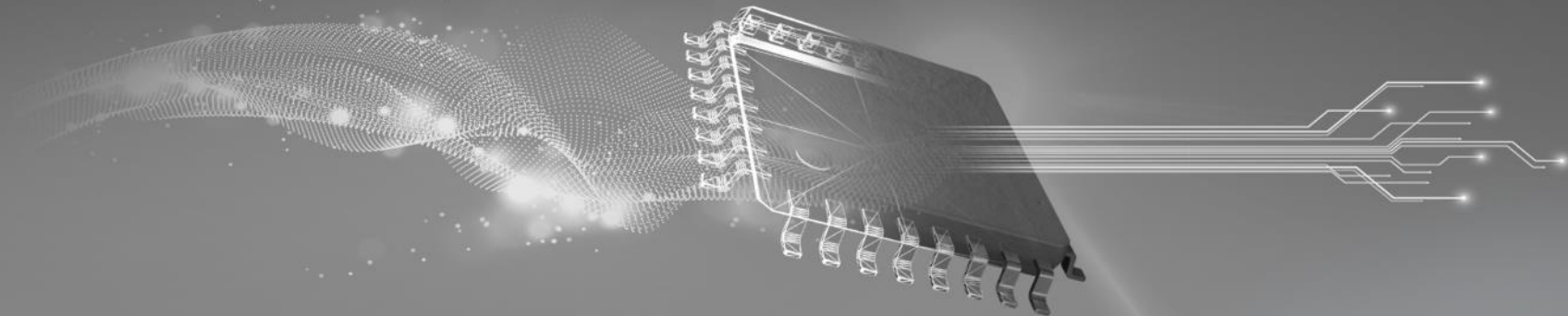


TI TECH DAYS



Say goodbye to 4-wire cables.

Learn how to transmit your RS-485 communication over a power bus, eliminating wires and optimizing system cost

Hao Liu

ASC/INT/TRX

Agenda

- 4-wire application becomes 2-wire!
 - Comparison with existing PLC technology
- Introduction to THVD8000
 - Driver
 - Receiver
- Implementation concerns and common questions
 - Carrier frequency, termination, L/C selection, grounding
- Special application circuits
 - Single-ended communication
 - Operate with line driver




When a 4-wire application only needs 2-wires

Traditionally the power line and data line are carried separately.

If data could be transmitted over power lines, the total wires would be reduced from 4 to 2.

- **Result: Up to 50% cost savings**

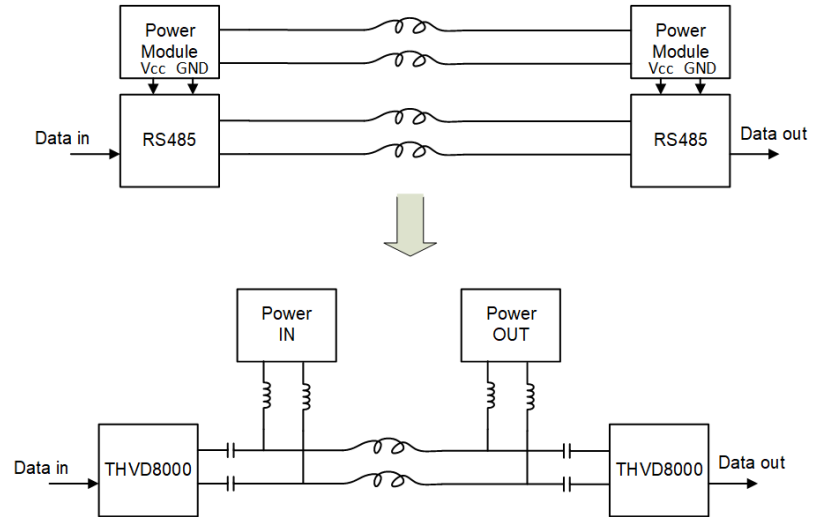Key applications include HVAC, E-meters, elevator, lighting, E-bike, etc.



When a 4-wire application only needs 2-wires


Data over power line technology

- Making power and data transmitting on the same wires
- Combine and separate power (low speed) and data (high speed) signals
- Existing solutions
 - PoE (Power over Ethernet)
 - Power line communications (PLC)
 - Powerline communication analog front-end (AFE)

THVD8000 applies OOK modulation to couple data to the power line for simple, flexible, and effective communication.



THVD8000 blocks

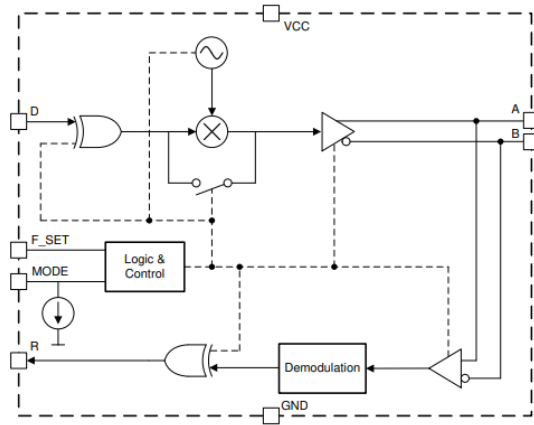- Driver – Same as RS-485 transceiver structure
- Internal clock to OOK modulate data
- Integrated bandpass filter for demodulation and envelop detection
- Variable data rate setting by external resistor at the F_SET pin



THVD8000 system

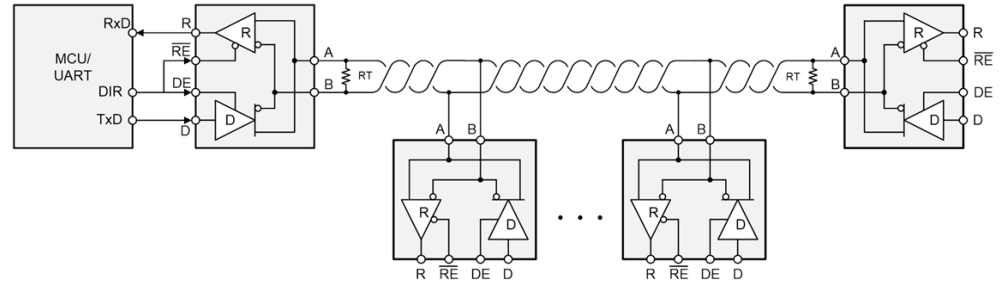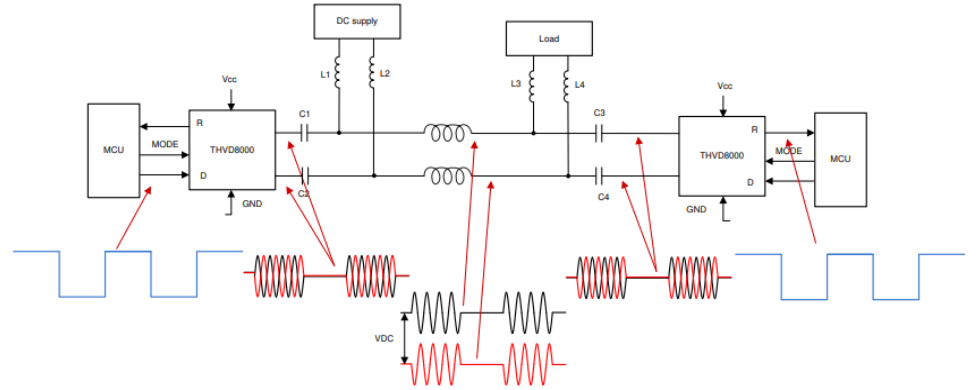- Leverage RS-485 signaling
- OOK modulated data
- PHY level replacement
- Flexible data rate
- Polarity free operation
- Multiple node network
- Long distance




THVD8000 benefits


- OOK modulation handled inside the RS-485 transceiver
 - Wide data rate operation
 - No data DC balancing needed
 - Electrical signaling parameters conforms to TIA/EIA-485A standard
- No controller/software updates needed (good for drop-in)
- All the benefits of RS-485
 - Physical layer definition only → Flexibility in implementation
 - Robust operation in noisy environments → Excellent EMC/EMI performance
 - Cost effective

THVD8000 setup and waveforms

Communication waveforms

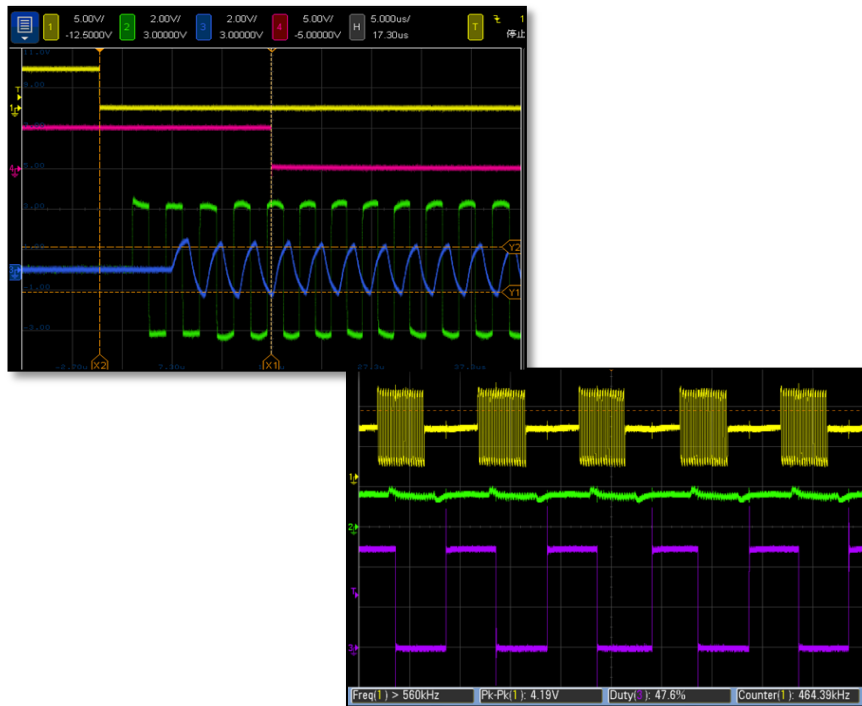

Lab bench setup example

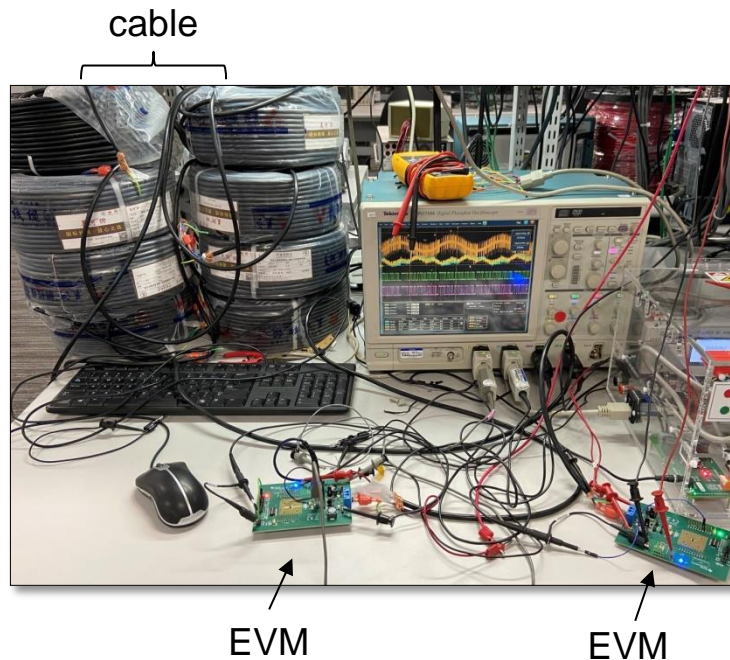


Design tips – Data rate and carrier frequency

- It is recommended to use a carrier frequency that is 10x higher than the data rate.
 - For example, for 9600 baud rate, 100kHz or higher carrier frequency can be chosen.
 - The OOK f_0 is not sensitive to the external resistor variation (+/- 2%).

R_{F_SET} (k Ω)	OOK f_0 (kHz)
77	125
50	187.5
19	500
12.5	750
9.3	1000
4.4	2000
1.5	5000

Design tips – Power delivery

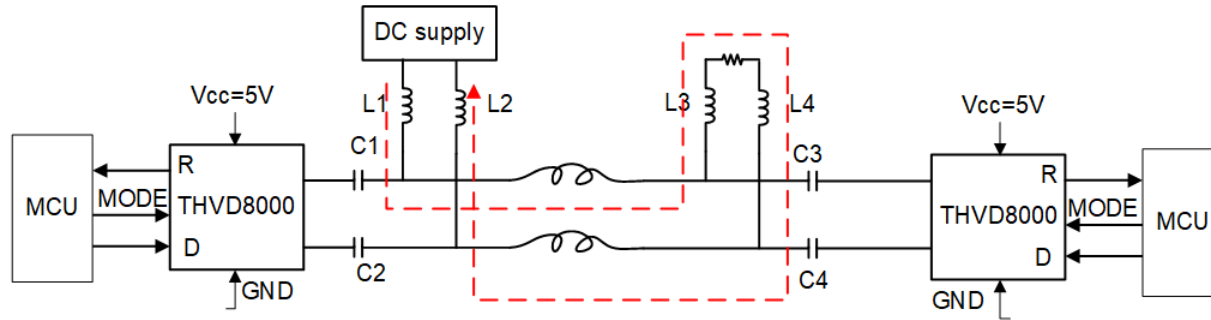- THVD8000 sits behind the AC coupled capacitor so the THVD8000 pins don't interface DC or AC power directly (ref 2).
- The capacitor needs to have high enough voltage rating
 - 24 VDC or 24 VAC are common applications
- The energy that can be transmitted depends on the inductor current rating and DC resistance, and the cable.




Design tips – Data rate vs. distance

- In applications, maximum distance that can be achieved at a given rate is mostly a function of the cable used.
- Transmitter output amplitude (drive strength) can be useful in low-speed/long-range applications that are limited by the DC resistance of the interconnect cable (ref 1.).
- At higher frequencies, the most critical factor is the insertion loss of the transmission line


Table 2. Cable Length Versus Carrier Frequency

		fo (kHz) (data rate = 1/10 fo)				
		125	300	500	750	1000
Cable Length (Meter)	300	y	y	y	y	y
	600	y	y	y	y	y
	900	y	y	y	y	n
	1200	y	y	y	n	n
	1500	y	y	n	n	n

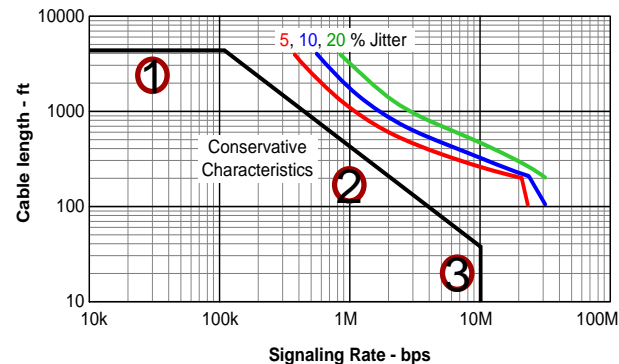

Design tips – Termination



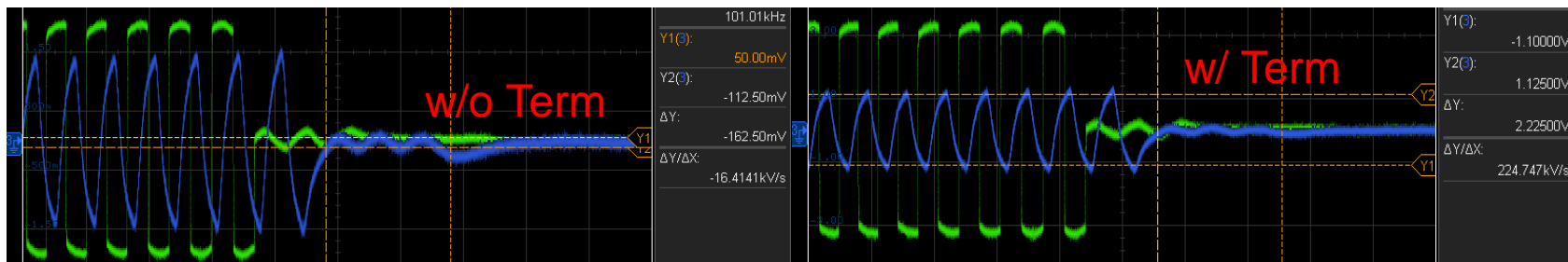
- Termination: Terminate the two furthest points of the bus with resistors equal to the characteristic impedance, Z_0 , of the bus, which improves the signal integrity (ref 5).
- THVD8000 works without termination, meaning topologies other than daisy-chain can be used.



- In designs, the signal should have enough time to settle in one bit time.



Design tips – Inductor selection

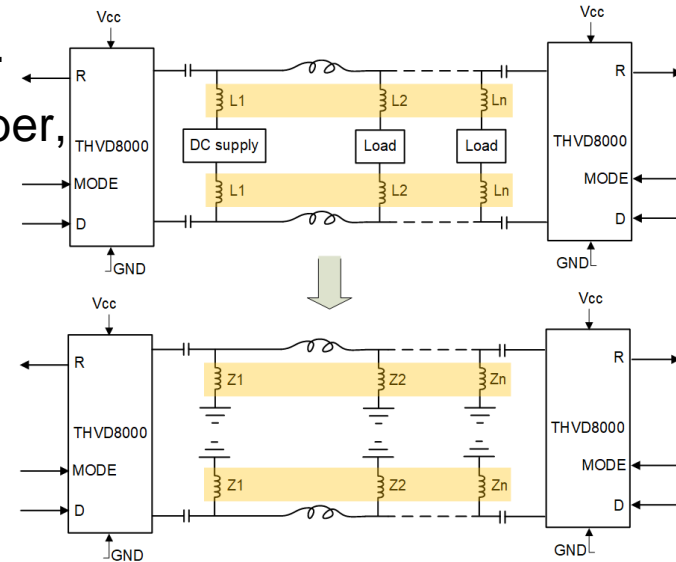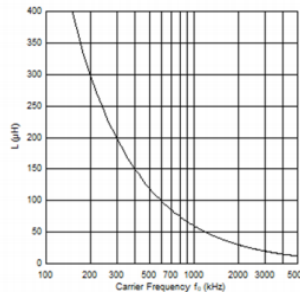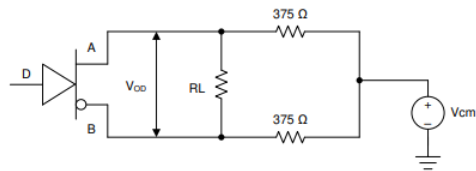- Inductor value is based on the impedance at the carrier frequency.
- 375 Ohm is the maximum load of the bus, which guarantees 1.5 V V_{od} .
- All active inductors need to be taken into account.
- More accurate result expressed as complex number, including R and C.
- Cable impedance also plays a role in evaluation.




Design tips – Capacitor selection

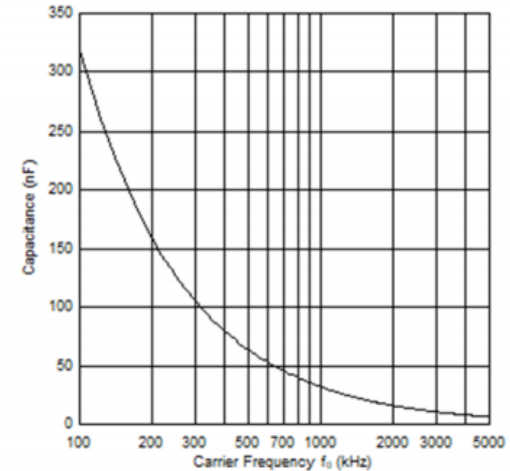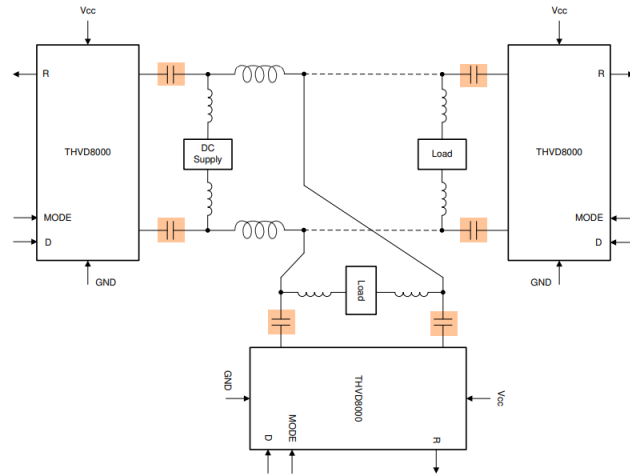- The impedance at the carrier frequency should be small ($< 5 \Omega$) to prevent attenuating the signal (ref 4).
- Each capacitor is evaluated individually.




Design tips – Grounding and noise

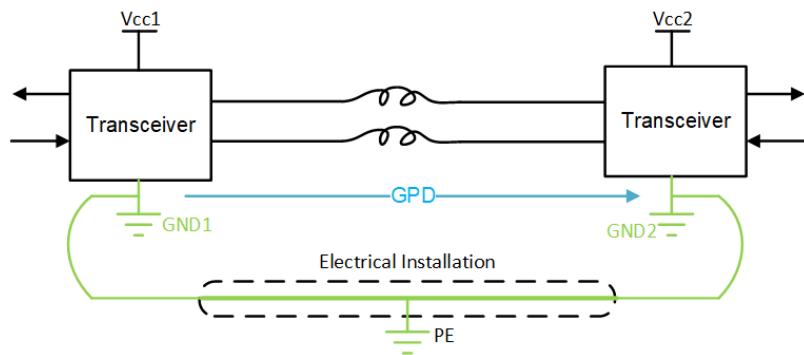- Noise sources:
 - High frequency (running compressor, etc)
 - Low frequency (adaptive DC-DC of load, 50/60Hz AC, etc)
- Common mode noise can become differential (power cables are usually not twisted pair)
- Floating grounding can pick up lots of noise in high impedance current return path (ref 3.)





Special applications – Single-ended setup

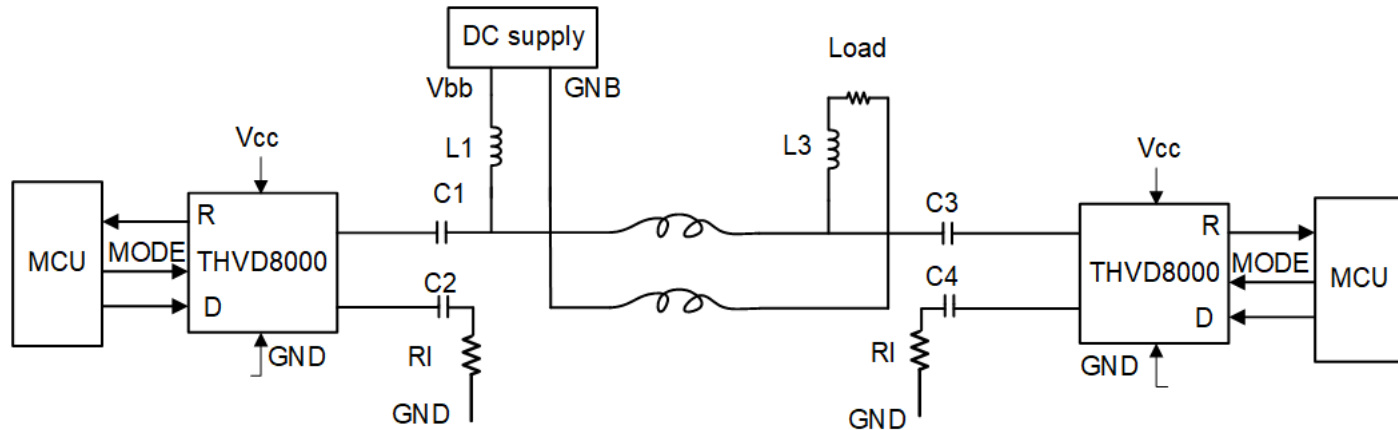- THVD8000 works with single-ended setup, although it generates differential signal.
- This setup further reduces the inductor number by half.



Special applications – Working with a line driver

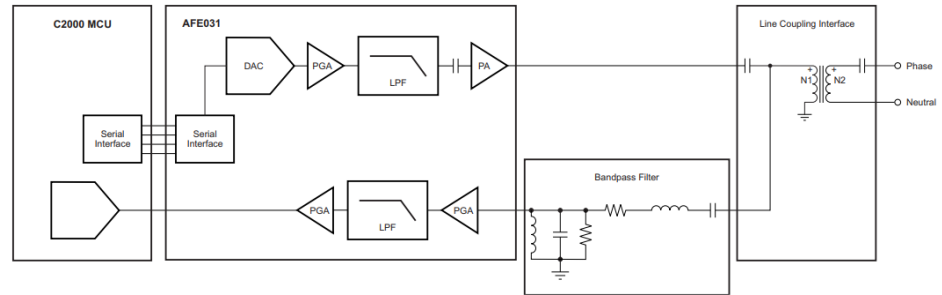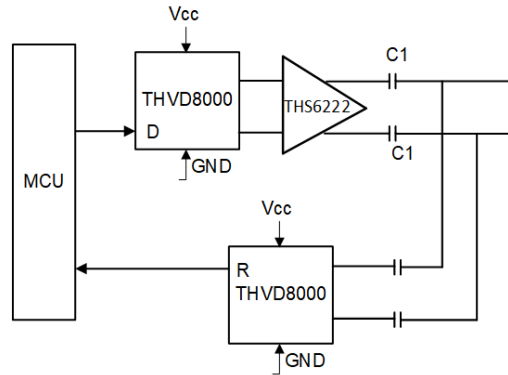- THVD8000 can work with a high-speed line driver to drive a low impedance AC line.
- This implementation is similar to the AFE application.
- Instead of FSK or OFDM, THVD8000 takes care of OOK modulation/demodulation (ref 6).



Summary

- THVD8000 is an RS-485 transceiver with on-off keying (OOK) modulation and demodulation built in for power line communication.
- Does THVD8000 fit your application?
 - What are the data rate requirements?
 - DC/AC power (and voltage) requirements?
 - Any restrictions on capacitor and inductor selections?
 - Emissions requirements?
 - Package preference?

Reference

1. [RS-485 design guide](#)
2. [THVD8000 design guide](#)
3. [Ground noise](#)
4. [Power over data bench simulation](#)
5. [Signal integrity and reflection](#)
6. [MCU interface with AFE](#)

Q & A

Visit our TI E2E™ support forums to receive direct support from our engineers throughout every step of your design.



<https://e2e.ti.com>



©2020 Texas Instruments Incorporated. All rights reserved.

The material is provided strictly "as-is" for informational purposes only and without any warranty.
Use of this material is subject to TI's **Terms of Use**, viewable at [TI.com](https://www.ti.com)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2020, Texas Instruments Incorporated