

Universal AC-Input 45W Low-Profile USB Power Delivery Charger Reference Design With Integrated GaN



Description


This reference design is a 45W, low-profile AC/DC USB Power Delivery (PD) charger reference design with integrated flyback controller and gallium nitride (GaN) power switch. This design can achieve less than 10mm height by using a low-profile planar PCB transformer. The flyback converter UCG28826 features V_{CC} self-bias and simplifies the planar transformer PCB winding by eliminating auxiliary winding as well as associated V_{CC} rectifier circuitry. The design can meet efficiency standards and regulations such as Department of Energy (DOE) Level VI and Code of Conduct (CoC) Version 5 (V5) Tier 2 standards. The design achieves less than 75mW standby power consumption at 230VAC.

Features


- <10mm height, low profile design with PCB planar transformer
- Achieves >92% efficiency at 90VAC
- Simplified PCB winding design with V_{CC} self-bias feature
- Meets DoE Level VI and CoC V5 Tier 2 efficiency standards
- No load power consumption, <75mW at 230VAC

Applications

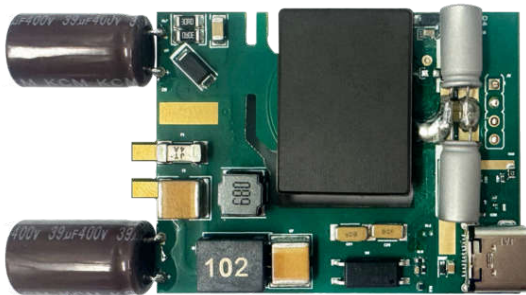
- [USB AC/DC adapter](#)
- [USB wall power outlet](#)
- [Battery charger](#)




Top View Photo

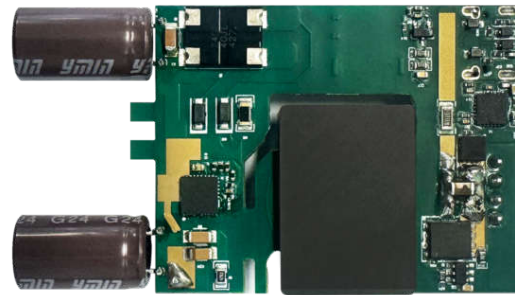

Bottom View Photo

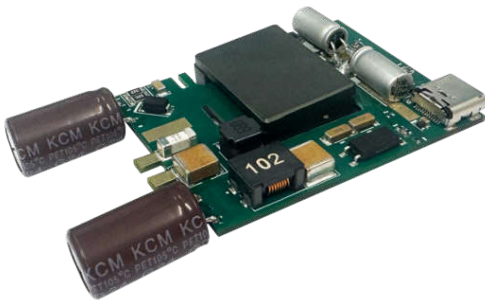

Angle View Photo

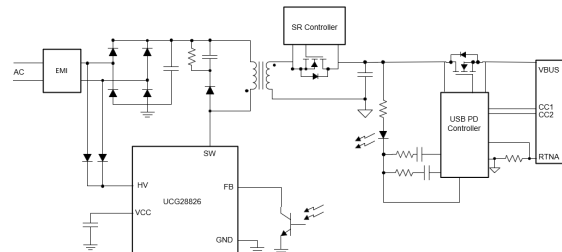

Block Diagram

1 Test Prerequisites

1.1 Voltage and Current Requirements

Table 1-1. Voltage and Current Requirements

Parameter	Specifications
Input voltage range	90VAC - 264VAC
Input voltage frequency	47HZ - 60Hz
Output power profile	5V, 3A, 9V, 3A, 15V, 3A, 20V, 2.25A

1.2 Required Equipment

- AC Source: Chroma Model 61601
- Digital Power Meter: Yokogawa WT310
- Power-Z P240 Bidirectional Multi-protocol Power Supply
- DC source: GWinstek, GPS-3303C
- Bidirectional Power Source: IT6010C-80-300
- Electronic load: Chroma, 6314A
- Oscilloscope: Tektronix, DPO 3054
- Infrared Thermal Camera: Fluke, TiS55
- True-RMS-Multimeter: Fluke, 287C

1.3 Dimensions

PCB board size: 39mm × 50.4mm × 10mm

1.4 Test Setup

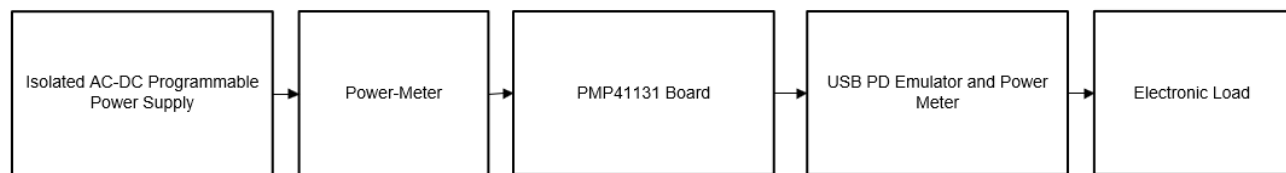


Figure 1-1. Test Setup

2 Testing and Results

2.1 Efficiency Graphs

Efficiency is shown in [Figure 2-1](#) through [Figure 2-7](#).

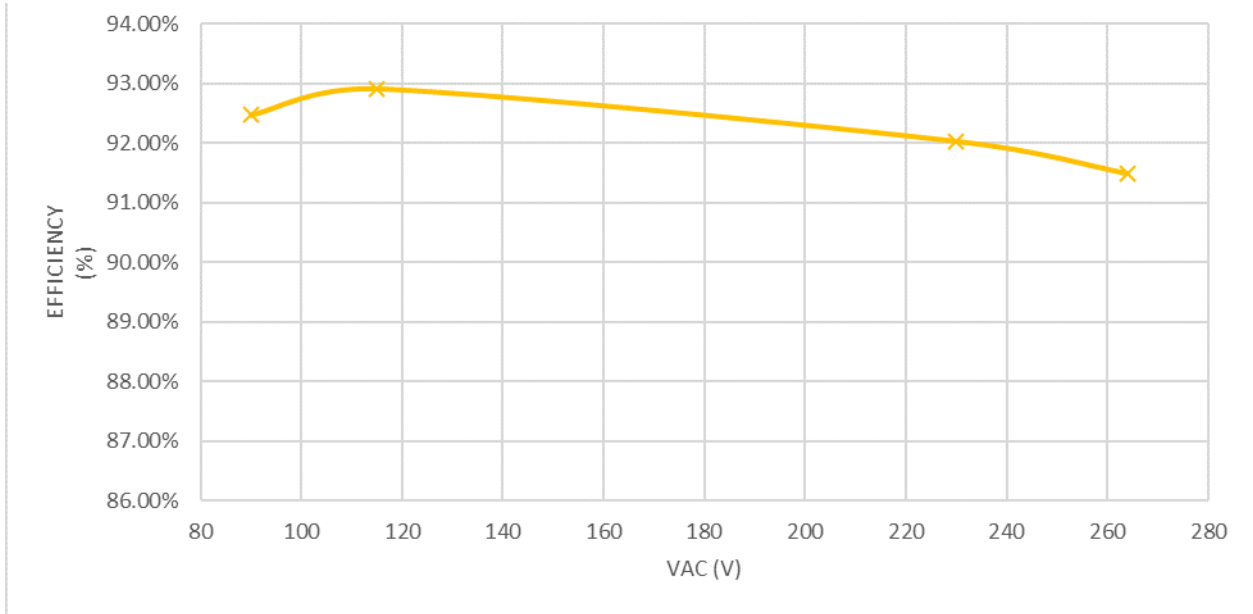


Figure 2-1. 20V Full-Load Efficiency Versus AC Input Voltage

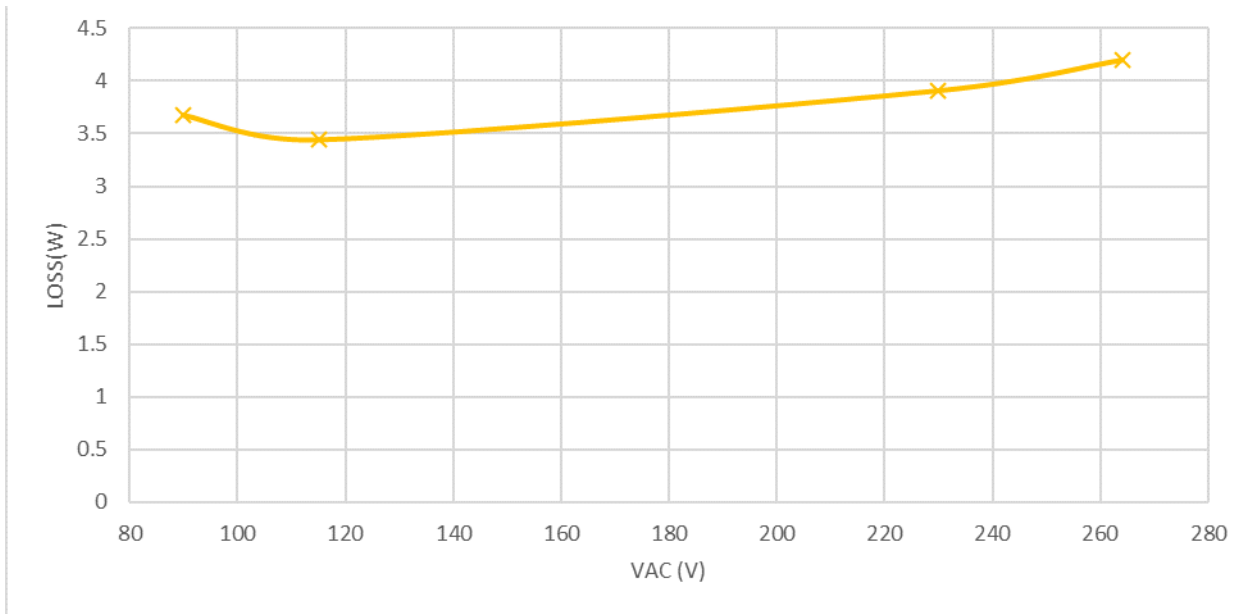


Figure 2-2. 20V Full-Load Power Loss Versus AC Input Voltage

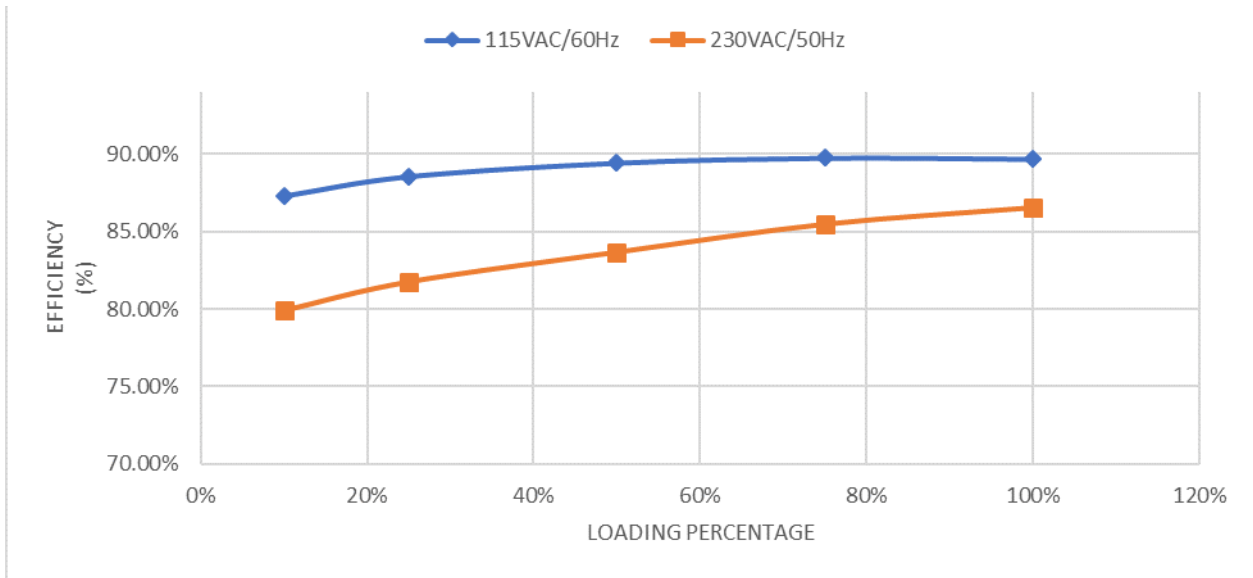


Figure 2-3. 5V, 3A

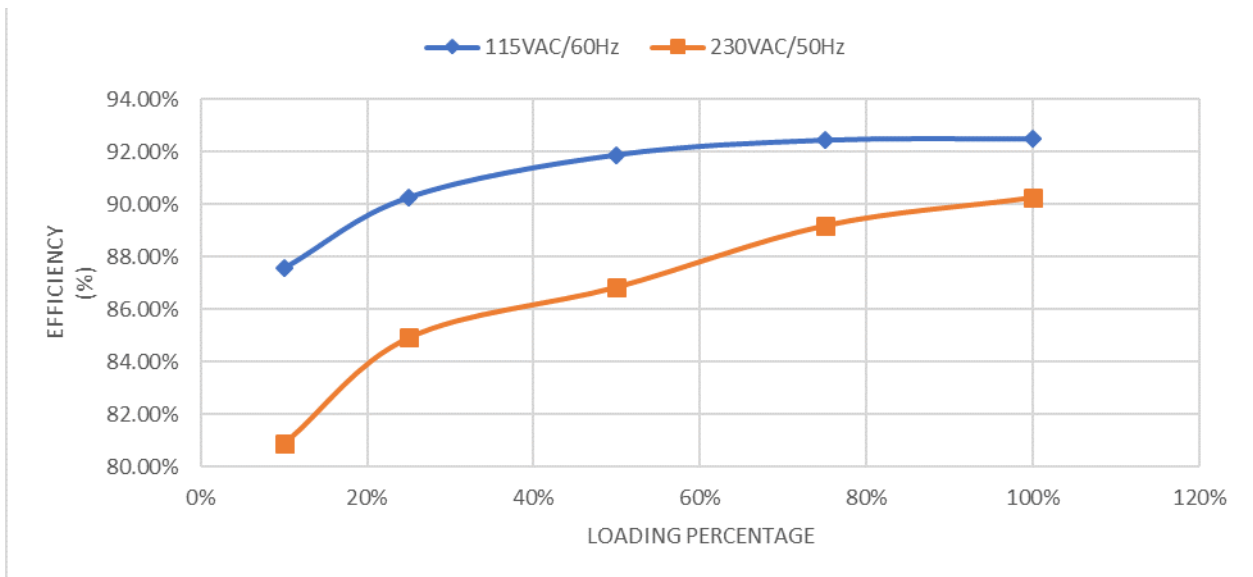


Figure 2-4. 9V, 3A

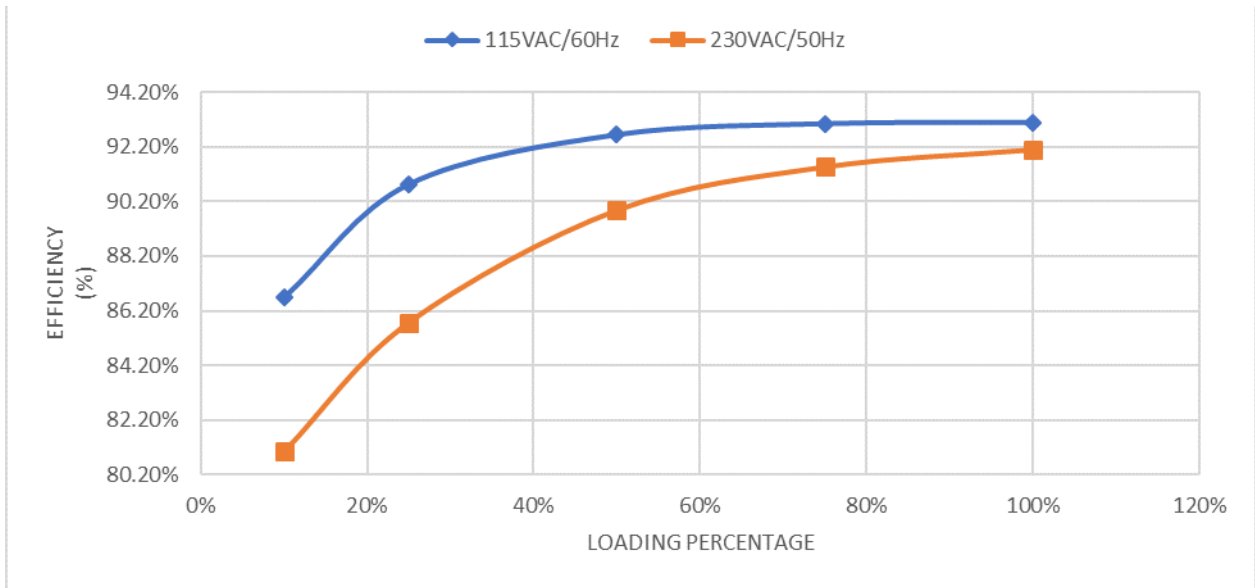


Figure 2-5. 15V, 3A

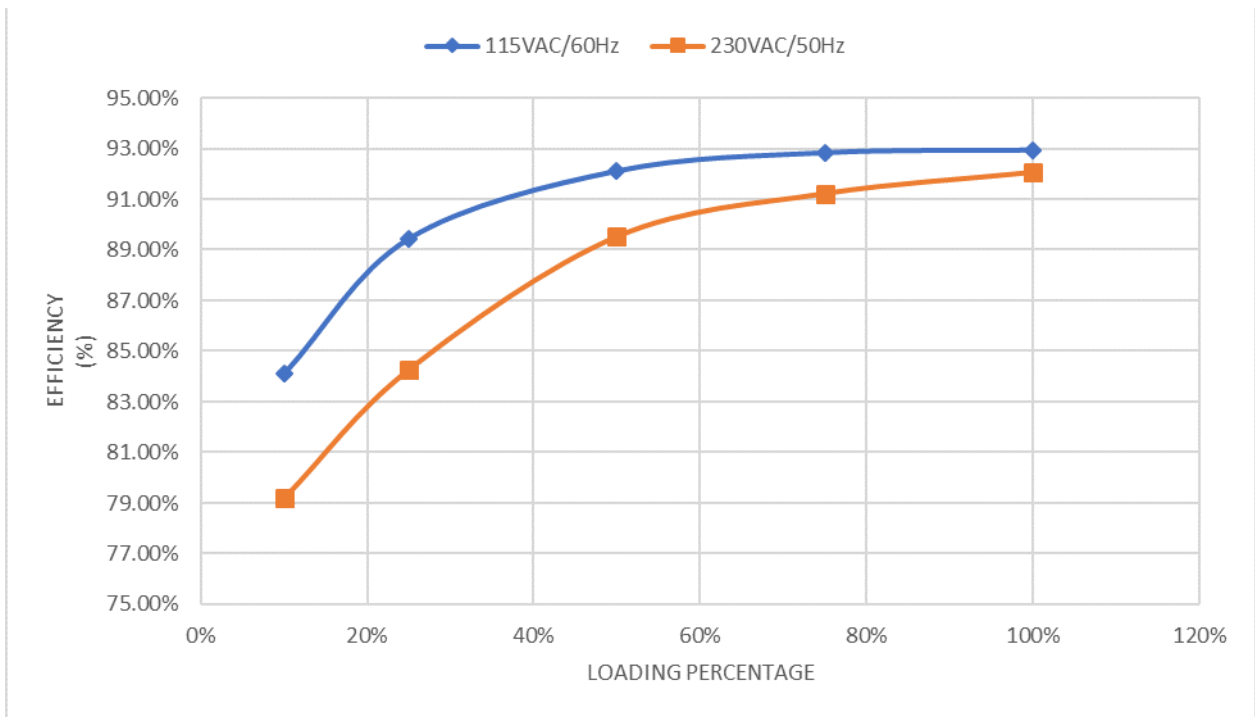


Figure 2-6. 20V, 2.25A

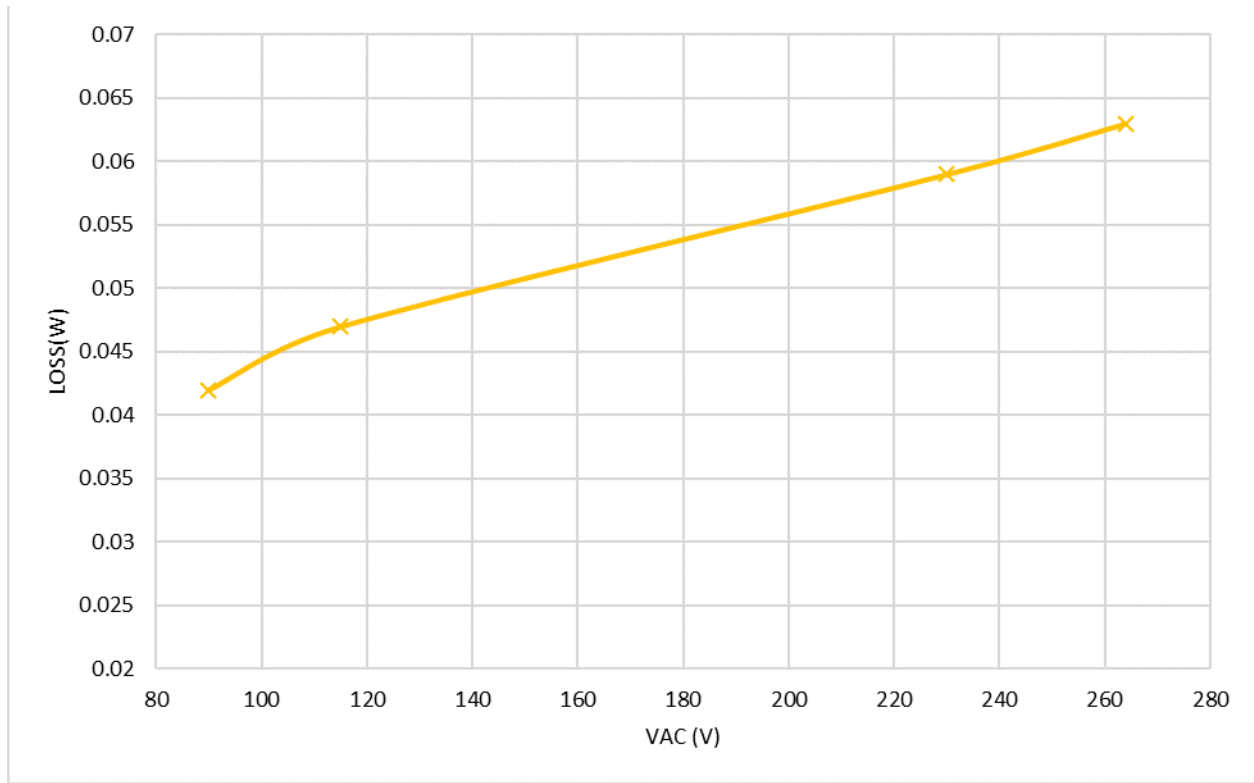


Figure 2-7. No Load Power Consumption

2.2 Voltage Regulation

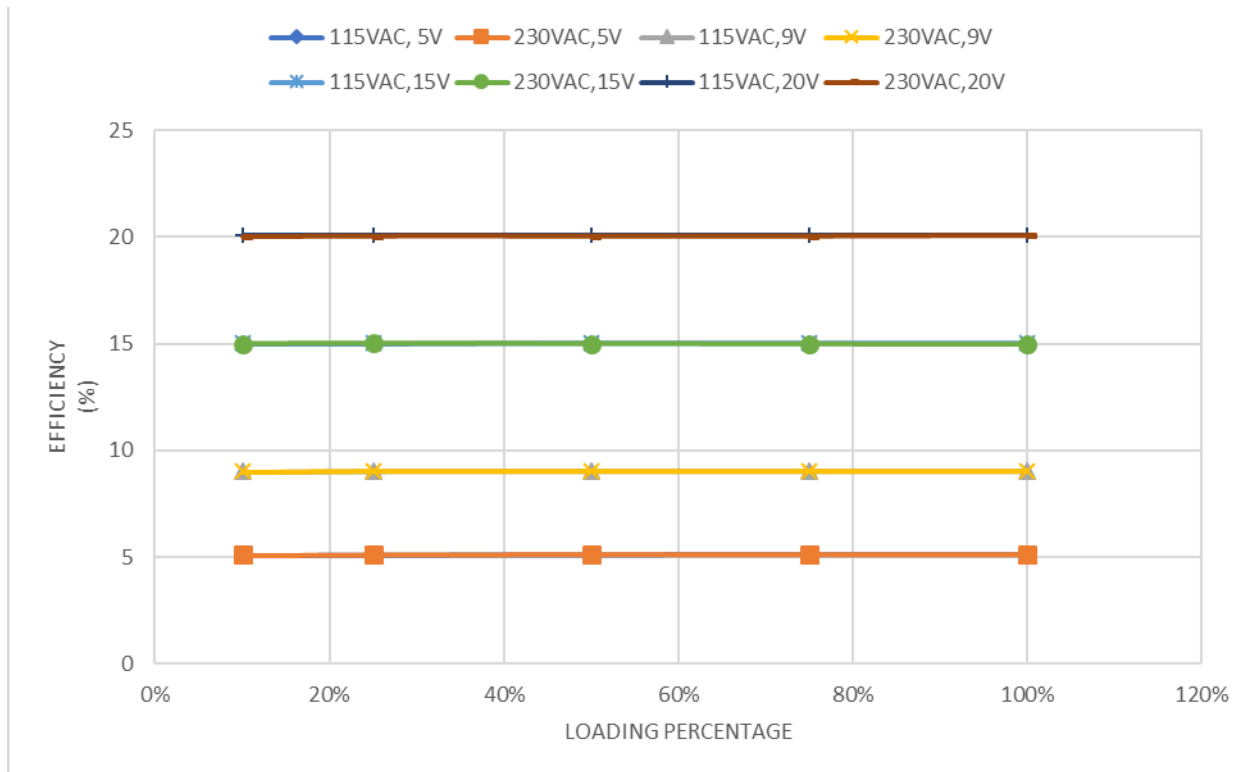


Figure 2-8. Voltage Regulation

2.3 Efficiency Data

Efficiency data is shown in [Table 2-1](#) through [Table 2-3](#).

Table 2-1. Efficiency Data

$V_{IN}(V)$	$P_{IN}(W)$	$V_{OUT}(V)$	$I_{OUT}(A)$	$P_{OUT}(W)$	Efficiency (%)
115	1.79	5.136	0.304	1.563	87.32
115	4.40	5.143	0.758	3.897	88.57
115	8.71	5.148	1.513	7.790	89.44
115	13.02	5.151	2.269	11.687	89.76
115	17.38	5.153	3.025	15.588	89.69
230	1.96	5.136	0.301	1.566	79.9
230	4.77	5.144	0.751	3.899	81.74
230	9.32	5.149	1.501	7.797	83.66
230	13.69	5.150	2.252	11.70	85.46
230	18.03	5.151	3.002	15.602	86.53
115	3.13	9.021	0.304	2.741	87.57
115	7.56	9.045	0.754	6.824	90.26
115	14.85	9.05	1.508	13.644	91.88
115	22.14	9.053	2.261	20.465	92.43
115	29.5	9.054	3.031	27.284	92.49
230	3.39	9.019	0.304	2.743	80.91
230	8.04	9.049	0.755	6.829	84.94
230	15.72	9.052	1.508	13.654	86.86
230	22.96	9.054	2.262	20.478	89.19
230	30.26	9.056	3.016	27.31	90.25
115	5.26	15.018	0.304	4.561	86.71
115	12.49	15.018	0.755	11.346	90.84
115	24.44	15.025	1.507	22.642	92.64
115	36.44	15.025	2.257	33.905	93.04
115	48.46	15.025	3.003	45.114	93.10
230	5.63	14.993	0.304	4.563	81.05
230	13.23	15.021	0.755	11.348	85.77
230	25.19	15.001	1.509	22.642	89.88
230	37.07	14.978	2.264	33.908	91.47
230	48.99	14.952	3.018	45.12	92.10
115	5.43	20.05	0.228	4.566	84.09
115	12.70	20.05	0.566	11.357	89.43
115	24.58	20.05	1.129	22.637	92.10
115	36.38	20.05	1.684	33.767	92.82
115	48.62	20.05	2.253	45.18	92.92
230	6.39	19.997	0.253	5.062	79.22
230	13.53	20.025	0.569	11.403	84.28

Table 2-1. Efficiency Data (continued)

$V_{IN}(V)$	$P_{IN}(W)$	$V_{OUT}(V)$	$I_{OUT}(A)$	$P_{OUT}(W)$	Efficiency (%)
230	25.30	20.025	1.131	22.646	89.51
230	37.04	20.025	1.687	33.782	91.20
230	49.10	20.026	2.257	45.19	92.04

Note: Variation of $\pm 0.3\%$ in 4-point average efficiency and $\pm 0.5\%$ in 10% efficiency can be observed.

Table 2-2. Full-Load Efficiency

$V_{IN}(V)$	$P_{IN}(W)$	$V_{OUT}(V)$	$I_{OUT}(A)$	$P_{OUT}(W)$	Power Loss(W)	Efficiency(%)
90	48.86	20.05	2.253	45.18	3.676	92.48
115	48.62	20.05	2.253	45.18	3.442	92.92
230	49.10	20.03	2.257	45.19	3.909	92.04
264	49.38	20.05	2.253	45.18	4.200	91.49

Table 2-3. No Load Power Consumption

Vac(V)	90	115	230	264
Standby power(mW)	45	47	59	63

2.4 Thermal Images

Thermal images are shown in [Figure 2-9](#) through [Figure 2-12](#). Thermal test was performed at room temperature, open frame, with 30-minute warm up.

Table 2-4. Thermal Test at 20V, Full-Load Condition

Temperature(°C)	90VAC	115VAC	230VAC	264VAC
AC Bridge	77.5	70.1	65.3	64.9
UCG28826	69.2	66.2	75.2	82.2
Transformer	83.4	80.8	85.5	86.5
SR MOSFET	73.5	74.1	74.8	76.2
SR Controller	80.4	80.2	81.3	82.2
RCD Snubber	67.8	66.2	64.2	63.5

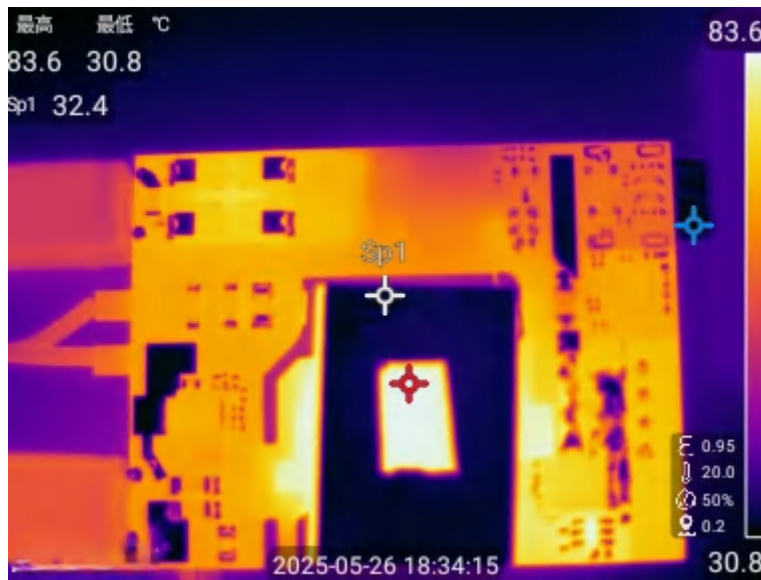


Figure 2-9. 90VAC, 20V, 2.25A



Figure 2-10. 115VAC, 20V, 2.25A

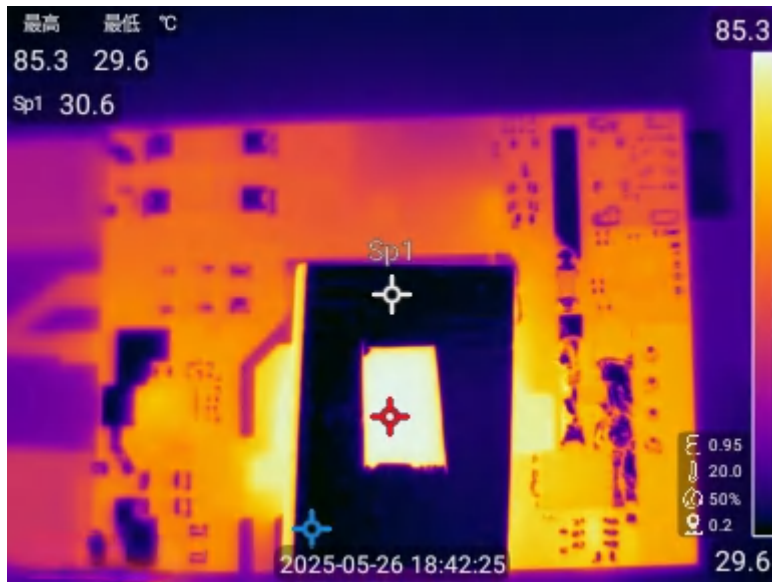


Figure 2-11. 230VAC, 20V, 2.25A

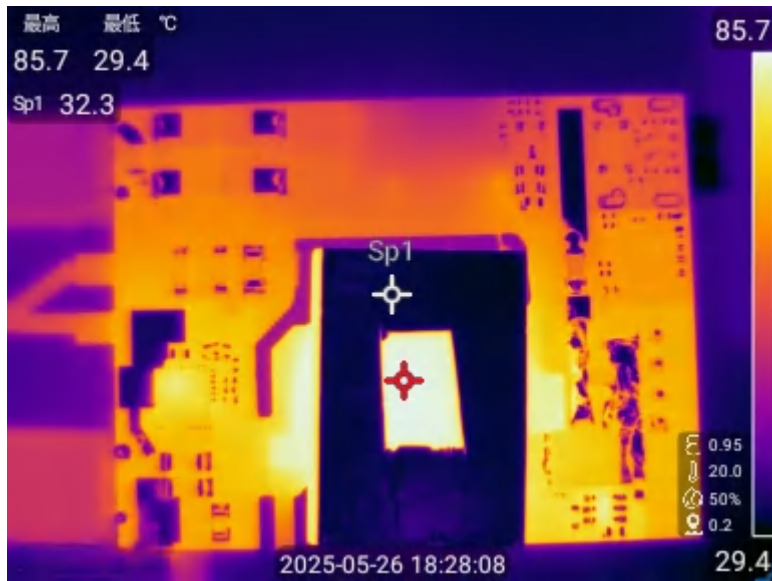


Figure 2-12. 264VAC, 20V, 2.25A

2.5 EMI

EMI is shown in [Figure 2-13](#) and [Figure 2-14](#).

EMI TEST REPORT

parameter		
Organization: AWK	Operator: Jerry	EUT: UCG2882-45W
Place: SZ	Time: 2025/5/16/21:18	Test equipment: KH3939
Detector: PK+AV	Test-time(ms): 30	SN: 1739409
Limit: EN55032	Transductor(PK/AV): PK / AV	JZ: 2,13,1966
Remark: B1-110V-CE		
freq, step		
Start(MHz)	End(MHz)	Step(MHz)
0.150	2.000	0.002
2.000	10.000	0.010
10.000	30.000	0.025
scan result		
dBuV		

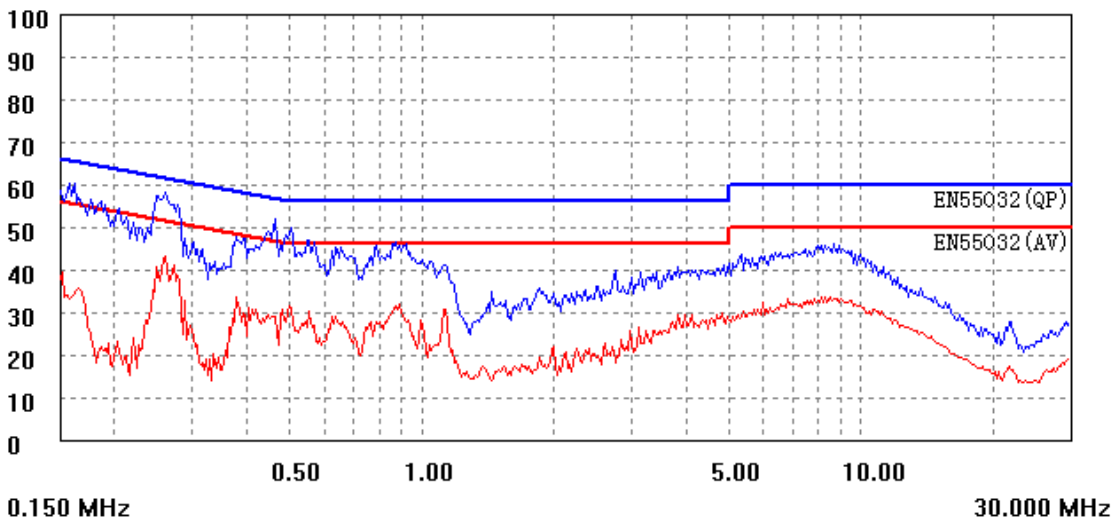


Figure 2-13. EMI at 115VAC, Full Load

EMI TEST REPORT

Organization: AWK	Operator: Jerry	EUT: UCG2882-45W
Place: SZ	Time: 2025/5/16/21:21	Test equipment: KH3939
Detector: PK+AV	Test-time(ms): 30	SN: 1739409
Limit: EN55032	Transductor(PK/AV): PK / AV	JZ: 2,13,1964
Remark: B1-220V-CE		

Start(MHz)	End(MHz)	Step(MHz)
0.150	2.000	0.002
2.000	10.000	0.010
10.000	30.000	0.025

dBuV

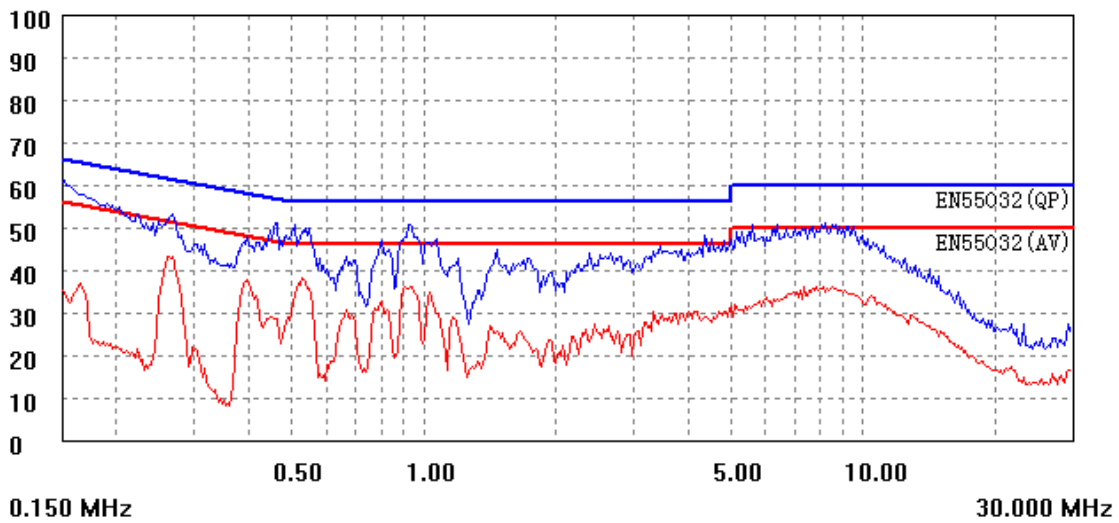


Figure 2-14. EMI at 230VAC, Full Load

3 Waveforms

3.1 AC Brown In and Brown Out

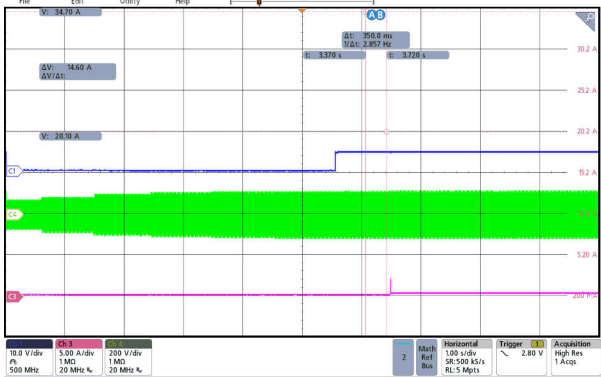


Figure 3-1. AC Brown In

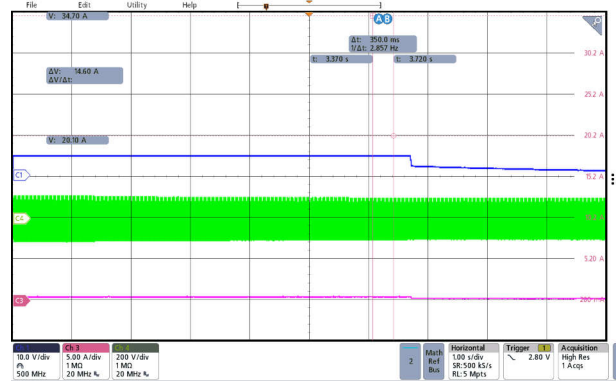


Figure 3-2. AC Brown Out

3.2 AC Start Up and Shut Down

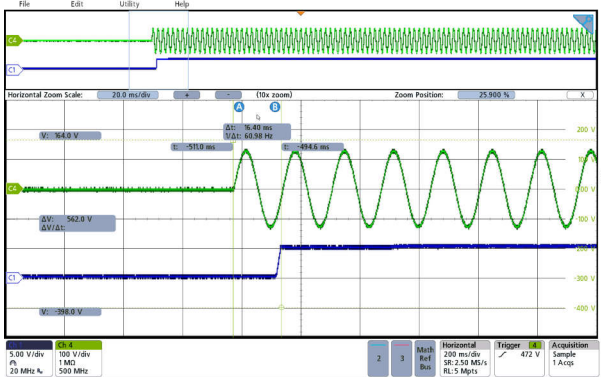


Figure 3-3. 90VAC, Start-Up

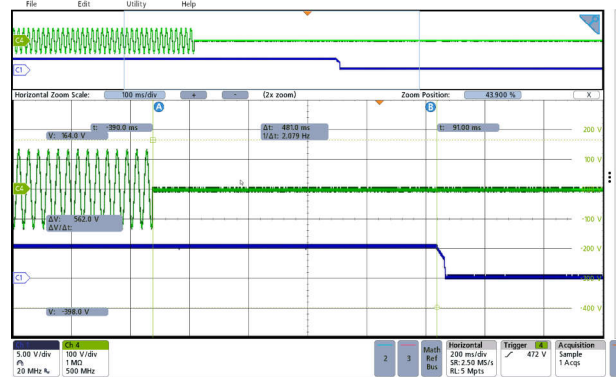


Figure 3-4. 90VAC, Shut-Down

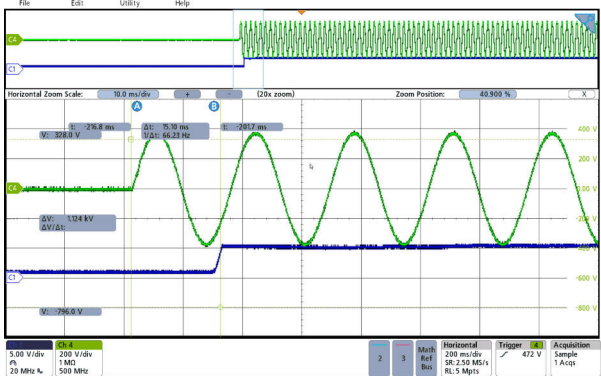


Figure 3-5. 264VAC, Start-Up

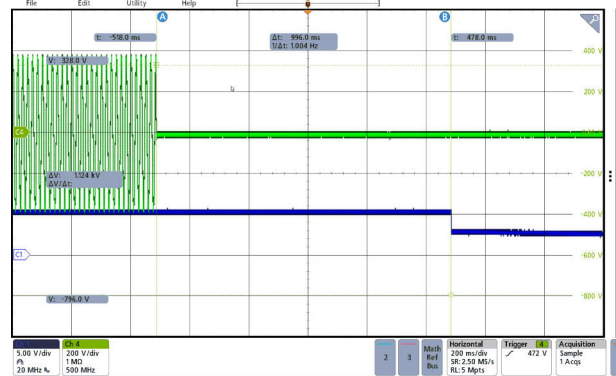


Figure 3-6. 264VAC, Shut-Down

3.3 Voltage Transition

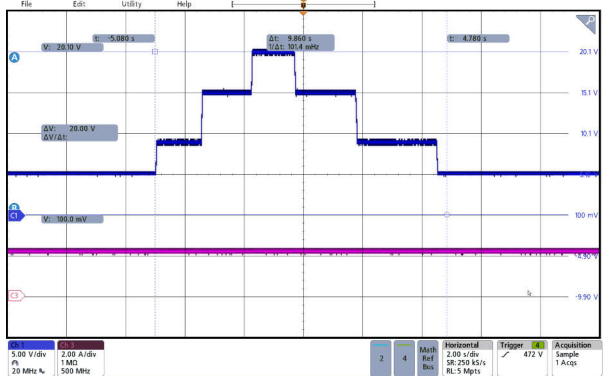


Figure 3-7. 115VAC, 20V to 5V Voltage Transition at 2.25A Load

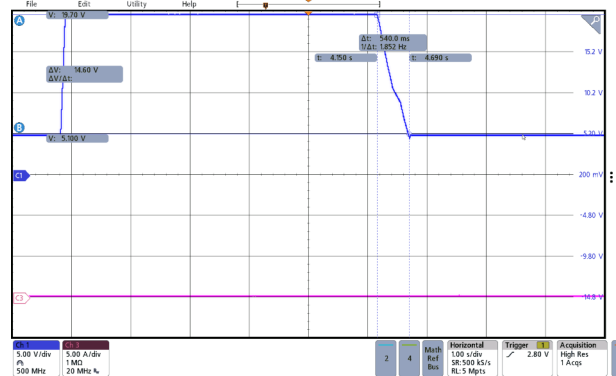


Figure 3-8. 115VAC, Voltage Transition from 20V to 5V at Open Load

3.4 Switching

Switching behavior is shown in Figure 3-9 and Figure 3-20.

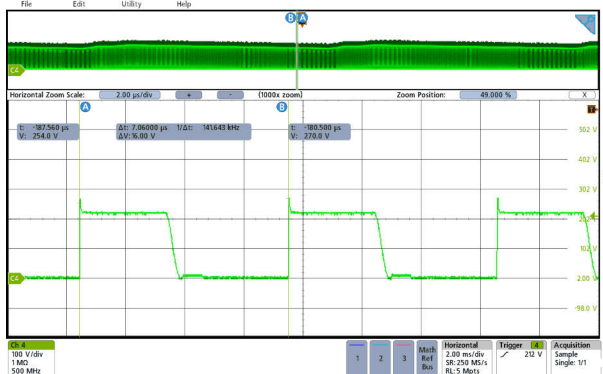


Figure 3-9. 90VAC, 20V, 2.25A, Vsw

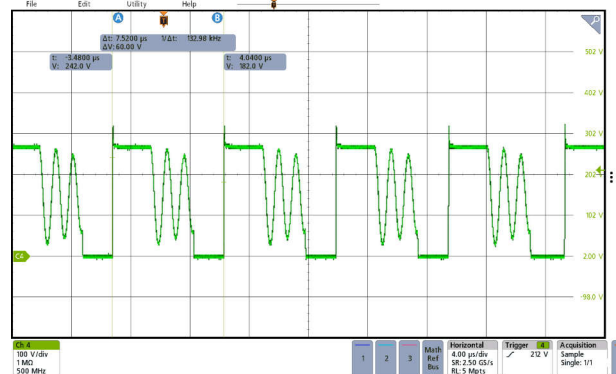


Figure 3-10. 110VAC, 20V, 2.25A, Vsw

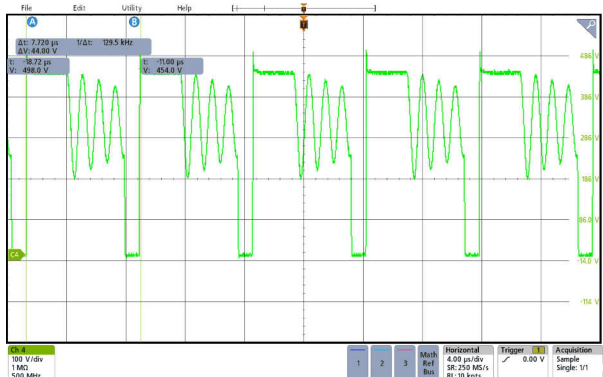


Figure 3-11. 230VAC, 20V, 2.25A, Vsw

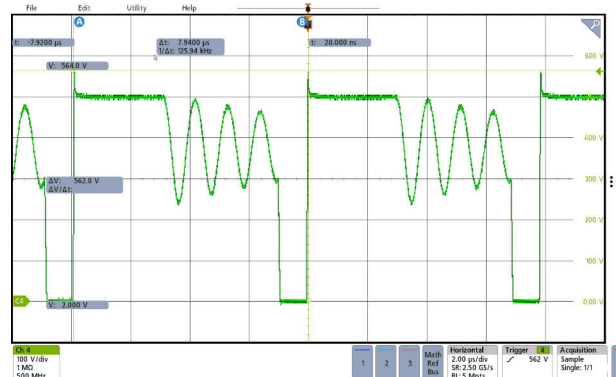


Figure 3-12. 264VAC, 20V, 2.25A, Vsw

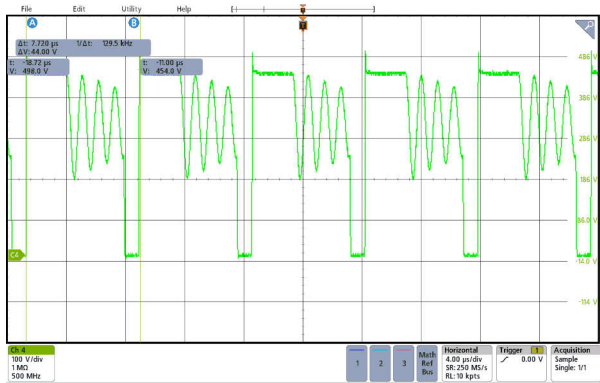


Figure 3-13. 230VAC, 20V, 2.25A, Vsw

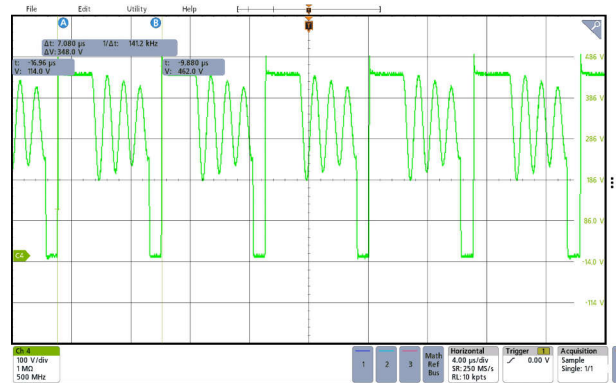


Figure 3-14. 230VAC, 20V, 1.68A, Vsw

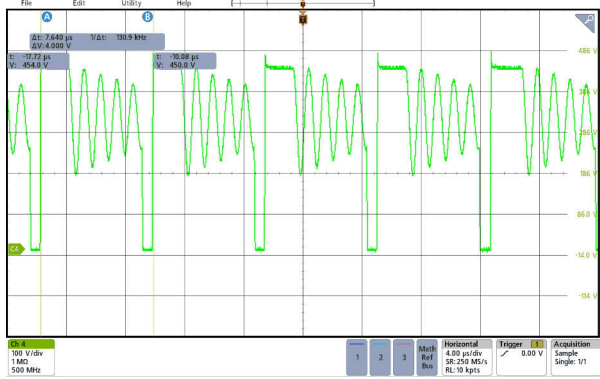


Figure 3-15. 230VAC, 20V, 1.125A, Vsw

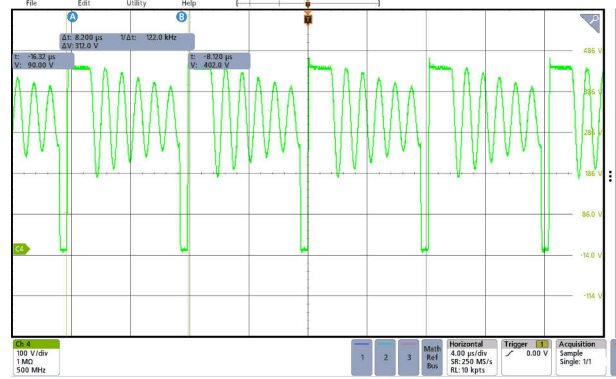


Figure 3-16. 230VAC, 20V, 0.565A, Vsw

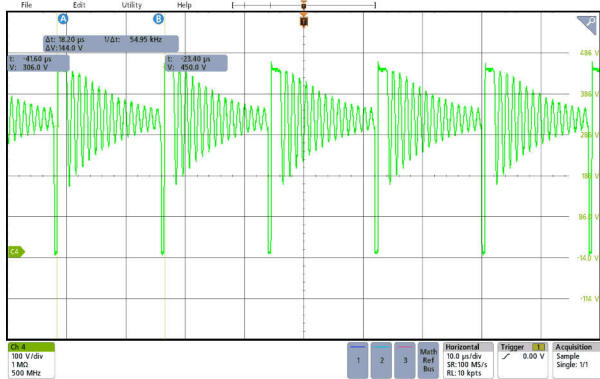


Figure 3-17. 230VAC, 20V, 0.225A, Vsw

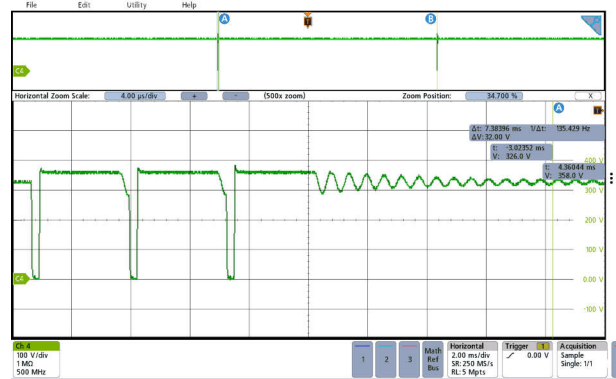


Figure 3-18. 230VAC, 5V Open Load, Vsw

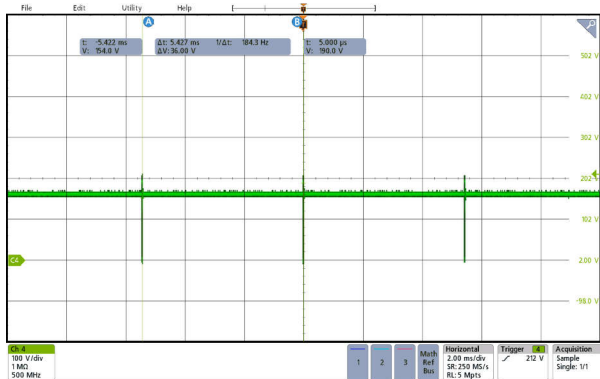


Figure 3-19. 115VAC, 5V Open Load, Vsw

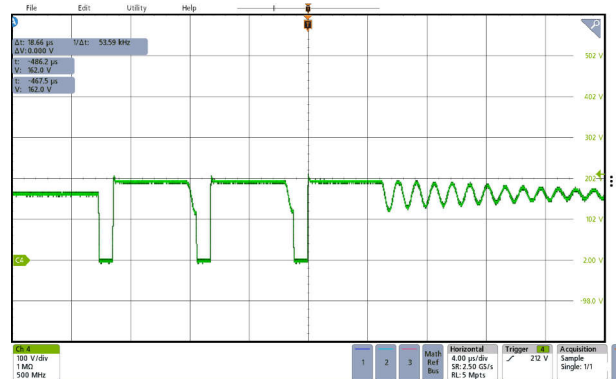


Figure 3-20. 115VAC, 5V Open Load, Vsw, Zoom

3.5 Output Voltage Ripple

Output voltage ripple is shown in [Figure 3-21](#) through [Figure 3-39](#).

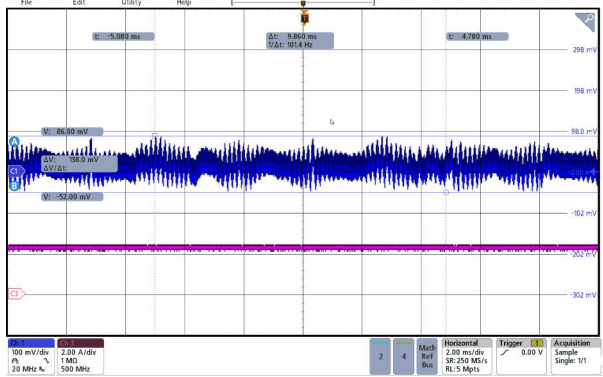


Figure 3-21. 90VAC, 20V, 45W Full Load, Output Ripple

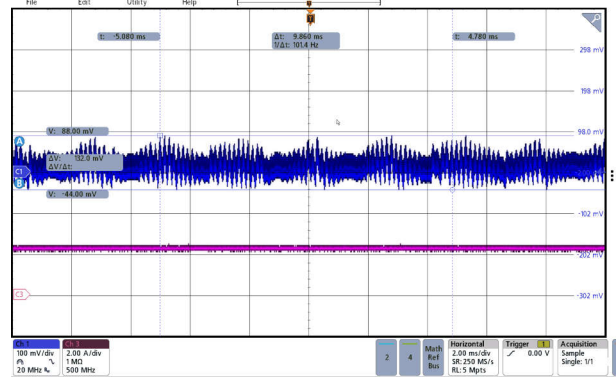


Figure 3-22. 115VAC, 20V, 45W Full Load, Output Ripple

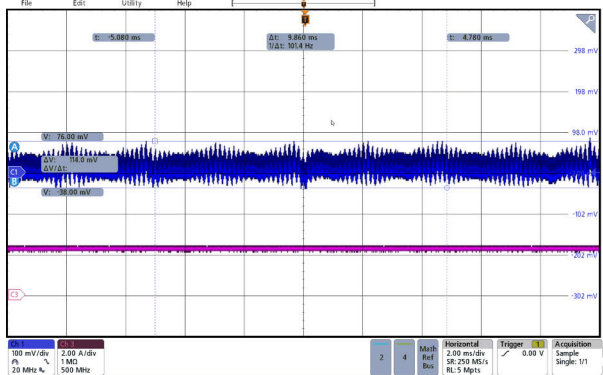


Figure 3-23. 230VAC, 20V, 45W Full Load, Output Ripple

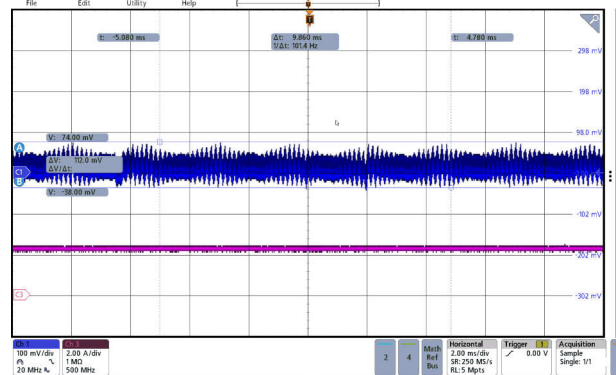


Figure 3-24. 264VAC, 20V, 45W Full Load, Output Ripple

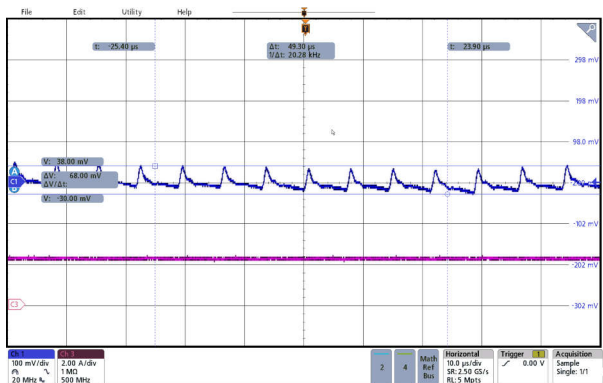


Figure 3-25. 264VAC, 20V, 45W Full Load, Output Ripple, Zoom

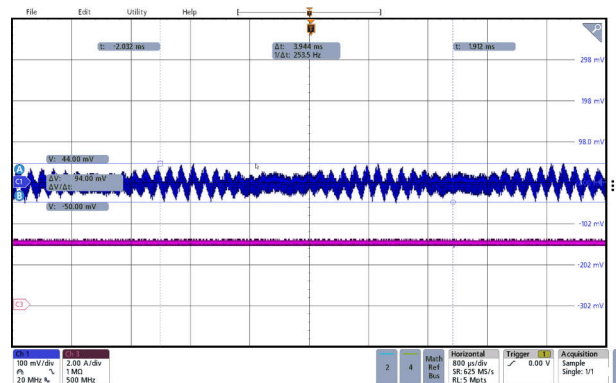


Figure 3-26. 115VAC, 5V, 3A, Output Ripple

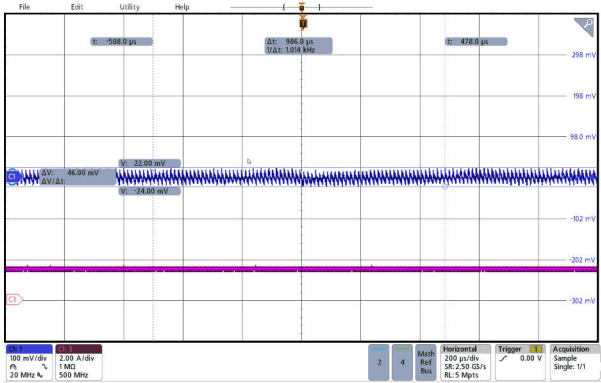


Figure 3-27. 115VAC, 5V, 1.5A, Output Ripple

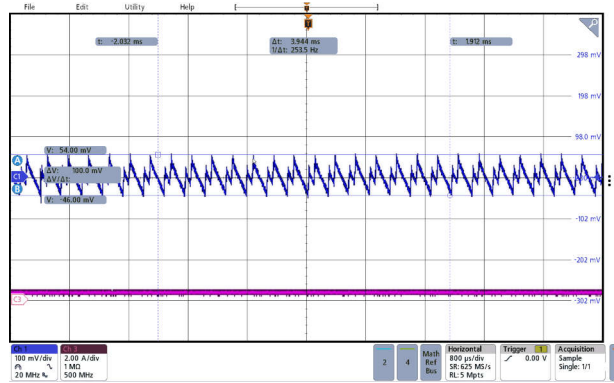


Figure 3-28. 115VAC, 5V, 0.3A, Output Ripple

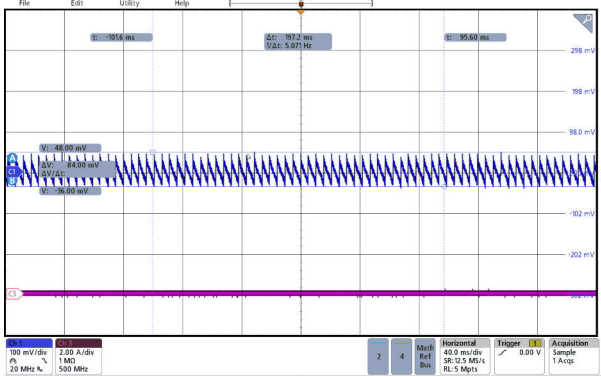


Figure 3-29. 115VAC, 5V, Open Load, Output Ripple

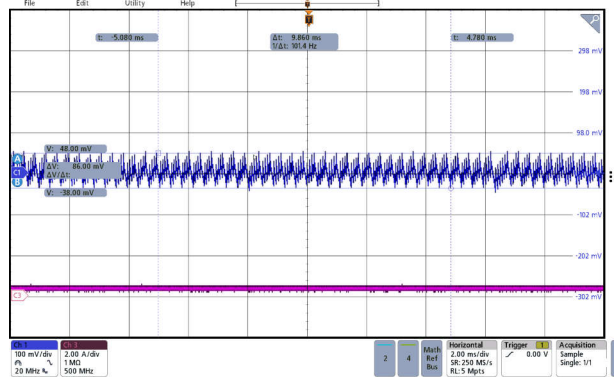


Figure 3-30. 115VAC, 9V, 0.3A, Output Ripple

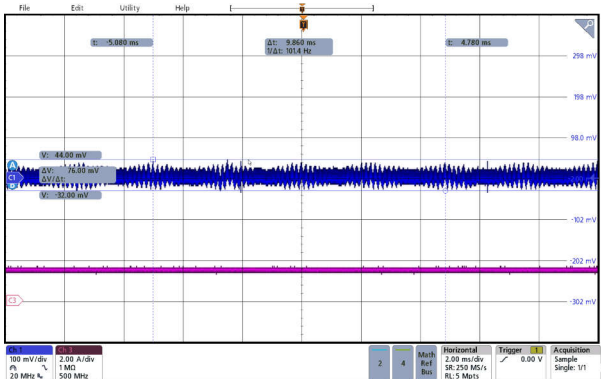


Figure 3-31. 115VAC, 9V, 1.5A, Output Ripple

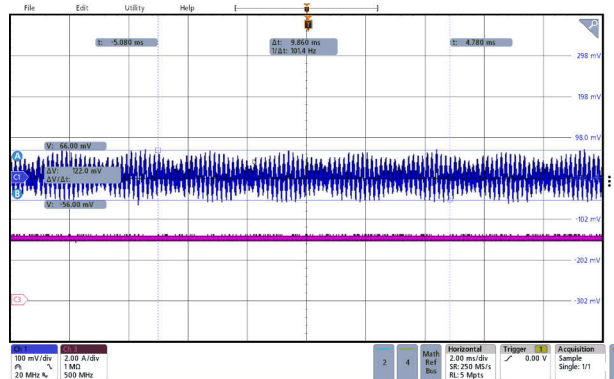


Figure 3-32. 115VAC, 9V, 3A, Output Ripple

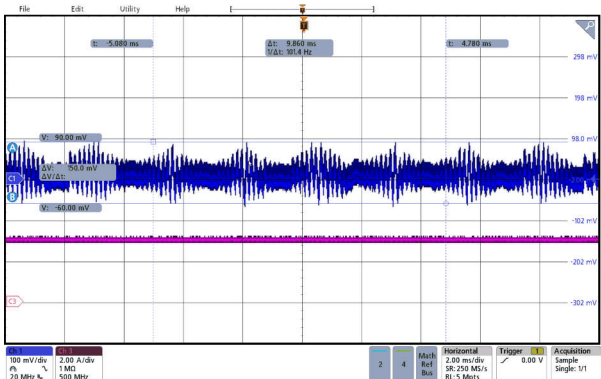


Figure 3-33. 115VAC, 15V, 3A, Output Ripple

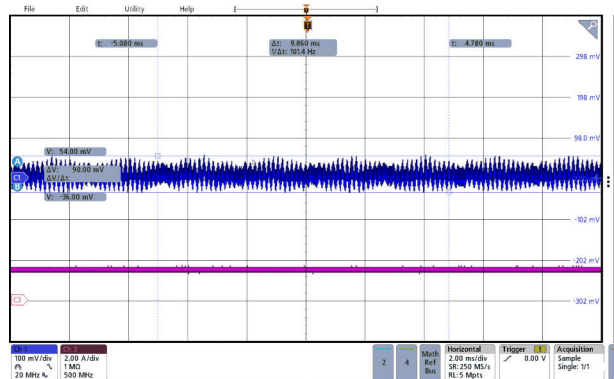


Figure 3-34. 115VAC, 15V, 1.5A, Output Ripple

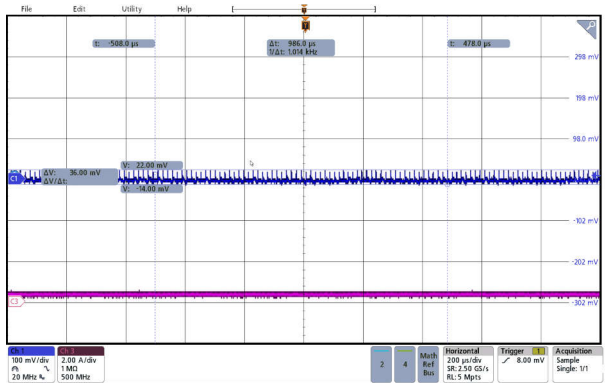


Figure 3-35. 115VAC, 15V, 0.3A, Output Ripple

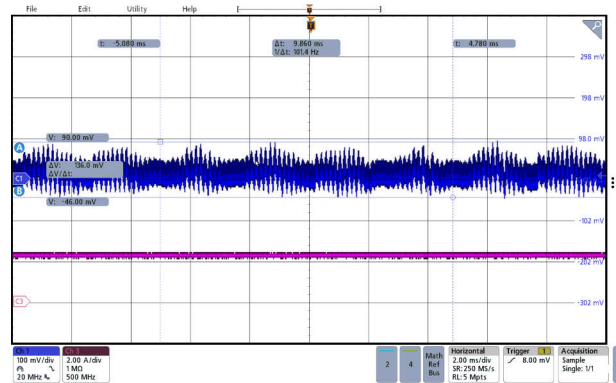


Figure 3-36. 115VAC, 20V, 2.25A, Output Ripple

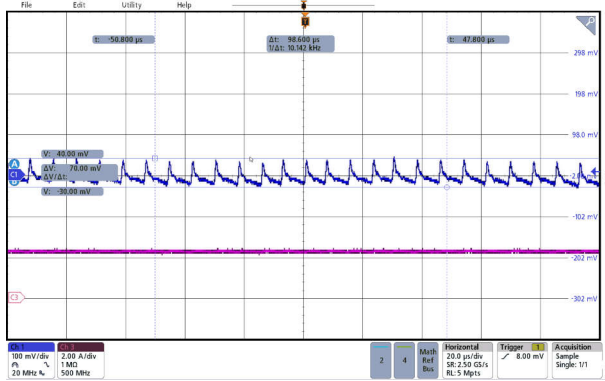


Figure 3-37. 115VAC, 20V, 2.25A, Zoom, Output Ripple, Zoom

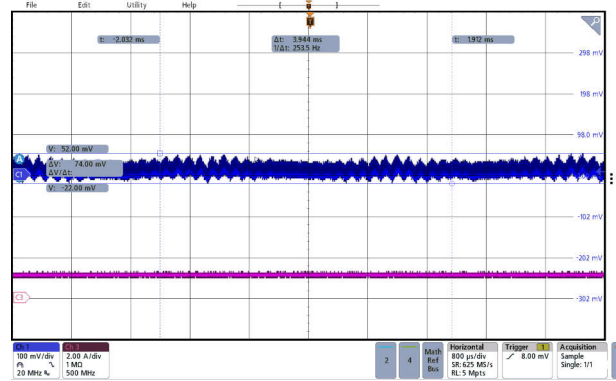


Figure 3-38. 115VAC, 20V, 1.12A, Output Ripple

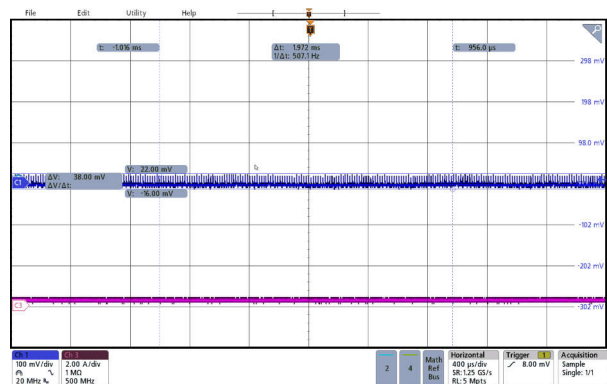


Figure 3-39. 115VAC, 20V, 0.225A, Output Ripple

3.6 Load Transient

Load transient waveform is shown in [Figure 3-40](#) through [Figure 3-44](#).

The load dynamic test was performed from 0.1A to full load. Output voltage was measured at the PCB end.

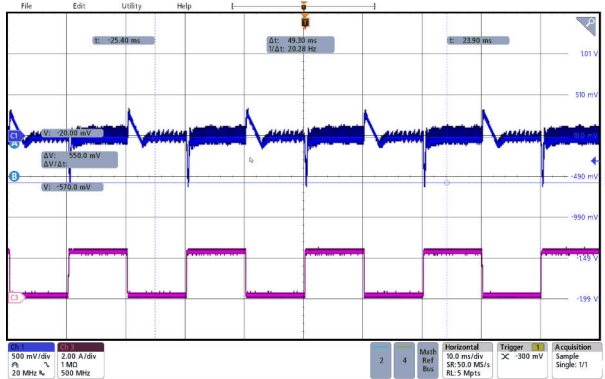


Figure 3-40. 115VAC, 20V, 0.1A to 2.25A Load Dynamic

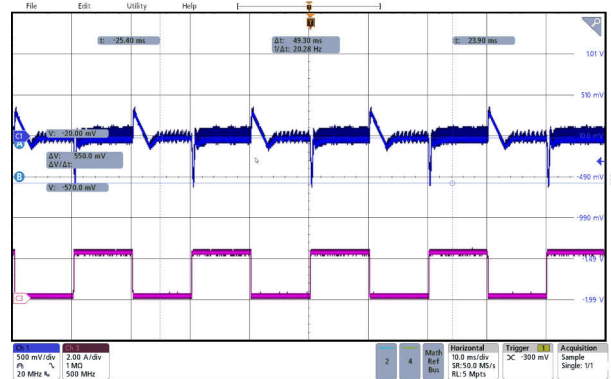


Figure 3-41. 230VAC, 20V, 0.1A to 2.25A Load Dynamic

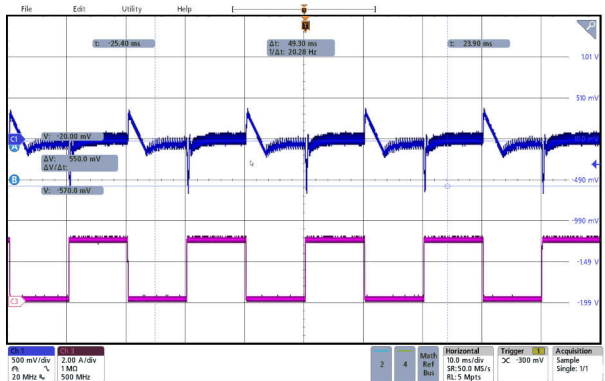


Figure 3-42. 115VAC, 5V, 0.1A to 3A Load Dynamic

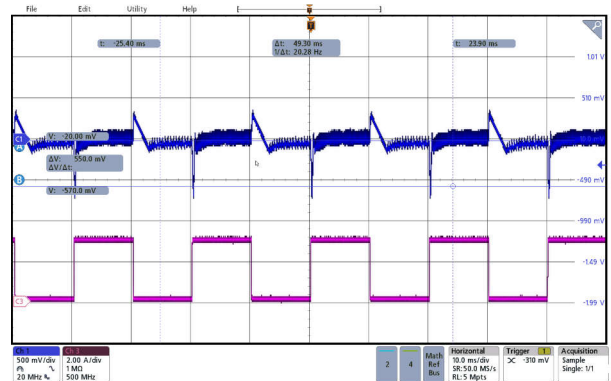


Figure 3-43. 115VAC, 9V, 0.1A to 3A Load Dynamic

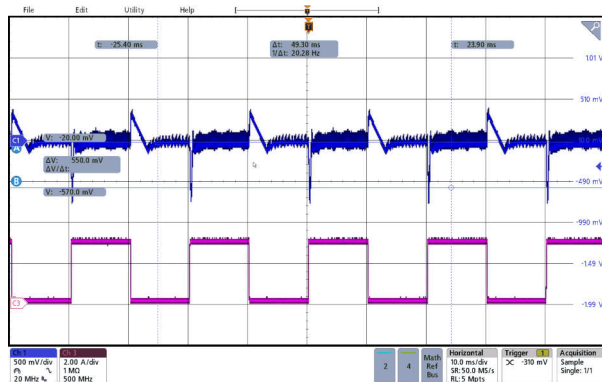


Figure 3-44. 115VAC, 15V, 0.1A to 3A Load Dynamic

3.7 Short-Circuit Protection

Short circuit protection was performed at PCB board end and goes to auto recovery after short is removed. CH1: V_{out} , CH3: I_{out} , CH4: V_{sw}

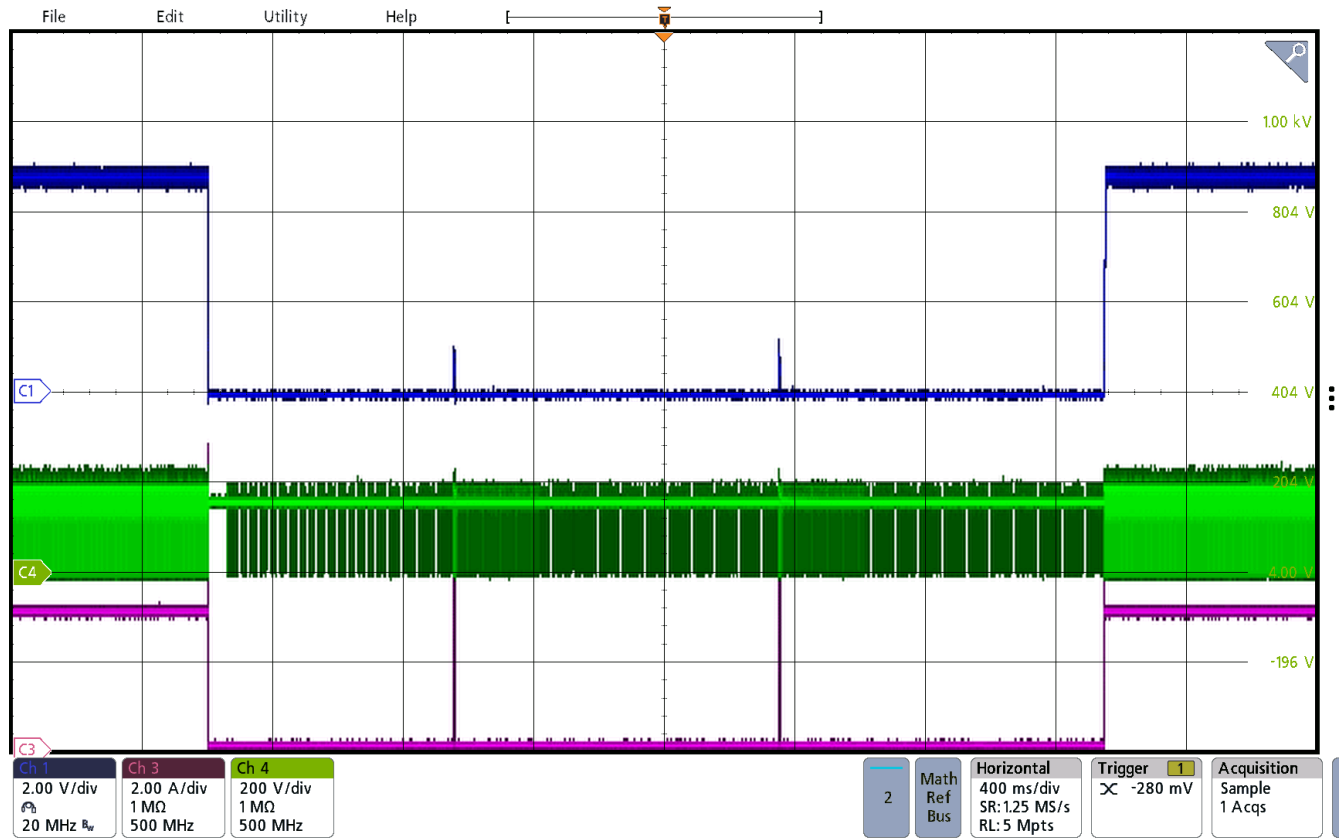


Figure 3-45. Short Circuit Protection at PCB End and Recovery After Short Removed

3.8 Feedback Loop Open Protection

By disconnecting output feedback, V_{out} ramps up and UCG28826 SW pin senses the output voltage. Once the sensed voltage triggers the OVP threshold, the OVP protection is triggered. The OVP set is latch protection.

CH2: V_{out} , CH4: Primary switching node

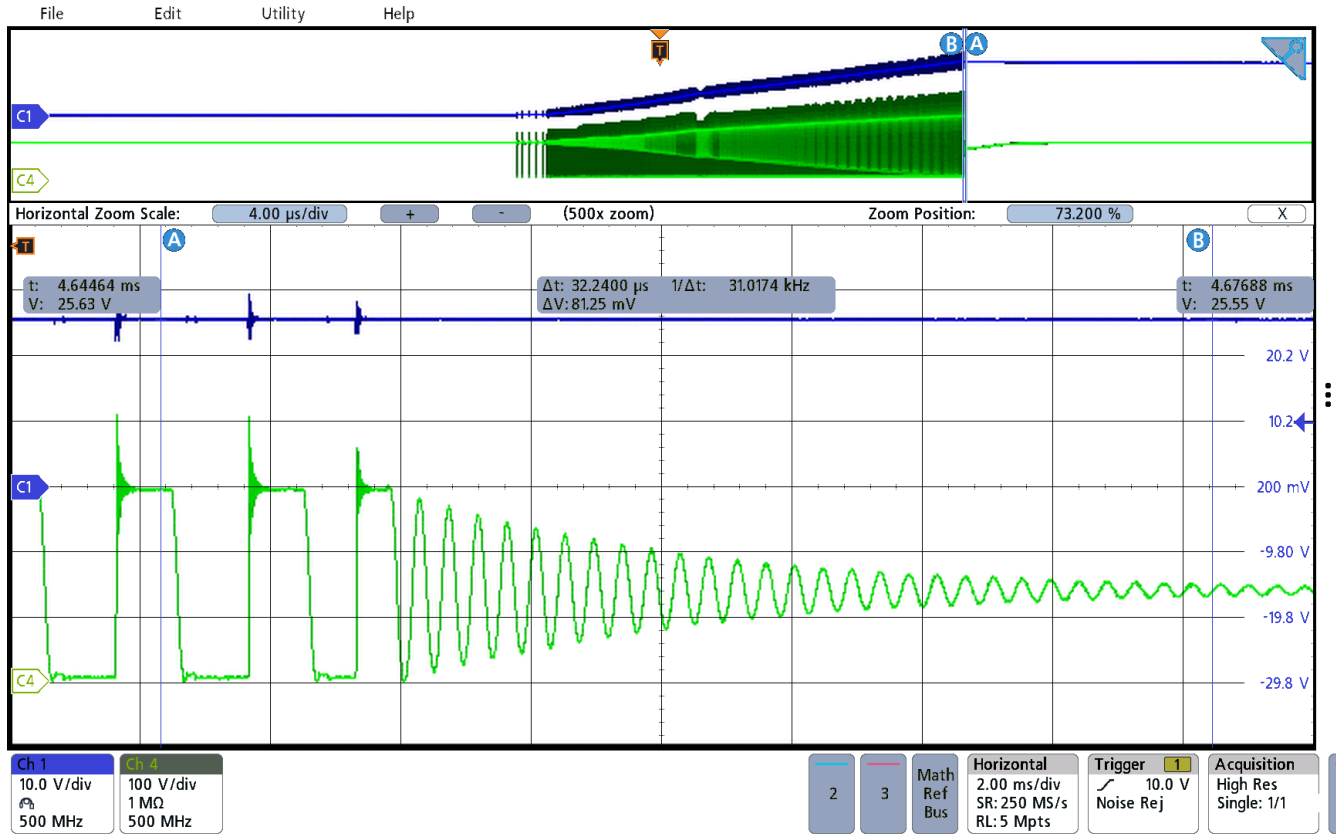


Figure 3-46. Feedback Loop Open, Output Over-Voltage Protection 25.6V

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2025, Texas Instruments Incorporated