

# Precision High-Voltage Current Sensing Using Zener-Shifted Floating Ground and Isolated Digital Interface



## Introduction

This application brief describes a compact, radiation tolerant design for accurate current measurement in high-voltage power systems where direct measurement is not possible due to limitations of available devices. By using a shifted *ground* for the sensing part of the design, low-voltage tolerant devices can be used to measure the current through a shunt resistor where the common-mode voltage is 200 to 400V.

## Application

High-voltage DC buses (80–400V) are increasingly adopted in space applications to minimize conduction losses, enabling lighter cables and connectors for mass-constrained systems. However, radiation tolerant current sense ICs are limited to less than 100V inputs, complicating integration in electric propulsion thrusters, lunar surface power generation, high-voltage battery banks, and solar panel arrays.

## Key Benefits

Higher voltage enables thinner cables, cutting system weight by up to 30%.

Radiation tolerant; 30krad, 43MeV·cm<sup>2</sup>/mg

High voltage isolation: up to 3000V (ISOS141-SEP), scalable with part selection.

Ease of integration: Digital SPI output to MCU/FPGA; no analog signals crossing voltage barrier.

## Circuit Description and Block Diagram

The design utilizes a Zener-shifted floating ground technique that allows a low-voltage current sense amplifier and an ADC to operate safely, far beyond standard IC ratings. For this application, a 4.7V zener diode was chosen. The characteristics of this part ensure that the Zener voltage does not exceed the maximum input voltage of the ADC. To create a *regulated* voltage, the Zener diode must be reverse biased with enough current to maintain the breakdown voltage. This current plus the current supplied to the amplifier and ADC passes through the bias resistor. Select a value of R bias based on the supplied voltage, Zener diode current, and the supply current needed.


$$R_{bias} = \frac{V_{in} - V_z}{I_z + I_{amp} + ADC} \quad (1)$$

A shunt resistor is used to generate the voltage input for the current sense amplifier. This voltage is amplified by a gain of 20V/V and connected directly to the ADC. The input range of the ADC is limited to the supply voltage set by the zener diode. This means that the usable voltage range on the sense resistor is 0V to: 4.7V

$$V_z / 20 \text{ V/V} \quad (2)$$

$$4.7\text{V} / 20 = 235\text{mV} \quad (3)$$


Adding a digital isolator to the ADC output allows the SPI data from the ADC to be utilized by a processor or FPGA operating at a normal voltage with a 0V ground reference.

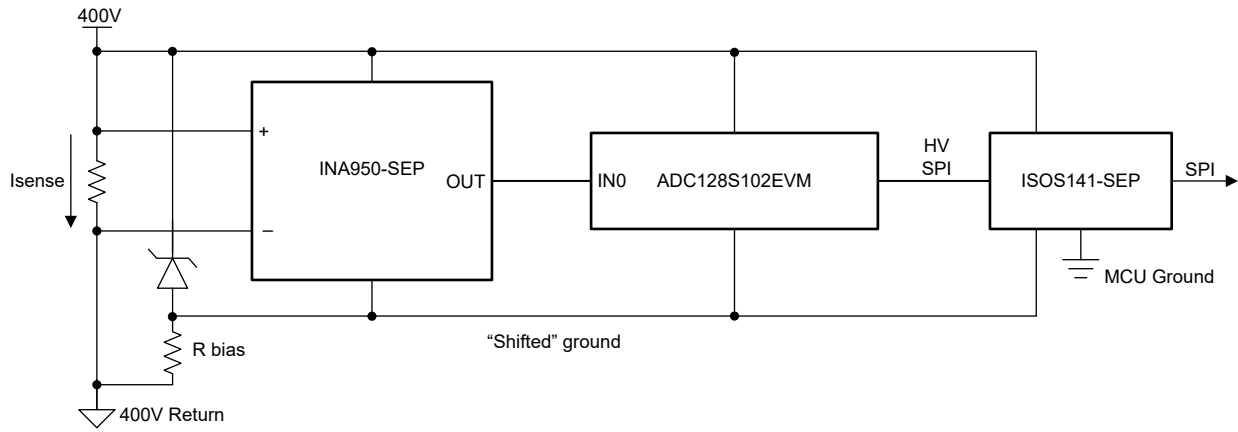

**Figure 1. Simplified Block Diagram**

### Testing

Circuit was tested by connecting INA950-SEP, ADC128S102-SEP, ISOS141-SEP EVMs according to the block diagram in [Figure 1](#). The voltage across the sense resistor adjusted in increments from 0 to 220mV. The corresponding sampled voltage was recorded from the ADC GUI. Test data was collected using the ADC128S102 EVM GUI and the ADC-PHI\_PRU\_EVM board.

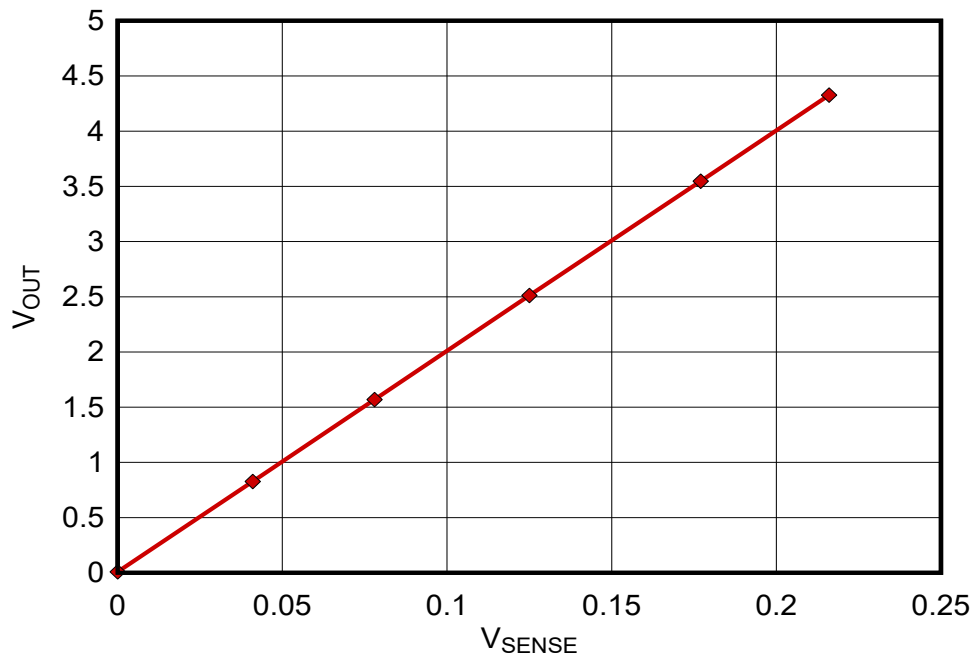

**Figure 2. Test Data**

## Target Applications

Space propulsion (Hall/Ion thrusters): 300–1000V; precise thrust vectoring through current control.

Lunar power grids: 400–1000V DC distribution; fault detection in harsh environments.

High-voltage battery banks: 400–800V packs; state-of-health monitoring.

Solar array strings: 600–1500V; per-string current for maximum power point tracking.

## Additional Resources

[\*Space-enhanced-product, 2.7V to 80V, 1.1MHz, ultra-precise, current-sense amplifier\*](#)

[\*Radiation-tolerant, eight-channel, 50-kSPS to 1-MSPS, 12-bit analog-to-digital converter \(ADC\)\*](#)

[\*Radiation tolerant quad-channel, 3/1 digital isolator in space enhanced plastic\*](#)

[\*Digital Isolator Design Guide\*](#)

[\*Adapter card to connect precision ADC evaluation modules to TMDS64GPEVM or TMDS243GPEVM PRU\*](#)

[\*Radiation Handbook for Electronics\*](#)

[\*Space Products Selection Guide\*](#)

[\*TI E2E Forums\*](#)

## Trademarks

All trademarks are the property of their respective owners.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you fully indemnify TI and its representatives against any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#), [TI's General Quality Guidelines](#), or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products. Unless TI explicitly designates a product as custom or customer-specified, TI products are standard, catalog, general purpose devices.

TI objects to and rejects any additional or different terms you may propose.

Copyright © 2025, Texas Instruments Incorporated

Last updated 10/2025