

How Comparator Topology Influences Propagation Delay

Mark Sellers

ABSTRACT

Contents

1	Abstract	2
	1.1 Trademarks	2
2	Introduction	2
3	Understanding the Supervisor Comparator	3
4	How Comparator Architecture Influences the System	4
5	Difference in Propagation Delay for Window and Undervoltage Supervisors	6
	5.1 State 1: No Fault Condition, RESET Deasserted	6
	5.2 State 2: Undervoltage Fault Condition, RESET Asserted	7
	5.3 State 3: Overvoltage Fault Condition, RESET Asserted.....	8
6	Analysis of Propagation Delay Differences.....	8
	6.1 Measuring Propagation Delay versus Overdrive Curve	8
	6.2 Analyzing the Overdrive Curve	11

List of Figures

1	Undervoltage Supervisor Block Diagram and Timing Diagram	2
2	Window Supervisor Block Diagram and Timing Diagram	3
3	Comparator with Active Pullup Current Source.....	4
4	Comparator with Push-Pull Output	4
5	Window Supervisor Architecture With a Single Output	5
6	Undervoltage Only Supervisor Architecture	6
7	Undervoltage Comparator Signal Trace	7
8	Overvoltage Comparator Signal Tracing	8
9	Measuring the Overdrive Voltage Curve.....	9
10	Current in Differential Pair for How Overdrive Voltage is Measured.....	9
11	Differential Pair Current During Normal Use.....	10
12	TPS3850 Undervoltage Propagation Delay vs Overdrive.....	11
13	TPS3850 Overvoltage Propagation Delay vs Overdrive	11

List of Tables

1	Fault Condition Based on Comparator Inputs.....	6
---	---	---

1 Abstract

When using microprocessors, field-programmable gate arrays (FPGAs), or systems-on-a-chip (SOCs) there are power supply tolerances that must be met. Because of these power supply requirements, external monitoring of the power supply is necessary to ensure that the processor is in reset mode when the supply voltage falls below (undervoltage) or rises above (overvoltage) the specified range. Many microprocessors, FPGAs, or SOC's have internal voltage monitoring, but external voltage monitoring is often necessary for redundancy. External monitoring is often required to prevent memory from being corrupted when these events occur. When external monitoring is required, there are three types of voltage monitors available: undervoltage, overvoltage, and window (a combination of undervoltage and overvoltage). As advances in the semiconductor industry continue, silicon devices have been pushed to lower and lower power levels. With an increase in the amount of products that run off of batteries, having a supervisor with a low supply current (I_{DD}) is essential. This report aims to discuss voltage supervisors and how the move towards lower power supervisors affects the propagation delay.

1.1 Trademarks

All trademarks are the property of their respective owners.

2 Introduction

Striving towards longer battery life has pushed all devices in the system to have low supply current, which is especially true of supporting circuitry that is always on (such as supervisory circuits). Supervisory circuits are used for initialization and startup, undervoltage detection, diagnostics, and adhering to safety regulations.

An undervoltage supervisor has a single comparator with hysteresis that monitors the SENSE pin voltage through a resistor divider, as shown in Figure 1. In an undervoltage supervisor when the voltage drops below the negative threshold the RESET output is asserted (driven low).

 


Figure 1. Undervoltage Supervisor Block Diagram and Timing Diagram

A window supervisor consists of two comparators, one monitoring the overvoltage threshold and one monitoring the undervoltage threshold. The signals from these two comparators are then ANDed together to make a $\overline{\text{RESET}}$ output, or can be used individually to create separate overvoltage (OV) and undervoltage (UV) outputs. Figure 2 shows the block diagram for a single $\overline{\text{RESET}}$ output window comparator. If the voltage on the SENSE pin drops below the negative threshold ($V_{IT-(UV)}$), then $\overline{\text{RESET}}$ is asserted (driven low). When the voltage on the SENSE pin is between the positive and negative threshold voltages, $\overline{\text{RESET}}$ deasserts after the $\overline{\text{RESET}}$ delay time, as shown in Figure 2.

 


Figure 2. Window Supervisor Block Diagram and Timing Diagram

3 Understanding the Supervisor Comparator

There are four main blocks to a supervisor: the voltage reference, comparator, reset delay timing, and the output (open-drain or push-pull). Figure 1 illustrates how these blocks interact to form a supervisor. This paper primarily focuses on the comparators and how different architecture choices affect both supply current and propagation delay. There are two types of outputs for comparators, one is an active pullup current source and the other is a push-pull output. Both of these topologies will work for producing a $\overline{\text{RESET}}$ signal, but each has their limitations.

Typically supervisors use the active pullup illustrated in Figure 3, as this output offers more control over the amount of supply current that is being used. When using the active pullup output, the maximum amount of current that can be used in the output stage is the current from the current source. When using the topology in Figure 4 with a push-pull output, there can be a large increase in the I_{DD} resulting from shoot-through current. Shoot-through current is where both of the transistors are on simultaneously and current passes straight through the two transistors. Using the push-pull topology, shoot-through current occurs whenever the voltage approaches the comparator threshold. In most applications this current increase is undesirable even though faster response times may result.

 


Figure 3. Comparator with Active Pullup Current Source

 


Figure 4. Comparator with Push-Pull Output

4 How Comparator Architecture Influences the System

Section 3 details why most comparators in supervisory circuits use the active pullup topology. This topology has a large impact on the system, specifically on how supply current and propagation delay is effected. The effect of comparator architecture is most evident in window comparators where there are both overvoltage and undervoltage thresholds. However, these effects can be seen in all supervisors.

Figure 5 illustrates the typical architecture for window comparators. In Figure 5 there are two comparators with a PMOS differential pair that are being loaded by an NMOS current mirror. One side of the differential pair is being tied to the reference voltage and the other side is attached to the resistor divider. All the comparators in Figure 5 and Figure 6 have the active pullup discussed in Section 3. These comparators are then followed by a Schmitt trigger and inverters. A Schmitt trigger is required on the output because this is a slow changing node. If a Schmitt trigger is not used there can be a large increase in supply current when the voltage is near the threshold.

The two comparators also have a difference in the data path that contributes to the difference in propagation delay. The undervoltage comparator only has a single inverter and the overvoltage comparator has two inverters. Because of this architecture there is a difference in propagation delay between the undervoltage and overvoltage faults. This difference comes from active load and the number of inverters. Section 5 discusses why having an active pullup on the comparators produces a difference in propagation delay.

 
 


Figure 5. Window Supervisor Architecture With a Single Output


Figure 6. Undervoltage Only Supervisor Architecture

5 Difference in Propagation Delay for Window and Undervoltage Supervisors

Table 1 shows the basic states of the two comparators along with the fault condition. In Table 1, V_{UV} is the input voltage to the undervoltage comparator and V_{OV} is the input voltage to the overvoltage comparator. Table 1 shows that when $V_{UV} > V_{REF}$ and $V_{OV} < V_{REF}$, there is no fault condition; otherwise, there is a fault condition and the supervisor is in either state 2 or 3. Now using Figure 5, each of the states will be examined to show why there is a difference in the overvoltage and undervoltage propagation delay.

Table 1. Fault Condition Based on Comparator Inputs

State	V_{UV}	V_{OV}	Fault
1	$V_{UV}^{(1)} > V_{REF}^{(2)}$	$V_{OV}^{(3)} < V_{REF}$	None
2	$V_{UV} < V_{REF}$	$V_{OV} < V_{REF}$	Undervoltage
3 ⁽²⁾	$V_{UV} > V_{REF}$	$V_{OV} > V_{REF}$	Overvoltage

⁽¹⁾ V_{UV} is the input voltage to the undervoltage comparator.

⁽²⁾ V_{REF} is the reference voltage that V_{UV} and V_{OV} are compared to.

⁽³⁾ V_{OV} is the input voltage to the overvoltage comparator.

5.1 State 1: No Fault Condition, \overline{RESET} Deasserted

In state 1 $V_{UV} > V_{REF}$ and $V_{OV} < V_{REF}$. Because of the PMOS input pair when $V_{UV} > V_{REF}$ M_2 conducts more current than M_1 ($I_2 > I_1$). When M_2 conducts more current than M_1 , M_5 turns off. The active pullup then charges the parasitic capacitance of M_5 , causing the drain of M_5 to rise to V_{DD} . In the overvoltage comparator $V_{OV} < V_{REF}$, M_6 then conducts more current than M_7 ($I_3 > I_4$), causing M_{10} to turn on and drag the drain of M_{10} to GND. Note that when there is no fault, M_5 is off and M_{10} is on.

5.2 State 2: Undervoltage Fault Condition, \overline{RESET} Asserted

There are two times when the supervisor is in state 2, the first is during startup when either V_{DD} or V_{SENSE} is still rising, the other is when the supervisor is leaving state 1 because of a transient on V_{DD} or V_{SENSE} . The most interesting case is when leaving state 1 to enter state 2 where $V_{UV} < V_{REF}$ and $V_{OV} < V_{REF}$. When in state 1, the drain of M_5 is at V_{DD} . Figure 7 shows how the signals in the differential pair and the output stage respond to the input signal V_{UV} . Upon entering state 2 V_{UV} drops below V_{REF} , causing M_1 to start conducting more current than M_2 ($I_1 > I_2$), which raises the voltage V_{G5} . As V_{G5} exceeds the threshold voltage of the NMOS device M_5 begins to turn on. As V_{G5} continues to rise V_{OUT1} begins to fall, and M_5 tries to pull this node to GND. When M_5 is turned on, an effective RC circuit is formed and the FET discharges the parasitic capacitances. The small resistance of the FET discharges this capacitance very quickly, causing the undervoltage trip to be much faster than the overvoltage; see Figure 12 and Figure 13.

 


Figure 7. Undervoltage Comparator Signal Trace

5.3 State 3: Overvoltage Fault Condition, **RESET** Asserted

An overvoltage fault causes the comparators to leave state 1 and enter state 3, $V_{UV} > V_{REF}$ and $V_{OV} > V_{REF}$. When in state 1 the drain of M_{10} is at GND. Figure 8 shows how the signals in the differential pair and the output stage respond to the input signal V_{OV} . Upon entering state 3, V_{OV} rises above V_{REF} and M_7 starts conducting more current than M_6 ($I_4 > I_3$), which causes V_{G10} to drop. As V_{G10} approaches the threshold voltage of the NMOS device M_{10} , M_{10} begins to turn off. As V_{G10} continues to fall V_{OUT2} begins to rise, and the active pullup tries to pull this node to V_{DD} . The small current source I_{OUT2} can take several microseconds to charge this node to V_{DD} because of the shoot-through current and parasitic capacitance. Because this node changes so slowly, a Schmitt trigger is required at the output to ensure there is no shoot-through current. The current source I_{OUT2} is not the only contributing factor causing the increase in propagation delay. Figure 5 also illustrates that the overvoltage comparator has a second inverter in the data path, this inverter also increases propagation delay. This extra inverter is necessary to ensure the correct logic at the output.

 


Figure 8. Overvoltage Comparator Signal Tracing

6 Analysis of Propagation Delay Differences

6.1 Measuring Propagation Delay versus Overdrive Curve

The propagation delay versus overdrive changes based on the measurement technique. There are two accepted methods for measuring the curve: the first is starting at a fixed voltage and stepping below the threshold by the required percentage. The other method is to start above the threshold by the percentage and then step below the threshold by the percentage; see Figure 9. The TPS3850 data sheet uses the second method to calculate the overdrive voltage curve. Using the second method results in a longer propagation delay than if starting at a fixed voltage and stepping above or below the threshold. The reason for this is further discussed in Figure 10. Figure 10 illustrates how the currents in the differential pair change with the overdrive voltage. When the voltage is at the trip point the currents through the two transistors are equal. However, for each measurement the voltage starts above the threshold by the overdrive voltage and then is stepped below the threshold. Starting over the threshold causes the currents to start skewed in the opposite direction of the transient. Figure 11 demonstrates that when a voltage supervisor is operated at the nominal monitored threshold one transistor in the differential pair conducts more current than the other. Then when the voltage is stepped below the threshold the amount of current through each transistor changes as M_1 begins to conduct more current than M_2 in an undervoltage supervisor.

 


Figure 9. Measuring the Overdrive Voltage Curve

 


Figure 10. Current in Differential Pair for How Overdrive Voltage is Measured


 
 


Figure 11. Differential Pair Current During Normal Use

 6.2 Analyzing the Overdrive Curve

As discussed in Figure 5 the overvoltage and undervoltage comparator have different propagation delay versus overdrive curves. There are three main factors that effect the propagation delay timing: the architecture of the comparator, the monitored threshold voltage of the comparator, and the measurement technique. The overvoltage comparator takes longer to respond than the undervoltage comparator, as shown in Figure 12 and Figure 13. Figure 12 shows that the propagation delay for the undervoltage comparator is approximately 40 μs faster than the overvoltage comparator. There is also a difference in the different voltage options. When comparing a 5-V supervisor and a 1.8-V supervisor there is an obvious difference in the propagation delay curves. The 5-V part has less propagation delay for the same percentage overdrive, which is largely a result of overdrive being measured in percentages. A 4% step over the threshold is approximately three times greater in magnitude for a 5-V threshold than the 1.8-V threshold.



IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2017, Texas Instruments Incorporated