



Daniel Hartung

ABSTRACT

The TPS7H500X family of devices can be used as a voltage mode converter with minimal changes. Using the internal ramp generated by the slope compensation circuit is all that is needed in order to generate the required ramp for voltage mode control.

Table of Contents

1 Introduction.....	2
2 Implementation.....	2
3 Summary.....	3
4 References.....	3

Trademarks


All trademarks are the property of their respective owners.

1 Introduction


The main difference between voltage mode and current mode control from an electrical implementation standpoint is how the control ramp that is compared to the error voltage is generated. For a current mode control design the ramp will be generated by sensing the current going through the control switch.

2 Implementation

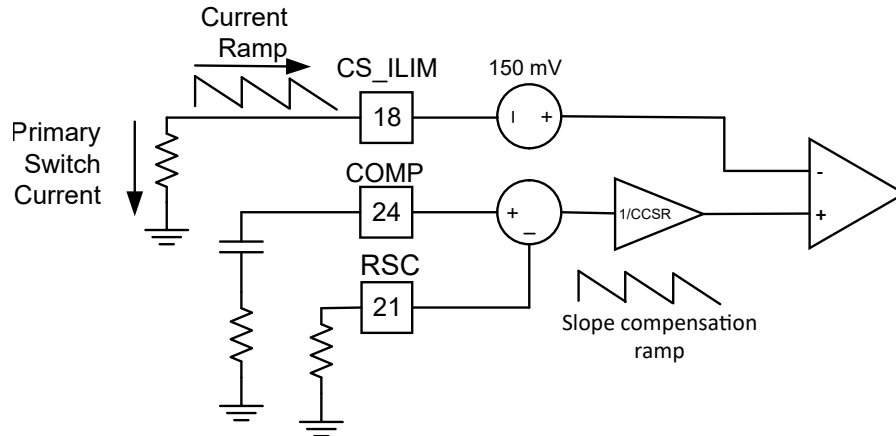For the TPS7H500X family of devices the current ramp information is done as an input into the CS_ILIM pin.



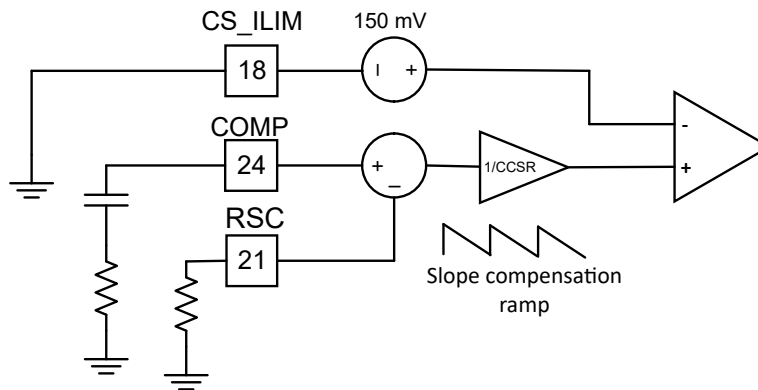By grounding the CS_ILIM pin and then changing the value of the RSC resistor, voltage mode can be achieved



The equation below details the RSC resistor value that will allow for the full output range of error amplifier to be used. Values below and above this value will still allow for the converter to run, but being close to this value is advised.

$$SC = f_{SW} \times 2V \tag{1}$$

Where f_{SW} is in MHz

$$R_{SC} = \frac{28.3}{SC^{1.1}} \tag{2}$$

Current limiting is disabled by doing using this method for voltage mode. One method for how to add a current limit is detailed in [Space-Grade, Overcurrent Protection Circuit for TPS7H500x-SP Family of Devices Using the INA901-SP](#)

Equations for compensation of voltage mode control a good reference is [Switch-mode power converter compensation made easy](#).

Two designs that use voltage mode control with the TPS7H500X family of devices are the [PMP23193](#) and the [PMP23552](#).

3 Summary

With proper techniques the TPS7H500X family of devices can be used as a voltage mode converter. Using the built in slope compensation, one can implement the control scheme with minimal external components. This method saves space over the more traditional method of generating the ramp signal from a resistor and capacitor combination.

4 References

1. Texas Instruments, [TPS7H500x-SP Radiation-Hardness-Assured 2MHz Current Mode PWM Controllers](#), datasheet.
2. Texas Instruments, [PMP23193](#), product page.
3. Texas Instruments, [PMP23552](#), product page.
4. Texas Instruments, [Switch-mode power converter compensation made easy](#), seminar.
5. Texas Instruments, [Space-Grade, Overcurrent Protection Circuit for TPS7H500x-SP Family of Devices Using the INA901-SP](#), application brief.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you fully indemnify TI and its representatives against any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#), [TI's General Quality Guidelines](#), or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products. Unless TI explicitly designates a product as custom or customer-specified, TI products are standard, catalog, general purpose devices.

TI objects to and rejects any additional or different terms you may propose.

Copyright © 2026, Texas Instruments Incorporated

Last updated 10/2025