

Understanding Basic Analog – Ideal Op Amps

Ron Mancini
Mixed Signal Products

ABSTRACT

This application report develops the equations for the ideal operational amplifier (op amp). It assumes that salient parameters are perfect. Several examples of op amp circuits are described.

Contents

Introduction	2
The Noninverting Op Amp	3
The Inverting Op Amp	4
The Adder	4
The Differential Amplifier	5
Complex Feedback Networks	6
Video Amplifiers	7
Capacitors	8
Conclusions	9

List of Figures

1 The Noninverting Op Amp	3
2 The Inverting Op Amp	4
3 The Adder Circuit	4
4 The Differential Amplifier	5
5 Differential Amplifier With Common-Mode Input Signal	6
6 T Network in Feedback Loop	6
7 Thevenin’s Theorem Applied to T Network	7
8 Video Amplifier	8
9 Low-Pass Filter	8
10 High-Pass Filter	9

Introduction

The name *Ideal Op Amp* is applied to this and similar analysis because the salient parameters of the op amp are assumed to be perfect. There is no such thing as an ideal op amp, but present day op amps come so close to ideal that *Ideal Op Amp* analysis becomes close to actual analysis. Op amps depart from the ideal in two ways. First, dc parameters, such as input offset voltage, are large enough to cause departure from the ideal. The ideal assumes that input offset voltage is zero. Second, ac parameters, such as gain, are a function of frequency, so they go from large values at dc to small values at high frequencies. Both error sources are treated in later *Understanding* application notes published in this series.

This assumption simplifies the analysis, thus it clears the path for insight. It is so much easier to see the forest when brush and huge trees do not surround you. Although the ideal op amp analysis makes use of perfect parameters, the analysis is often valid because some op amps approach perfection. In addition, when working at low frequencies, several kHz, the ideal op amp analysis produces accurate answers. Voltage feedback op amps are covered in this application note, and current feedback op amps are covered in later application notes.

Several assumptions have to be made before the ideal op amp analysis can proceed. First, assume that the current flow into the input leads of the op amp is zero. This assumption is almost true in FET op amps where input currents can be less than a pA, but this is not always true in bipolar high-speed op amps where tens of μA input currents are found.

Second, the op amp gain is assumed to be infinite, hence it drives the output voltage to any value required to satisfy the input conditions. This assumes that the op amp output voltage can achieve any value. Saturation occurs when the output voltage comes close to a power supply rail, but reality does not negate the assumption, it only bounds it.

Also, implicit in the infinite gain assumption is the need for zero input signal. The gain drives the output voltage until the voltage between the input leads (the error voltage) is zero. This leads to the third assumption that the voltage between the input leads is zero. The implication of zero voltage between the input leads means that if one input is tied to a hard voltage source such as ground, then the other input is at the same potential. The current flow into the input leads is zero, so the input impedance of the op amp is infinite.

Four, the output impedance of the ideal op amp is zero. The ideal op amp can drive any load without an output impedance dropping voltage across it. The output impedance of most op amps is a fraction of an ohm for low current flows, so this assumption is valid in most cases. Five, the frequency response of the ideal op amp is flat; this means that the gain does not vary as frequency increases. By constraining the use of the op amp to the low frequencies, we make the frequency response assumption true.

PARAMETER NAME	PARAMETERS SYMBOL	VALUE
Input current	I_{IN}	0
Input offset voltage	V_{OS}	0
Input impedance	Z_{IN}	∞
Output impedance	Z_{OUT}	0
Gain	a	∞

The Noninverting Op Amp

The noninverting op amp has the input signal connected to its noninverting input, thus its input source sees an infinite impedance. There is no input offset voltage because $V_{OS} = V_E = 0$, hence the negative input must be at the same voltage as the positive input. The op amp output drives current into R_F until the negative input is at the voltage, V_{IN} . This action causes V_{IN} to appear across R_G .

The voltage divider rule is used with V_{OUT} being the input to the voltage divider, and V_{IN} being the output of the voltage divider. Since no current can flow into either op amp lead, use of the voltage divider rule is allowed. Equation 1 is written with the aid of the voltage divider rule, and algebraic manipulation yields equation 2 in the form for a gain parameter.

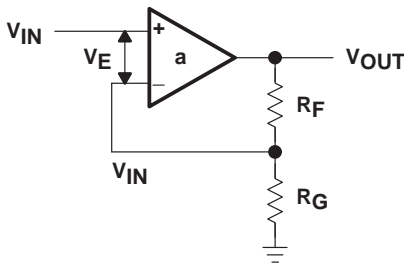


Figure 1. The Noninverting Op Amp

$$V_{IN} = V_{OUT} \frac{R_G}{R_G + R_F} \quad (1)$$

$$\frac{V_{OUT}}{V_{IN}} = \frac{R_G + R_F}{R_G} = 1 + \frac{R_F}{R_G} \quad (2)$$

When R_G becomes very large with respect to R_F , $R_F/R_G \Rightarrow 0$ and equation 2 reduces to equation 3.

$$V_{OUT} = 1 \quad (3)$$

Under these conditions $V_{OUT} = 1$ and the circuit becomes a unity gain buffer. R_G is usually deleted to achieve the same results, and when R_G is deleted, R_F can also be deleted (R_F must be shorted when it is deleted). When R_F and R_G are deleted, the op amp output is connected to its inverting input with a wire. Some op amps are self-destructive when R_F is left out of the circuit, so R_F is used in many buffer designs. When R_F is included in a buffer circuit, its function is to protect the inverting input from an over voltage, and it can have almost any value (20k is often used). R_F can never be left out of the circuit in a current feedback amplifier design because R_F determines stability in current feedback amplifiers.

Notice that the gain is only a function of the feedback and gain resistors, so the feedback has accomplished its function of making the gain independent of the op amp parameters. The gain is adjusted by varying the ratio of the resistors. The actual resistor values are determined by the impedance levels that the designer wants to establish. If $R_F = 10K$ and $R_G = 10K$ the gain is two as shown in equation 2, and if $R_F = 100K$ and $R_G = 100K$ the gain is still two. The impedance levels of 10 K or 100 K determine the current drain, the effect stray capacitance will have, and a few other points. The impedance level does not set the gain; the ratio of R_F/R_G does.

The Inverting Op Amp

The noninverting input of the inverting op amp circuit is grounded. One assumption we made is that the input error voltage is zero, so the feedback keeps inverting the input of the op amp at a virtual ground (not actual ground but acting like ground). The current flow in the input leads is assumed to be zero, hence the current flowing through R_G equals the current flowing through R_F . Using Kirchoff's law, we write equation 4. Algebraic manipulation gives us equation 5.

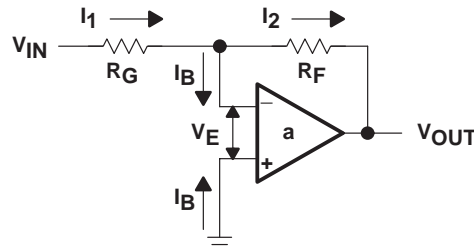


Figure 2. The Inverting Op Amp

$$I_1 = \frac{V_{IN}}{R_G} = -I_2 = -\frac{V_{OUT}}{R_F} \quad (4)$$

$$\frac{V_{OUT}}{V_{IN}} = -\frac{R_F}{R_G} \quad (5)$$

Notice that the gain is only a function of the feedback and gain resistors, so the feedback has accomplished its function of making the gain independent of the op amp parameters. The actual resistor values are determined by the impedance levels that the designer wants to establish. If $R_F=10K$ and $R_G=10K$ the gain is minus one as shown in equation 5, and if $R_F=100K$ and $R_G=100K$ the gain is still minus one. The impedance levels of 10K or 100K determine the current drain, the effect stray capacitance will have, and a few other points, but the impedance level does not set the gain; the ratio of R_F/R_G does.

One final note; the output signal is the input signal amplified and inverted. The input impedance is set by R_G because the inverting input lead is held at a virtual ground.

The Adder

An adder circuit can be made by connecting more inputs to the inverting op amp. The opposite end of the resistor connected to the inverting input is held at virtual ground by the feedback; therefore, adding new inputs does not affect the response of the existing inputs.

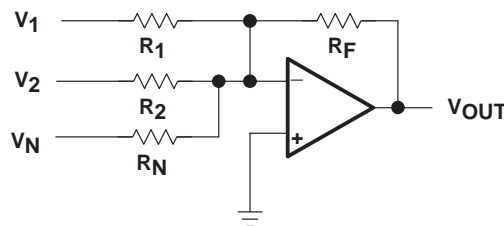


Figure 3. The Adder Circuit

Superposition is used to calculate the output voltages resulting from each input, and the output voltages are added algebraically to obtain the total output voltage. Equation 6 is the output equation when V_1 and V_2 are grounded. Equations 7 and 8 are the other superposition equations, and the final result is given in equation 9.

$$V_{OUTN} = -\frac{R_F}{R_N} V_N \quad (6)$$

$$V_{OUT1} = -\frac{R_F}{R_1} V_1 \quad (7)$$

$$V_{OUT2} = -\frac{R_F}{R_2} V_2 \quad (8)$$

$$V_{OUT} = -\left(\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 + \frac{R_F}{R_N} V_N\right) \quad (9)$$

The Differential Amplifier

The differential amplifier circuit amplifies the difference between signals applied to the inputs. Superposition is used to calculate the output voltage resulting from each input voltage, and then the two output voltages are added to arrive at the final output voltage.

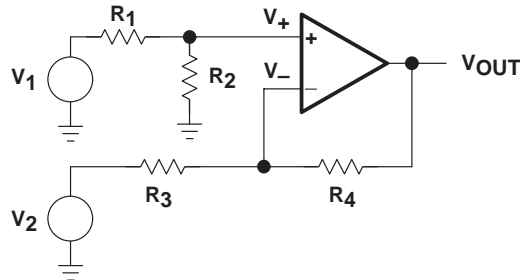


Figure 4. The Differential Amplifier

The op amp input voltage resulting from the input source, V_1 , is calculated in equations 10 and 11. The voltage divider rule is used to calculate the voltage, V_+ , and the noninverting gain equation (equation 2) is used to calculate the noninverting output voltage, V_{OUT1} .

$$V_+ = V_1 \frac{R_2}{R_1 + R_2} \quad (10)$$

$$V_{OUT1} = V_+(G_+) = V_1 \frac{R_2}{R_1 + R_2} \left(\frac{R_3 + R_4}{R_3}\right) \quad (11)$$

The inverting gain (equation 5) is used to calculate the stage gain for V_{OUT2} in equation 12. These inverting and noninverting gains are added in equation 13.

$$V_{OUT2} = V_2 \left(-\frac{R_4}{R_3}\right) \quad (12)$$

$$V_{OUT} = V_1 \frac{R_2}{R_1 + R_2} \left(\frac{R_3 + R_4}{R_3}\right) - V_2 \frac{R_4}{R_3} \quad (13)$$

When $R_2 = R_4$ and $R_1 = R_3$, equation 13 reduces to equation 14.

$$V_{OUT} = (V_1 - V_2) \frac{R_4}{R_3} \quad (14)$$

It is now obvious that the differential signal, $(V_1 - V_2)$, is multiplied by the stage gain, so the name differential amplifier suits the circuit. Because it only amplifies the differential portion of the input signal, it rejects the common-mode portion of the input signal. A common-mode signal is illustrated in Figure 5. Because the differential amplifier strips off or rejects the common-mode signal, this circuit configuration is often employed to strip dc or injected common-mode noise off a signal.

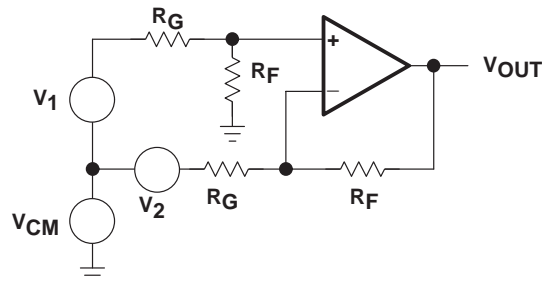


Figure 5. Differential Amplifier With Common-Mode Input Signal

The disadvantage of this circuit is that the two input impedances cannot be matched when it functions as a differential amplifier, thus there are two and three op amp versions of this circuit specially designed for high performance applications requiring matched input impedances.

Complex Feedback Networks

When complex feedback networks are put into the feedback loop, the circuits get harder to analyze because the gain equations can not be used. The usual technique is to write node or loop equations, and to solve these equations. Because a component is grounded, superposition is not of any use, but Thevenin's theorem usually can be used as is shown in the example problem given below.

Sometimes it is desirable to have a low resistance path to ground in the feedback loop. Standard inverting op amps can not do this when the driving circuit sets the input resistor value, and the gain specification sets the feedback resistor value. Inserting a *T* network in the feedback loop yields a degree of freedom that enables both specifications to be met with a low dc resistance path in the feedback loop.

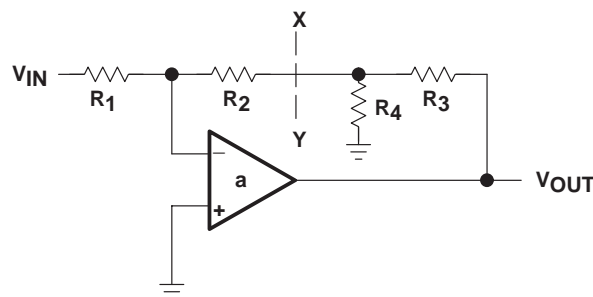


Figure 6. T Network in Feedback Loop

Break the circuit at point X–Y, stand on the terminals looking into R_4 , and calculate the Thevenin equivalent voltage as shown in equation 15. The Thevenin equivalent impedance is calculated in equation 16.

$$V_{TH} = V_{OUT} \frac{R_4}{R_3 + R_4} \quad (15)$$

$$R_{TH} = R_3 \parallel R_4 \quad (16)$$

Replace the output circuit with the Thevenin equivalent circuit as shown in Figure 7, and calculate the gain with the aid of the inverting gain equation as shown in equation 17.

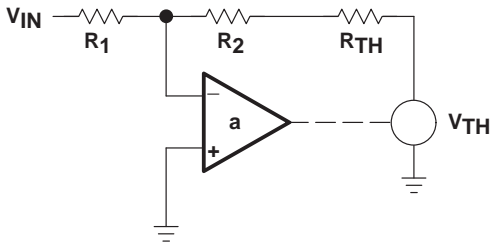


Figure 7. Thevenin's Theorem Applied to T Network

Substituting the Thevenin equivalents into equation 17 yields equation 18.

$$-\frac{V_{TH}}{V_{IN}} = \frac{R_2 + R_{TH}}{R_1} \quad (17)$$

$$-\frac{V_{OUT}}{V_{IN}} = \frac{R_2 + R_{TH}}{R_1} \left(\frac{R_3 + R_4}{R_4} \right) = \frac{R_2 + (R_3 \parallel R_4)}{R_1} \left(\frac{R_3 + R_4}{R_4} \right) \quad (18)$$

Algebraic manipulation yields equation 19.

$$-\frac{V_{OUT}}{V_{IN}} = \frac{R_2 + R_3 + \frac{R_2 R_3}{R_4}}{R_1} \quad (19)$$

Specifications for the circuit you are required to build are an inverting amplifier with an input resistance of 10K ($R_G = 10K$), a gain of 100, and a feedback resistance of 20K or less. The inverting op amp circuit can not meet these specifications because R_F must equal 1000K. Inserting a T network with $R_2 = R_4 = 10K$ and $R_3 = 485K$ does meet the specifications.

Video Amplifiers

Video signals contain high frequencies, and they use coaxial cable to transmit and receive signals. The cable connecting these circuits has a characteristic impedance of 75 Ω . To prevent reflections, which cause distortion and ghosting, the input and output circuit impedances must match the 75 Ω cable.

Matching the input impedance is simple for a noninverting amplifier because its input impedance is very high; just make $R_{IN} = 75 \Omega$. R_F and R_G can be selected as very high values, in the k Ω range, so that they have minimal affect on the impedance of the input or output circuit. A matching resistor, R_M , is placed in series with the op amp output to raise its output impedance to 75 Ω ; a terminating resistor, R_T , is placed at the input of the next stage to match the cable.

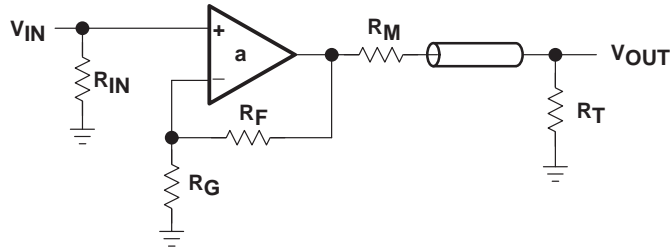


Figure 8. Video Amplifier

The matching and terminating resistors are equal in value, and they form a voltage divider of $1/2$ because R_T is not loaded. Very often R_F is selected equal to R_G so that the op amp gain equals two. Then the system gain, which is the op amp gain multiplied by the divider gain, is equal to one ($2 \times 1/2 = 1$).

Capacitors

Capacitors are a key component in a circuit designer's tool kit, thus a short discussion on evaluating their affect on circuit performance is in order. Capacitors have an impedance of $X_C = 1 \div (2\pi fC)$. Note that when the frequency is zero the capacitive impedance (also known as reactance) is infinite, and that when the frequency is infinite the capacitive impedance is zero. These end-points are derived from the final value theorem, and they are used to get a rough idea of the affect of a capacitor. When a capacitor is used with a resistor, they form what is called a break-point. Without going into complicated math, just accept that the break frequency occurs at $f = 1/(2\pi RC)$ and the gain is -3 dB at the break frequency.

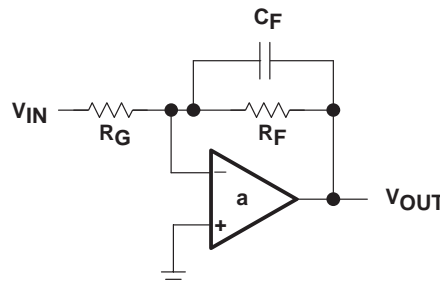


Figure 9. Low-Pass Filter

The low pass filter circuit has a capacitor in parallel with the feedback resistor. The gain for the low pass filter is given in equation 20.

$$\frac{V_{OUT}}{V_{IN}} = - \frac{X_C \parallel R_F}{R_G} \quad (20)$$

At very low frequencies $X_C \Rightarrow \infty$, so R_F dominates the parallel combination in equation 20, and the capacitor has no effect. The gain at low frequencies is $-R_F/R_G$. At very high frequencies $X_C \Rightarrow 0$, so the feedback resistor is shorted out, thus reducing the circuit gain to zero. At the frequency where $X_C = R_F$ the gain is reduced to half or -3 dB because equal impedances in parallel equal half the value of either impedance.

Connecting the capacitor in parallel with R_G where it has the opposite effect makes a high pass filter. Equation 21 gives the equation for the high pass filter.

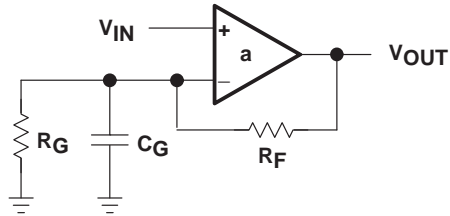


Figure 10. High-Pass Filter

$$\frac{V_{OUT}}{V_{IN}} = 1 + \frac{R_F}{X_C \parallel R_G} \quad (21)$$

At very low frequencies $X_C \Rightarrow \infty$, so R_G dominates the parallel combination in equation 21, and the capacitor has no effect. The gain at low frequencies is $1+R_F/R_G$. At very high frequencies $X_C \Rightarrow 0$, so the gain setting resistor is shorted out thus increasing the circuit gain to maximum.

This simple technique is used to predict the form of a circuit transfer function rapidly. Better analysis techniques are presented in more advanced application notes for those applications requiring more precision.

Conclusions

When the proper assumptions are made, the analysis of op amp circuits is straightforward. These assumptions, which include zero input current, zero input offset voltage, and infinite gain, are not an unrealistic assumption because the new op amps make them true in many applications.

When the signal is comprised of low frequencies, the gain assumption is valid because op amps have very high gain at low frequencies. When CMOS op amps are used, the input current is in the femto amp range; close enough to zero for most applications. Laser trimmed input circuits reduce the input offset voltage to a few micro volts; close enough to zero for most applications. The ideal op amp is becoming real; especially for undemanding applications.

The math required for ideal op amp analysis is not rigorous, thus most people should be able to analyze simple op amp circuits. The more advanced applications require complex op amp circuits, but there are many of these shown in the applications literature. Grab a TI op amp and have fun.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com