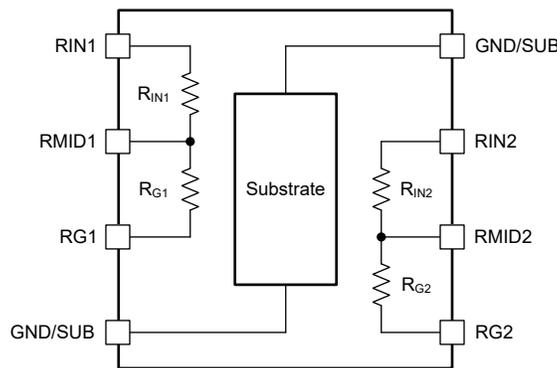


Navigating Precision Resistor Networks



What are matched resistor pairs?

A resistor pair is made up of two resistors connected in series making up a resistor divider. With matched pairs, each pair functions independently and is made up of an R_{IN} and an R_G with $R_{IN1} = R_{IN2}$ and $R_{G1} = R_{G2}$. A tap point can be found between the resistors of each divider, labeled R_{MID1} and R_{MID2} in the [Functional Block Diagram](#). Additionally, one of the two GND pins can be used to bias the substrate for best AC performance.



Functional Block Diagram

To determine the value of the resistors, consider the ratio of the RES11Axx device in question. The divider ratio for a resistor pair is R_{IN} divided by R_G , where R_{IN} is fixed to 1k Ω for all RES11A-Q1 and R_G is the variable gain resistor that sets the dividing ratio. Each orderable part number (OPN) is associated with a different ratio, as noted in the [RES11A-Q1 Ratios](#) table. For example, a RES11A20 has a 1:2 ratio, thus the resistor has a 1k Ω R_{IN} and a 2k Ω R_G . For additional specifications see the [RES11A-Q1 Automotive, Matched, Thin-Film Resistor Dividers With 1-k \$\Omega\$ Inputs](#) data sheet.

RES11A-Q1 Ratios

OPN	R_{IN} (Nominal)	R_G (Nominal)	Maximum Differential Divider Voltage (R_{INX} Pin to R_{GX} Pin) ¹
RES11A00	1k Ω	10k Ω	44.7V
RES11A10	1k Ω	1k Ω	24.4V
RES11A15	1k Ω	1.5k Ω	20.3V
RES11A16	1k Ω	1.667k Ω	19.9V
RES11A20	1k Ω	2k Ω	18.3V
RES11A25	1k Ω	2.5k Ω	28.4V
RES11A30	1k Ω	3k Ω	32.5V
RES11A40	1k Ω	4k Ω	30.5V
RES11A50	1k Ω	5k Ω	29.9V
RES11A90	1k Ω	9k Ω	40.7V

¹ The maximum sustained differential voltage rating per divider is determined by a number of factors, including the maximum junction temperature and the self-heating associated with a given voltage and divider impedance. See the specifications section of the [RES11A-Q1 Automotive, Matched, Thin-Film Resistor Dividers With 1-k \$\Omega\$ Inputs](#) data sheet for more details.

Ratio Tolerance vs Initial Tolerance

The RES11A-Q1 features a $\pm 0.05\%$ maximum ratio tolerance (t_{D1} and t_{D2}) meaning that the ratio of $R_{IN1}:R_{G1}$ and $R_{IN2}:R_{G2}$ are at most 0.05% off of the specified ratio values at a room temperature of 25°C. The initial tolerance (t_{abs}) of 14% refers to the part-to-part variation of the individual resistors to the nominal or printed resistance. The four resistors within the device track each other much more closely, with a typical absolute error span of 235 ppm. This means a RES11A-Q1 (which has a nominal R_{IN1} of 1k Ω) can have an R_{IN1} value as high as 1140 Ω ; however, because of the maximum ratio tolerance specification this means all other resistors (R_{IN2} , R_{G1} , R_{G2}) have values approximately 14% above the nominal values of these resistors.

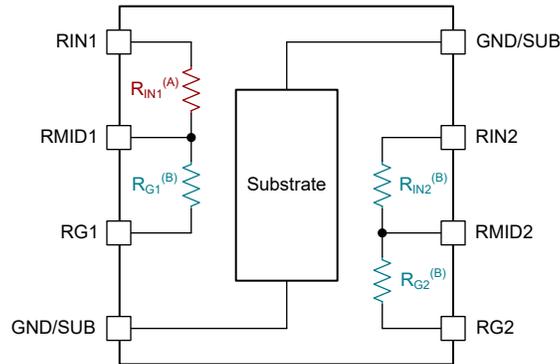


Figure 2. Resistor Ratio Matching

Considerations for use

- Connect only one of the two GND pins to a low-impedance ground or bias point. Float the other pin to avoid the formation of current return paths through the device substrate. See the [RES11A-Q1](#) data sheet for more information.
- The RES11A-Q1 is AEC-Q200 Grade 1 qualified and has an operating temperature range of -40°C to 125°C , desirable for industrial and automotive applications. AEC-Q200 is the worldwide standard for stress and temperature resistance that all passive electric components must meet to be qualified for use in the automotive industry. Pair the RES11A-Q1 with AEC-Q100 active components (amplifiers, comparators, ADC, DAC, and so forth) for a full automotive qualified design.
- Though labeled R_{INX} and R_{GX} there is no requirement for the direction of current flow. The RES11A can be rotated 180° for an attenuating gain configuration. With R_{GX} used as the input and R_{INX} as the output the divider ratio becomes inverted. For example, a RES11A-Q1 with a nominal resistance ratio of 1:2 has a 1:0.5 ratio when R_{GX} is used as the input.

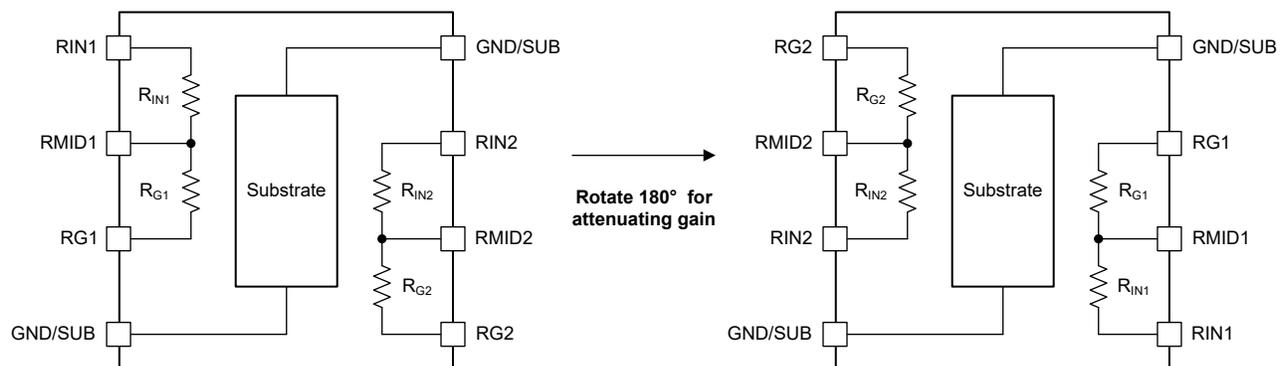


Figure 3. Attenuating Gain Configuration

Importance of Matched Resistors For Maximizing CMRR in Discrete Amplifier Implementations

Consider a standard differential amplifier as [Figure 3](#) shows. When simplified to $R_1 = R_2$, and $R_3 = R_4$, CMRR can be expressed as $CMRR(dB) = 20 \times \log[(1 + R_3 / R_1) / (4T / 100)]$ where T is resistor tolerance in percent. This means CMRR is expected to be only 54dB in a unity gain configuration ($R_1 = R_3$) with unmatched 0.1% tolerance resistors. If both divider ratios are matched to a 0.05% ratio tolerance then the value for T in this formula is 0.025% resulting in an improved CMRR of 66dB. See the application information section in the [RES11A-Q1](#) data sheet to learn more about how this number is calculated. An operational amplifier has infinite CMRR, which is a specification pertaining to the amount of the common mode signal present at the output of an amplifier. Ultimately, CMRR is a factor impacting the output signal noise. Learn more about CMRR with the [Common-mode rejection ratio](#) TI Precision Labs video on this topic.

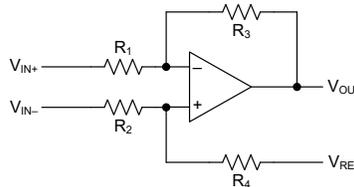


Figure 4. Standard Differential Amplifier

Discrete Implementations of Difference and Instrumentation Amplifiers

Difference Amplifier

Utilizing an operational amplifier such as the OPA392 and a single RES11A-Q1 in the [Difference Amplifier Configuration](#) yields a differential amplifier topology including differential inputs and a single-ended output. The gain of the amplifier can be calculated by the formula in [Equation 1](#).

$$G = R_G / R_{IN} \tag{1}$$

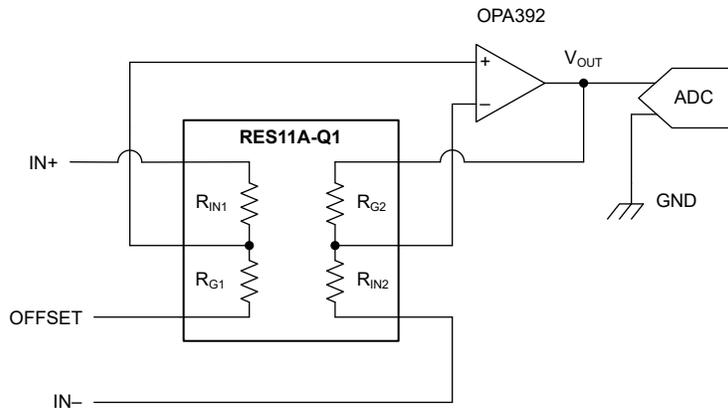


Figure 5. Difference Amplifier Configuration

Instrumentation Amplifier

Utilizing two operational amplifiers such as OPA392 and a single RES11A-Q1 in the *Instrumentation Amplifier Configuration* yields an instrumentation amplifier topology with two high-impedance inputs and differential output. In some cases, a weak path for input bias current is needed². The gain of the amplifier is calculated using Equation 2.

$$G = 1 + R_G / R_{IN} \tag{2}$$

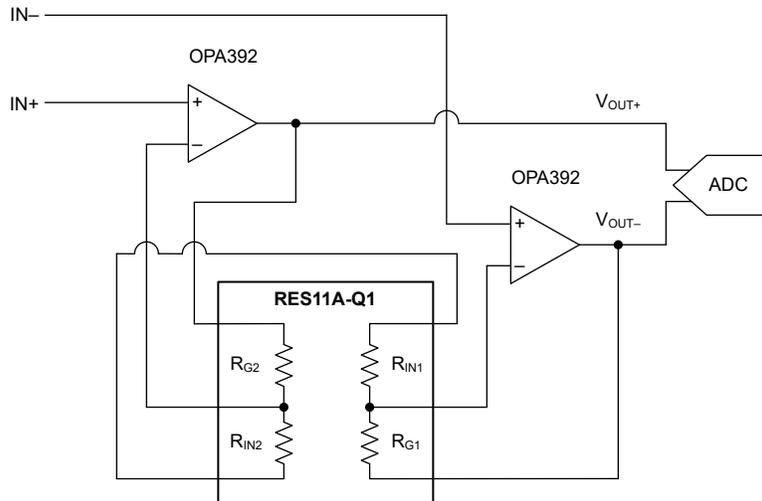


Figure 6. Instrumentation Amplifier Configuration With Differential Output

Utilizing two operational amplifiers such as OPA392 and a single RES11A-Q1 as illustrated in Figure 6 yields an instrumentation amplifier topology with two high-impedance differential inputs, one single-ended output, and a reference input. It is important to simulate the design to check that the input common mode ranges and output swings meet the requirements of the desired application. The gain of the amplifier is calculated with Equation 3.

$$G = 1 + R_{IN} / R_G \tag{3}$$

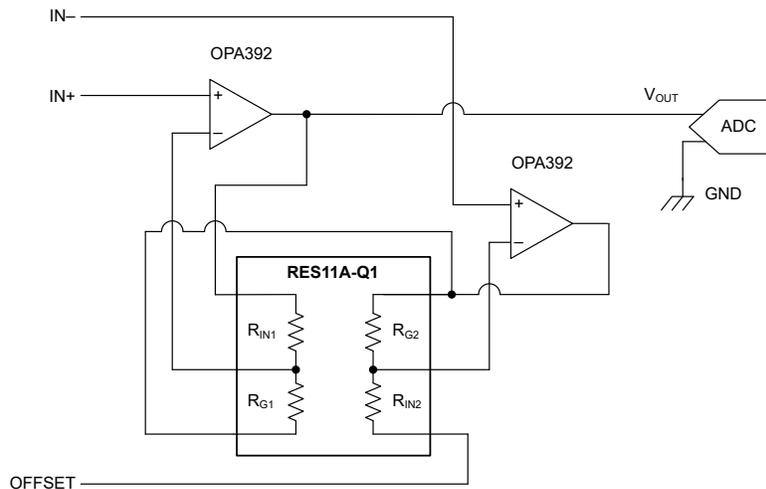


Figure 7. Instrumentation Amplifier Configuration With Reference Input

² See the [Importance of Input Bias Current Return Paths in Instrumentation Amplifier Applications](#) application note for applications such as AC-coupled measurements or thermocouple measurements.

Fully-Differential Amplifier

A fully-differential amplifier requires resistors to set the gain as [Figure 7](#) illustrates. The ratio between these resistors determines the gain, thus matching is important to make sure the circuit behaves as intended. [Equation 4](#) shows the formula for gain in this configuration.

$$G = R_G / R_{IN}$$

(4)

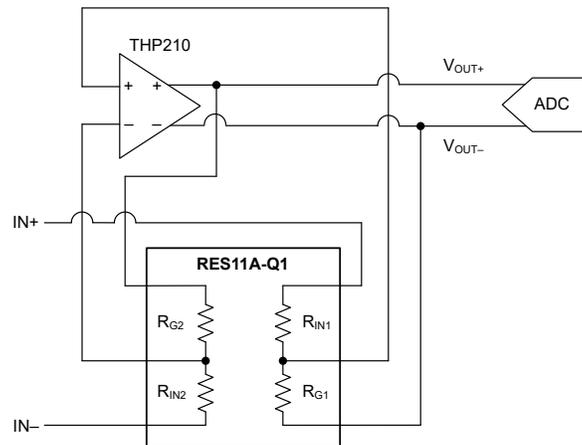


Figure 8. Fully-Differential Amplifier Configuration

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2024, Texas Instruments Incorporated