# Application Note How to Co-Layout Three Common SOT-563 Package Pinouts



Lucia Gao, Bruce Lu, Edwin Zang

#### ABSTRACT

Buck converter applications commonly require co-layout between devices with different pinouts due to the design flexibility this provides. This application note focuses on how to co-layout among three types of SOT-563 packages. First, the pinout of TPS56x252/7, TPS56x242/7, and TPS56x203/6 are compared. Next, the schematic design is introduced. Finally, this application design is verified based on experiments.

### **Table of Contents**

1 Introduction	2
2 Comparison of Pinout	2
3 Schematic Diagram	3
3.1 How to Co-layout Among Three Types of SOT-563	
3.2 How to Co-Layout Between TPS56x252/7 and TPS56x242/7	4
3.3 How to Co-layout Between TPS56x252/7 and TPS56x203/6	4
3.4 How to Co-Layout Between TPS56x242/7 and TPS56x203/6	5
4 Experimental Results	6
5 Summary	6
6 References	
7 Revision History	7

### List of Figures

Figure 2-1. TPS56x203/6 Pinout	2
Figure 2-2. TPS56x242/7 Pinout	2
Figure 2-3. TPS56x252/7 Pinout	2
Figure 3-1. Co-layout Schematic Among Three Types of SOT-563	3
Figure 3-2. Co-Layout Schematic for TPS56x252/7 and TPS56x242/7	4
Figure 3-3. Co-layout Schematic for TPS56x252/7 and TPS56x203/6	4
Figure 3-4. Co-Layout Schematic for TPS56x242/7 and TPS56x203/6	5
Figure 4-1. TPS564242 12V Input to 1.05V Output at 4A	6
Figure 4-2. TPS563203 12V Input to 1.05V Output at 3A	6
Figure 4-3. TPS563252 12V Input to 1.05V Output at 3A	6

### List of Tables

Table 2-1. Pin Functions	2
Table 3-1. Solder Information for Different Part	
Table 3-2. Comparison of EN Pin Configuration	
Table 3-3. Solder Information for TPS56x252/7 and TPS56x203/6	
Table 3-4. Solder Information for TPS56x242/7 and TPS56x203/6	

### Trademarks

All trademarks are the property of their respective owners.

2


SLUAAO5A - JANUARY 2023 - REVISED JANUARY 2024

# 1 Introduction

The TPS56x252/7, TPS56x242/7 and TPS56x203/6 are all single output, adaptive on-time, D-CAP3<sup>™</sup> control mode, synchronous buck converter that require very low external component count in SOT-563 packages. However, each device's pinout is slightly different. This application note mainly discusses how to do co-layout among TPS56x252/7, TPS56x242/7, and TPS56x203/6.

## 2 Comparison of Pinout

Figure 2-1 shows TPS56x203/6 pinout with SOT-563 package. TPS56x203/6 pinout is quite common in the industry. Figure 2-2 shows TPS56x242/7 pinout with SOT-563 package which has been optimized. It integrates BST capacitor and add AGND for pin 4. Figure 2-3 shows TPS56x252/7 pinout with SOT-563 package. It integrates BST capacitor and add PG for pin 4. As shown in Table 2-1, these three device families have the same pin functionality aside from pin 4. With compatible external circuitry, co-layout can be achieved for the three packages.

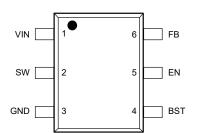

VIN \_\_\_\_\_ 1 \_\_\_\_ 6 \_\_\_\_ FB SW \_\_\_\_ 2 \_\_\_ 5 \_\_\_\_ EN GND \_\_\_\_ 3 \_\_\_ 4 \_\_\_\_ AGND

Figure 2-2. TPS56x242/7 Pinout

Figure 2-1. TPS56x203/6 Pinout



3

FB

ΕN

PG

6

5

VIN

SW

GND

### Table 2-1. Pin Functions

Pin		Description	
No.	Name	Description	
1	VIN	ut voltage supply pin. Connect the input decoupling capacitors between VIN and GND.	
2	SW	witch node pin. Connect the output inductor to this pin.	
3	GND	GND pin source terminal of the low-side power NFET as well as the ground terminal for controller circuit.	
	PG	Open-drain power-good indicator.	
4	AGND	Ground of the internal analog circuitry. Connect AGND to the GND plane.	
	BST	Supply input for the high-side NFET gate driver circuit. Connect 0.1-uF capacitor between BST and SW pins.	
5	EN	Enable input control. Driving EN high enables the converter.	
6	FB	Converter feedback input. Connect to the output voltage with a feedback resistor divider.	






### **3 Schematic Diagram**
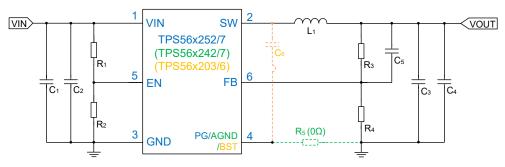
### 3.1 How to Co-layout Among Three Types of SOT-563

Since pin 4 definitions are different for TPS56x252/7, TPS56x242/7, and TPS56x203/6, the compatible schematic is designed to achieve co-lay. Figure 3-1 shows the co-lay schematic. There are several differences for the BOM, also note that TPS56x203/6 allows EN pin to connect to Vin by only one pullup resistor. Table 3-1 shows solder information for different part. Table 3-2 shows comparison of EN pin configuration.



### Figure 3-1. Co-layout Schematic Among Three Types of SOT-563

Part Number	Description
TPS56x252/7	<ol> <li>If PG function is not needed, PG can be floating or connected with GND. PG tied to GND can get better thermal performance.</li> <li>C<sub>6</sub> needs to be floating. R<sub>5</sub> can be soldered or floating.</li> <li>EN pin max voltage is 6V, need two voltage divider resistors.</li> </ol>
TPS56x242/7	<ol> <li>R<sub>5</sub> needs to be soldered to connect AGND to GND.</li> <li>C<sub>6</sub> needs to be floating.</li> <li>EN pin max voltage is 6V, need two voltage divider resistors.</li> </ol>
TPS56x203/6	<ol> <li>C<sub>6</sub> needs to be tied to SW.</li> <li>R<sub>5</sub> needs to be floating.</li> <li>EN pin max voltage is 6V, allow two voltage resistors or one 100k pullup resistor.</li> </ol>

#### Table 3-1. Solder Information for Different Part

#### Table 3-2. Comparison of EN Pin Configuration

Part Number	TPS56325x/TPS56425x	TPS562242	TPS56x203/6	TPS56x242/7
EN Default Status	Low	High	Low	Low
EN ABS Voltage	6V	6V	6V	6V
If Have A Zener Diode in Internal EN Pin	No	No	Yes	No
Support only 100k top resistor directly to Vin	No	No	Yes	No



### 3.2 How to Co-Layout Between TPS56x252/7 and TPS56x242/7

Figure 3-2 shows the co-lay schematic for TPS56x252/7 and TPS56x242/7. If PG function of TPS56x252/7 is not used, PG of TPS56x252/7 can be directly connected with GND and TPS56x252/7 and TPS56x242/7 are exactly pin to pin.

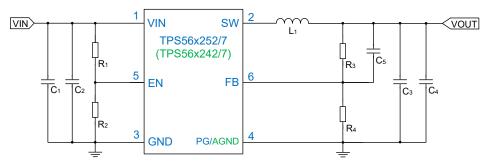


Figure 3-2. Co-Layout Schematic for TPS56x252/7 and TPS56x242/7

### 3.3 How to Co-layout Between TPS56x252/7 and TPS56x203/6

Figure 3-3 shows the co-lay schematic for TPS56x252/7 and TPS56x203/6. Table 3-3 shows solder information for TPS56x252/7 and TPS56x202/7.

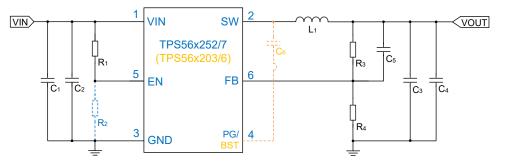


Figure 3-3. Co-layout Schematic for TPS56x252/7 and TPS56x203/6

Part Number	Description
TPS56x252/7	<ol> <li>If PG function is not needed, PG can be floating or connected with GND.</li> <li>C<sub>6</sub> needs to be floating.</li> <li>EN pin max voltage is 6V, need two voltage divider resistors.</li> </ol>
TPS56x203/6	<ol> <li>C<sub>6</sub> needs to be tied to SW.</li> <li>EN pin max voltage is 6V, allow two voltage resistors or one 100k pullup resistor.</li> </ol>



### 3.4 How to Co-Layout Between TPS56x242/7 and TPS56x203/6

Figure 3-4 shows the co-lay schematic for TPS56x242/7 and TPS56x203/6. Table 3-4 shows solder information for TPS56x242/7 and TPS56x203/6.

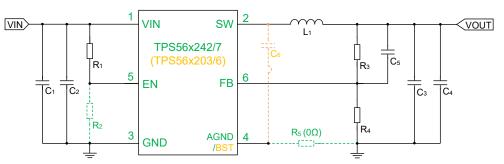


Figure 3-4. Co-Layout Schematic for TPS56x242/7 and TPS56x203/6

Part Number	Description
TPS56x242/7	<ol> <li>R<sub>5</sub> needs to be soldered to connect AGND to GND.</li> <li>C<sub>6</sub> needs to be floating.</li> <li>EN pin max voltage is 6V, need two voltage divider resistors.</li> </ol>
TPS56x203/6	<ol> <li>C<sub>6</sub> needs to be tied to SW.</li> <li>R<sub>5</sub> needs to be floating.</li> <li>EN pin max voltage is 6V, allow two voltage resistors or one 100k pullup resistor.</li> </ol>

## **4 Experimental Results**

Figure 4-1, Figure 4-2, and Figure 4-3 are tested at 12V input voltage, 1.05V output voltage. All three devices work stably in steady state operation.

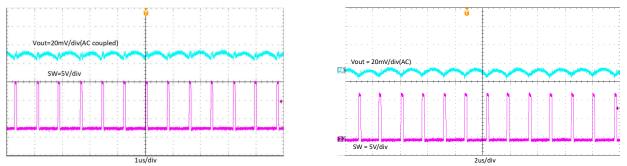


Figure 4-1. TPS564242 12V Input to 1.05V Output at Figure 4-2. TPS563203 12V Input to 1.05V Output at 4A 3A

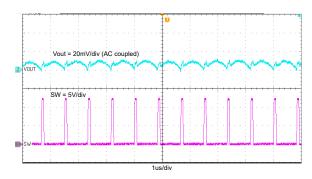


Figure 4-3. TPS563252 12V Input to 1.05V Output at 3A

### **5** Summary

This application note introduces how to co-layout among TPS56x252/7, TPS56x242/7, and TPS56x203/6 with SOT-563 package, which helps simplify the power design. Pinout is also compared and compatible schematic recommendations are given. Finally, the experiment verification results of the co-layout design proves all three devices can work stably in steady state operation.

Page



### 6 References

- Texas Instruments, *TPS56325x 3-V to 16-V Input, 3-A Synchronous Buck Converters in SOT-563 Package* data sheet.
- Texas Instruments, TPS56524x 3-V to 16-V Input Voltage, 5-A Synchronous Buck Converter in SOT-563 Package data sheet.
- Texas Instruments, *TPS56424x 3-V to 16-V Input Voltage, 4-A Synchronous Buck Converter in SOT-563 Package* data sheet.
- Texas Instruments, TPS56320x 4.2-V to 17-V Input, 3-A Synchronous Buck Converter in SOT563 data sheet.

### **7 Revision History**

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

### Changes from Revision \* (January 2023) to Revision A (January 2024)

•	Replaced TPS56x202/7 with TPS56x203/61
---	--

### IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2024, Texas Instruments Incorporated