
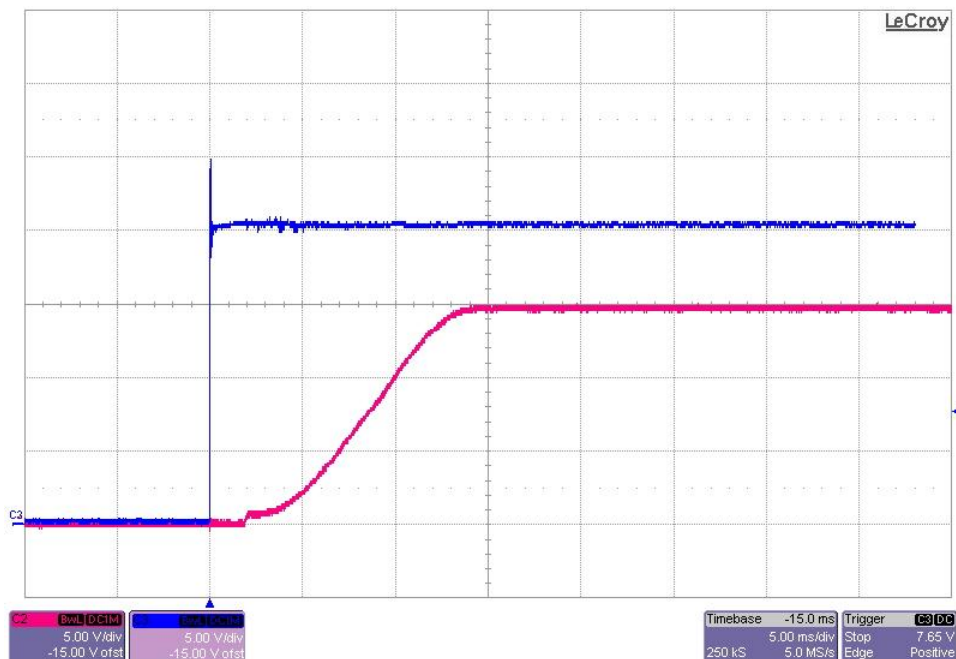

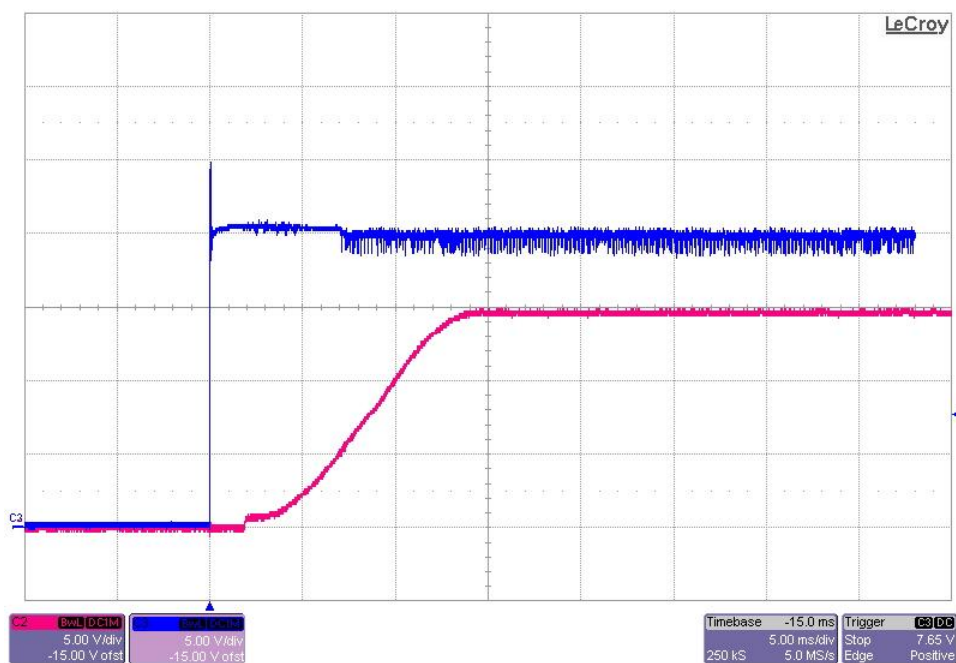
## 1 Startup

The photo below shows the output voltage startup waveforms after the application of 20V in. The 15V output was loaded to 0A. (5V/DIV, 5mS/DIV)




The photo below shows the output voltage startup waveforms after the application of 20V in. The 15V output was loaded to 5A. (5V/DIV, 5mS/DIV)



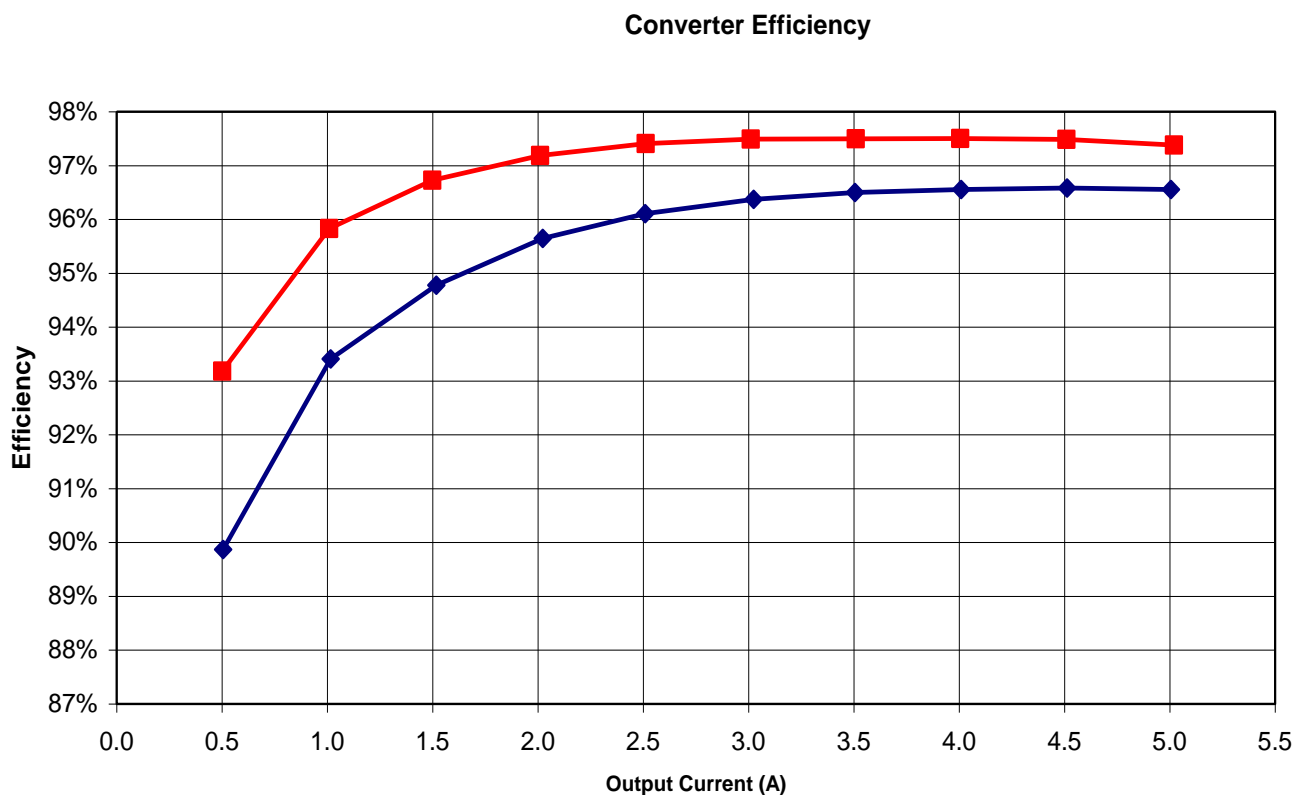
## 2 Efficiency

The converter efficiency is shown in the figure below for  $V_{out} = 15V$ .




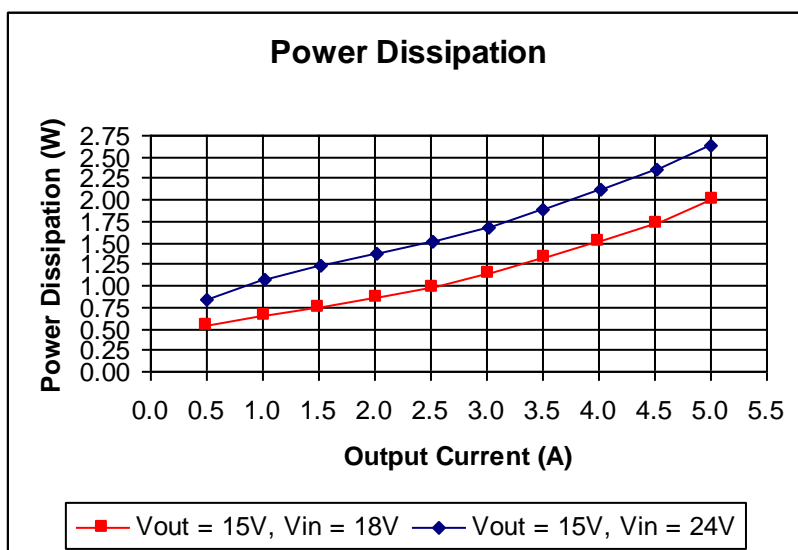—■—  $V_{out} = 15V, V_{in} = 18V$  —◆—  $V_{out} = 15V, V_{in} = 24V$




—■—  $V_{out} = 15V, V_{in} = 18V$  —◆—  $V_{out} = 15V, V_{in} = 24V$

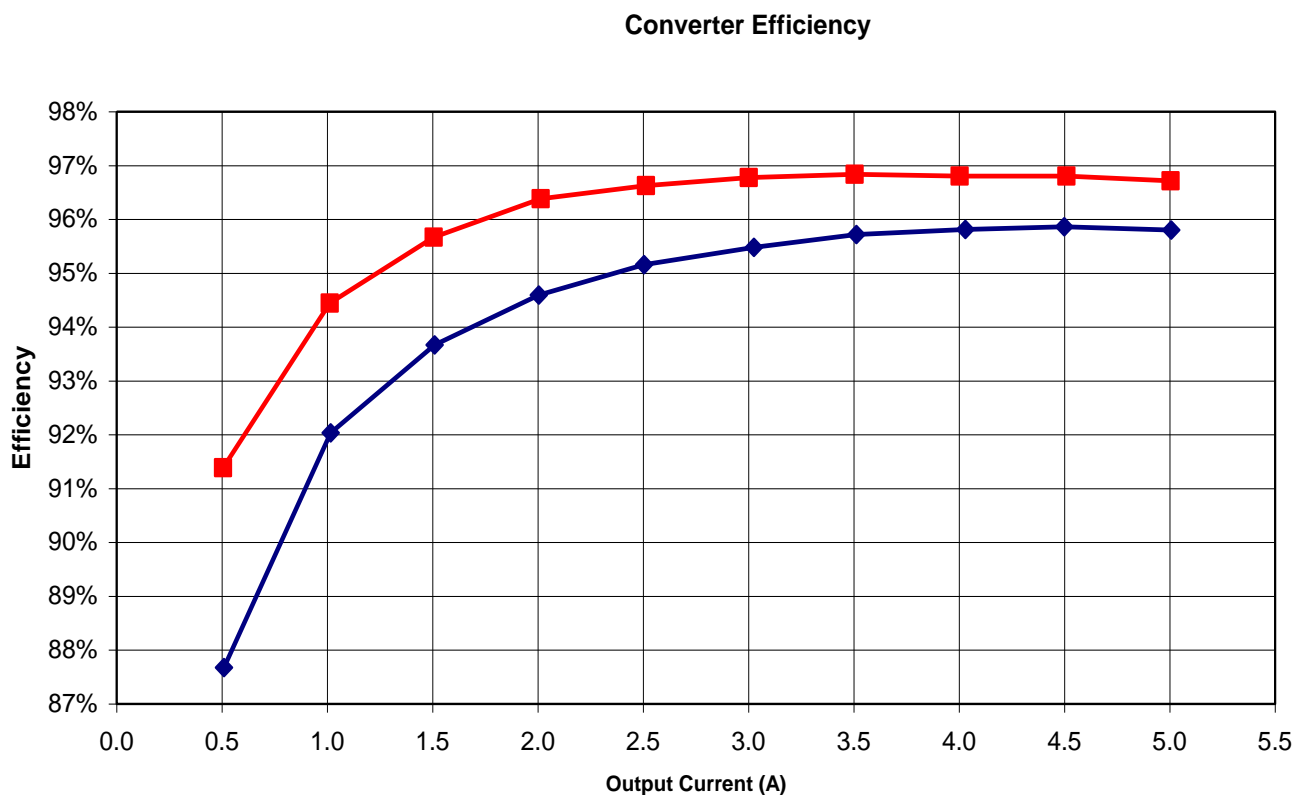The converter efficiency is shown in the figure below for  $V_{out} = 12V$ .



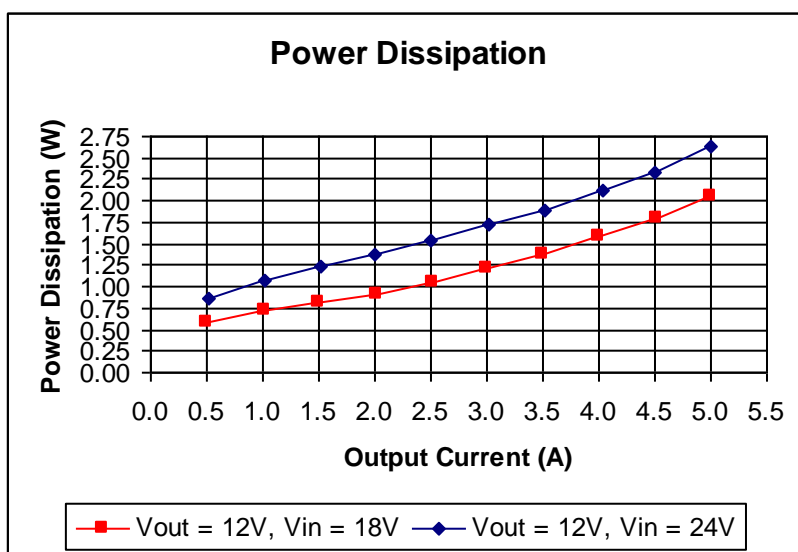
■  $V_{out} = 12V, V_{in} = 18V$     ◆  $V_{out} = 12V, V_{in} = 24V$




■  $V_{out} = 12V, V_{in} = 18V$     ◆  $V_{out} = 12V, V_{in} = 24V$
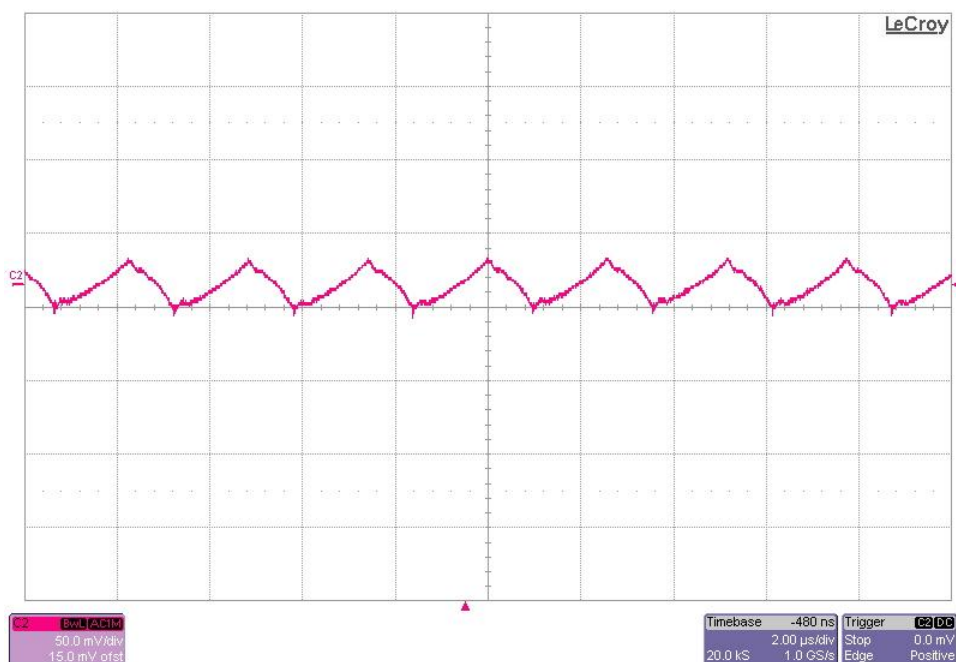
### 3 Output Ripple Voltage

The output ripple voltage is shown in the figure below. The image was taken with the 15V output loaded to 5A. The input voltage set to 24V. (50mV/DIV, 2uS/DIV)




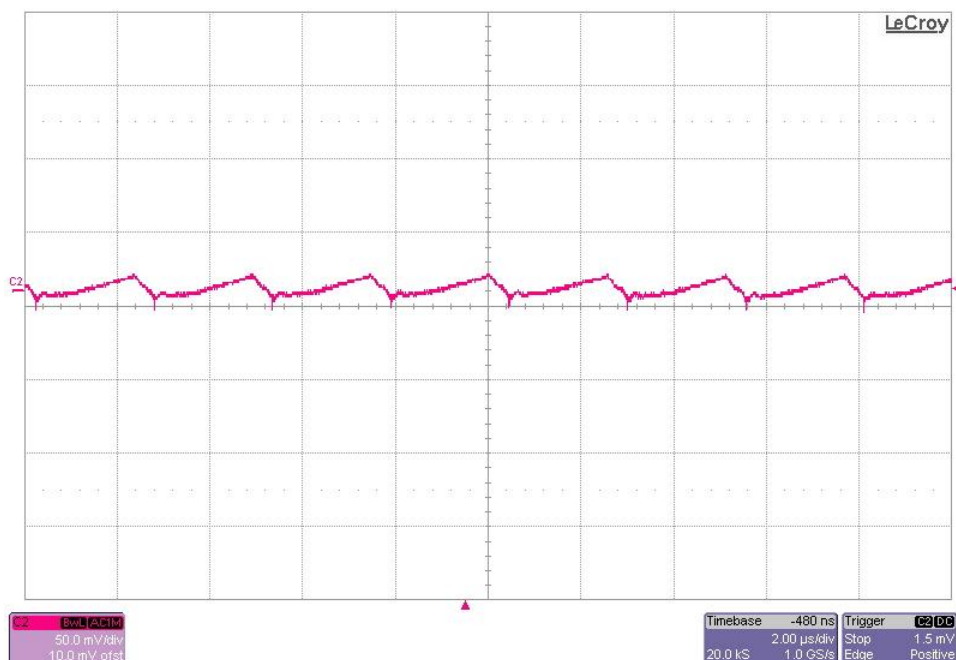The output ripple voltage is shown in the figure below. The image was taken with the 15V output loaded to 5A. The input voltage set to 18V. (50mV/DIV, 2uS/DIV)



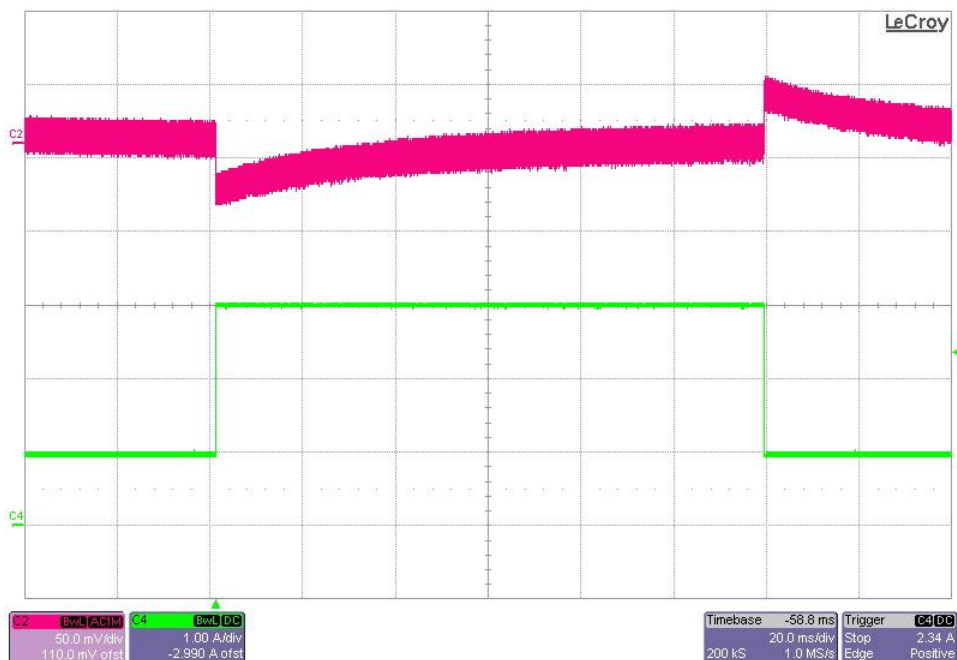
## 4 Load Transients

The photo below shows the 15V output voltage (ac coupled) when the load current is stepped between 1A and 3A.  $V_{in} = 20V$ . (50mV/DIV, 1A/DIV, 20mS/DIV)



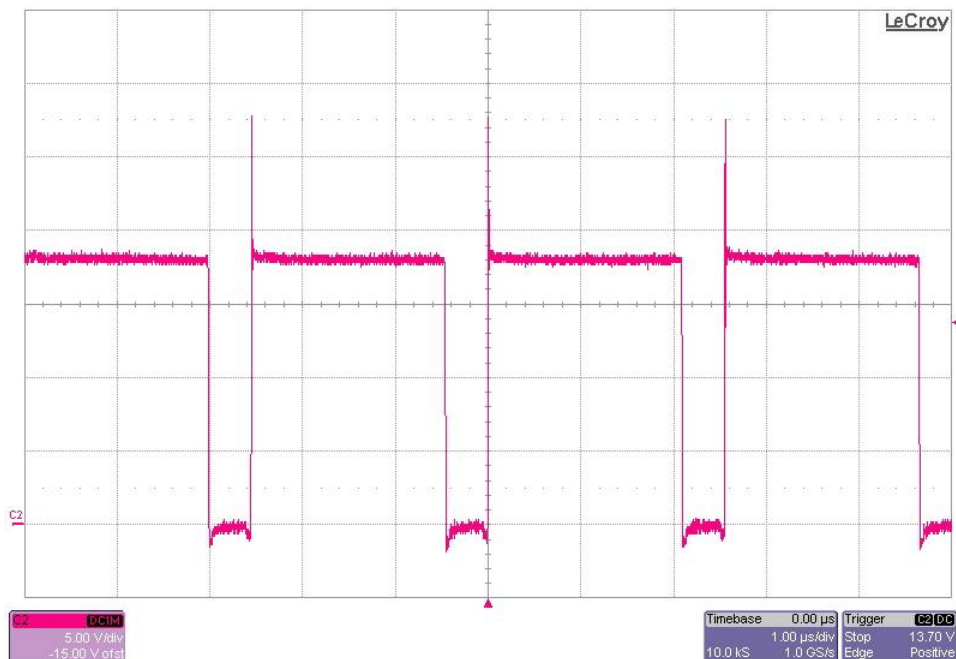
## 5 Switch Node Waveforms


The photo below shows the switch node measured with 200MHz bandwidth. The input voltage is 18V and the output is loaded to 5A. (5V/DIV, 1uS/DIV)



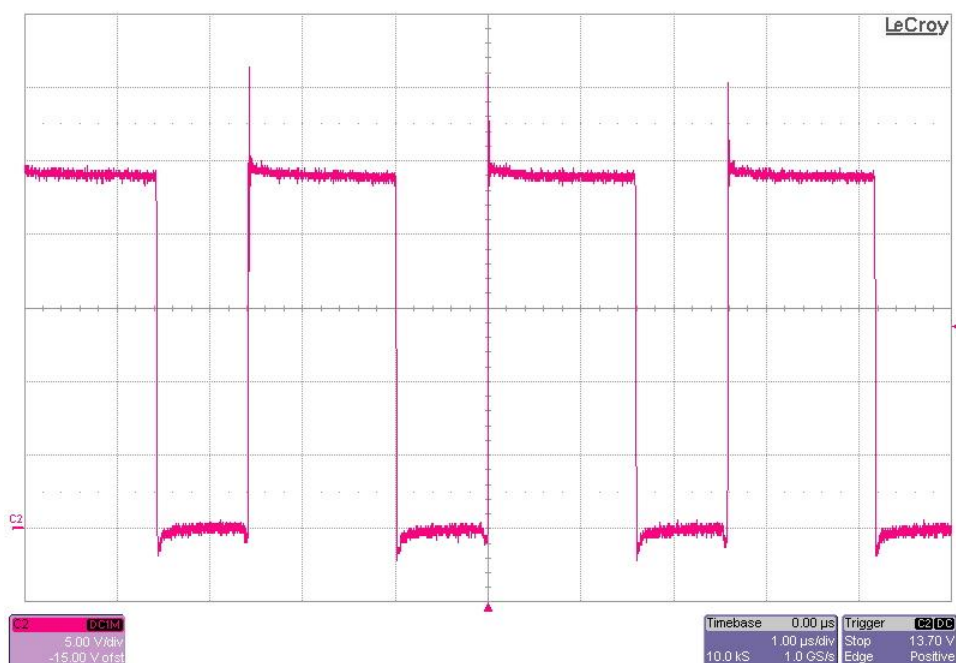
The photo below shows the switch node measured with 200MHz bandwidth. The input voltage is 24V and the output is loaded to 5A. (5V/DIV, 1uS/DIV)



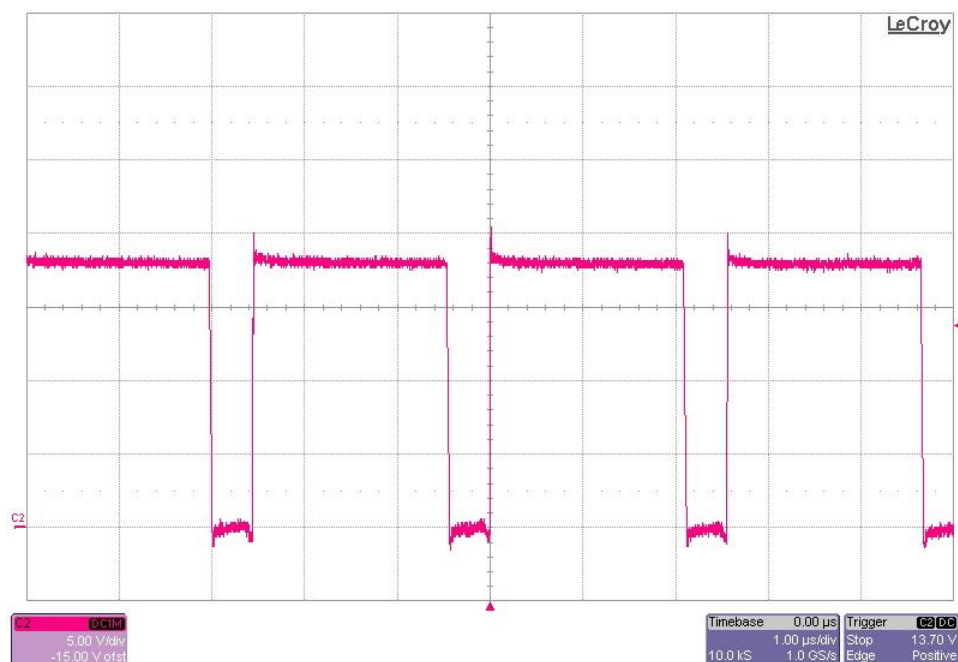
The photo below shows the switch node measured with 200MHz bandwidth. The input voltage is 18V and the output is loaded to 1A. (5V/DIV, 1uS/DIV)



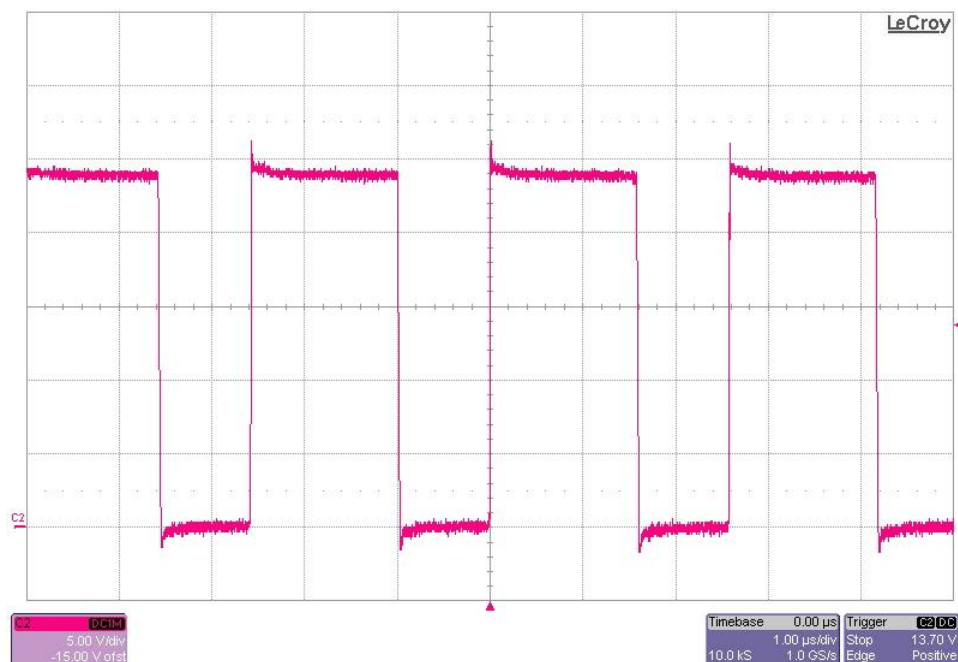
The photo below shows the switch node measured with 200MHz bandwidth. The input voltage is 24V and the output is loaded to 1A. (5V/DIV, 1uS/DIV)



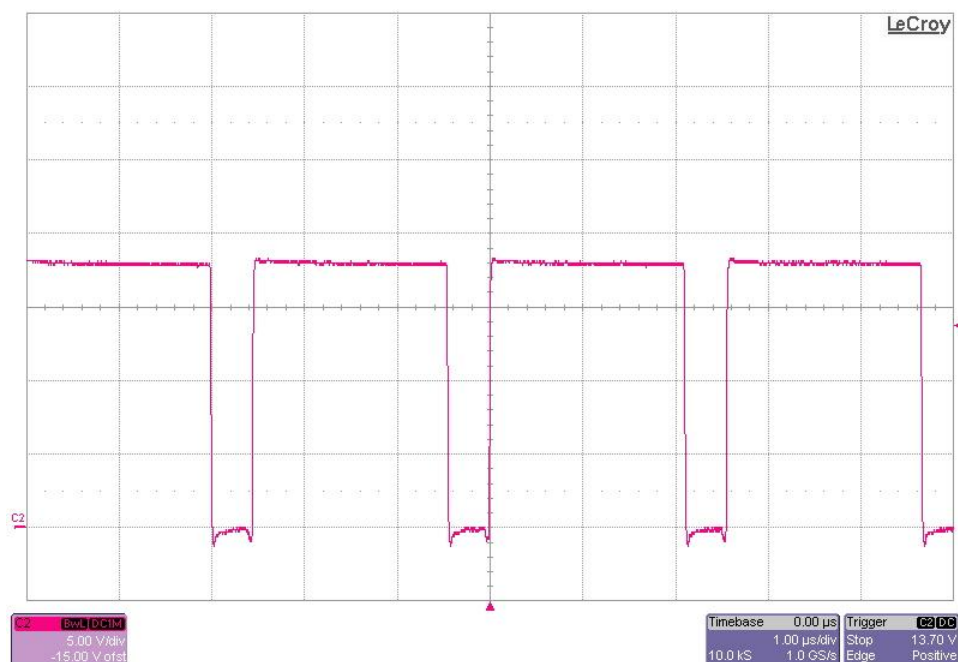The photo below shows the switch node measured with 20MHz bandwidth. The input voltage is 18V and the output is loaded to 5A. (5V/DIV, 1uS/DIV)



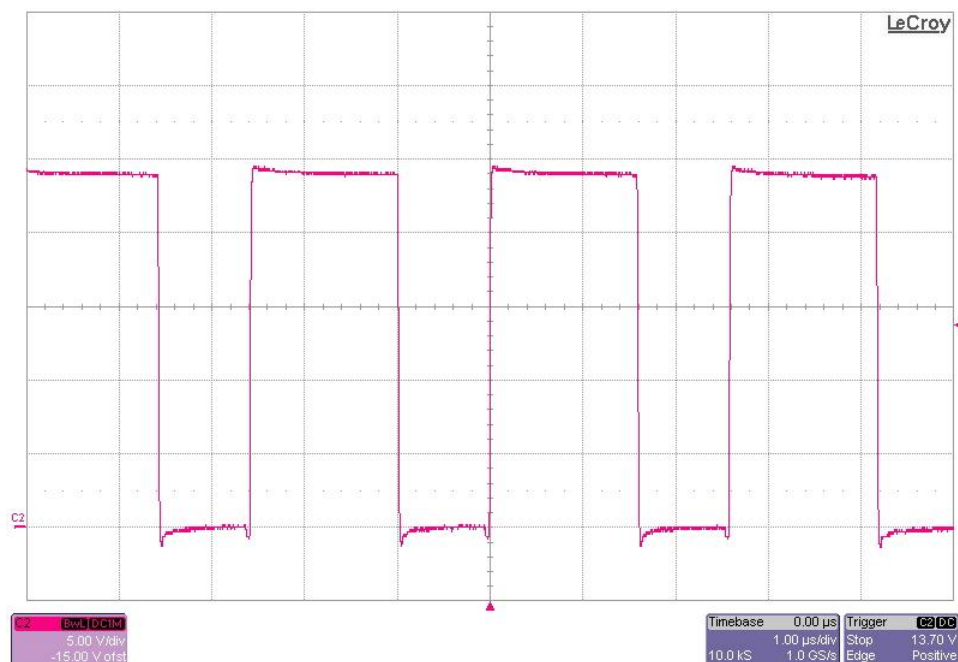
The photo below shows the switch node measured with 20MHz bandwidth. The input voltage is 24V and the output is loaded to 5A. (5V/DIV, 1uS/DIV)





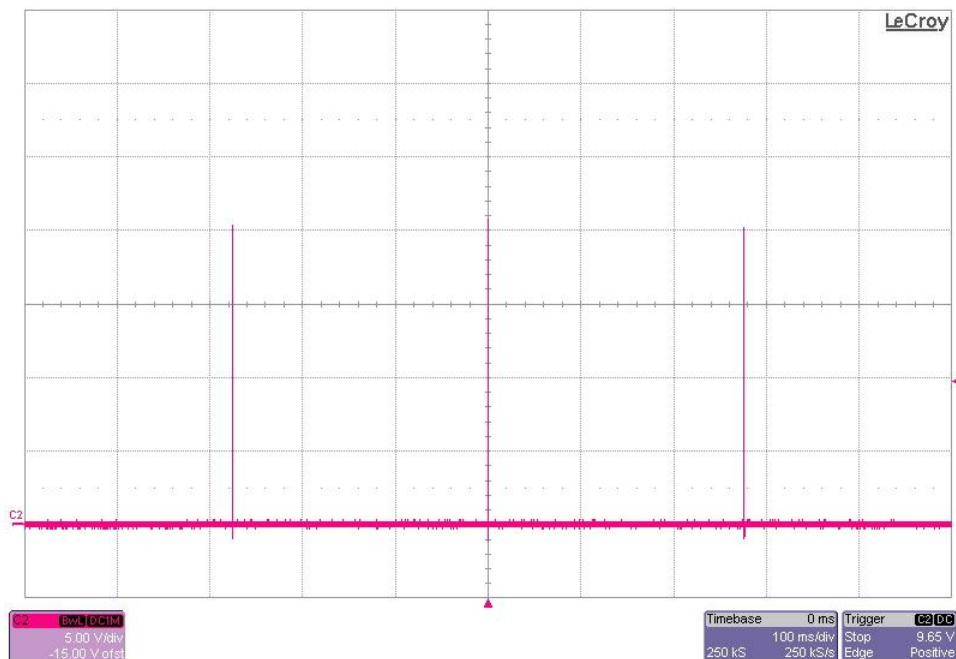
## 6 Short Circuit Waveforms

The photo below shows the switch node during a hard short across the 15V output. The input voltage is 20V and the output was previously loaded to 5A. (5V/DIV, 100mS/DIV)



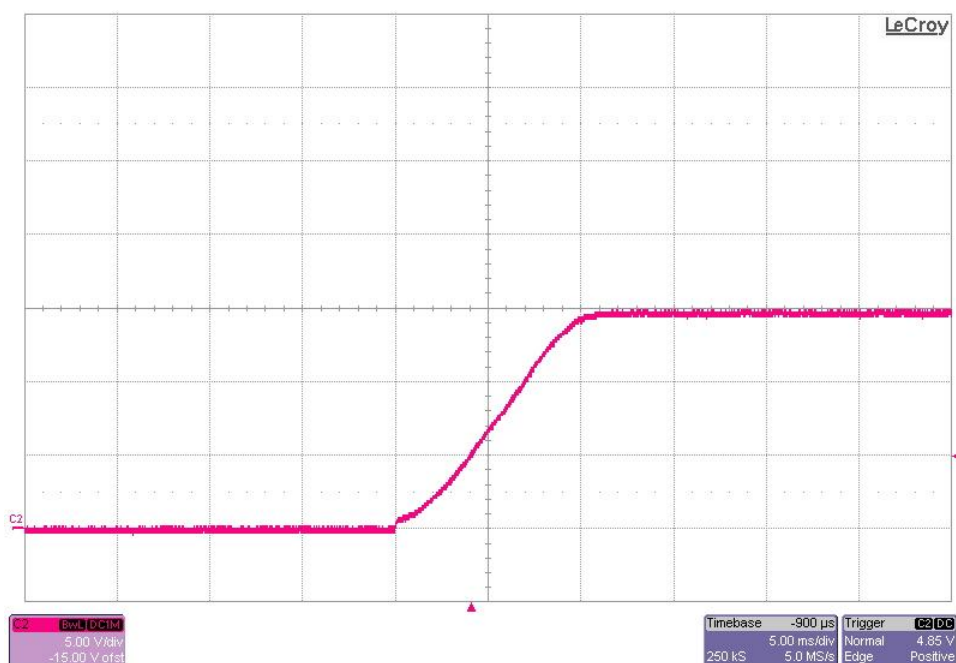The photo below shows the output voltage recovery after the removal of a hard short across the 15V output. The input voltage is 20V and the output was loaded to 5A. (5V/DIV, 5mS/DIV)



## 7 Control Loop Gain / Stability

The plot below shows the loop gain and phase margin with the input voltage at 20V and the output voltage at 15V.

1A Output:


Band Width = 50.0KHz

Phase Margin = 71 degrees

5A Output:

Band Width = 53.4KHz

Phase Margin = 68 degrees

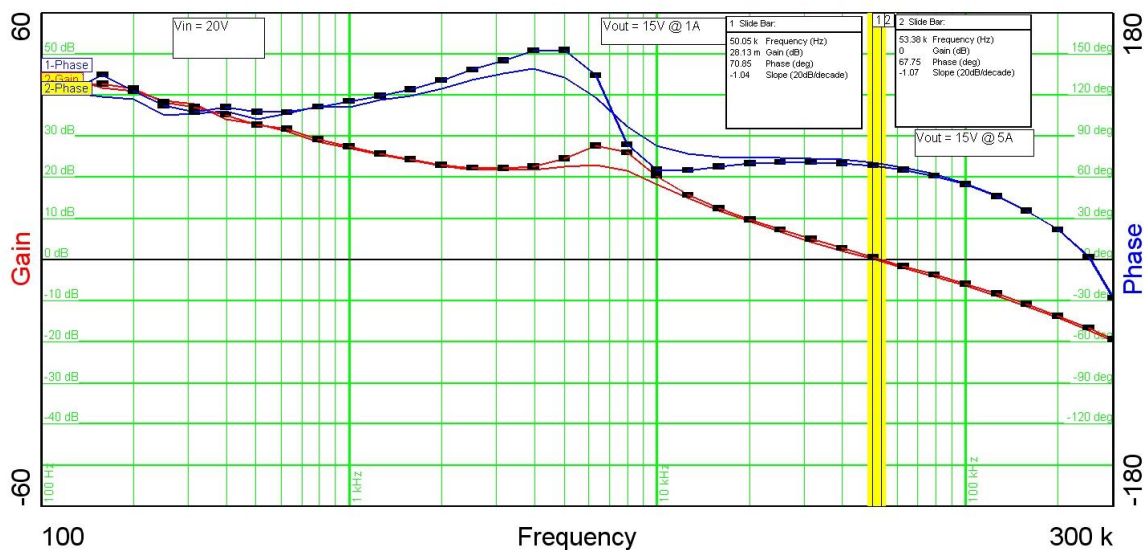

The plot below shows the loop gain and phase margin with the output current at 3A and the output voltage at 15V.

Vin = 18V:


Band Width = 54.1KHz

Phase Margin = 68 degrees

Vin = 24V:


Band Width = 49.3KHz

Phase Margin = 68 degrees

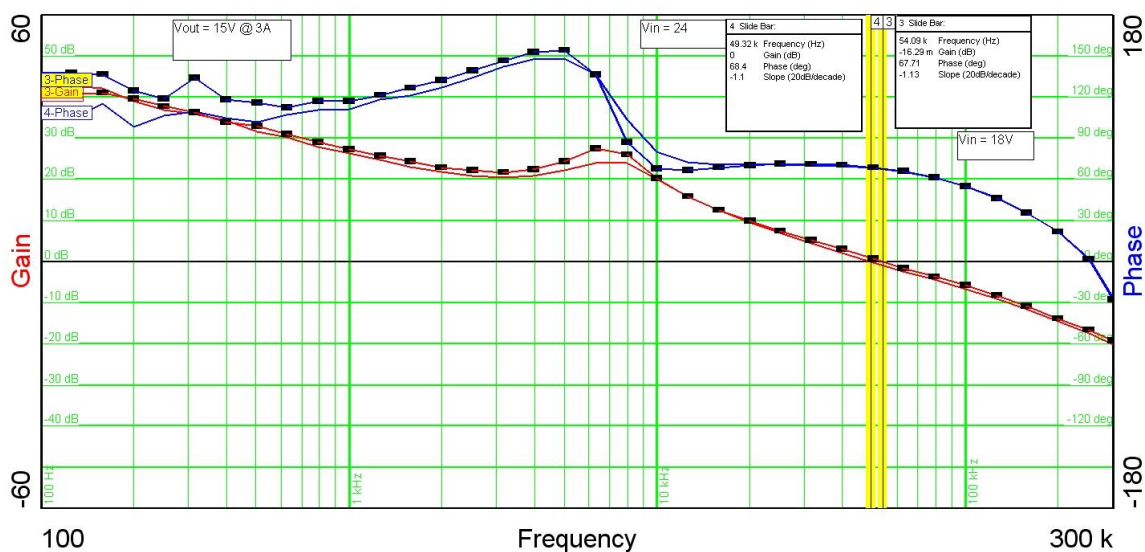

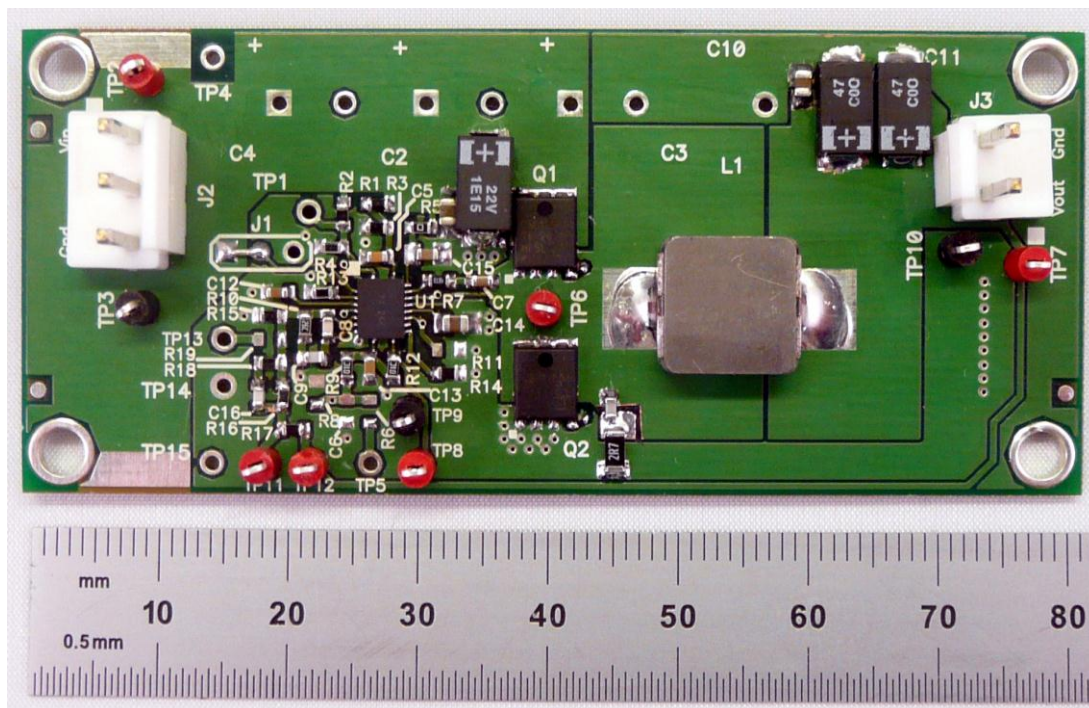
## 8 Photo

The photo below shows the PMP8493 REVB assembly built on the PMP5959 REVA PWB, with mods.


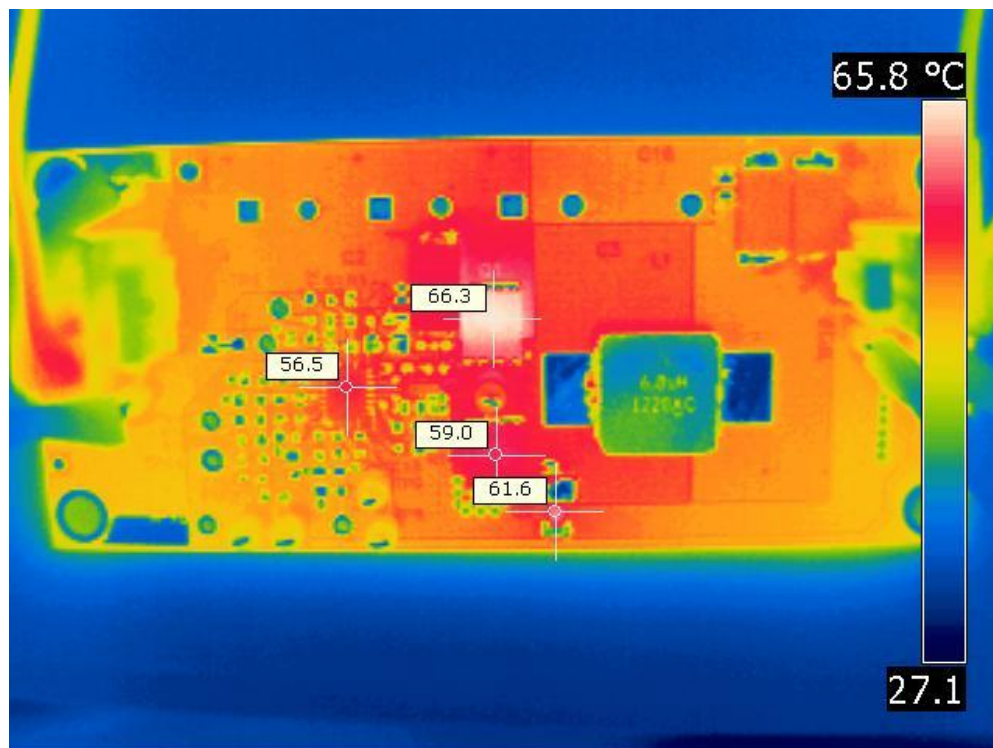
## 9 Thermal Image

A thermal image is shown below when operating at 20V input and 15V@ 5A output, with no airflow.



## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated