

PR433
Virtex™-4 Design 3
SWIFT™ (TPS54350 series) DC/DC Converter-based Power Management Solution
Providing up to 3A for $V_{IN} = 12V$

FEATURES:

- High efficiency converters minimize heat
- Modifiable for input voltages between 4.5V and 20V
- Use of the TPS54350 adjustable devices allow
 - o use of smallest inductor and/or specific type of output capacitor
 - o flexibility to re-compensate as needed, depending on the bypass/decoupling capacitors used with the FPGA
- Additional V_{CCO} rails easily added and sequenced (if desired) using the TPS54350 PWRGD and ENABLE.

IMPORTANT WEB LINKS:

- Link to the TI home page for Xilinx FPGA power management solutions at <http://www.ti.com/xilinuxfpga> for more information and other reference designs.
- Link to datasheets at <http://focus.ti.com/lit/ds/symlink/TPS54350.pdf>
- Link to SWIFT™ design software tool at <http://focus.ti.com/docs/toolsw/folders/print/swift-sw.html> to assist further optimization/customization of design.

IMPLEMENTATION NOTES:

- **Sequencing:** Per Xilinx DS302 v1.3, Virtex-4 power rails can be turned on in any sequence, though V_{CCAUX} must power on before or with V_{CCO} for the minimum power-on current specifications shown in the Xilinx datasheet to apply. For this reason and to reduce the risk that large currents for charging bulk capacitance forces the point of load converter into current limit and/or pulls down the input supply at power up, the following recommended design techniques were used:
 - o Integrated soft-start configured with a capacitor to provide up to 5 ms monotonic rise time for V_{CCINT} , V_{CCAUX} and V_{CCO}
 - o Sequencing V_{CCINT} , V_{CCAUX} then V_{CCO} using PWRGD and ENABLE
- **Bulk Capacitance:** The TPS54350 converters used for the V_{CCINT} , V_{CCAUX} and V_{CCO} rails have been compensated and soft-started to allow for a certain amount of additional bulk capacitance on the output rail, as specified below.


Capacitor (uF)	V _{CCO} QTY	V _{CCAUX} QTY	V _{CCINT} QTY
0.047	51	14	38
0.22	39	7	19
0.68	15	4	10
2.2	15	3	7
330 (0.15 Ω ESR)	15	1	3

If the amount of bulk capacitance increases, the TPS54350 control loop may need to be re-compensated and/or the soft-start timing may need to change. The SWIFT design software can help with these design changes.

- **V_{CCAUX}** : V_{CCAUX} powers time-critical resources in the FPGA, including the Digital Clock Managers (DCMs). Therefore, this supply voltage is especially susceptible to power supply noise. V_{CCAUX} can share a power plane with V_{CCO}, but only if V_{CCO} does not have excessive noise. Changes in V_{CCAUX} voltage should take place no faster than 10 mV/ms.
- **Modifications** : For input voltages other than 12V, use the SWIFT design software to make design modifications.

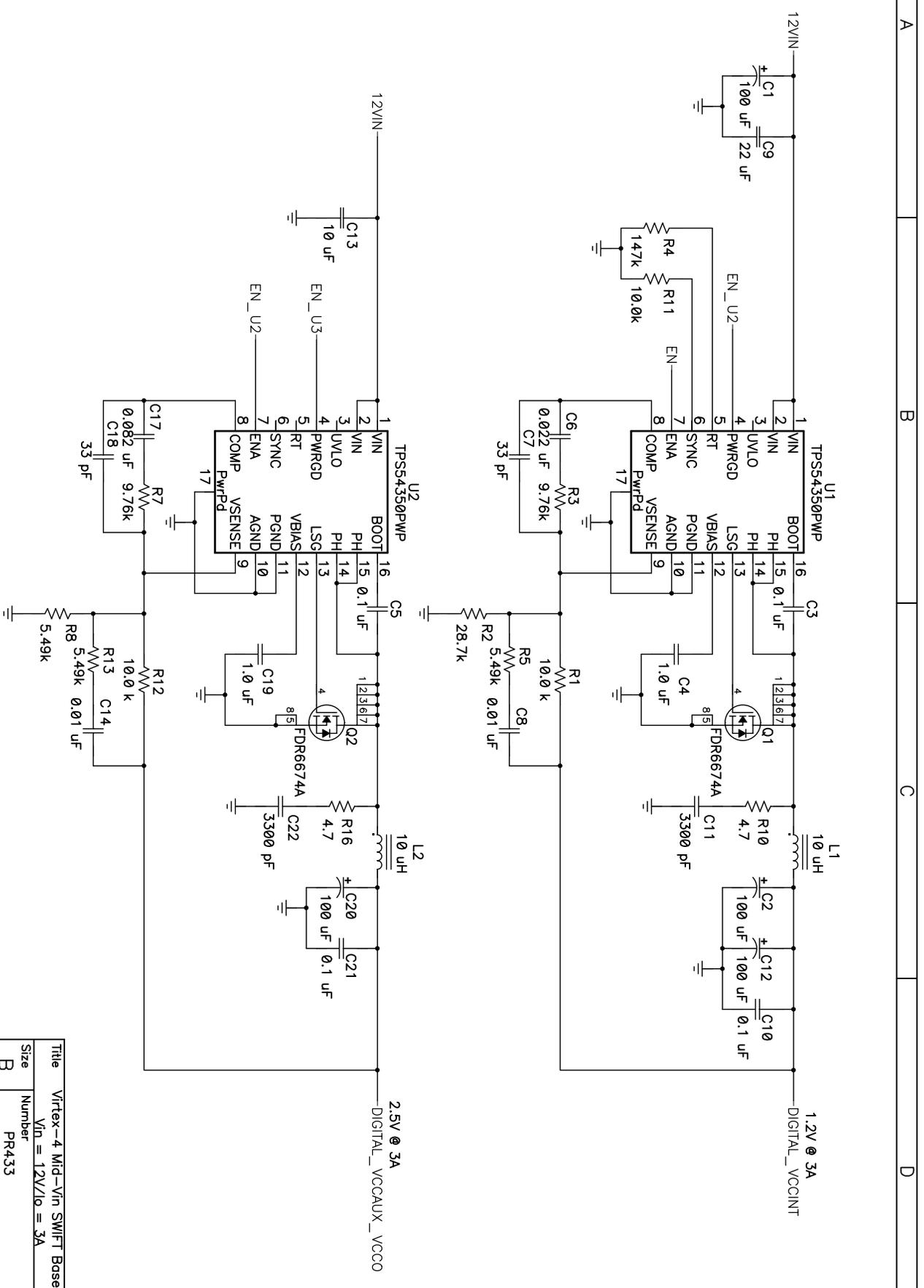QUESTIONS?

- Send an email to <mailto:fpgasupport@list.ti.com>



Title		Virtex-4 Mid-Vin SWIFT Based	
Size		Vin = 12V/Io = 3A	
Number	PR433	Rev	
Date	2/21/05	Drawn by	
Filename	pr433.sch	Sheet	1 of 2

Filename: PR433e-2_bom.xls					
Date: 06/26/2005					
PR433e-2 BOM					
COUNT	RefDes	Description	Size	Part Number	MFR
2	C1, C12	Capacitor, POSCAP, 100-uF, 6.3-V, 45-milliohm, 20%	7343(D)	6TPC100M	Sanyo
3	C10, C21, C30	Capacitor, Ceramic, 0.1 uF, 16-V, X7R, 10%	0603	C1608X7R1C104K	Std
3	C11, C22, C31	Capacitor, Ceramic, 3300-pF, 50-V, X7R, 10%	0603	C1608X7R1H332K	TDK
2	C13, C15	Capacitor, Ceramic, 10-uF, 25-V, X7R, 10%	1210	C3225X7R1E106K	TDK
1	C17	Capacitor, Ceramic, 0.022-uF, 50-V, X7R, 10%	0603	GRM188R71H223KA01	muRata
3	C2, C20, C29	Capacitor, POSCAP, 100-uF, 6.3-V, 45-milliohm, 20%	7343 (D)	6TPC100M	Sanyo
1	C23	Capacitor, Ceramic, 0.022-uF, 25-V, X7R, 10%	0603	GRM188R71E223KA01	muRata
1	C24	Capacitor, Ceramic, 0.068-uF, 50-V, X7R, 10%	0603	C1608X7R1H682K	TDK
1	C26	Capacitor, Ceramic, 0.012-uF, 50-V, X7R, 10%	0603	GRM188R71H123KA01	muRata
3	C3, C5, C16	Capacitor, Ceramic, 0.1-uF, 16-V, X7R, 10%	0603	C1608X7R1C104K	TDK
3	C4, C19, C28	Capacitor, Ceramic, 1.0-uF, 16-V, X7R, 10%	1206	C3216X7R1C105K	TDK
1	C6	Capacitor, Ceramic, 0.022-uF, 50-V, X7R, 10%	0603	GRM188R71H223KA01	muRata
3	C7, C18, C27	Capacitor, Ceramic, 33-pF, 50-V, C0G, 5%	0603	GRM1885C1H330JZ01	muRata
2	C8, C14	Capacitor, Ceramic, 0.01-uF, 50-V, X7R, 10%	0603	GRM188R71H103KA01	muRata
1	C9	Capacitor, Ceramic, 22-uF, 16-V, X5R, 10%	1210	C3225X5R1C226K	TDK
3	L1, L2, L3	Inductor, SMT, 10-uH, 8-A, 20-milliohm	0.51 x 0.51	IHLP-5050CZ	Vishay
3	Q1, Q2, Q3	Transistor, MOSFET, Nch, 11.5A, 30V 9.5 milliohm	0.160 x 0.130	FDR6674A	Fairchild
3	R1, R12, R18	Resistor, Chip, 10.0k-Ohms, 1/16-W, 1%	0603	Std	Std
3	R10, R16, R22	Resistor, Chip, 4.7-Ohms, 1/2 W, 5%	2010	Std	Std
1	R11	Resistor, Chip, 10.0k-Ohms, 1/16-W, 1%	0603	Std	Std
1	R14	Resistor, Chip, 37.4k-Ohms, 1/16-W, 1%	0603	Std	Std
1	R17	Resistor, Chip, 3.74k-Ohms, 1/16-W, 1%	0603	Std	Std
1	R19	Resistor, Chip, 2.26k-Ohms, 1/16-W, 1%	0603	Std	Std
1	R2	Resistor, Chip, 28.7k-Ohms, 1/16-W, 1%	0603	Std	Std
1	R20	Resistor, Chip, 2.00k-Ohms, 1/16-W, 1%	0603	Std	Std
2	R3, R7	Resistor, Chip, 9.76k Ohms, 1/16-W, 1%	0603	Std	Std
1	R4	Resistor, Chip, 147k-Ohms, 1/16-W, 1%	0603	Std	Std
3	R5, R8, R13	Resistor, Chip, 5.49k-Ohms, 1/16-W, 1%	0603	Std	Std
3	U1, U2, U3	IC, 3-A Output Synchronous PWM Switcher	PWP16	TPS54350PWP	TI

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
Low Power Wireless	www.ti.com/lpw	Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265