 


TI TECH DAYS



How to resolve op-amp stability issues using SPICE simulations




Presented by Marek Lis
High Precision Products

Speaker: Marek Lis





- Senior analog applications engineer on PA team
- Supports:
 - Operational amplifiers
 - Voltage references
 - Macro-models
 - Long-term stability
 - Statistical guarantee of specs
- Worked for ten years at Burr-Brown Corporation as an analog IC design engineer
- Designed over 20 new products from op amps to voltage LDO regulators
- Managed development of series voltage references and instrumentation amplifiers
- Co-invented Green-Lis op amp macro-model; state-of-the-art PSpice-based architecture
- Studied electrical engineering at the University of Michigan and the University of Arizona

Op amp stability issue

 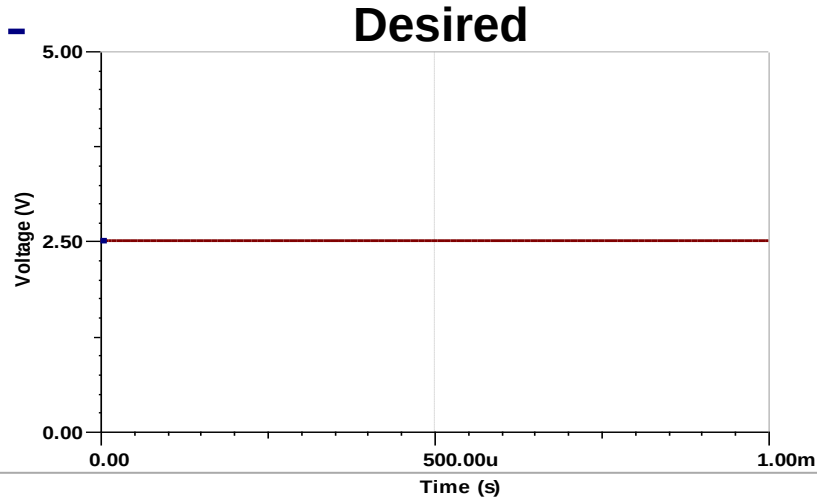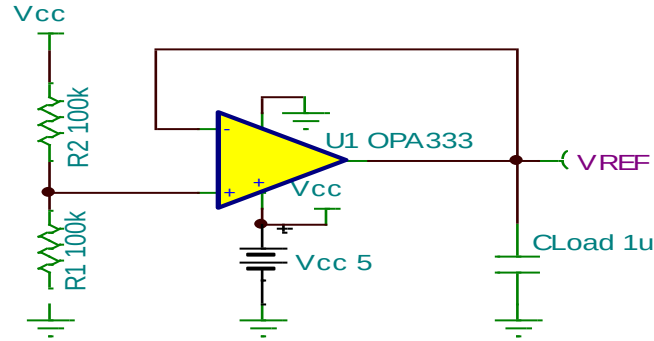


Simplified cause of op amp stability issues

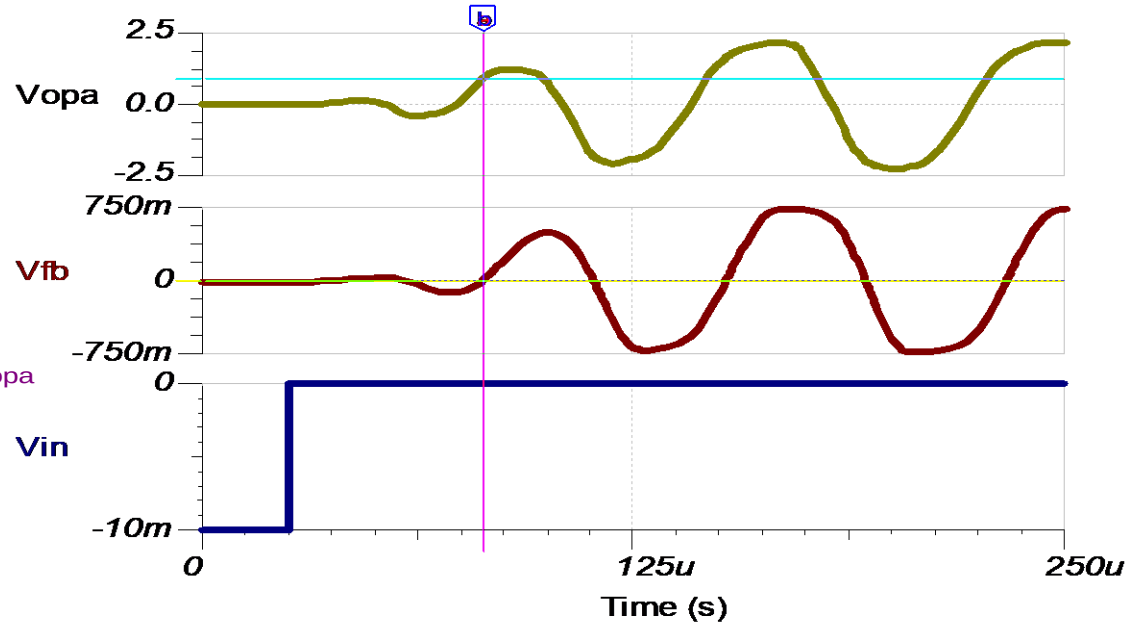 Issues happen because of too much delay from output to feedback!




Delay happens in many circuits

 

Identify stability issues in the lab

 - Suggested tools:
 - Oscilloscope
 - Signal generator
- Other useful tools:
 - Gain / phase analyzer




Identify stability issues in the lab


- Oscilloscope – time domain analysis:

- Oscillations
- Overshoot and ringing
- Unstable DC voltages
- High distortion



Output response to step input

 

Output response to square wave input

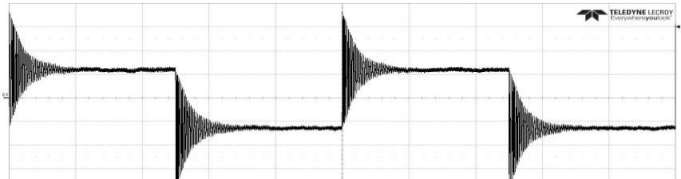

  
Sustained output oscillation with DC input




Identify stability issues in the lab

- Gain / phase analyzer – frequency domain:
 - Peaking, unexpected gains, rapid phase shifts


Simulated

 


Measured

 

Solving op amp stability issues

 

Bode plots – pole

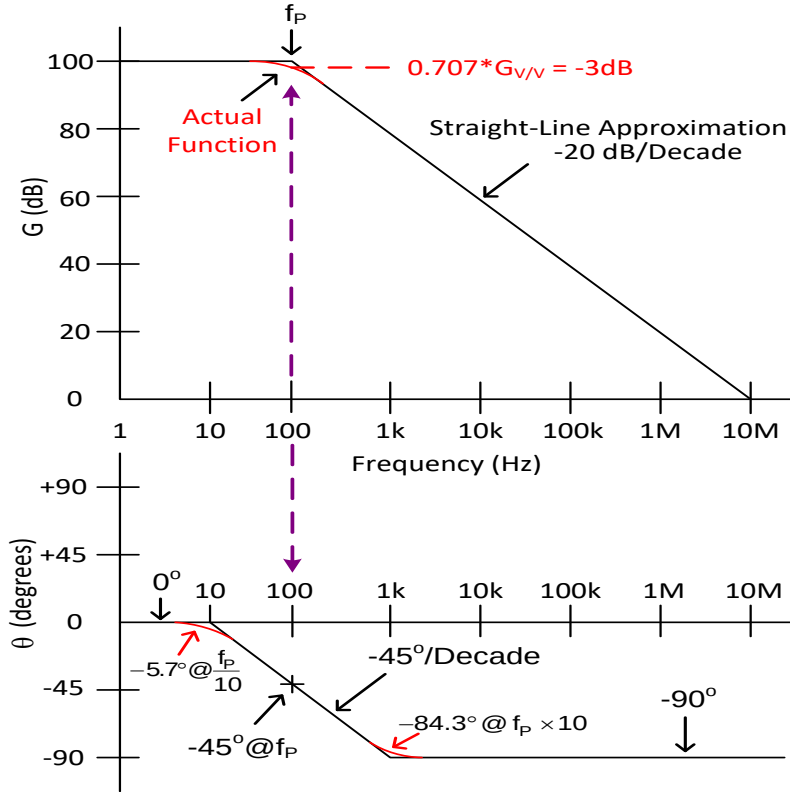

$$G_{v/v} = \frac{V_{out}}{V_{in}} = \frac{G_{dc}}{i \left(\frac{f}{f_p} \right) + 1}$$

As a complex number

$$G_{v/v} = \frac{V_{out}}{V_{in}} = \frac{G_{dc}}{\sqrt{\left(\frac{f}{f_p} \right)^2 + 1}}$$

Magnitude

$$\Theta = -\tan^{-1} \left(\frac{f}{f_p} \right)$$


Phase

$$G_{dB} = 20\text{Log}(G_{v/v})$$

Magnitude in dB

- Pole Location = f_p (Cutoff Freq)
- Magnitude ($f < f_p$) = G_{dc} (e.g. 100dB)
- Magnitude ($f = f_p$) = -3dB
- Magnitude ($f > f_p$) = -20dB/Decade
- Phase ($f = f_p$) = -45°
- Phase ($0.1f_p < f < 10f_p$) = -45°/Decade
- Phase ($f > 10f_p$) = -90°
- Phase ($f < 0.1f_p$) = 0°

Bode plots – zero

 

$$G_{v/v} = \frac{V_{out}}{V_{in}} = G_{dc} \left[i \left(\frac{f}{f_z} \right) + 1 \right] \quad \text{As a complex number}$$




$$G_{v/v} = \frac{V_{out}}{V_{in}} = G_{dc} \sqrt{\left(\frac{f}{f_z} \right)^2 + 1} \quad \text{Magnitude}$$

$$\Theta = \tan^{-1} \left(\frac{f}{f_z} \right) \quad \text{Phase}$$



$$G_{dB} = 20 \log(G_{v/v}) \quad \text{Magnitude in dB}$$

- Zero Location = f_z
- Magnitude ($f < f_z$) = 0dB
- Magnitude ($f = f_z$) = +3dB
- Magnitude ($f > f_z$) = +20dB/Decade
- Phase ($f = f_z$) = +45°
- Phase ($0.1f_z < f < 10f_z$) = +45°/Decade
- Phase ($f > 10f_z$) = +90°
- Phase ($f < 0.1f_z$) = 0°

Op amp open loop model

   

Op amp closed loop model

  

A_{ol} = Open loop Gain

$$\beta = \text{Feedback Factor} = \frac{V_{fb}}{V_{out}} = \frac{R_1}{R_1 + R_f}$$

$$A_{cl} = \text{Closed Loop Gain} = \frac{A_{ol}}{1 + A_{ol}\beta}$$

$A_{ol}\beta$ = Loop Gain

$$A_{cl} = \lim_{A_{ol} \beta \rightarrow \infty} \left(\frac{A_{ol}}{1 + A_{ol}\beta} \right) = \frac{1}{\beta} = 1 + \frac{R_f}{R_1}$$

When is an amplifier unstable?

$$A_{CL} = \frac{A_{OL}}{1 + A_{OL}\beta}$$


- A circuit is unstable when $A_{OL}\beta = -1$
- $A_{OL}\beta = -1$ sets the denominator of $A_{CL} = 0$
- $A_{OL}\beta = -1$ when $A_{OL}\beta(\text{dB}) = 0\text{dB}$ and phase shift($A_{OL}\beta$) = 180°
 - Phase shift is relative to the DC phase

Phase margin (PM)




How close the system is to a 180° phase shift in $A_{OL}\beta$

- $\text{PM} = \text{Phase}(A_{OL}\beta)$ when $\text{Gain}(A_{OL}\beta) = 0\text{dB}$
- Ex: 10° phase margin = 170° phase shift in $A_{OL}\beta$

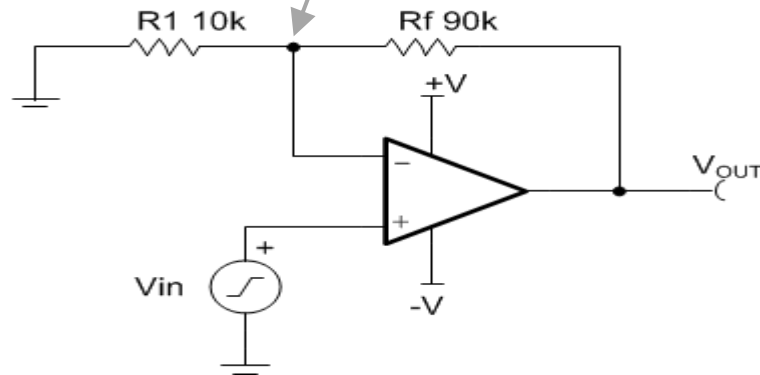$A_{OL}\beta = -1$ when the phase at V_{FB} has shifted 180° relative to V_{in}



Loop gain magnitude – $A_{OL}\beta$

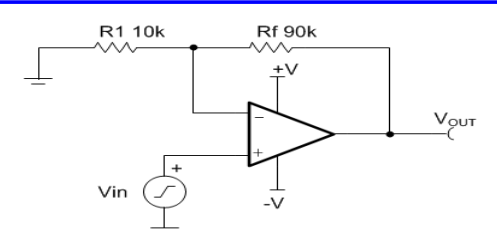  

$$\frac{1}{\beta} = \frac{V_{OUT}}{V_{FB}} = \frac{R_F}{R_1} + 1 = 10 \text{ V/V}$$

$$\frac{1}{\beta} \text{ (dB)} = 20 \log(10) = 20 \text{ dB}$$



Loop gain in dB:

$$20 \log(A_{OL}\beta) = 20 \log(A_{OL}) - 20 \log\left(\frac{1}{\beta}\right)$$

$$A_{OL}\beta \text{ (dB)} = A_{OL} \text{ (dB)} - \frac{1}{\beta} \text{ (dB)}$$

Note: $A_{OL}\beta \text{ (dB)} = 0 \text{ dB}$ when A_{OL} and $\frac{1}{\beta}$ intersect

Loop gain phase – phase($A_{OL}\beta$)

  


C1 introduces a zero in $\frac{1}{\beta}$

$$\frac{1}{\beta} = \frac{Z_f}{Z_1} + 1$$

At DC the capacitor is open, so gain = 10V/V. At high frequency the capacitor causes Z_1 to decrease, so gain increases by +20dB/decade

Phase margin

 


Rule of thumb:

Phase margin $> 45^\circ$ is required for optimal stability!

Phase margin $< 45^\circ$ is considered “marginally stable.”


This does not ensure a robust design over process variation.

Rate of closure – unstable example

 

Rule of thumb:

 Rate of closure = 20dB is required for optimal stability!



$$\frac{1}{\beta} = \frac{V_{OUT}}{V_{FB}} = 10 \left(\frac{f}{f_c} + 1 \right)$$


$1/\beta(\text{dB}) = 20\text{dB}$ at DC, then increases by +20dB/decade after the zero frequency

$$\text{Rate of Closure} = \left| \text{Slope}(A_{OL}) - \text{Slope} \left(\frac{1}{\beta} \right) \right|$$

$$\text{Rate of Closure} = |-20\text{dB} - (+20\text{dB})| = 40\text{dB}$$

Unstable because rate of closure > 20dB!

Rate of closure – stable example

 


$$\frac{1}{\beta} = \frac{V_{OUT}}{V_{FB}} = \frac{R_F}{R_1} + 1 = 10 \text{ V/V}$$

$$\frac{1}{\beta} (\text{dB}) = 20 \log(10) = 20 \text{ dB}$$

Rule of thumb:

 Rate of closure = 20dB is required for optimal stability!




$$\text{Rate of Closure} = \left| \text{Slope}(A_{OL}) - \text{Slope}\left(\frac{1}{\beta}\right) \right|$$

$$\text{Rate of Closure} = |-20 \text{ dB} - 0 \text{ dB}| = 20 \text{ dB}$$

Stable because rate of closure = 20dB!


Rate of closure (ROC) and phase margin

 


ROC (dB/decade)	Phase margin (°)
20	$45 < PM < 90$
$20 < ROC < 40$	45
40	$0 < PM < 45$

Indirect phase margin measurements

 Phase margin can be measured indirectly on closed-loop circuits!





Time domain → percent overshoot

 

AC gain/phase → AC peaking



Indirect phase margin measurements

  

$$\% \text{Overshoot} = \left(\frac{14.3\text{mV} - 10\text{mV}}{10\text{mV}} \right) * 100\% = 43\%$$

43% overshoot → 29° phase margin

Indirect phase margin measurements



 
 


$$\text{AC peaking} = 6\text{dB} - 0\text{dB} = 6\text{dB}$$

6dB AC peaking → **29° phase margin**





Quiz

    - Which one of these A_{OL} and $1/\beta$ curves is unstable?




Quiz

    - Which one of these A_{OL} and $1/\beta$ curves is unstable?




Quiz

 - Find the phase margin of each system according to the % overshoot.



 
$$\% \text{Overshoot} = \left(\frac{16.4\text{mV} - 10\text{mV}}{20\text{mV}} \right) * 100\% = 32\%$$




$$\% \text{Overshoot} = \left(\frac{19.6\text{mV} - 10\text{mV}}{20\text{mV}} \right) * 100\% = 48\%$$

Phase margin vs Percentage Overshoot




 


Phase margin vs Percentage Overshoot

 


Quiz

    - Find the phase margin of each system according to the AC peaking.




Quiz

 - Find the phase margin of each system according to the Bode plot.




45° phase margin

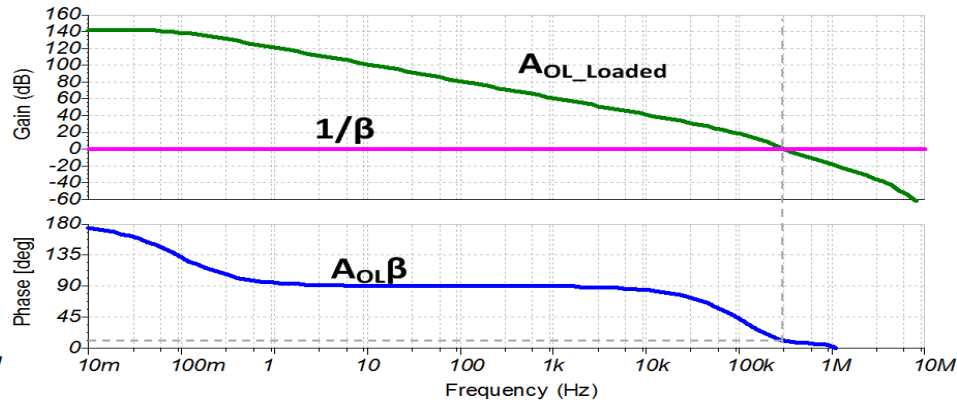

~15° phase margin

TI TECH DAYS


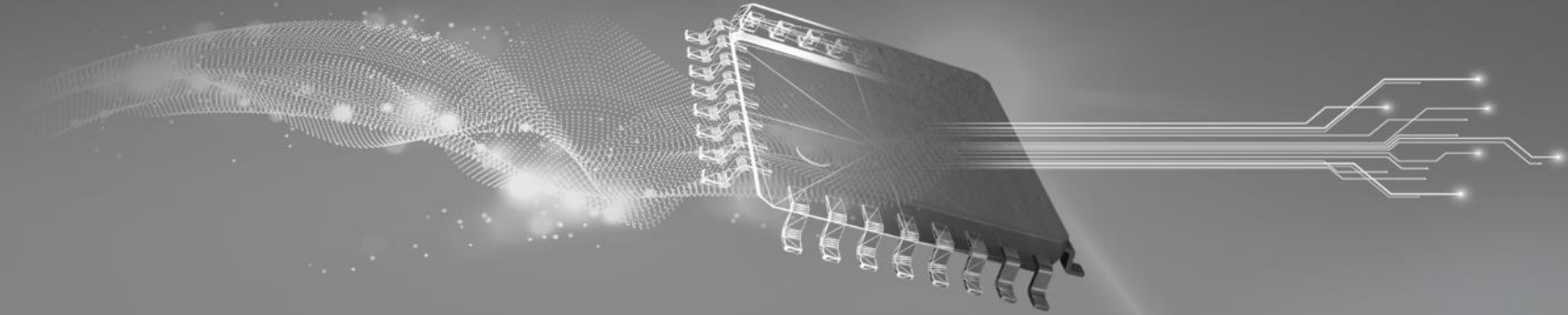


How to resolve op-amp stability issues using SPICE simulations – Part 2

Presented by Marek Lis
High Precision Products

Simulating open-loop circuits

  
No DC biasing produces erroneous results!



Simulating open-loop circuits


DC: closed loop needed for SPICE operation

 AC: open loop needed for stability analysis




Standard open-loop SPICE configuration

 We need an open-loop circuit (no feedback) to generate open-loop gain (A_{OL}), $1/\beta$, and loop gain ($A_{OL}\beta$) curves



 
$$A_{OL_LOADED} = V_o / V_{fb}$$
$$1/\beta = 1 / V_{fb}$$
$$A_{OL}\beta = V_o$$



Check DC operating point

 Click **Analysis** → **DC Analysis** → **Calculate Nodal Voltages**



Generating open-loop curves

Run an AC transfer characteristic analysis over the appropriate frequency range:

Click **Analysis** → **AC Analysis** → **AC Transfer Characteristic**


The screenshot displays a circuit simulation software interface. The **Analysis** menu is open, showing the path: **Analysis** → **AC Analysis** → **AC Transfer Characteristic**. The **AC Transfer Characteristic** dialog box is open, showing the following settings:

- Start frequency: 1 [Hz]
- End frequency: 10M [Hz]
- Number of points: 100
- Sweep type: ☒ Logarithmic
- Diagram: ☒ Amplitude & Phase

The circuit diagram shows an operational amplifier (OP AMP) configured as a voltage follower. The input is connected to a voltage source V_{fb} through a resistor $R1$ (1k). The output is connected to the input through a resistor $R2$ (1k) and a capacitor $C1$ (1T). The output is also connected to a load capacitor $L1$ (1T) and a voltage source V_{G1} . The output voltage is labeled V_o .

Generating open-loop curves

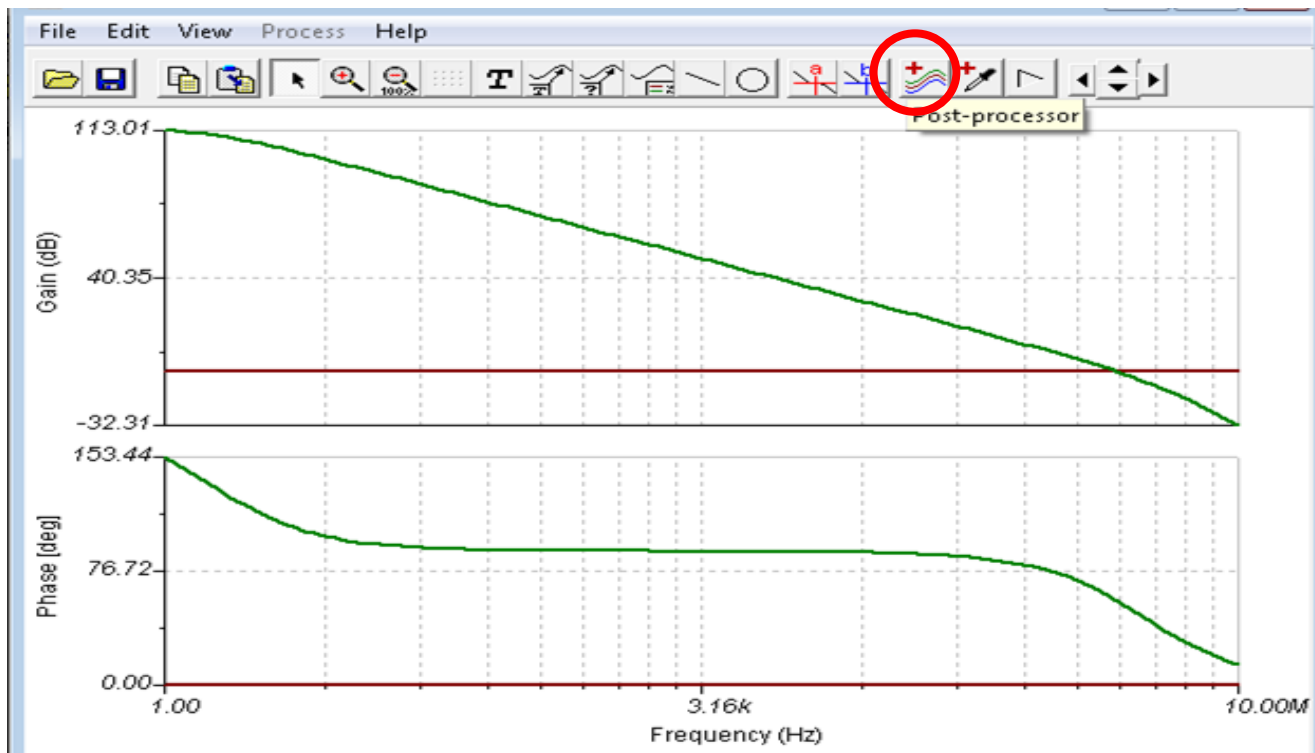Click the “Post-Processor” button to add the desired curves





Generating open-loop curves

Perform math on the existing curves to create the new curves:

$$A_{OL} = V_o / V_{fb}$$


$$1/\beta = 1/V_{fb}$$

$$A_{OL}\beta = V_o$$

  


Generating open-loop curves

Unformatted results with all curves:

 



Generating open-loop curves

 Use a cursor to determine the frequency where $Aol\beta = 0\text{dB}$, f_c , and place legend to show corresponding magnitudes and phases





Phase Margin =
 $Aol\beta$ Phase @ f_c

  Why do capacitive loads cause instability?




Simulate the effects of output capacitance

  Run open-loop analysis on buffer circuit with capacitive load





Phase margin = 4°

Capacitive loads – stability theory

 

Capacitive loads – stability theory

  

Transfer function:


$$\frac{V_o}{V_{in}}(s) = \frac{1}{1 + s * R_o * C_{LOAD}}$$

Pole equation:

$$f_{POLE} = \frac{1}{2 * \pi * R_o * C_{LOAD}}$$


Capacitive loads – stability theory

A_{OL} (from data sheet)

 


X


A_{OL} load

 

Loaded A_{OL} =

 


Compensation method 1: R_{iso}

 


Method 1: R_{ISO} – results


Theory: Adds a zero to cancel the pole in loaded A_{OL}

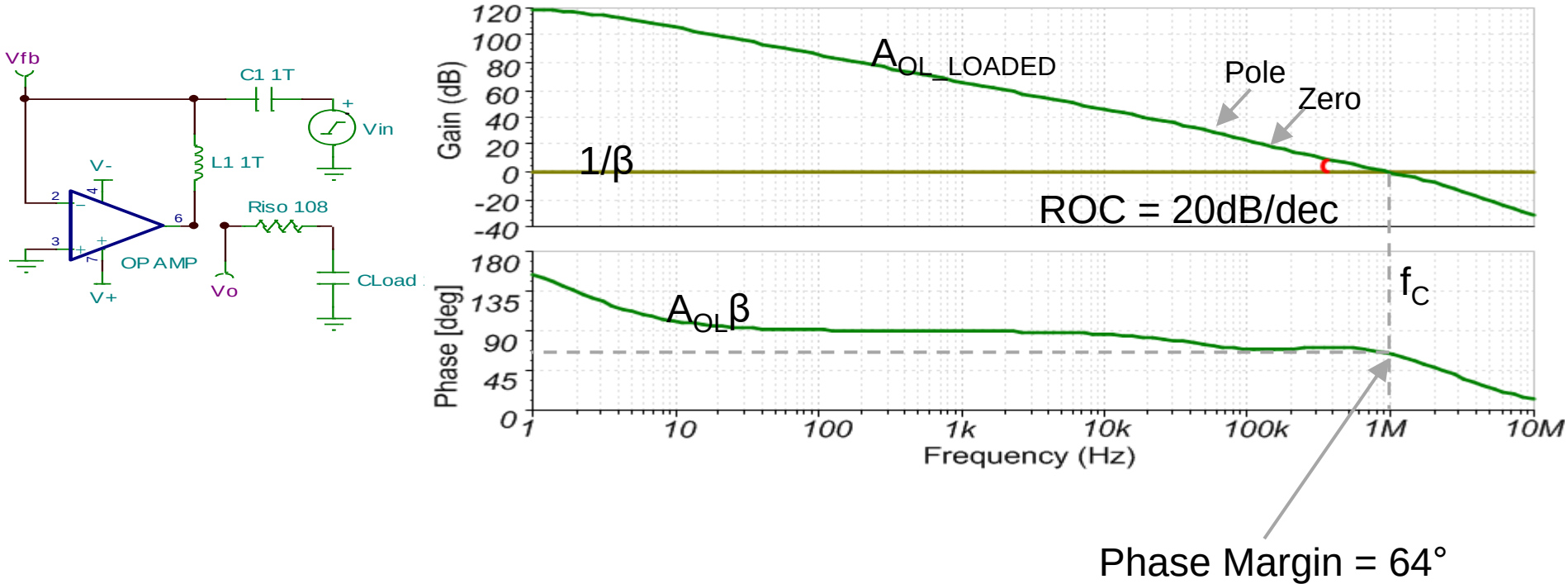


Method 1: R_{ISO} – theory

 

Resistor divider analogy

 
 
$$\frac{V_o}{V_{IN}} = \frac{R_2}{R_2 + R_1}$$



$$\frac{V_o}{V_{IN}} = \frac{Z_2}{Z_2 + Z_1}$$

$$\frac{V_o}{V_{IN}} = \frac{R_{ISO} + \frac{1}{s * C_{LOAD}}}{\left(R_{ISO} + \frac{1}{s * C_{LOAD}}\right) + R_O}$$


$$\frac{V_o}{V_{IN}} = \frac{1 + s * R_{ISO} * C_{LOAD}}{1 + s * (R_{ISO} + R_O) * C_{LOAD}}$$

Zero: R_{ISO} & C_{LOAD}

Pole: R_O , R_{ISO} , and C_{LOAD}


Method 1: R_{ISO} – theory

A_{OL} (from data sheet)

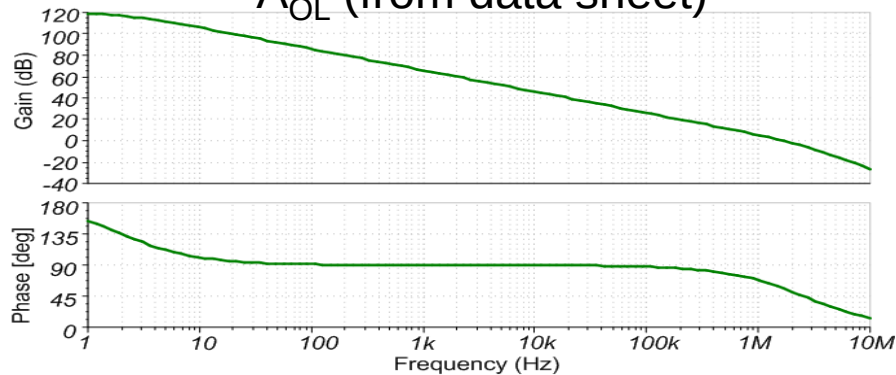


X



A_{OL} Load

 

Loaded A_{OL} =

 

Method 1: R_{ISO} – theory

  

Transfer function:

$$\frac{V_o}{V_{in}}(s) = \frac{1 + s * R_{ISO} * C_{LOAD}}{1 + s * (R_O + R_{ISO}) * C_{LOAD}}$$

Zero equation:

$$f_{ZERO} = \frac{1}{2 * \pi * R_{ISO} * C_{LOAD}}$$

Pole equation:

$$f_{POLE} = \frac{1}{2 * \pi * (R_O + R_{ISO}) * C_{LOAD}}$$

Method 1: R_{ISO} – design


Design steps:

- 1.) Find the zero frequency, f_{ZERO} , where $A_{OL_Loaded} = 20$ dB
- 2.) Calculate R_{iso} to set the zero at f_{ZERO}
This will yield between 60° and 90° degrees of phase margin



R_{ISO} equation:

$$R_{iso} = \frac{1}{2 * \pi * f_{ZERO} * C_{LOAD}}$$
$$R_{iso} = \frac{1}{2 * \pi * 146.5\text{kHz} * 10\text{nF}}$$



$$R_{iso} = 108\Omega$$

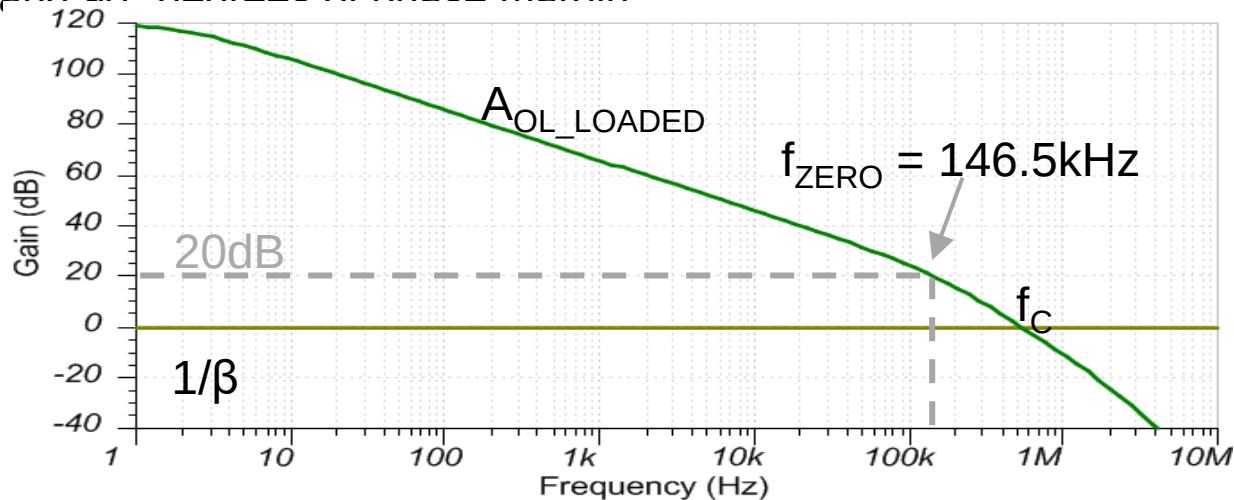


Method 1: R_{ISO} – design summary

 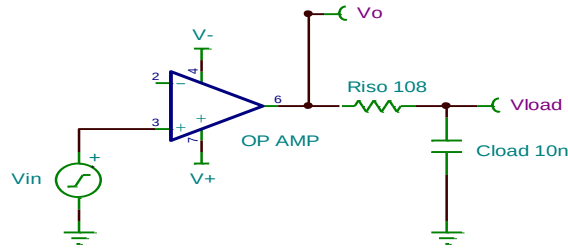

Unstable vs. stable transient results

  

No compensation - unstable

 


Riso compensation - stable


Method 1: R_{ISO} – disadvantage

Disadvantage:

Voltage drop across R_{ISO} may not be acceptable for certain applications!

 

Method 2: R_{ISO} + dual feedback

 


Method 2: R_{ISO} + dual feedback – theory

DC circuit

C_F : Open

R_F : Closes the feedback around R_{ISO}

$$V_{LOAD} = V_{IN}$$

 


AC circuit

C_F : Short

$R_F \gg Z_{CF}$, therefore R_F is effectively open

Behaves like R circuit

 

Method 2: R_{ISO} + dual feedback - design

Design steps:

1) Set R_{ISO} using Method 1: R_{ISO} techniques

2) Set R_F : $\frac{5 \times R_{iso} \times C_L}{R_{F_LOAD}} \leq C_F \leq \frac{10 \times R_{iso} \times C_L}{R_F}$

3) Set C_F : $\frac{R_{F_LOAD}}{C_F} \leq C_F \leq \frac{R_{F_LOAD}}{C_F}$

lower values of C_F = faster settling, higher overshoot

Rule 3 ensures that the two feedback paths will never create a resonance that would cause instability


$$R_{ISO} = 108\Omega$$

$$R_F \geq R_{ISO} * 100$$

$$R_F \geq 10.8k\Omega$$

$$\frac{5 \times R_{iso} \times C_L}{R_{F_LOAD}} \leq C_F \leq \frac{10 \times R_{iso} \times C_L}{R_F}$$



$$420pF \leq C_F \leq 720pF$$

 


Phase Margin = 66°

Method 2: R_{ISO} + dual feedback - results



 
 
- V_{LOAD} matches V_{IN} – No voltage divider error!
- This topology has some limitations on settling time and capacitive load range







Summary – solving op amp stability

 





Solving op amp stability

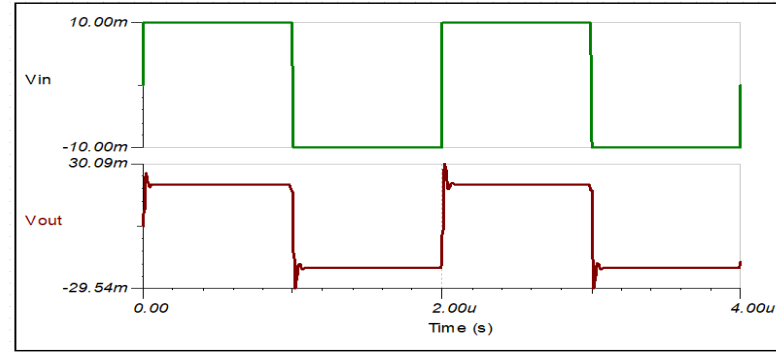   

Solving Op Amp Stability

   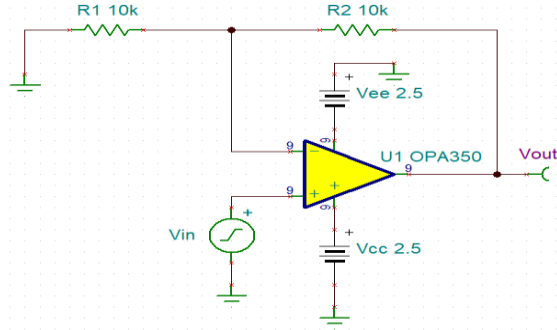

Solving op amp stability

    

Questions?

Thanks for your time!



©2020 Texas Instruments Incorporated. All rights reserved.

The material is provided strictly "as-is" for informational purposes only and without any warranty.
Use of this material is subject to TI's **Terms of Use**, viewable at [TI.com](https://www.ti.com)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2020, Texas Instruments Incorporated