

TPS79918 RF LDO supports migration to StrataFlash® Embedded Memory (P30)

By Michael Day (Email: m-day@ti.com)

Power Management Products/Portable Power dc/dc Applications

Introduction

The Texas Instruments (TI) TPS79918 low dropout (LDO) linear regulator provides the performance required to power the new Intel® StrataFlash® Embedded Memory (P30). Intel is migrating from its third-generation 180-nm StrataFlash Embedded Memory (J3) to its fourth-generation 130-nm StrataFlash Embedded Memory (P30). This migration from J3 to P30 memory allows systems to operate at a lower overall current consumption because the P30 V_{CC} voltage requirement has dropped to 1.8 V. Intel Application Note 812¹ recommends using an LDO linear regulator to provide the new 1.8-V voltage rail.

TPS79918 features

The TPS79918 LDO offers exceptional electrical performance in a small package. It provides a high (greater than 66-dB) power supply rejection ratio (PSRR), low noise, fast startup, and excellent line and load transient response. It consumes only 40 μ A of ground current at full load. No input capacitor is required for operation. The TPS79918 is stable with a small ceramic output capacitor and uses an advanced BiCMOS fabrication process to yield a 110-mV dropout voltage at the full 200-mA output load. Its precision voltage reference and feedback loop achieve a 2% overall accuracy over all load, line, process, and temperature

variations. The addition of an optional noise-reduction capacitor provides an extremely low-noise output voltage. It is fully specified from $T_J = -40^\circ\text{C}$ to $+125^\circ\text{C}$ and is offered in three packages: ThinSOT-23, wafer chip-scale (WCSP), and 2×2 SON-6. The difference between the three packages is size and power dissipation. If we assume a 60°C ambient temperature, the power dissipation for the three packages is 142 mW, 156 mW, and 526 mW, respectively. That corresponds to a maximum continuous load current of 119 mA, 130 mA, and 438 mA, respectively.

Figure 1 shows the TPS79918 internal block diagram. The active-high enable signal turns the device on after the input voltage goes above the undervoltage lockout (UVLO) level. UVLO ensures that the input voltage is available, which provides a clean start-up waveform. The IC features current-limit and thermal-shutdown protection in case of a system failure. The internal 500-k Ω resistor, along with an external noise-reduction capacitor on the NR pin, provides an RC filter to reduce the bandgap noise, resulting in a low-noise output voltage. The quickstart switch initially shorts out this resistor to provide a fast 40- μ s start-up time. This IC has excellent transient response enhanced by the Overshoot Detect circuit that during a heavy load actively pulls the output voltage down to a light-load transient.

Figure 1. TPS79918 internal block diagram


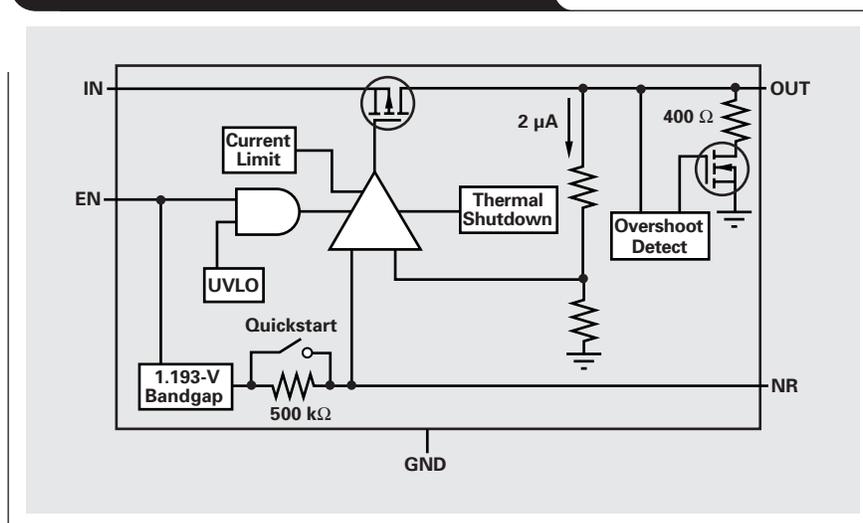


Figure 2. TPS79918 load transient

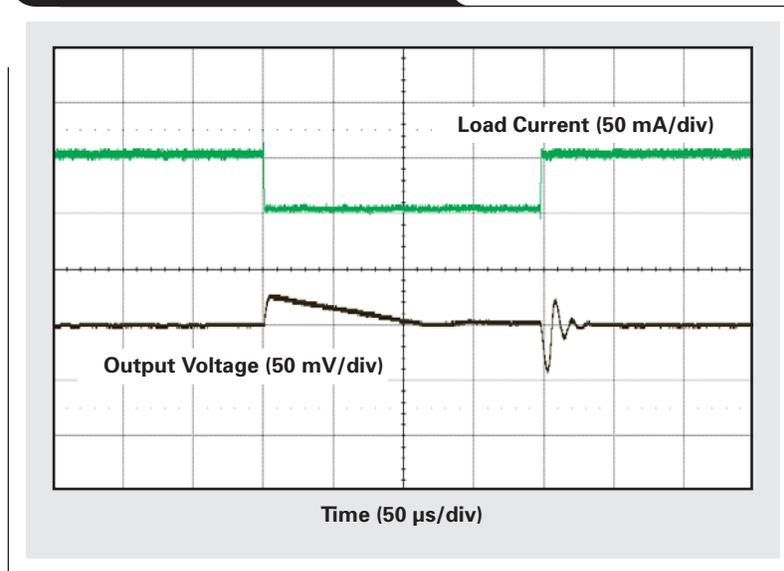

Intel StrataFlash Embedded Memory (P30) requirements

Migrating existing J3 memory systems to the new P30 memory requires regulating the existing 3.0-V core voltage down to 1.8 V. The 1.8-V core voltage requires regulation within ± 0.1 V, which is met by the TPS79918's tight 2% voltage tolerance. The LDO performs well with the load transients caused by rising and falling edges of CE# and OE#. Figure 2 shows that even with a 1- to 50-mA load transient, the output voltage drops only 40 mV. This performance meets the P30 memory input voltage requirement. Taking system-level requirements into consideration, Intel's application note cautions the designer to consider both standby current and active current. Figure 3 shows that, unlike some LDOs, the TPS79918's low quiescent current is constant over changes in input voltage and load current. The low quiescent current extends battery life in portable applications.

Figure 3. TPS79918 quiescent current vs. line and load

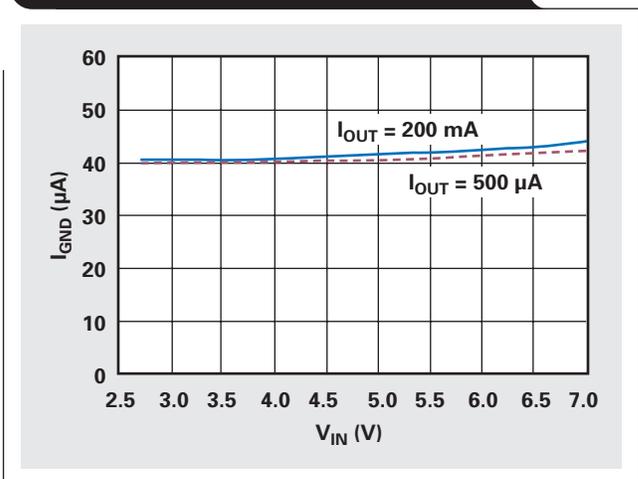


Figure 4 shows the simplicity of a TPS79918 powering a P30 memory module. The only required components are the LDO itself and its output capacitor. The input capacitor is required only if the 3.0-V output capacitor is not physically located near the LDO. The noise-reduction capacitor is needed only to power noise-sensitive applications, so it is not required in this application.

Intel specifically recommends the TI LDOs in Table 1 for its StrataFlash Embedded Memory (P30). These LDOs meet the electrical and temperature requirements for the new P30 memory.

Table 1. Recommended TI LDOs for Intel StrataFlash Embedded Memory (P30)

DEVICE	V _o (V)	I _o (mA)	I _q (μA)	PSRR (dB)	PACKAGE	DIMENSIONS (mm)
TPS79918DDC	1.8	200	40	70	TSOT-23	2.9 x 2.8 x 1.0
TPS79918DRV	1.8	200	40	70	2 x 2 SON-6	2.0 x 2.0 x 0.75
TPS79918YZU	1.8	200	40	70	WCSP	1.36 x 1.00 x 0.62

Conclusion

The TI TPS79918 LDO is ideally suited to power Intel's next-generation StrataFlash Embedded Memory (P30). The three packaging options allow the designer to optimize the solution size while the LDO's electrical performance meets the system-level requirements for low standby current, transient response, and peak current.


Reference

1. "Migration Guide for Intel StrataFlash® Memory (J3) to Intel StrataFlash® Embedded Memory (P30)," Intel Application Note 812, June 3, 2005, www.intel.com/design/flcomp/aplnots/306667.htm

Related Web sites

power.ti.com
www.intel.com

Figure 4. Typical StrataFlash configuration with LDO

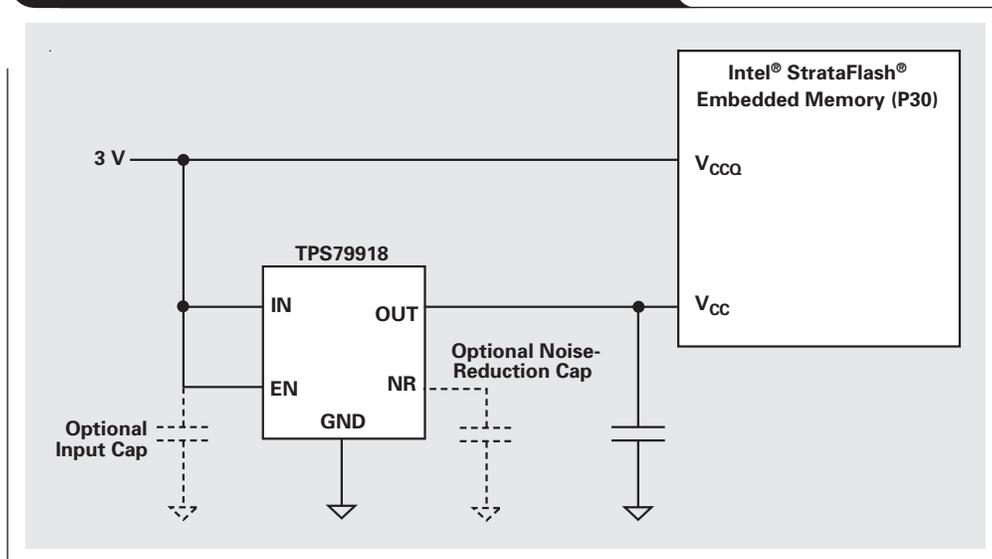

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DSP	dsp.ti.com
Interface	interface.ti.com
Logic	logic.ti.com
Power Management	power.ti.com
Microcontrollers	microcontroller.ti.com

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital control	www.ti.com/digitalcontrol
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page
support.ti.com

TI Semiconductor KnowledgeBase Home Page
support.ti.com/sc/knowledgebase

Product Information Centers

Americas

Phone	+1(972) 644-5580	Fax	+1(972) 927-6377
Internet/Email	support.ti.com/sc/pic/americas.htm		

Europe, Middle East, and Africa

Phone			
Belgium (English)	+32 (0) 27 45 54 32	Netherlands (English)	+31 (0) 546 87 95 45
Finland (English)	+358 (0) 9 25173948	Russia	+7 (0) 95 363 4824
France	+33 (0) 1 30 70 11 64	Spain	+34 902 35 40 28
Germany	+49 (0) 8161 80 33 11	Sweden (English)	+46 (0) 8587 555 22
Israel (English)	180 949 0107	United Kingdom	+44 (0) 1604 66 33 99
Italy	800 79 11 37		
Fax	+(49) (0) 8161 80 2045		
Internet	support.ti.com/sc/pic/euro.htm		

Japan

Fax			
International	+81-3-3344-5317	Domestic	0120-81-0036
Internet/Email			
International	support.ti.com/sc/pic/japan.htm		
Domestic	www.tij.co.jp/pic		

Asia

Phone			
International	+886-2-23786800		
Domestic	Toll-Free Number		
Australia	1-800-999-084	Malaysia	1-800-80-3973
China	800-820-8682	New Zealand	0800-446-934
Hong Kong	800-96-5941	Philippines	1-800-765-7404
India	+91-80-51381665 (Toll)	Singapore	800-886-1028
Indonesia	001-803-8861-1006	Taiwan	0800-006800
Korea	080-551-2804	Thailand	001-800-886-0010
Fax	+886-2-2378-6808	Email	tiasia@ti.com
Internet	support.ti.com/sc/pic/asia.htm		
			ti-china@ti.com

C120905

Safe Harbor Statement: This publication may contain forward-looking statements that involve a number of risks and uncertainties. These "forward-looking statements" are intended to qualify for the safe harbor from liability established by the Private Securities Litigation Reform Act of 1995. These forward-looking statements generally can be identified by phrases such as "TI or its management believes," "expects," "anticipates," "foresees," "forecasts," "estimates" or other words or phrases of similar import. Similarly, such statements herein that describe the company's products, business strategy, outlook, objectives, plans, intentions or goals also are forward-looking statements. All such forward-looking statements are subject to certain risks and uncertainties that could cause actual results to differ materially from those in forward-looking statements. Please refer to TI's most recent Form 10-K for more information on the risks and uncertainties that could materially affect future results of operations. We disclaim any intention or obligation to update any forward-looking statements as a result of developments occurring after the date of this publication.

Trademarks: All trademarks are the property of their respective owners.

Mailing Address: Texas Instruments
Post Office Box 655303
Dallas, Texas 75265

© 2006 Texas Instruments Incorporated