

Bandstop filters and the Bainter topology

By Bonnie C. Baker

Senior Applications Engineer

Many applications, such as tone-signaling, audio-signal, hearing-aid feedback, or mains rejection systems, require bandstop (notch) filters to eliminate undesirable signals. One can achieve these signal reductions by using active bandstop analog filters.

The bandstop filter circuit topologies considered in this article are Sallen-Key, multiple-feedback, and Bainter. Each circuit produces a second-order bandstop filter, with one pole and one zero in the transfer function.

A starting point is to define the bandstop filter characteristics. In Figure 1, the bandstop filter disallows signals within a certain bandwidth (BW_P), while passing frequencies above and below the rejected frequency area.

This standard generic diagram highlights the key bandstop filter parameters; passband, stopband, f_0 , BW_P , A_0 , A_{SB} , BW_S , and R_p .

The three filter-response regions are the low-frequency passband, the stopband, and the high-frequency passband. In both of the passband frequency regions, signals pass freely from the input to the filter's output. In the stopband region, frequency signals are attenuated per the diagram in Figure 1. The notch filter's center frequency is f_0 .

BW_P (passband bandwidth) defines the -3-dB bandwidth inside the bandstop filter. This bandwidth also defines the quality factor or Q (See Reference 1) of the filter, where $Q = (f_0 / BW_P)$. BW_S defines the stopband bandwidth. In the region below the BW_S point, the bandstop filter creates a notch, sometimes dipping -100 dB or more.

The stopband attenuation ranges from A_0 to the A_{SB} (stopband magnitude). A_0 (passband gain) and A_{SB} along with the specified stopband attenuation, defines the speed of the notch's attenuation. Finally, for Chebyshev approximations, the definition of the ripple magnitude is R_p .

The bandpass/notch filter requires pairs of poles and zeroes in the transfer function. The corner frequency of the poles and zeroes resides at or near f_0 .

The transfer function of the bandstop/notch filter is:

$$H(s) = \frac{H_0(s^2 + w_z^2)}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2} \quad (1)$$

For comparison purposes, the following discussion includes the Sallen-Key, multiple-feedback, and Bainter filter topologies to realize a bandstop filter.

Figure 1. Frequency response of the bandstop filter


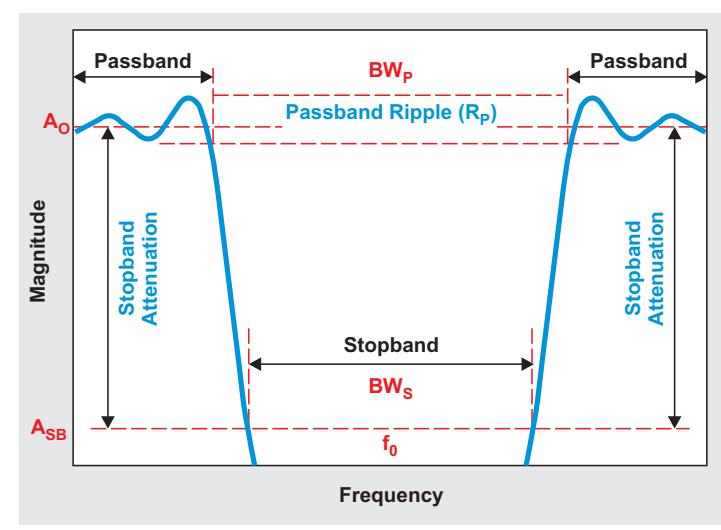


Figure 2. Second-order Sallen-Key bandstop or notch filter

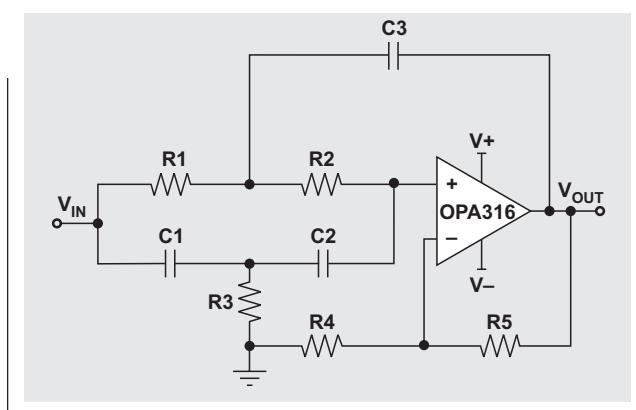

Sallen-Key circuit topology

The Sallen-Key topology in Figure 2 implements a second-order bandstop filter. This particular circuit is valued for its simplicity, as it has one amplifier, five resistors, and three capacitors. One advantage of this circuit is that the ratio of the largest resistor to the smallest resistor is small, as well as the capacitor high and low values. This is beneficial to the manufacturability of the filter.

While the Sallen-Key filter is widely used in low-pass and high-pass filters, it has several serious drawbacks for bandstop filters. The Sallen-Key is not easily tuned because of the interaction of the component values on the center frequency (f_0) and Q . The open-loop output resistance

also interferes while attempting to produce the ideal notch-filter characteristics (Figure 3). Additionally, f_0 cannot be easily adjusted because of component interaction.

A sixth-order filter is implemented by cascading three second-order filters (Figure 2) in series. Figure 3 shows the sixth-order, closed-loop response of a Sallen-Key circuit. This figure shows the Sallen-Key's circuit closed-loop gain response of 4.58 V/V with a linear phase 0.5° approximation type and f_0 equal to 1 kHz.

The construct of this sixth-order filter uses ideal resistors (15), capacitors (9), and amplifiers (3). With ideal components and devices in the circuit, the closed-loop frequency response has three spurs going down and shows that there is only about -15 dB of attenuation within the notch.

As a consequence of these shortcomings, the Sallen-Key notch filter is not a recommended topology for bandstop filter construction.

Multiple-feedback circuit topology

The multiple-feedback (MFB) topology in Figure 4 implements a second-order bandstop. The MFB circuit is also valued for its simplicity, having one op amp, three resistors, and two capacitors in the first stage. In the final stage, there is one op amp and three resistors. The second stage of this filter provides a summing function to add high-pass and low-pass responses at the end of the circuit. If it were a sixth-order filter, the final stage of this filter is at the end of the signal line, while there are three proceeding first stages.

While the MFB filter topology is widely used in low-pass, high-pass, and bandpass filters, it has several serious drawbacks for bandstop filters. The dependence of the transfer function on the op amp parameters is greater than the Sallen-Key realization. It is also hard to generate high-Q, high-frequency sections because of the limited open-loop gain of the amplifier at high frequencies.

Figure 5 shows the sixth-order, closed-loop response of a MFB circuit. A sixth-order filter is implemented by cascading three second-order filters (Figure 4) in series. In Figure 5, the MFB's circuit closed-loop gain of 4.58 V/V with an approximation type of linear phase 0.5° and f_0 equal to 1 kHz.

The filter in Figure 5 uses ideal resistors (12), capacitors (6), and amplifiers (4). With ideal components and devices in the circuit, the closed-loop frequency response shows that there is approximately -36.6 dB of attenuation within the notch. However, on either side of the notch, the filter gain increases by an undesirable amount of about 1.4 dB. These two humps are a consequence of the challenge to match the high-pass and low-pass filter in this system with the final-stage summing function.

Figure 3. Closed-loop frequency response of sixth-order Sallen-Key notch filter

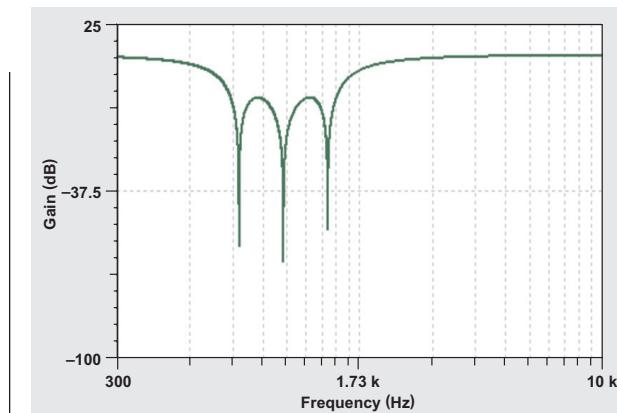


Figure 4. A second-order multiple-feedback bandstop or notch filter


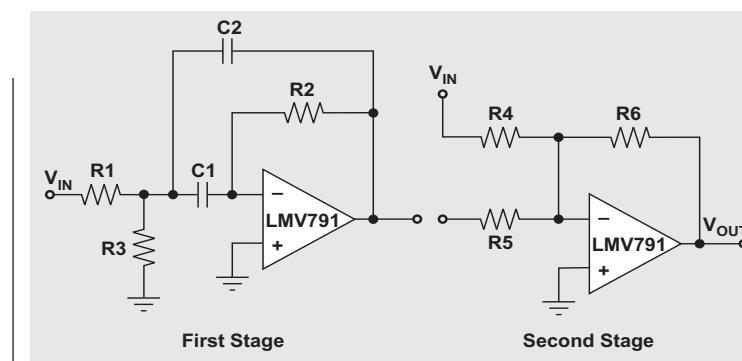


Figure 5. Closed-loop frequency response of sixth-order MFB notch filter

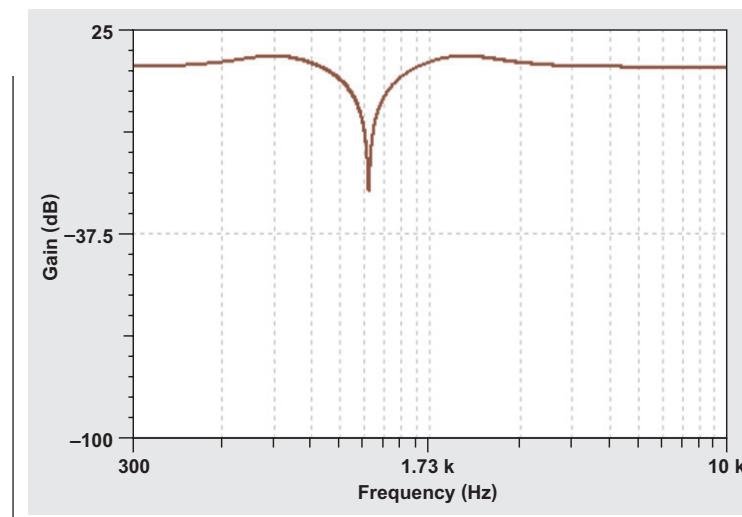

As a consequence of these shortcomings, the MFB notch filter is not a recommended topology for bandstop-filter construction.

Bainter circuit topology

As Figure 6 shows, the Bainter filter topology^[2] has three simple amplifier circuit blocks with two feedback loops. The frequency response served at the output of A1 is a high-pass filter. The frequency response at the output of A2 is a low-pass filter, and A3 acts as a summer by providing the entire notch function at its output.

The circuit in Figure 6 has several fascinating properties. The Q of the notch is dependent on the gain of the amplifiers as opposed to component matching. Consequently, the notch depth is not sensitive to temperature drift or aging. The notch depth remains relatively constant even though the filter's frequency, f_0 , may shift. Additionally, the component sensitivity of this filter is very low, about 0.5.

Figure 7 shows the sixth-order, closed-loop response of a Bainter circuit. A sixth-order filter is formed by cascading three second-order filters (Figure 6) in series. In Figure 7, the Bainter's circuit closed-loop gain is 4.58 V/V with an approximation type of linear phase 0.5° and f_0 equal to 1 kHz.

The construct of this filter uses ideal resistors (21), capacitors (6), and amplifiers (9). With ideal components and devices in the circuit, there is a less than -100 dB of attenuation for the closed-loop frequency response. Additionally, in contrast to the Sallen-Key and MFB filters, this is a very clean notch filter.

The Bainter notch filter is definitely a recommended topology for bandstop filter construction.

Conclusion

When evaluating the correct topology for a bandstop filter, it is important to examine the closed-loop frequency response. Industry implementations of bandstop filters may use the Sallen-Key or MFB circuits. Both of these circuit topologies have their problems in the bandstop regions and in the passband regions with poor notch characteristics and unnecessary gain peaking in the passband region. The Bainter filter far surpasses the bandstop performance of these two filters by creating a clean notch filter.

The WEBENCH® Filter Designer is an effective tool that will help you create your own filter. You will be able to easily design low-pass, high-pass, bandpass, and bandstop filters. This filter design system will help you design your filter, find the appropriate amplifier and components, as well as provide a SPICE simulation platform for further evaluations.

Figure 6. A second-order Bainter bandstop or notch filter


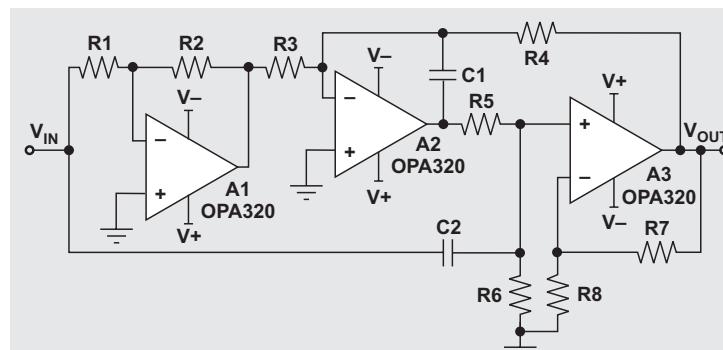


Figure 7. Closed-loop frequency response of sixth-order Bainter notch filter

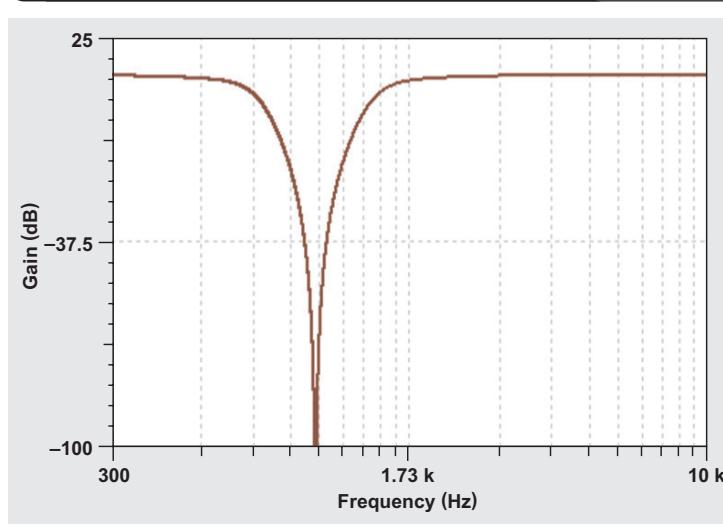

References

1. "Analog Filters and Specifications Swimming: Selecting the right bandwidth," Baker, On board with Bonnie, 11/8/13. Available: e2e.ti.com/blogs/
2. "Active filter has stable notch, and response can be regulated," Bainter, James, Electronics, October 2, 1975. Available: www.google.com/

Related Web sites

WEBENCH® Filter Designer
www.ti.com/webenchfilters
www.ti.com/lq15-OPA316
www.ti.com/lq15-OPA320
www.ti.com/lq15-LMV791

TI Worldwide Technical Support

Internet

TI Semiconductor Product Information Center Home Page

support.ti.com

TI E2ETM Community Home Page

e2e.ti.com

Product Information Centers

Americas Phone +1(512) 434-1560

Brazil Phone 0800-891-2616

Mexico Phone 0800-670-7544

Fax +1(972) 927-6377

Internet/Email support.ti.com/sc/pic/americas.htm

Europe, Middle East, and Africa

Phone

European Free Call 00800-ASK-TEXAS
(00800 275 83927)

International +49 (0) 8161 80 2121

Russian Support +7 (4) 95 98 10 701

Note: The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax +(49) (0) 8161 80 2045

Internet www.ti.com/asktexas

Direct Email asktexas@ti.com

Japan

Fax International +81-3-3344-5317

Domestic 0120-81-0036

Internet/Email International support.ti.com/sc/pic/japan.htm

Domestic www.tij.co.jp/pic

Asia

Phone Toll-Free Number

Note: Toll-free numbers may not support mobile and IP phones.

Australia 1-800-999-084

China 800-820-8682

Hong Kong 800-96-5941

India 000-800-100-8888

Indonesia 001-803-8861-1006

Korea 080-551-2804

Malaysia 1-800-80-3973

New Zealand 0800-446-934

Philippines 1-800-765-7404

Singapore 800-886-1028

Taiwan 0800-006800

Thailand 001-800-886-0010

International +86-21-23073444

Fax +86-21-23073686

Email tiasia@ti.com or ti-china@ti.com

Internet support.ti.com/sc/pic/asia.htm

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A021014

© 2015 Texas Instruments Incorporated. All rights reserved.

E2E is a trademark and WEBENCH is a registered trademark of Texas Instruments. All other trademarks are the property of their respective owners.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products	Applications
Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity
	TI E2E Community
	e2e.ti.com